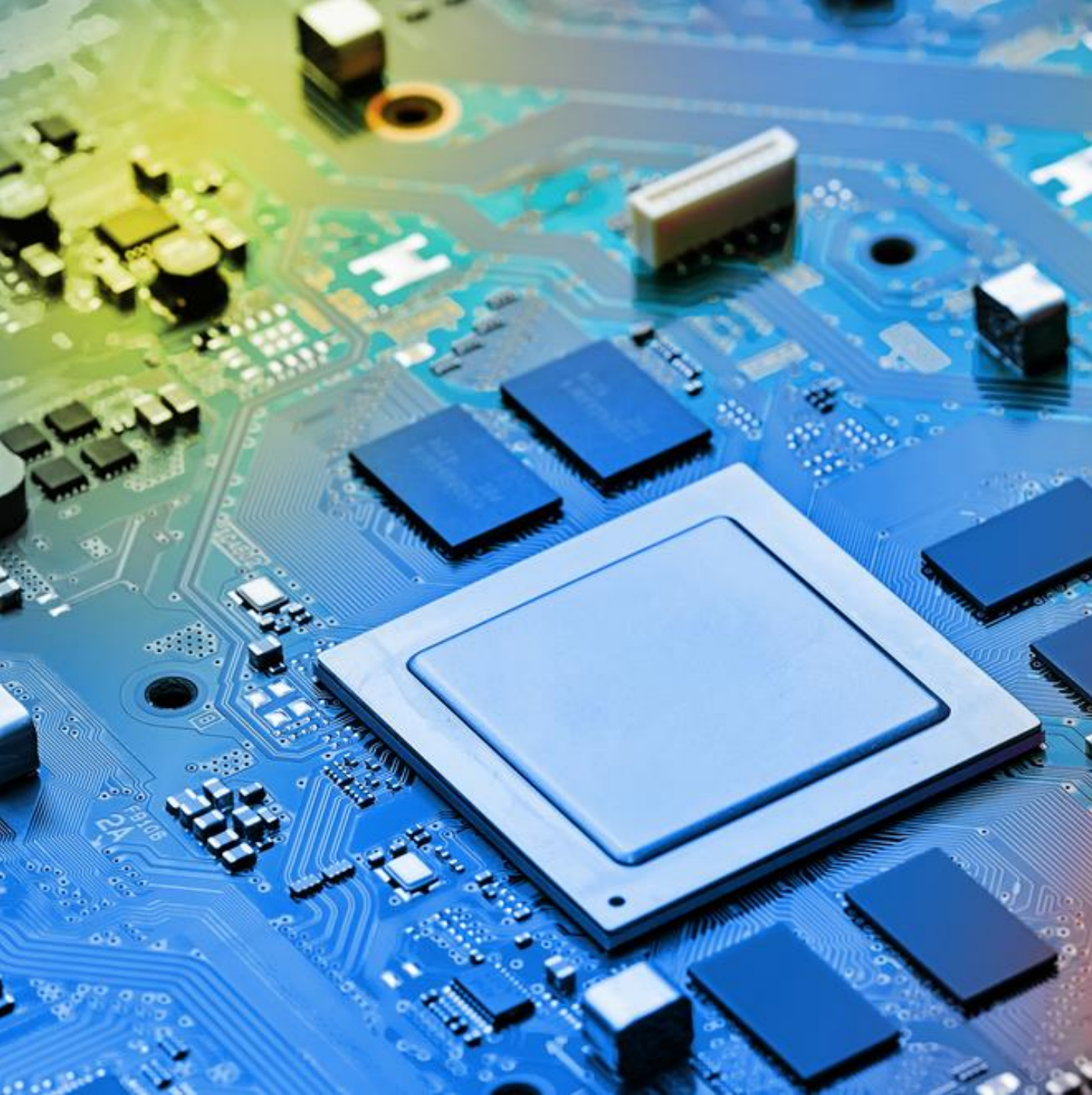




**NANYANG
TECHNOLOGICAL
UNIVERSITY**
SINGAPORE

EE3019 – Integrated Electronics


Part 1d – Feedback Circuits



Learning Objectives

By the end of this lesson, you should be able to:

- Explain the general feedback structure and characteristics of a negative feedback amplifier.
- Explain the advantages of a negative feedback amplifier.
- Discuss the four feedback topologies.
- Describe the procedures of feedback amplifier analysis.
- Analyse the loading effect of feedback analysis.
- Execute the examples on negative feedback amplifier.
- Identify the Gain (A_f), Input Impedance (R_{if}) and Output Impedance (R_{of}) of a feedback amplifier.

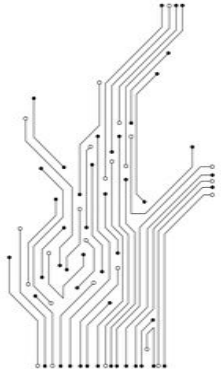

Feedback: Outline

The General **Feedback Structure**

01

Characteristics of **Negative Feedback Amplifier**

02

Examples of Feedback Amplifier Analysis

06

The 4 Basic Feedback **Topologies**

03

Loading Effect of Feedback network



05

Procedures of Feedback Amplifier **Analysis**

04

Reference:

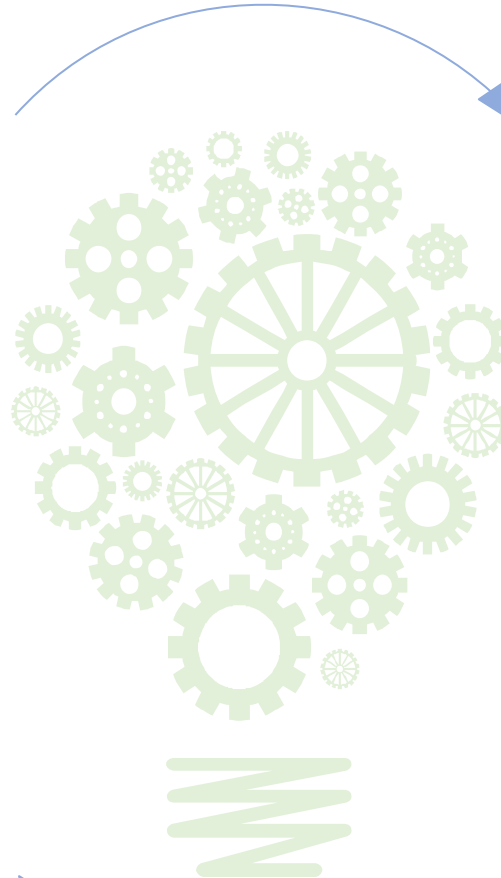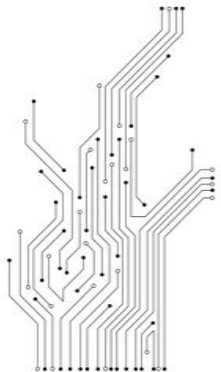● Sedra and Smith, "Microelectronic Circuits", 5th Edition, 2014 Chapter 8.



1. The General Feedback Structure




Single-loop Feedback Amplifier

$$X_i = X_s - X_f \quad - (1)$$

$$X_o = AX_i \quad - (2)$$

$$X_f = \beta X_o \quad - (3)$$

$$A = 100 \pm 20$$

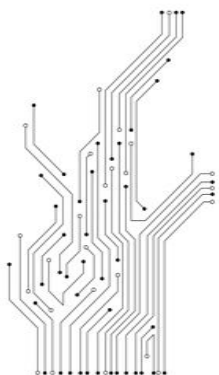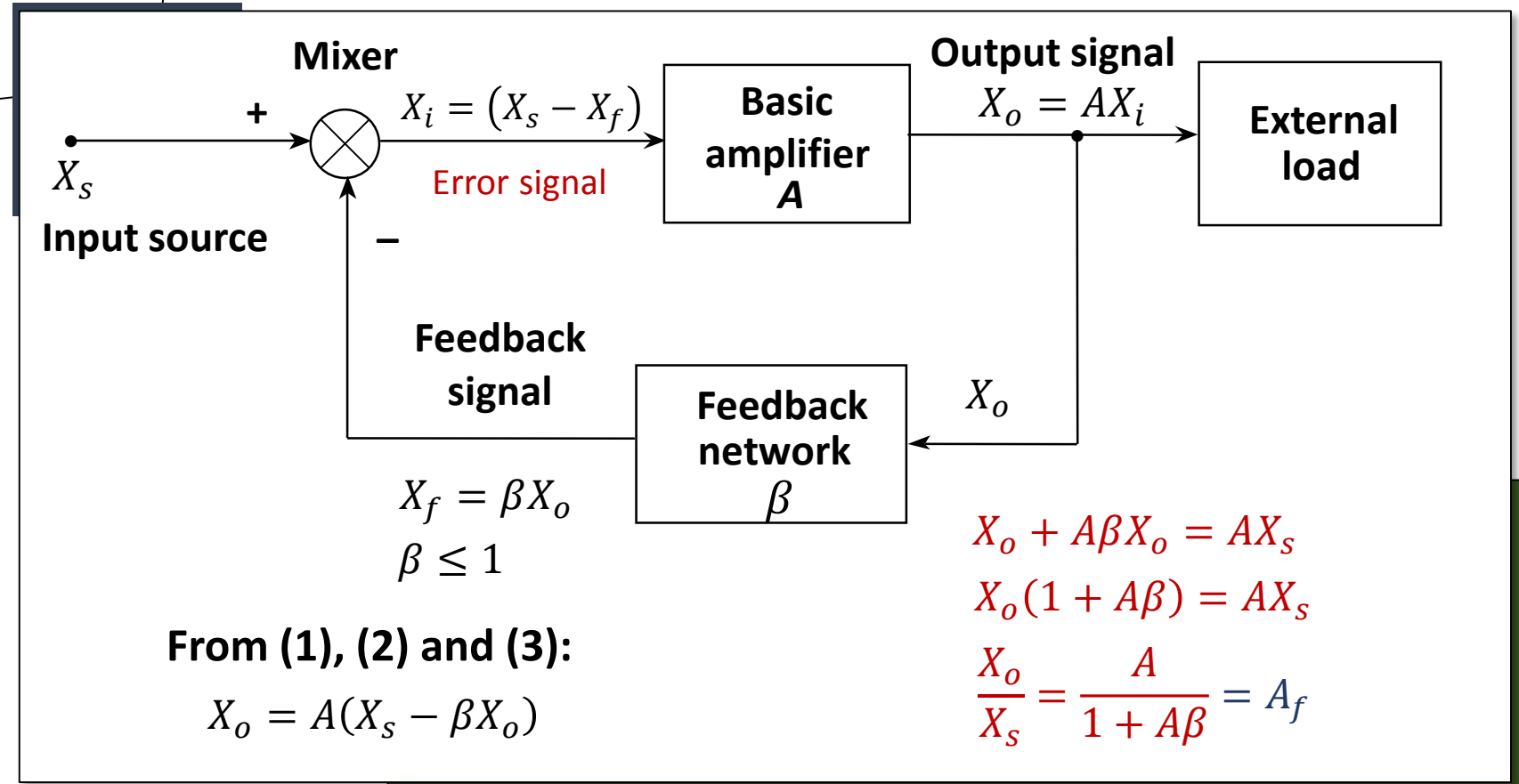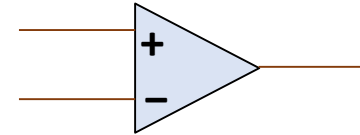



Gain of Negative Feedback Amplifier

Gain of Feedback amplifier:

$$A_f = \frac{X_o}{X_s} = \frac{A}{1 + A\beta}$$

In many circuits, $A\beta \gg 1$ then:

$$A_f \approx \frac{1}{\beta}$$

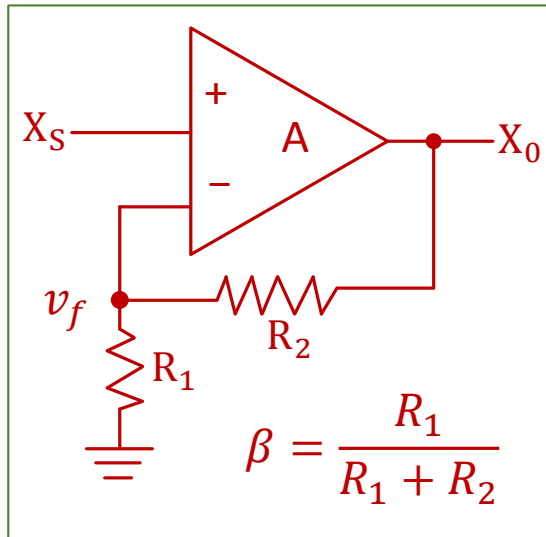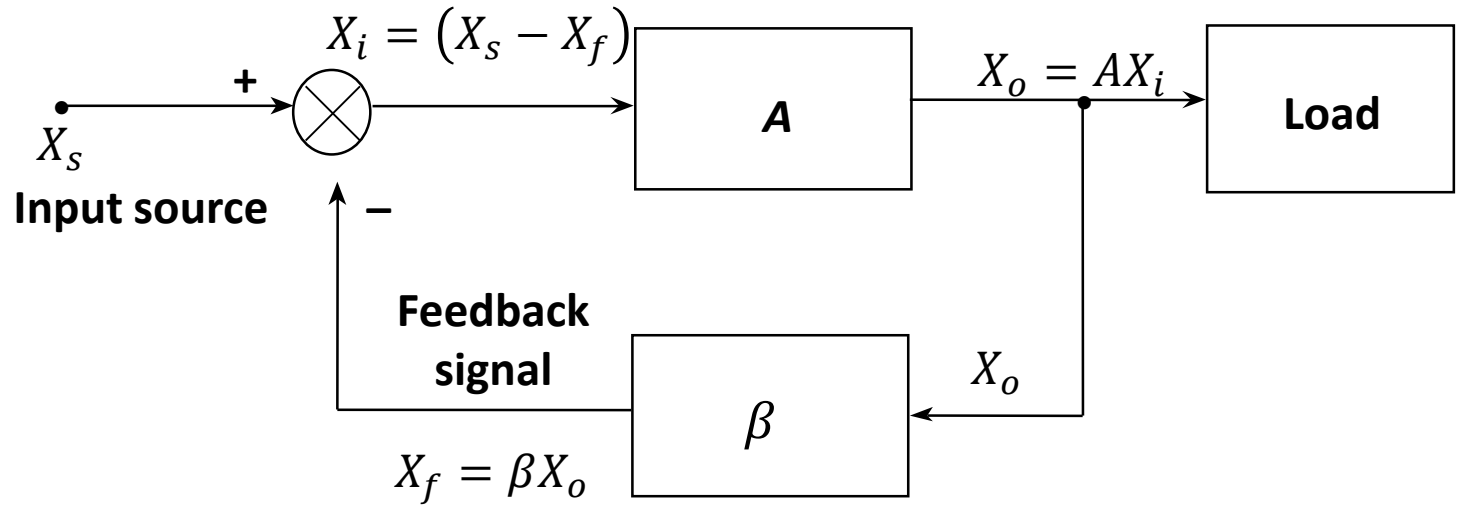

Notation:


A : Basic Amp. Open-loop Gain (without feedback)

β : Feedback factor

$A\beta$: Loop gain (determine the stability of the feedback Amp)

$1+A\beta$: Amount of feedback

A_f : Closed-loop Gain (with feedback)

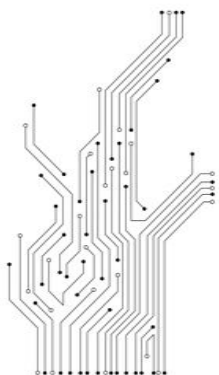

2. Characteristics of Negative Feedback Amplifier

Advantages

A. Gain De-sensitivity


B. Reduced Frequency Distortion

C. Noise Reduction

D. Reduced Non-Linear Distortion

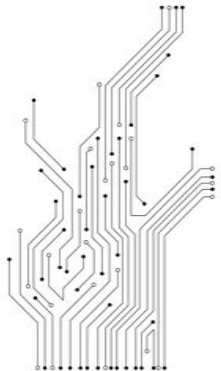E. I/P and O/P Impedance Change

All these are obtained at the expense of **GAIN REDUCTION**.



A. Gain De-sensitivity

$$\text{Closed-loop Gain, } A_f = \frac{A}{1 + A\beta} \quad - (1)$$

Taking Differential on both sides:


$$\text{i.e. } dA_f = \frac{(1 + A\beta)dA - A\beta dA}{(1 + A\beta)^2} \Rightarrow dA_f = \frac{dA}{(1 + A\beta)^2} \quad - (2)$$

$d\left(\frac{u}{v}\right) = \frac{vdu - u dv}{v^2}$

$$\frac{(2)}{(1)}: \frac{dA_f}{A_f} = \frac{1}{(1 + A\beta)} \frac{dA}{A} \quad - (3)$$


Gain sensitivity of A_f is reduced by $1 + A\beta$

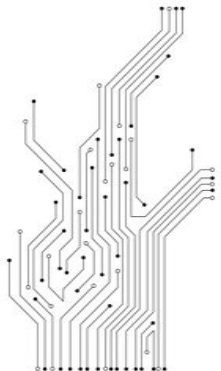The de-sensitivity factor is $(1 + A\beta)$, which is the amount of feedback.



A. Gain De-sensitivity

Example 1

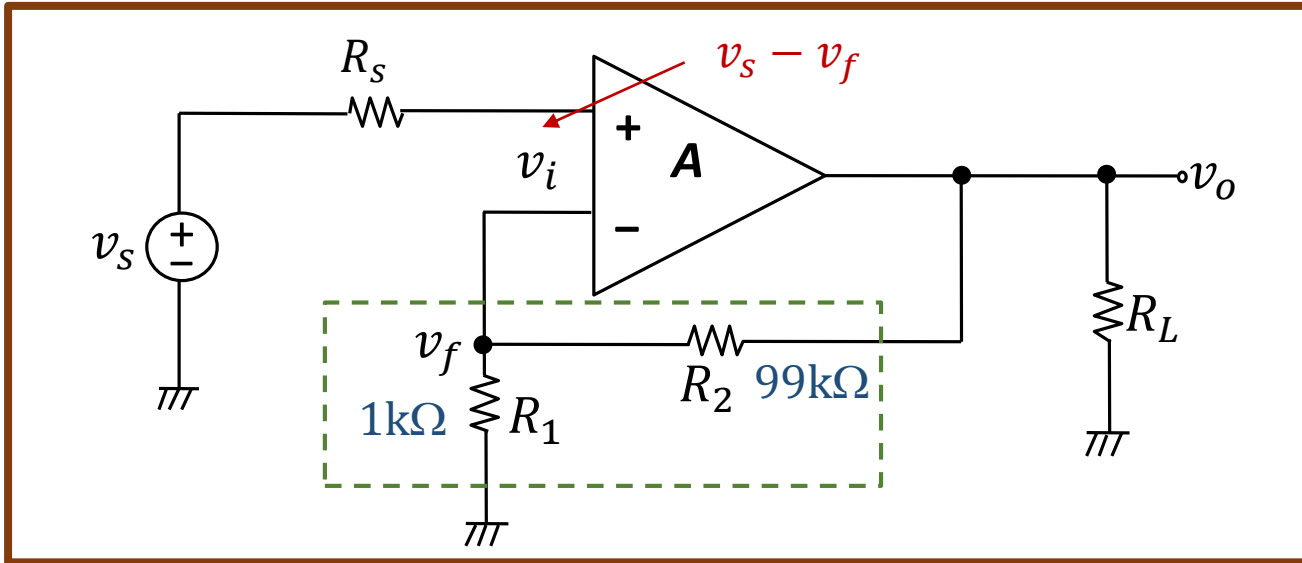

$$v_f = \frac{R_1}{R_1 + R_2} v_o \Rightarrow \beta = \frac{v_f}{v_o} = \frac{R_1}{R_1 + R_2}$$


If $A = \infty$ (idea)

$$\frac{v_o}{v_s} = 1 + \frac{R_2}{R_1} = 1 + \frac{99}{1} = 100$$

If $A = 10^5$ and $\beta = 0.01$, then closed-loop gain is:

$$A_f = \frac{A}{1 + A\beta} = \frac{10^5}{1 + 10^5 \times 10^{-2}} = \frac{10^5}{1001} = 99.9$$
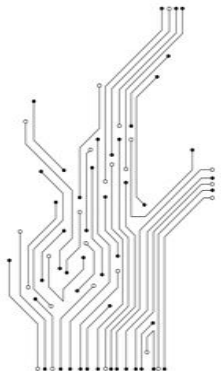
$$20\log A_f = 20\log\left(\frac{A}{1 + A\beta}\right) = \underbrace{20\log A}_{\text{dB}} - \underbrace{20\log(1 + A\beta)}_{\text{dB}}$$



A. Gain De-sensitivity

Example 1 (Contd.)

Loop gain, $A\beta = 10^3$. Amount of feedback, $1 + A\beta = 1001$

$A = 10^5$, $\beta = 0.01$ and $A_f = 99.9$

Expressed in dB: $A_f(\text{dB}) = A(\text{dB}) - (1 + A\beta)(\text{dB})$

In dB, the difference between open-loop gain, A , and closed-loop gain, A_f , is the amount of feedback ($1 + A\beta$).


If the op-amp gain of A decreased by 10%, the corresponding decrease in A_f is given by:

Gain de-sensitivity reduces by 1001 times.

$$\begin{aligned}\frac{dA_f}{A_f} &= \frac{1}{(1 + A\beta)} \frac{dA}{A} \\ &= \frac{1}{1001} \times \frac{-10}{100} = -0.01\%\end{aligned}$$

where $(1 + A\beta)$ is also known as the desensitivity factor

(very small)


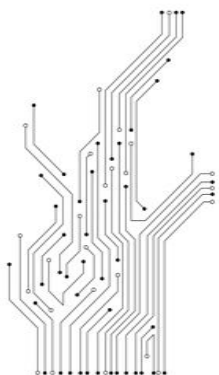


B. Bandwidth Extension



Reduction of frequency distortion

For a basic amplifier, A :

a. Without **negative feedback**:

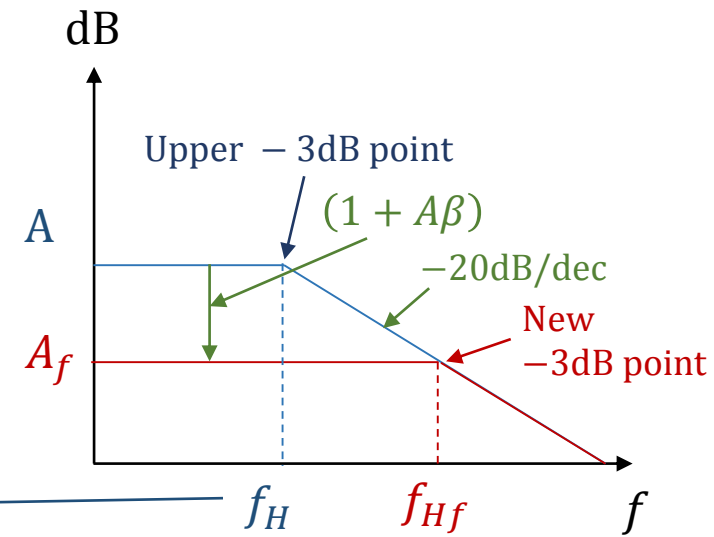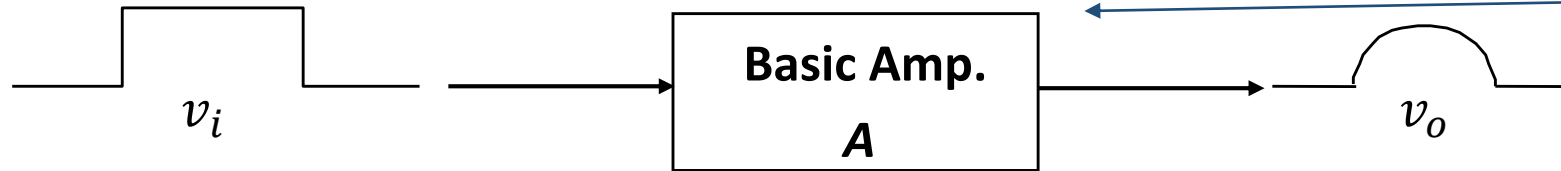

b. With **negative feedback** added :

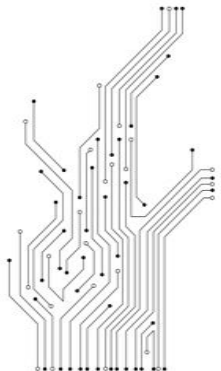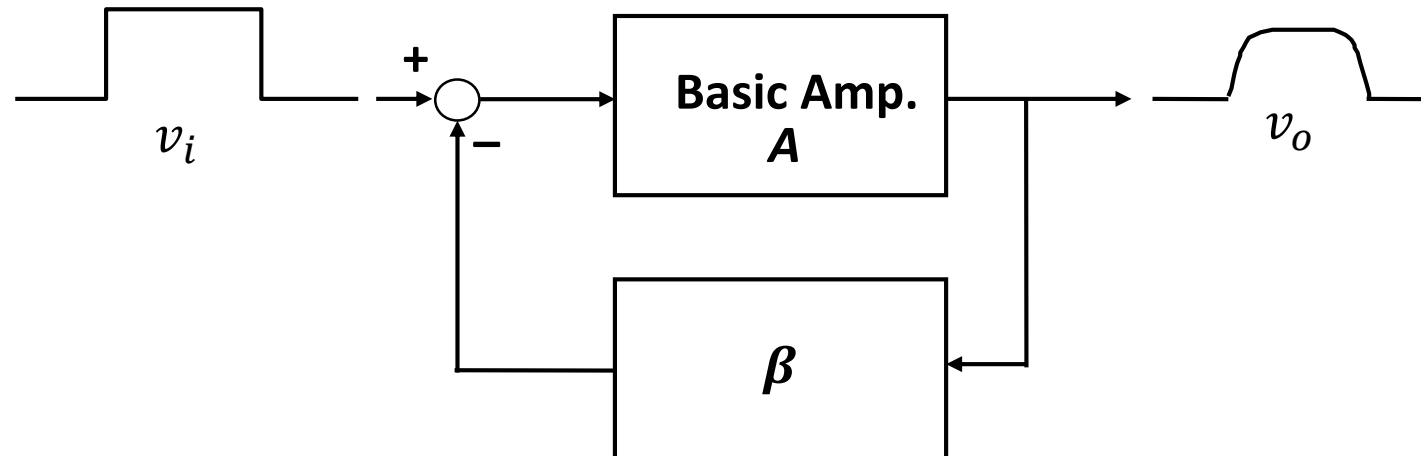

(a) Extension of Bandwidth : $\omega_H = 2\pi f_H$

Mid-band gain

Low pass function

$$A(s) = A_m F_H(s)$$



Low pass response

Consider the case where $F_H(s)$ is characterised by a dominant pole.

$$A(s) = \frac{A_m}{1 + \frac{S}{\omega_H}} = \frac{A_m}{1 + \frac{j\omega}{\omega_H}} \quad F_H = \frac{1}{1 + \frac{S}{\omega_H}}$$

The closed-loop gain is given by:
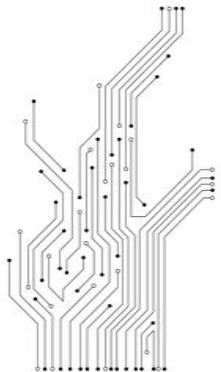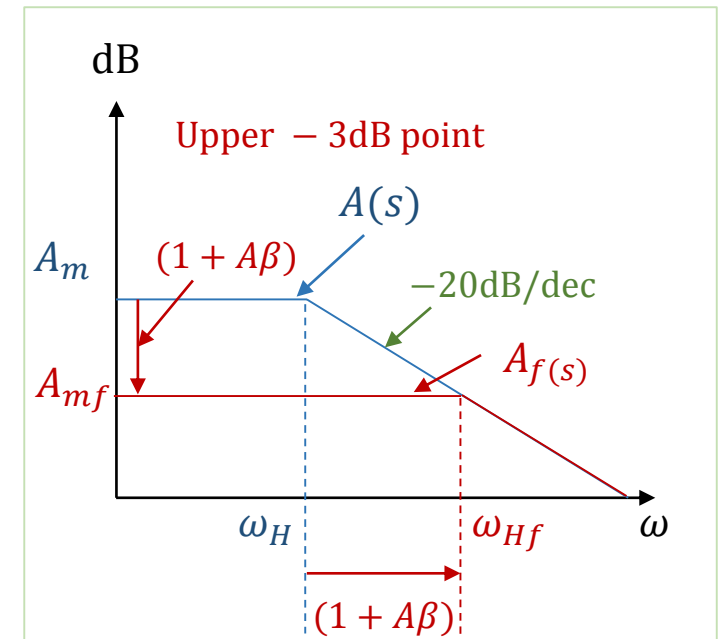
$$A_f(s) = \frac{A(s)}{1 + A(s)\beta} = \frac{\frac{A_m}{1 + \frac{S}{\omega_H}}}{1 + \frac{A_m \beta}{1 + \frac{S}{\omega_H}}}$$



(a) Extension of Bandwidth : ω_H (Contd.)


$$\therefore A_f(s) = \frac{\overbrace{\frac{A_m}{1 + A_m\beta}}^{A_{mf}}}{1 + \underbrace{\frac{s}{\omega_H(1 + A_m\beta)}}_{\omega_{Hf}}} = \frac{A_{mf}}{1 + \frac{s}{\omega_{Hf}}}$$

Closed-loop Amp
Mid-band gain

where $A_{mf} = \frac{A_m}{1 + A_m\beta}$

$\omega_{Hf} = \omega_H(1 + A_m\beta)$

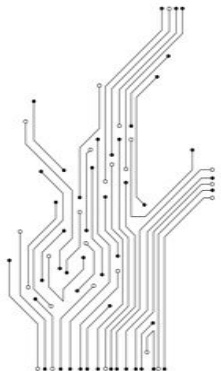Upper 3-dB frequency is increased by a factor equal to the amount of feedback $(1 + A_m\beta)$ when negative feedback is applied.




(b) Extension of Bandwidth : ω_L

$$A(s) = A_m F_L(s) \quad \leftarrow \text{High pass response}$$


Consider $F_L(s)$ being characterised by a dominant pole, ω_L and a zero at 0.

$$A(s) = A_m \frac{s}{s + \omega_L}$$

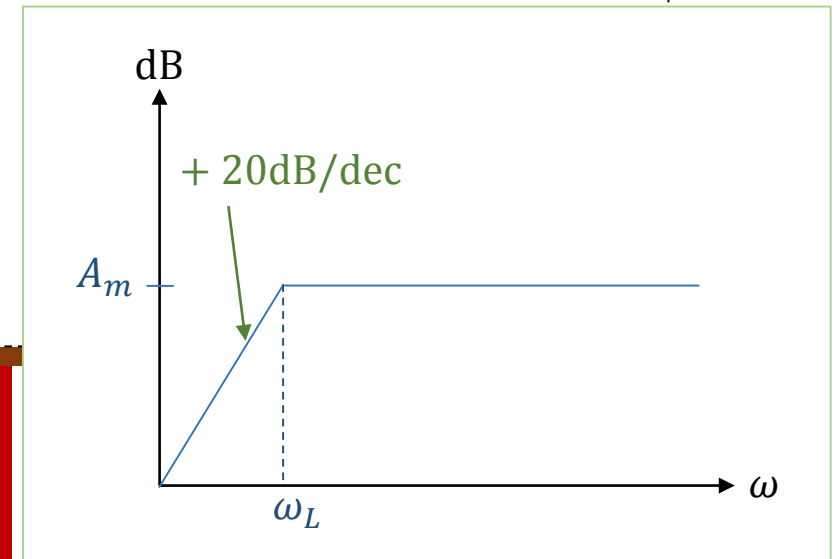

The closed-loop gain is:

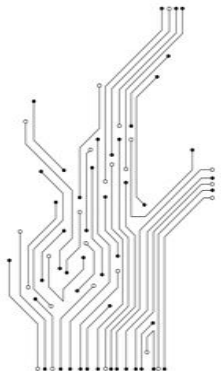
$$A_f(s) = \frac{A(s)}{1 + A(s)\beta} = \frac{A_m \frac{s}{s + \omega_L}}{1 + \frac{A_m \beta s}{s + \omega_L}}$$



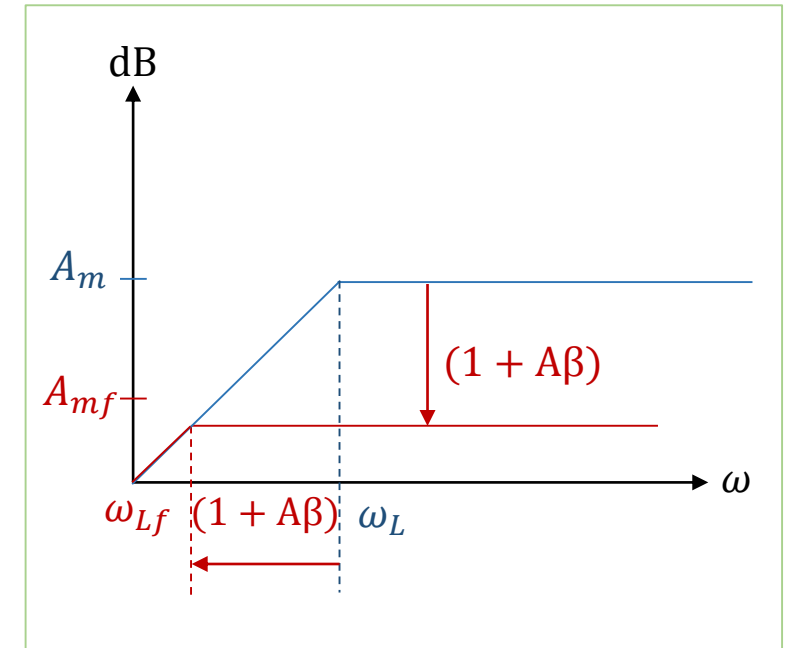
(b) Extension of Bandwidth : ω_L (Contd.)

$$A_f(s) = \frac{\overbrace{\frac{A_m}{1 + A_m\beta}}^{A_{mf}} s}{s + \underbrace{\frac{\omega_L}{1 + A_m\beta}}_{\omega_{Lf}}}$$


$$\therefore A_f(s) = \frac{A_{mf} s}{s + \omega_{Lf}} \quad \begin{aligned} A_{mf} &= \frac{A_m}{1 + A_m\beta} \\ \omega_{Lf} &= \frac{\omega_L}{1 + A_m\beta} \end{aligned}$$



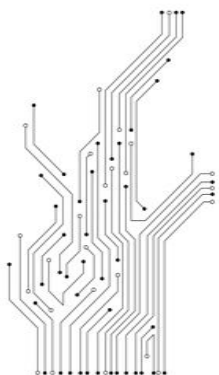\therefore Lower 3-dB frequency is decreased by $\frac{1}{1 + A_m\beta}$ when negative feedback is applied.



Graphical Representation

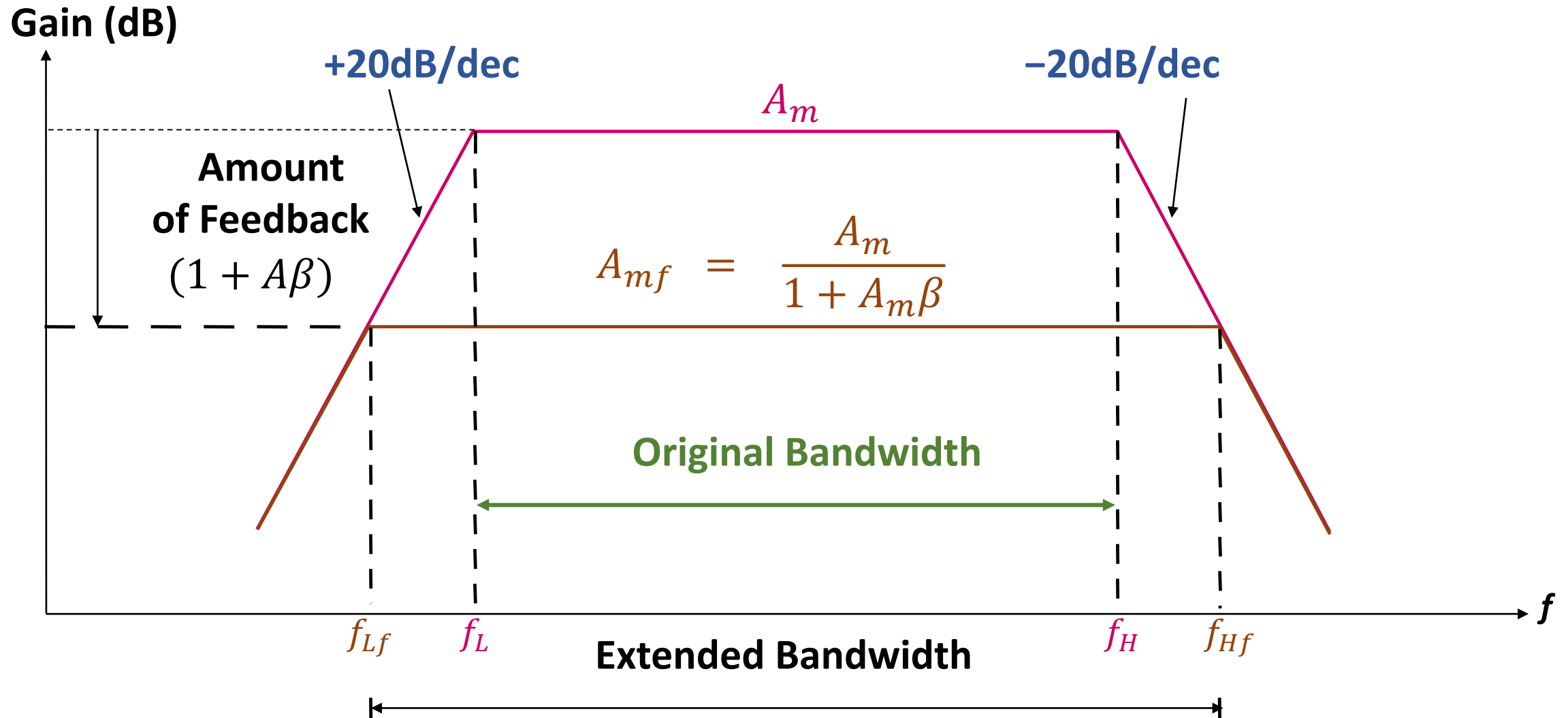

Example 2

Given:

$$A = 10^5$$




$$\beta = \frac{1}{100} = \frac{v_f}{v_o}$$

$$F_H = 10 \text{ kHz},$$

$$F_{Hf} = (1 + A\beta)F_H$$

$$\left(1 + 10^5 \times \frac{1}{100}\right) 10 \text{ kHz}$$


$$= \mathbf{10.01 \text{ MHz}}$$

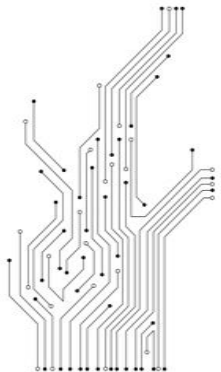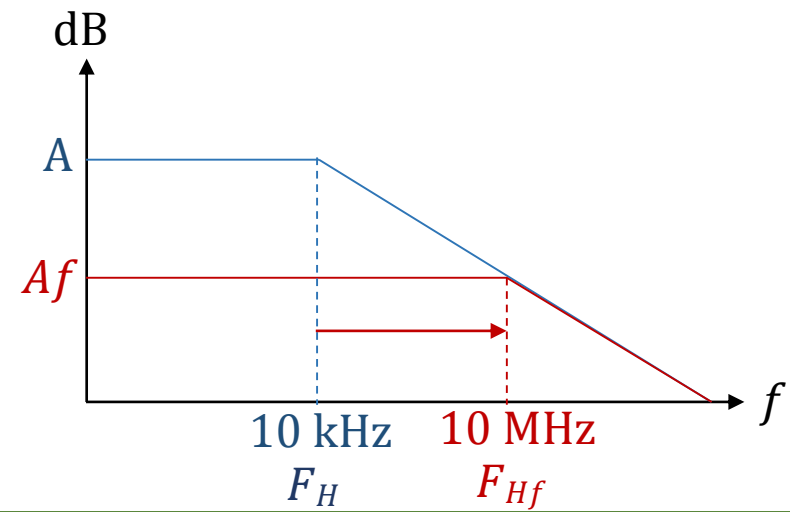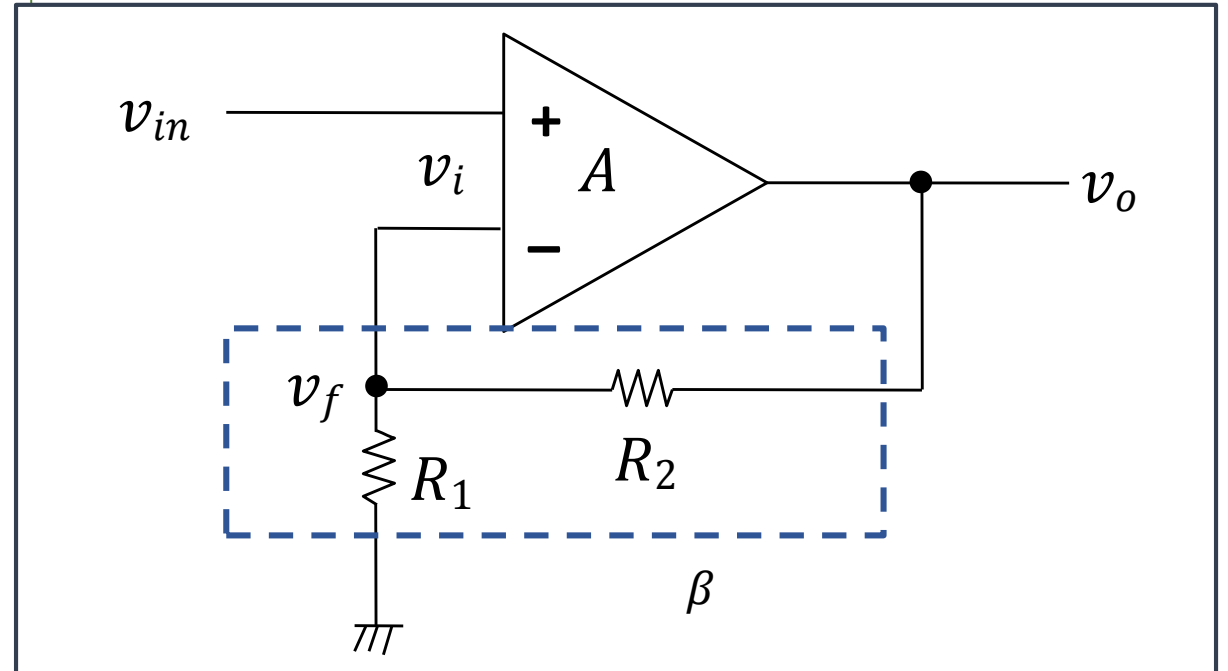

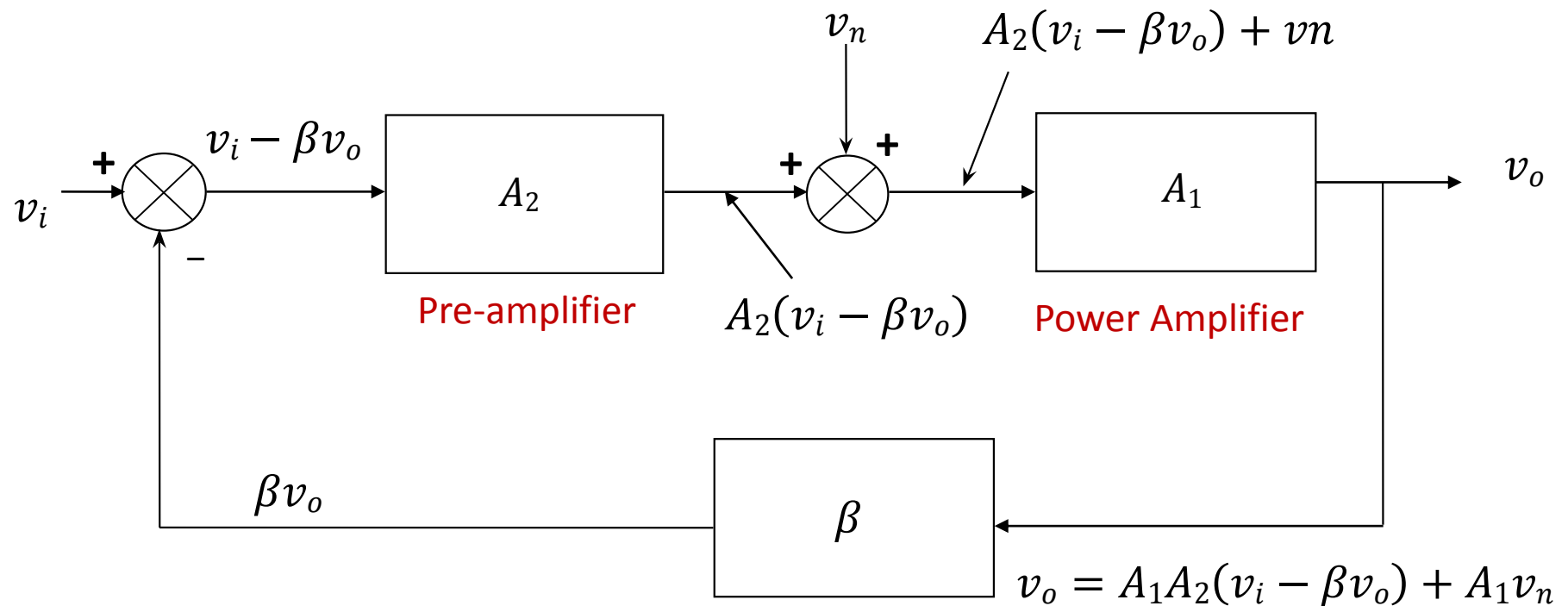C. Noise Reduction

Noise reduction by negative feedback is possible with the special configuration displayed below.

Here A_1 is a noisy amplifier and A_2 is a noise-free amplifier.




C. Noise Reduction

Output, $v_o = A_1 A_2 (v_i - \beta v_o) + A_1 v_n$

$$v_o = \underbrace{\frac{A_1 A_2}{1 + A_1 A_2 \beta}}_{\text{Signal}} v_i + \underbrace{\frac{A_1}{1 + A_1 A_2 \beta}}_{\text{Noise}} v_n$$

Signal-to-noise Ratio at output: $\therefore \frac{S}{N_f} = \frac{A_1 A_2 v_i}{A_1 v_n} = A_2 \frac{v_i}{v_n}$


Improved by A_2 with negative feedback

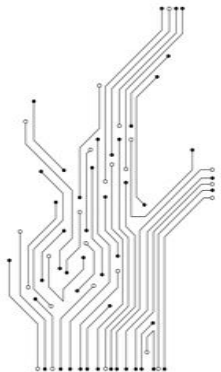


D. Non-linear Distortion Reduction

With negative feedback, the slope of the transfer curve has been reduced.


The resulting curve is less non-linear.

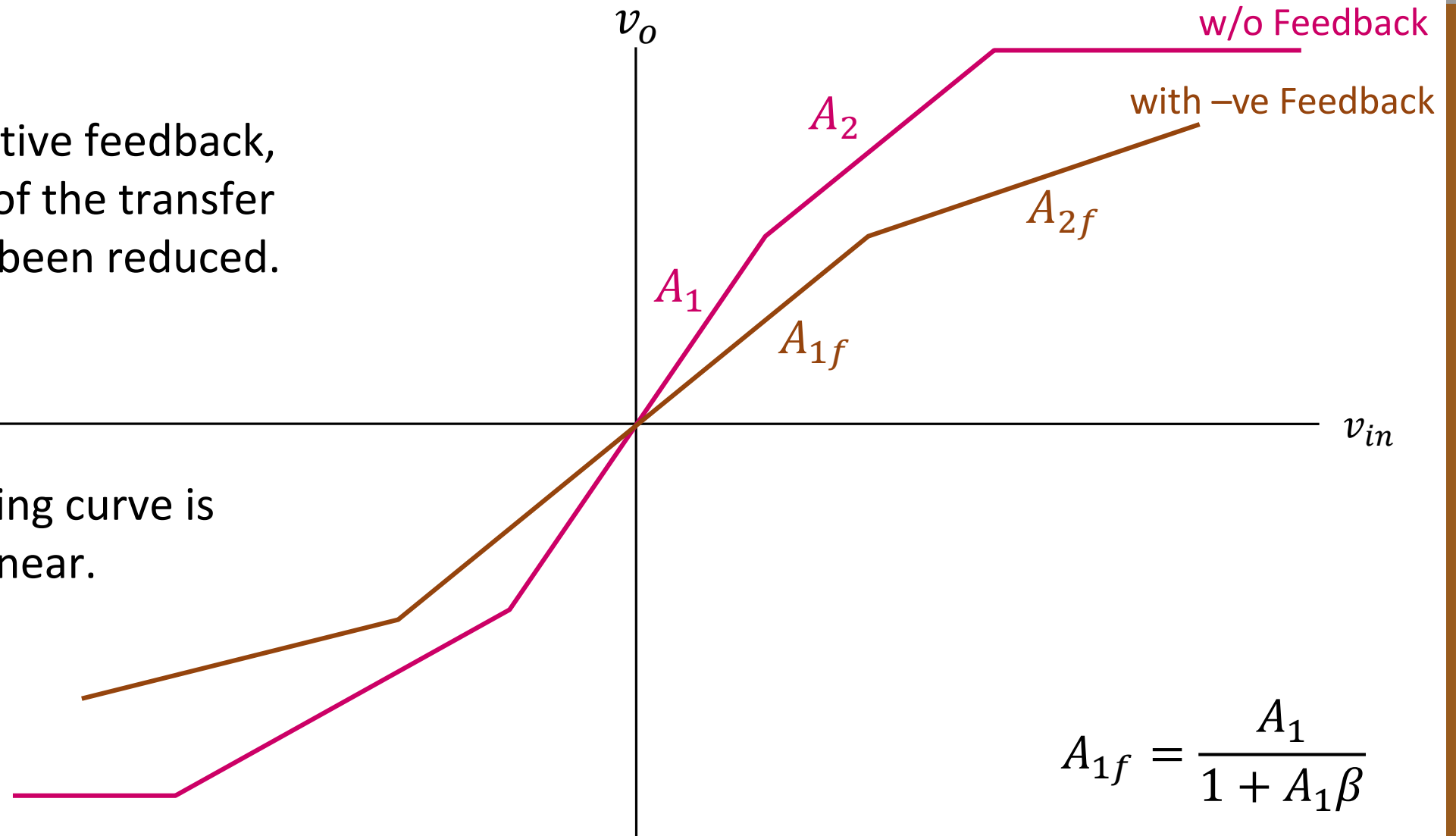


$$A_{1f} = \frac{A_1}{1 + A_1\beta}$$

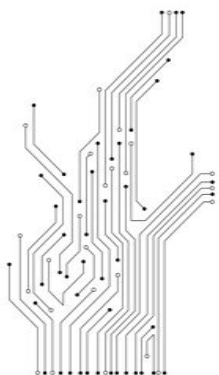

D. Non-linear Distortion Reduction

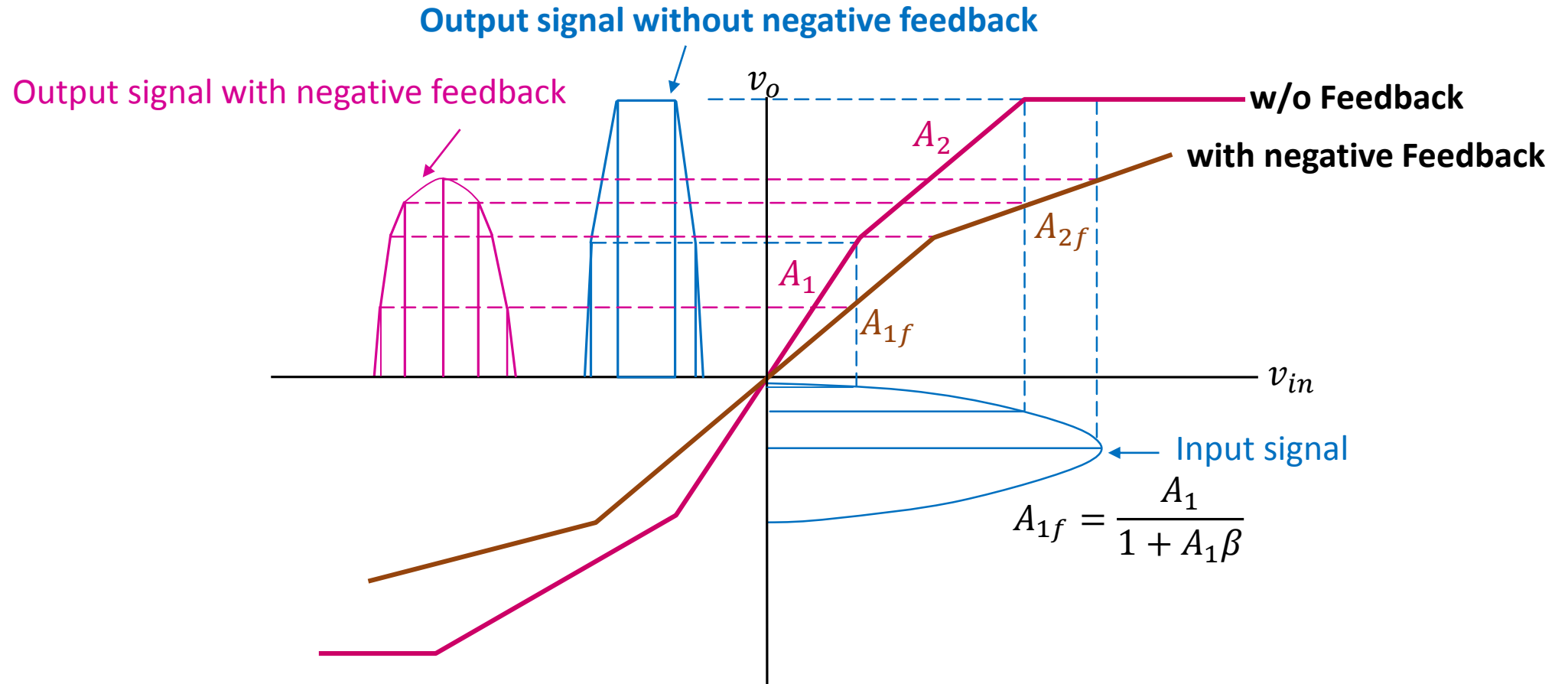

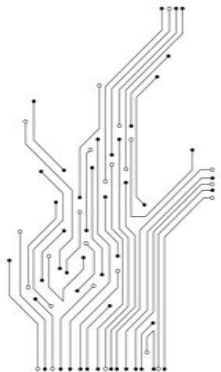With negative feedback, the slope of the transfer curve has been reduced.
The resulting curve is less non-linear.



Basic Feedback Topologies

Overview

There are four basic feedback topologies:

Mixing : Sampling

I/P

O/P

A. Voltage Amplifier + Example: Series-Shunt Feedback

Voltage or parallel sampling $\leftarrow \frac{v_o}{v_i}$

B. Current Amplifier + Example: Shunt-Series Feedback


Current or series sampling $\leftarrow \frac{I_o}{I_i}$

C. Trans-conductance Amplifier + Example: Series-Series Feedback

$\frac{I_o}{v_i}$


D. Trans-resistance Amplifier + Example: Shunt-Shunt Feedback

$\frac{v_o}{I_i}$

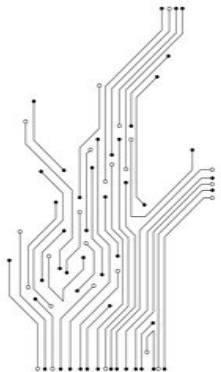


Feedback Topologies – Sampling (at output)

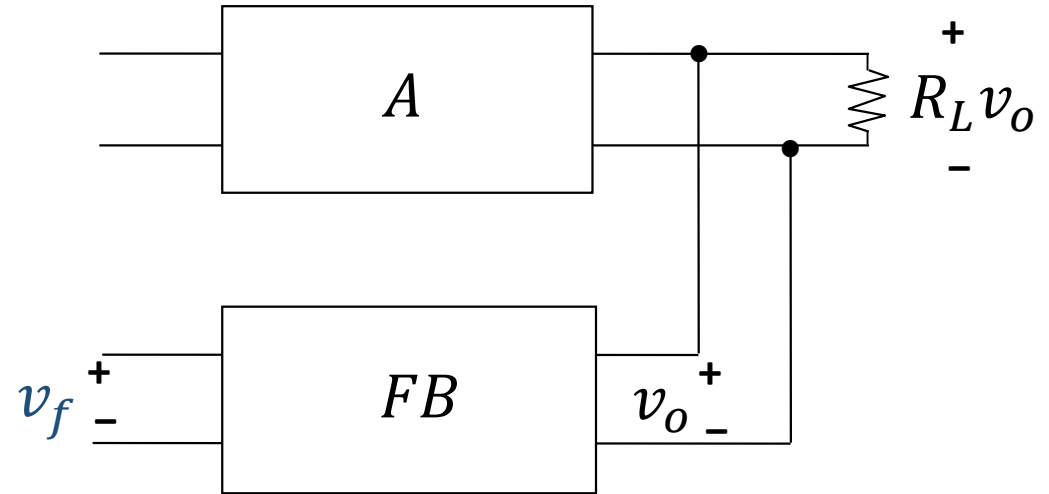
The sampling of the output signal of an amplifier can be in series with the load or in shunt with the load depending on the type of output signal (i.e. voltage or current).




Voltage Sampling (Shunt-Sampling)

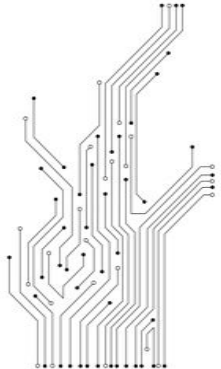


Feedback Topologies – Sampling (Contd.)

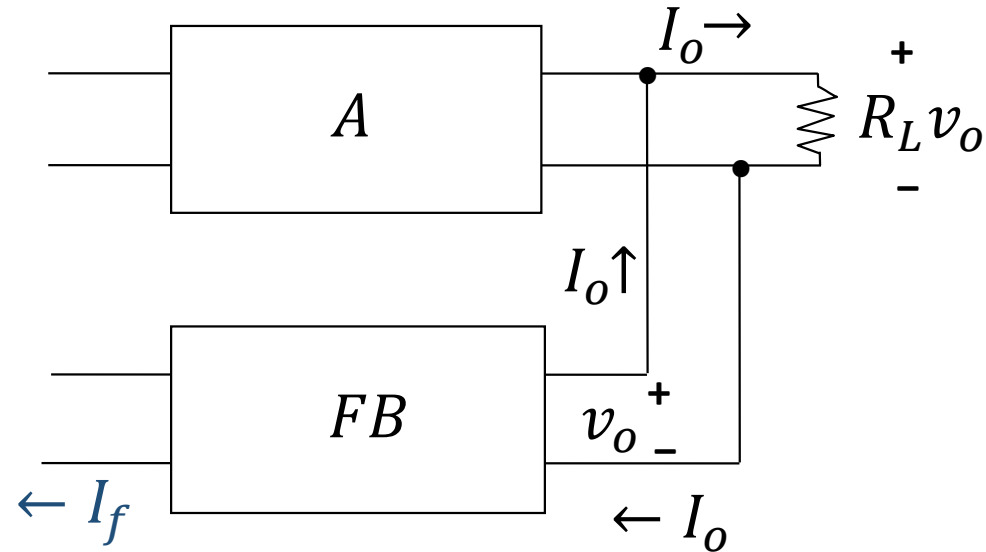

Current Sampling (Series-Sampling)

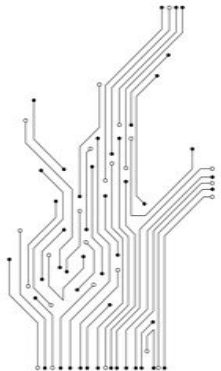




A summing junction is represented by a circle with an 'X' inside. Two input arrows point into the circle: one from the left labeled v_s with a '+' sign above it, and one from the bottom labeled v_f with a '-' sign below it. An output arrow points to the right, labeled v_o .



Voltage mixing (Series-mixing)

Feedback Topologies – Mixing (Contd.)

$$I_i = I_s - I_f$$

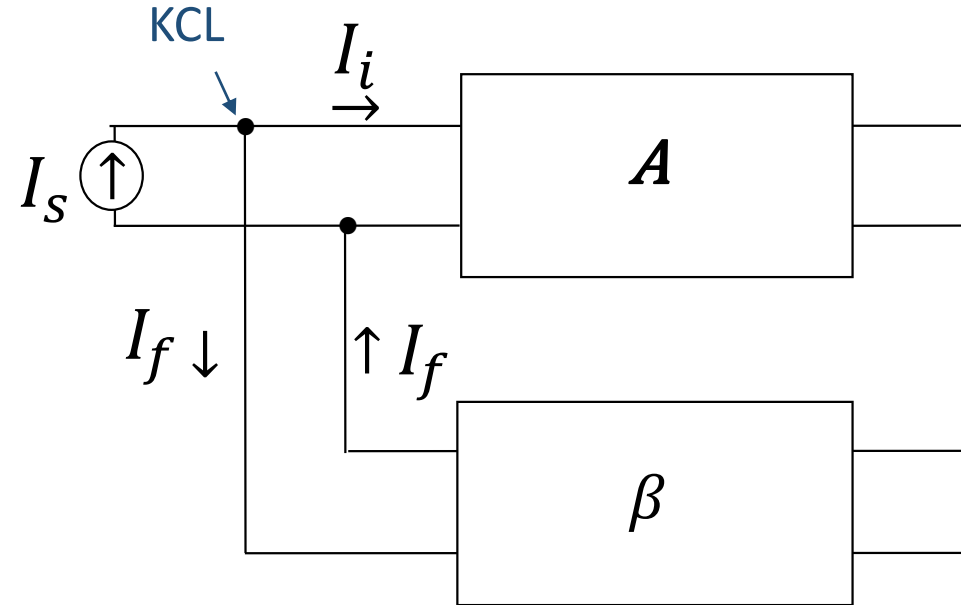

Current mixing (Shunt-mixing)


Feedback Topology

The Feedback Topology depends on:

The **type of amplifier** used for the basic amplifier block.

∴ The type of signal (**voltage** or **current**) of the input and output of the feedback network block must be identical to those of the basic amplifier block.

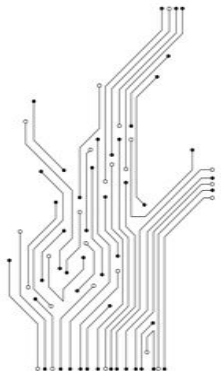∴ There are **FOUR** basic feedback topologies with four different types of amplifier.




A. Voltage Amplifier

- • Feedback Topology is **voltage** mixing (at input) and **voltage** sampling (at output).


Input Signal : **Voltage**, v_i
Output Signal : **Voltage**, v_o

$$A_v = \frac{v_o}{v_i}$$

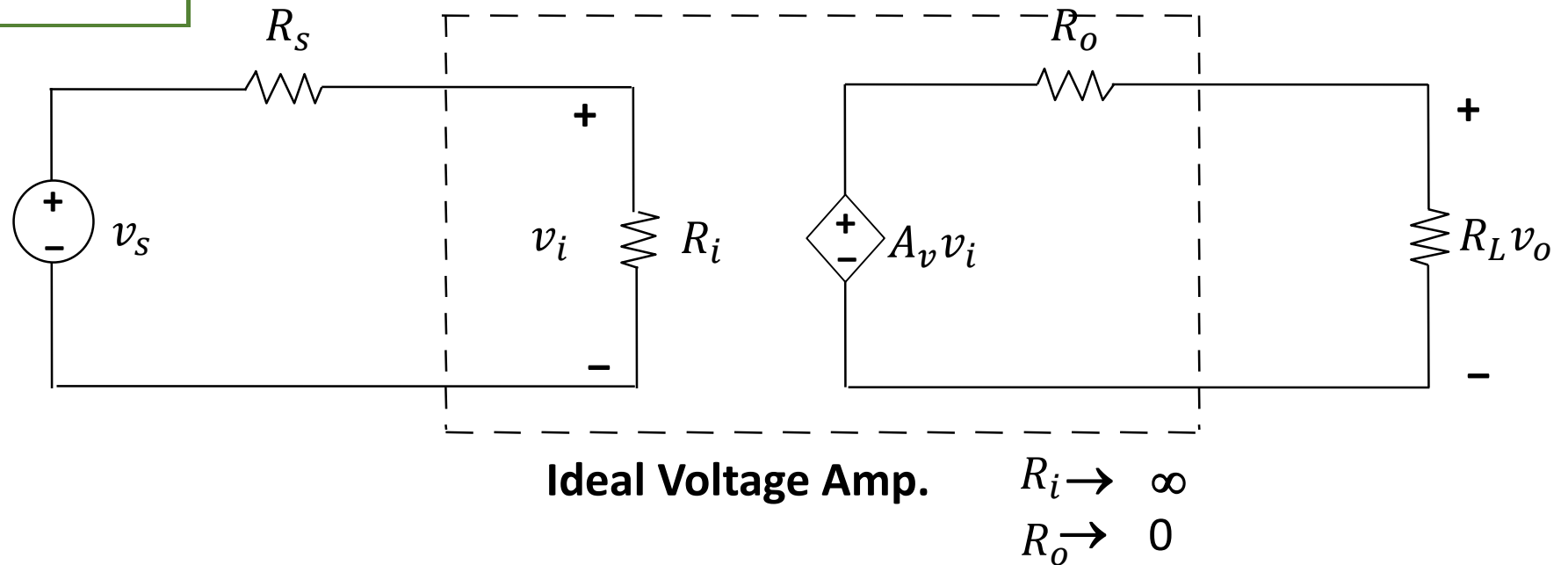

i.e. A voltage amplifier with negative feedback is a **Series – Shunt** feedback amplifier.



↑ ↑
Mixing Sampling

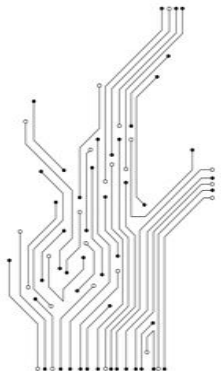

Series-Shunt Feedback Amplifier

Example 3


(Voltage Mixing
- Voltage
Sampling)

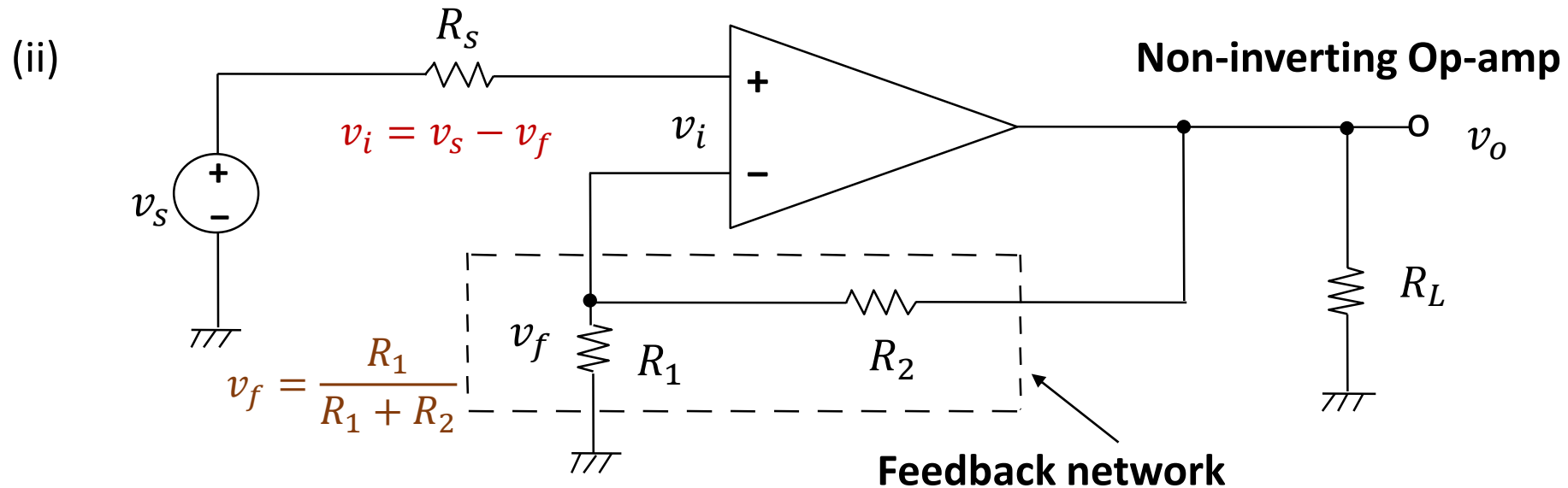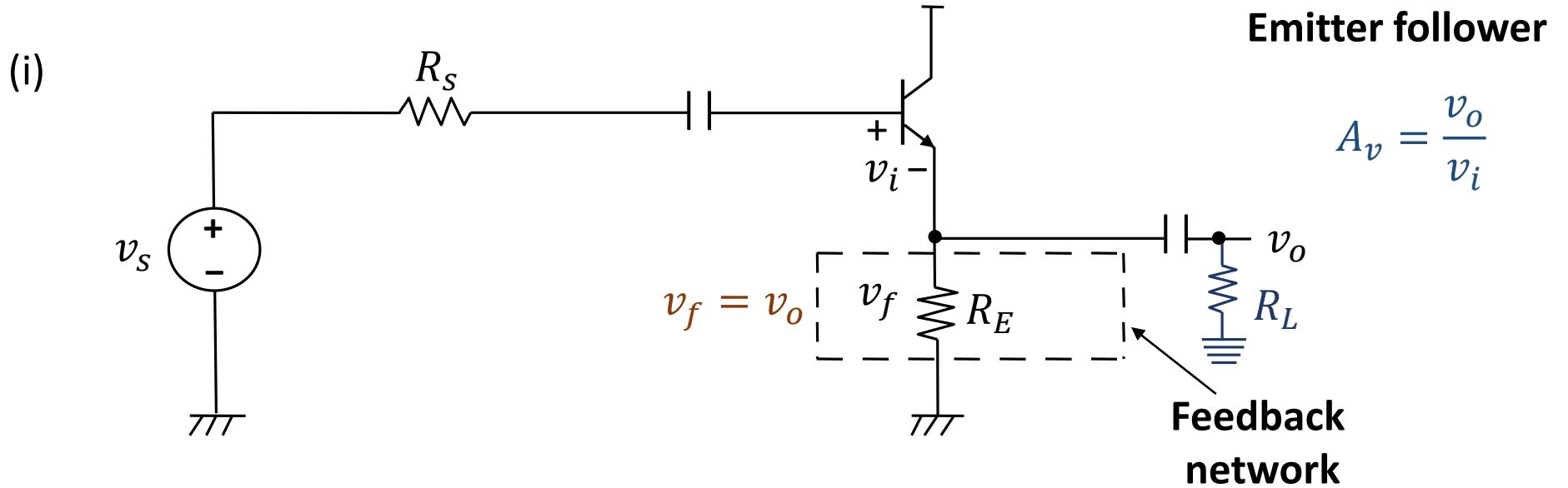

(Voltage Mixing - Voltage Sampling)

KVL

$$v_i = v_s - v_f$$

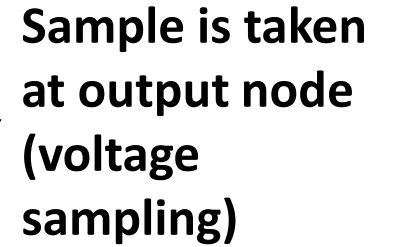

$$A_v = \frac{v_o}{v_s}$$

$$v_f = \frac{R_E}{R_E + R_F} v_o$$




**Feedback from collector
(voltage sampling) at output to
emitter at input**

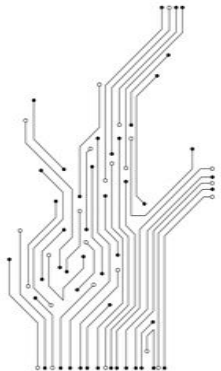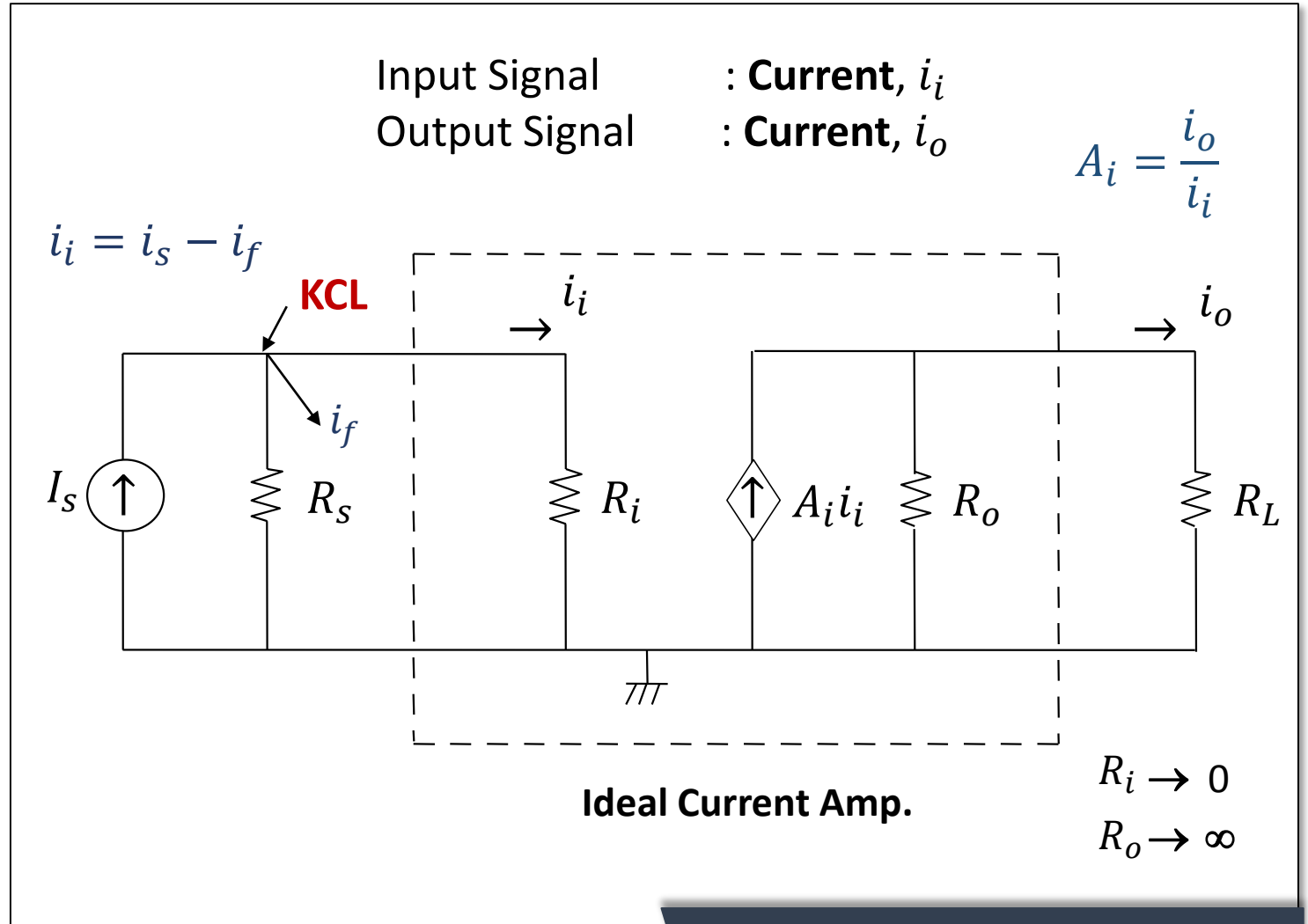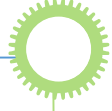B. Current Amplifier



∴ Feedback topology for current amplifier is **current** mixing (at input) and **current** sampling (at output).


i.e. A current amplifier with negative feedback is a **Shunt - Series** feedback amplifier.



Shunt-Series Feedback Amplifier


Example 4:

(Current mixing
- Current
sampling)

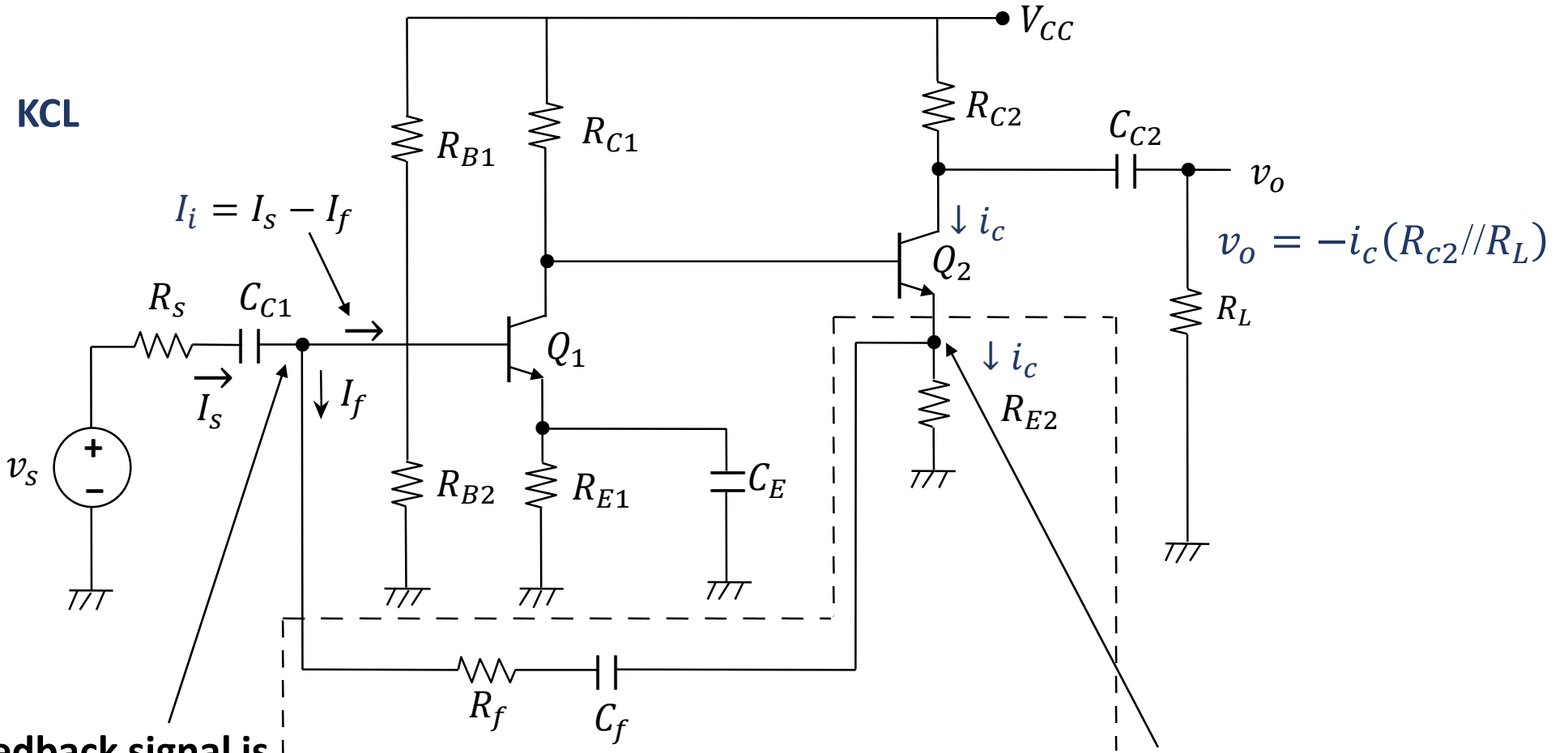


Feedback signal is
connected in parallel
with external source
(Current mixing)

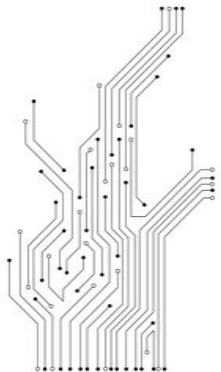
Sample is taken from the
output loop, not the output
node (Current sampling)



C. Trans-conductance Amplifier

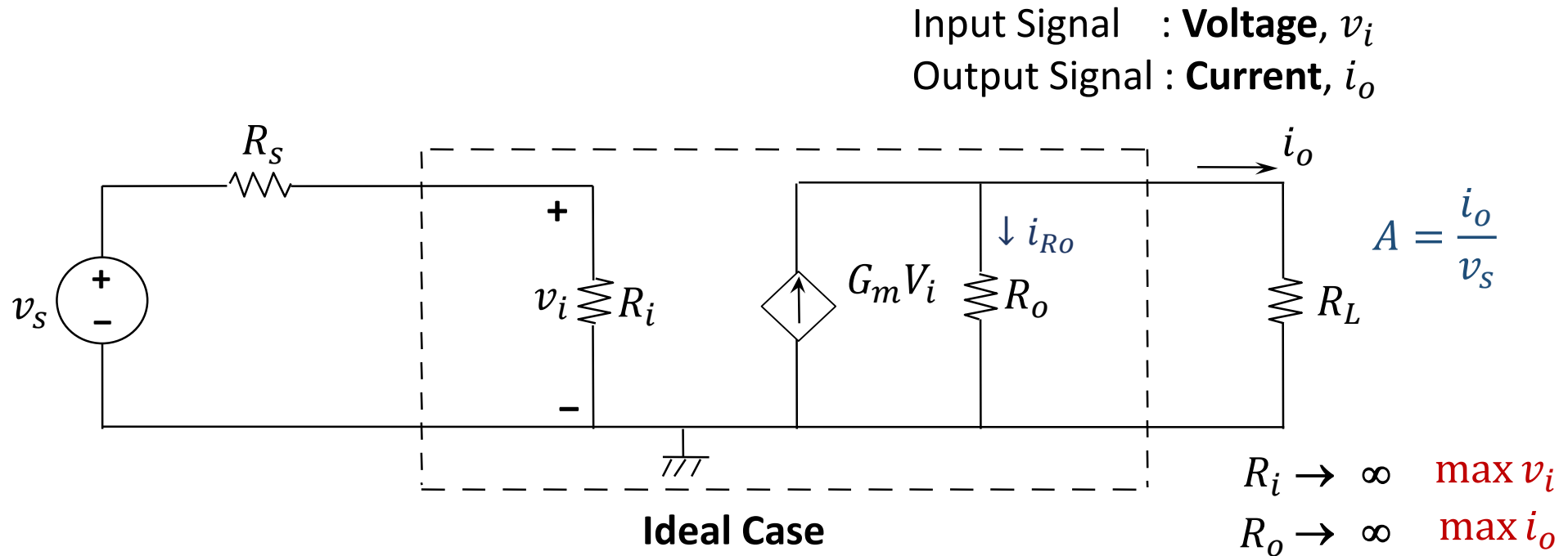



\therefore Feedback network I/O signal:

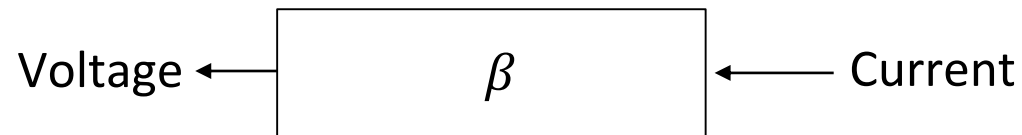

Feedback topology is **current** sampling (at o/p) and **voltage** mixing (at i/p) i.e.
Trans-conductance Amp. with negative feedback is a **Series-Series** Feedback Amplifier.

Series-Series Feedback Amplifier

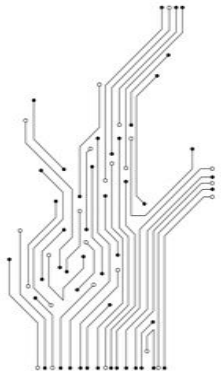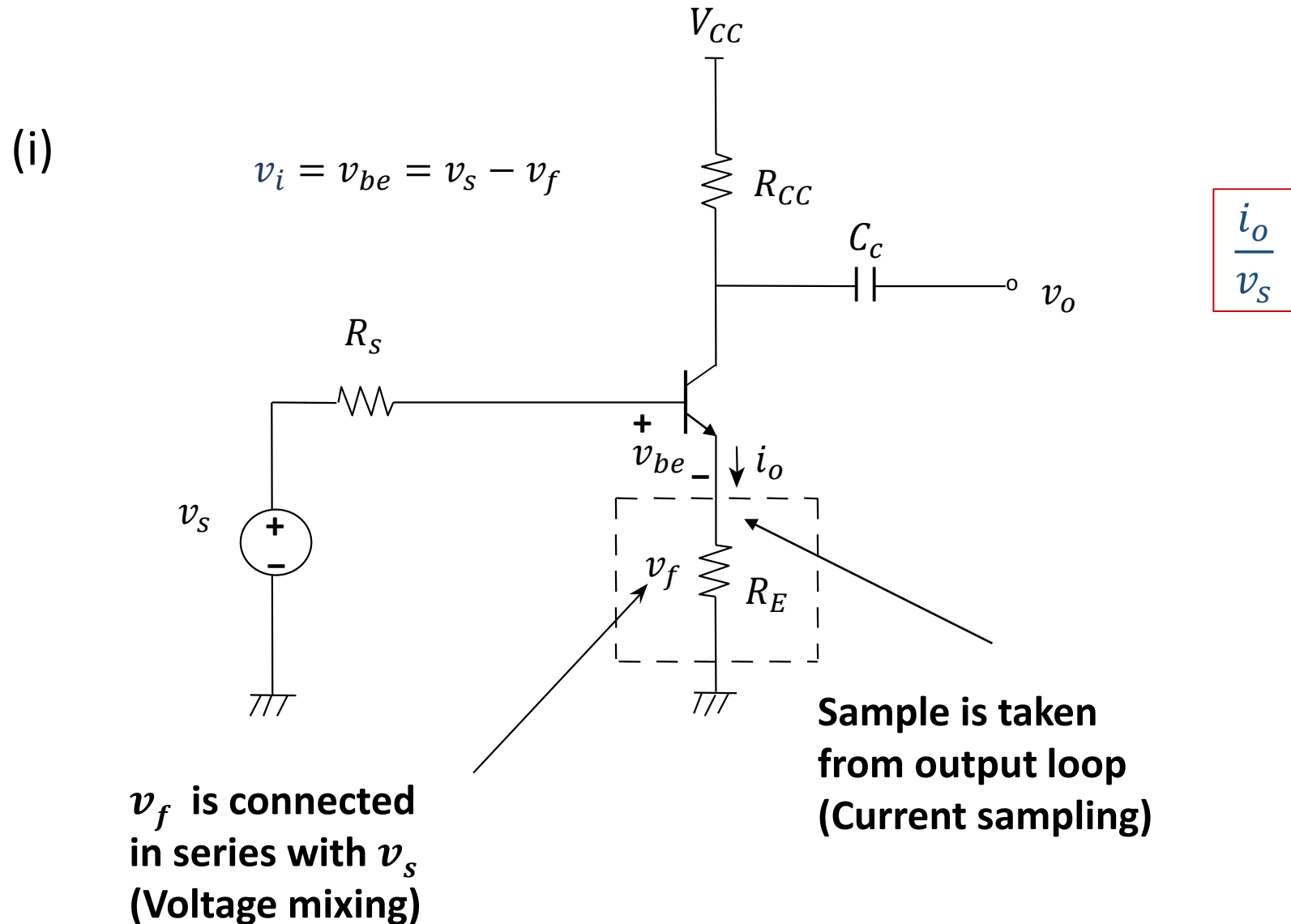
Example 5:
(Voltage Mixing –
Current Sampling)




Series-Series Feedback Amplifier

Example 5: (Contd.)


(Voltage Mixing
- Current
Sampling)

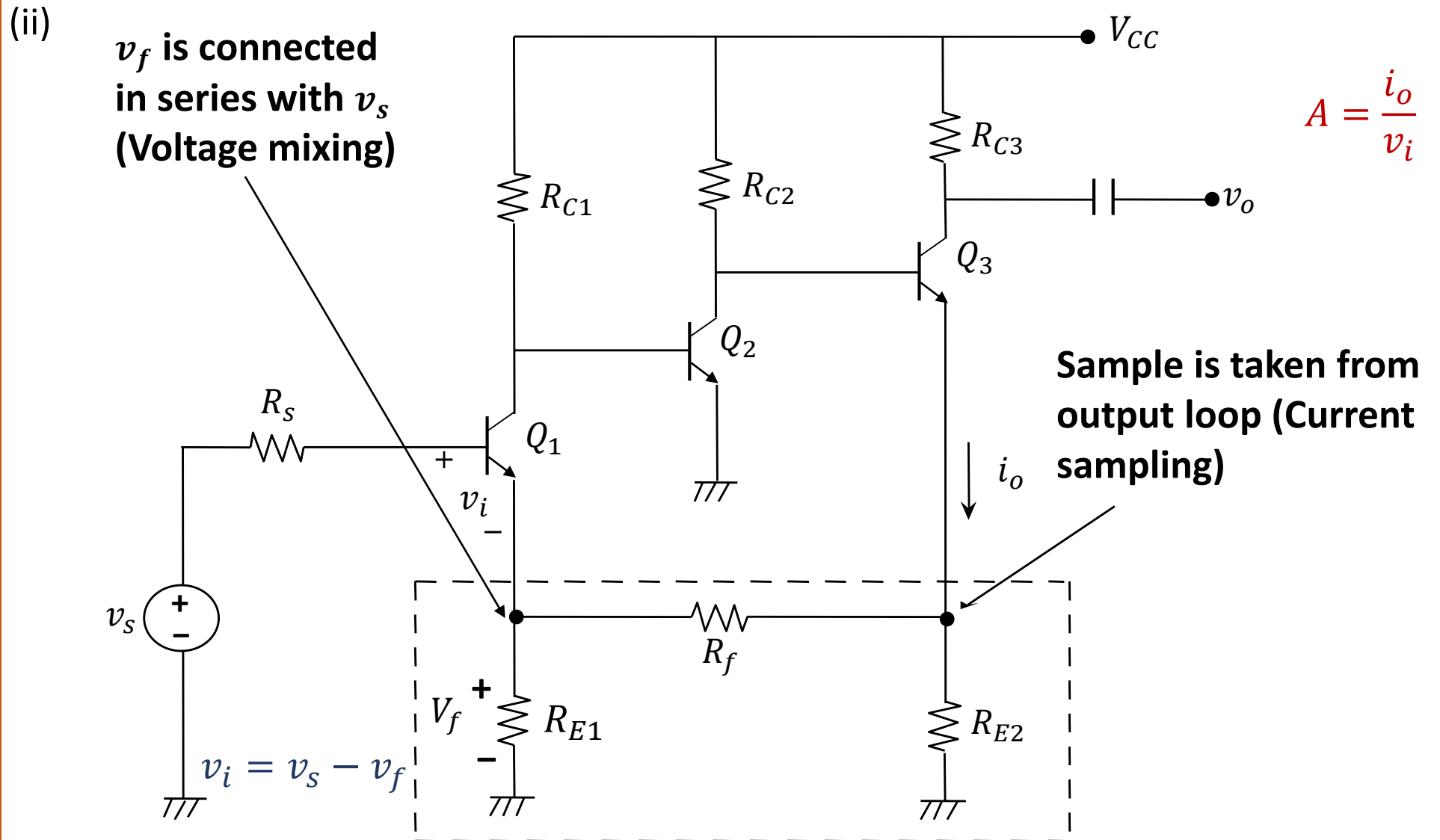

D. Trans-resistance Amplifier

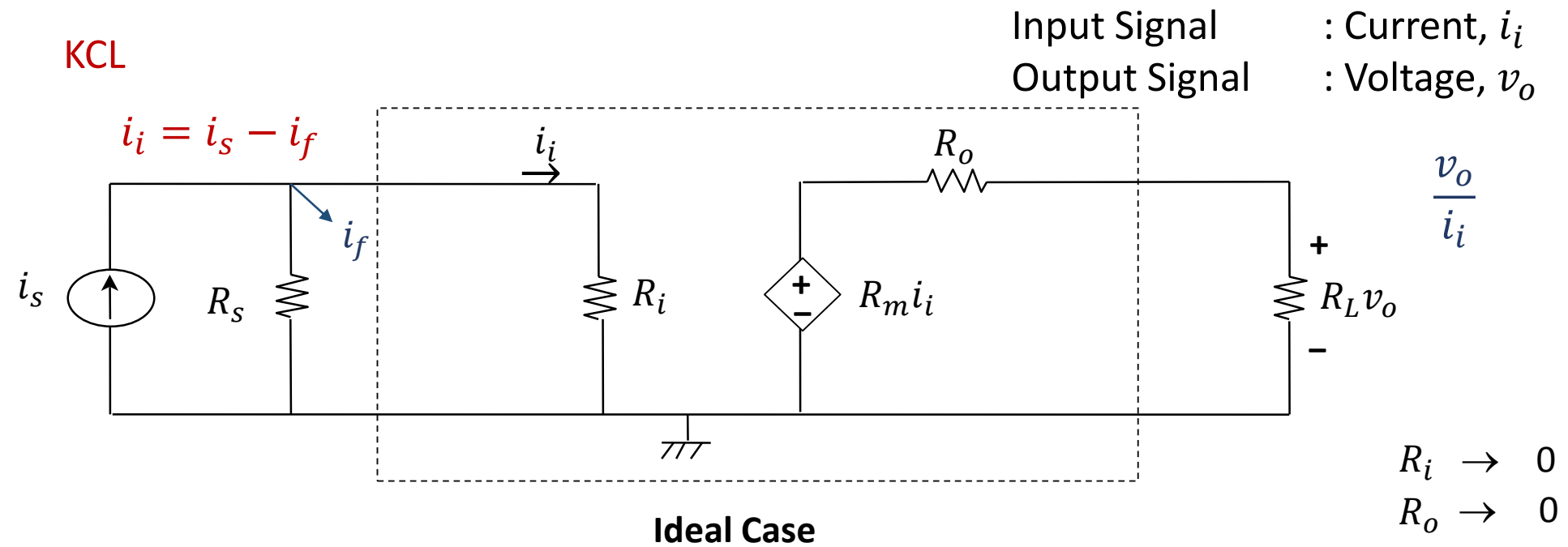

Feedback network I/O signal:

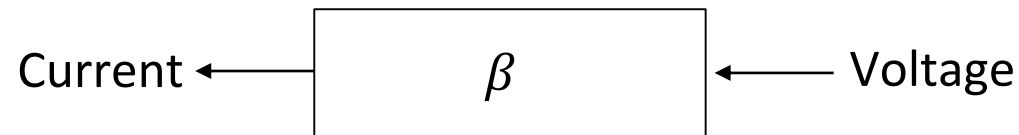


Feedback topology is **voltage** sampling and **current** mixing, i.e., Trans-resistance Amp. with Negative Feedback is Shunt-Shunt Feedback Amplifier.

Shunt-Shunt Feedback Amplifier

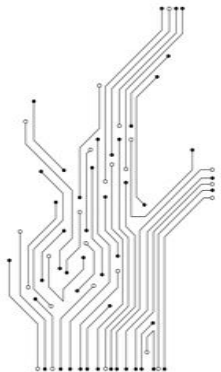
Example 6:

Shunt-Shunt Feedback Amplifier (current mixing – voltage sampling)




(i)

KCL

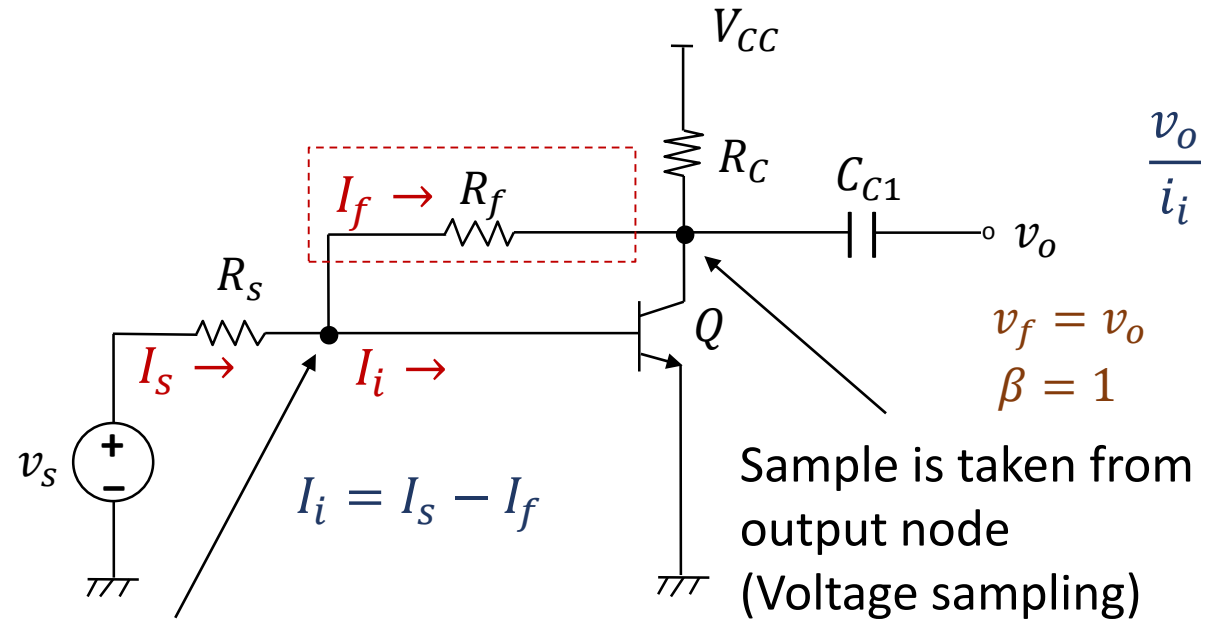

(ii)

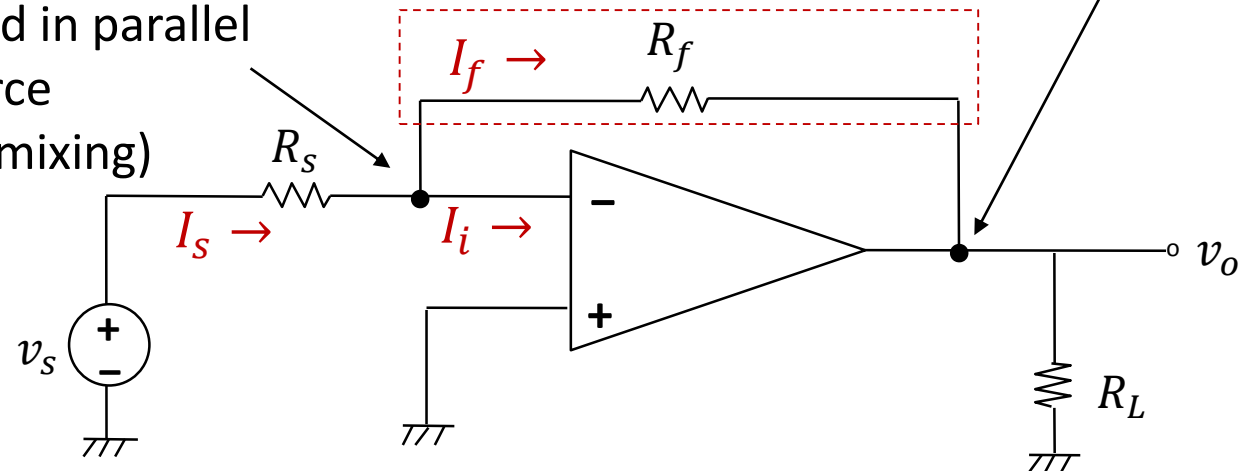Feedback signal is connected in parallel with source (Current mixing)



Input and Output Resistance of an Amplifier

Effect of feedback on Input and Output Resistance of an Amplifier

Change of R_{in} and R_{out} depends on:

- (i) Mixing method
- (ii) Sampling method

To maximise the o/p drive

Series $R \uparrow$

Multiply

For **Series-Mixing** or **Series-Sampling**

$$R_f = R(1 + A\beta)$$

i.e. with feedback, the I/O resistance is increased by a factor equal to the amount of feedback


For **Shunt-Mixing** or **Shunt-sampling**

$$R_f = \frac{R}{(1 + A\beta)}$$


i.e. I/O resistance decreases by a factor equal to the amount of feedback

Parallel $R \downarrow$

Divide

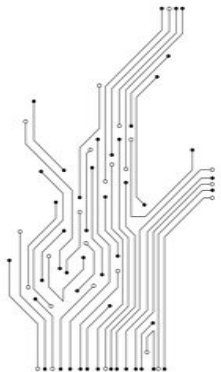

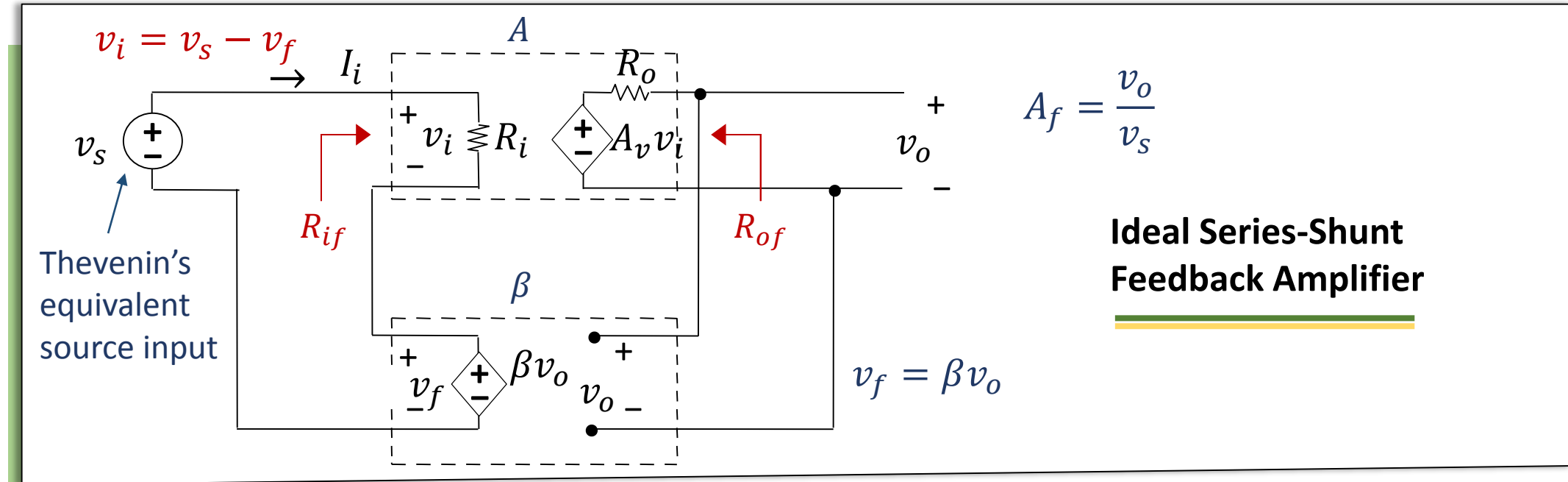
R_{if} and R_{of} of the Series-Shunt Feedback Amplifier



$$R_{if} = R_i(1 + A\beta): \text{Series}$$

$$R_{of} = \frac{R_o}{(1 + A\beta)}: \text{(Shunt)}$$

$$A_f = \frac{A}{1 + A\beta}$$

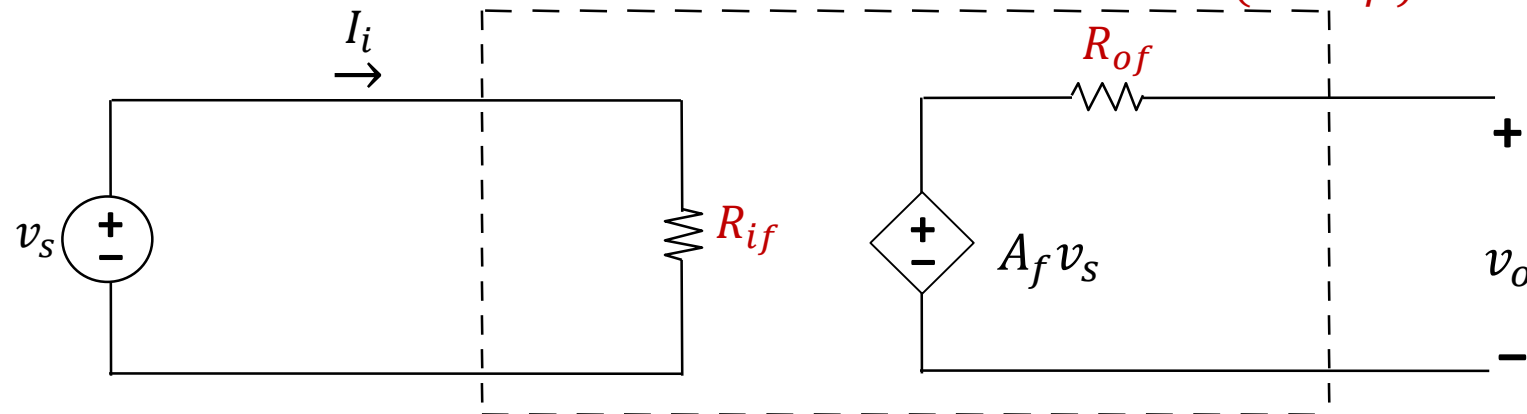

Input Resistance, R_{if}

$$v_s = v_i + v_f$$

But

$$v_f = \beta v_o$$



Ideally

$$v_o = A_v v_i$$

$$\therefore v_s = (1 + A_v \beta) v_i \quad - (1)$$

$$I_i = \frac{v_i}{R_i} \quad - (2)$$
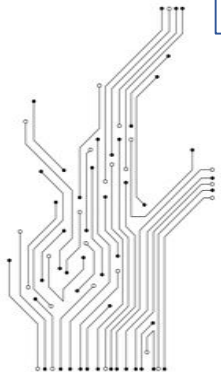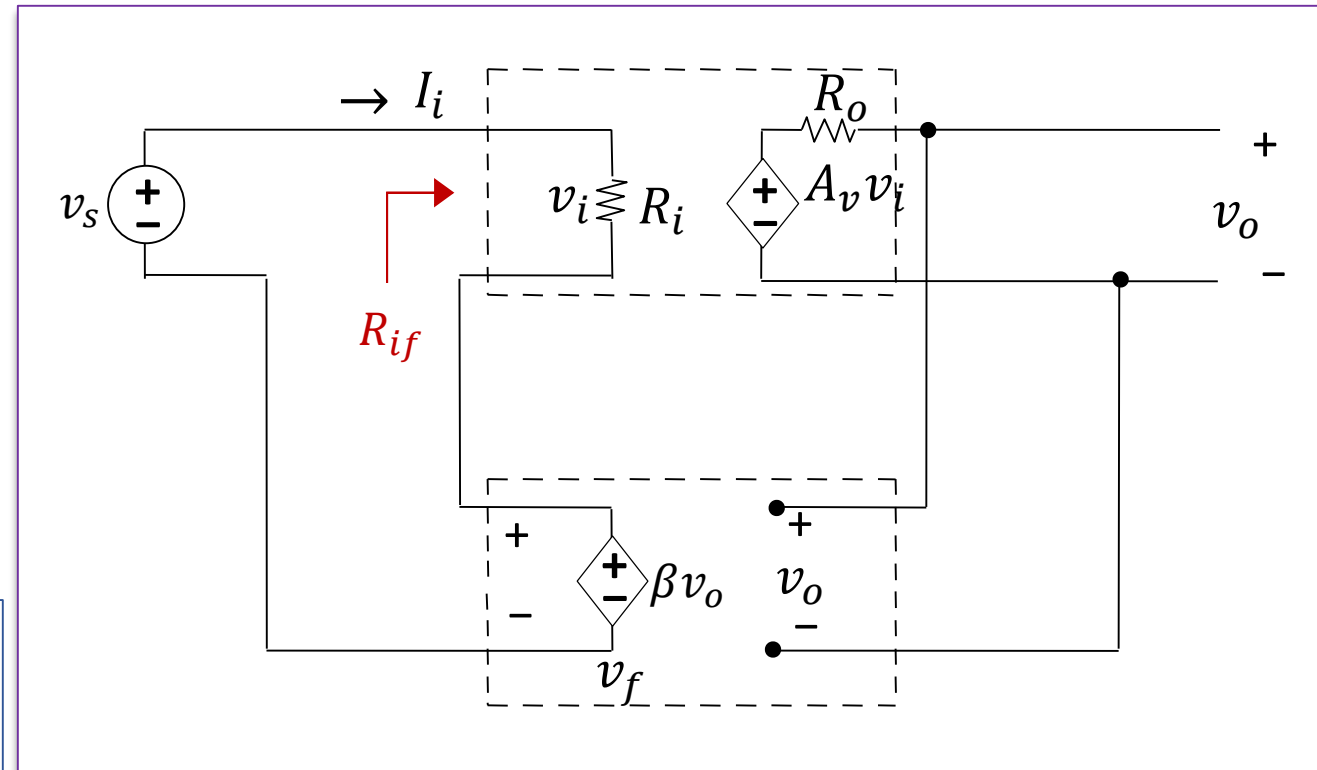
$$\frac{(1)}{(2)}: R_{if} = \frac{v_s}{I_i} = R_i(1 + A_v \beta) \text{ (Series-Mixing)}$$



Output Resistance, R_{of}


(Short v_s and apply v_t at output)

$$v_i = -v_f = -\beta v_t$$


$$v_t = I_t R_o + A_v v_i$$

$$\therefore v_t = I_t R_o - A_v \beta v_t$$

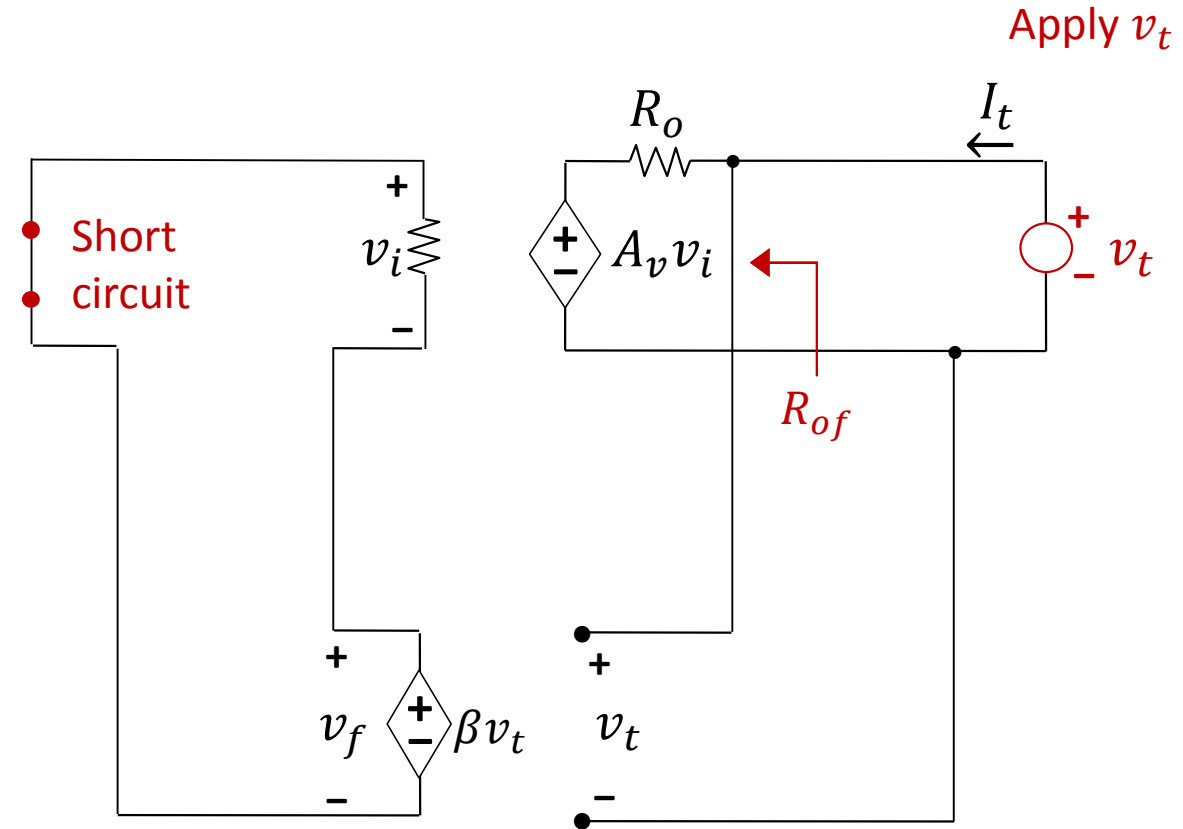
$$\text{or } v_t(1 + A_v \beta) = I_t R_o$$


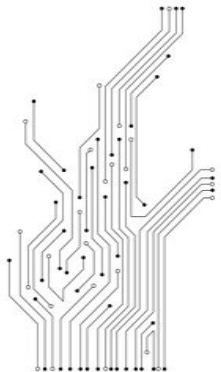
$$\text{Hence } R_{of} = \frac{v_t}{I_t} = \frac{R_o}{(1 + A_v \beta)} \quad (\text{Shunt-sampling})$$



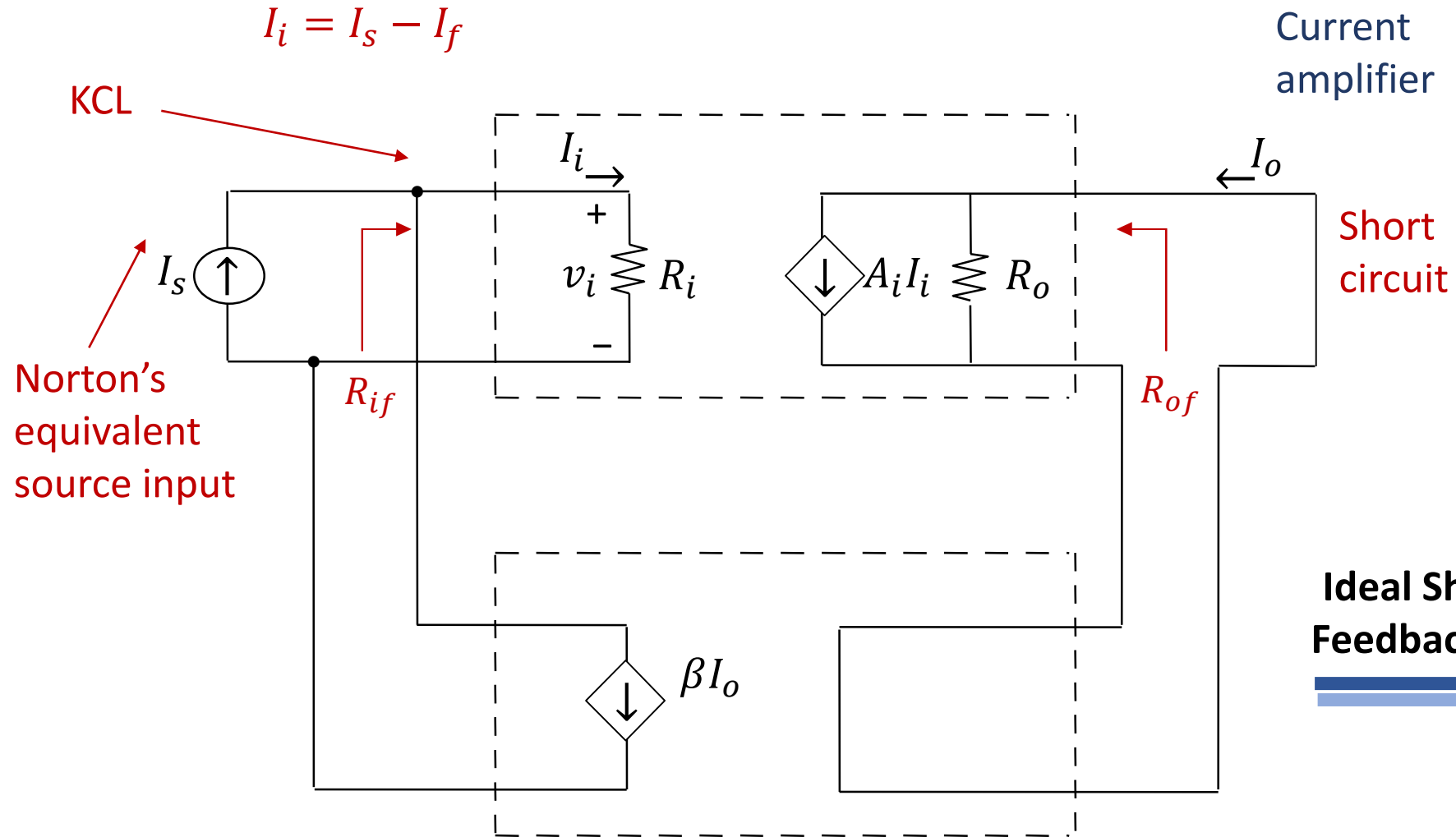R_{if} and R_{of} of the Shunt-Series Feedback Amplifier



Input Resistance, R_{if}

$$I_i = I_s - I_f$$

But ideally:

$$I_f = \beta I_o \text{ and } I_o = A_i I_i$$


$$I_s = I_i(1 + A_i\beta) \quad - (1)$$

$$v_i = I_i R_i \quad - (2)$$


$$(2)/(1)$$

$$\text{Hence } R_{if} = \frac{v_i}{I_s} = \frac{R_i}{(1 + A_i\beta)} \quad (\text{Shunt-mixing})$$

Current amplifier: **Shunt Series**

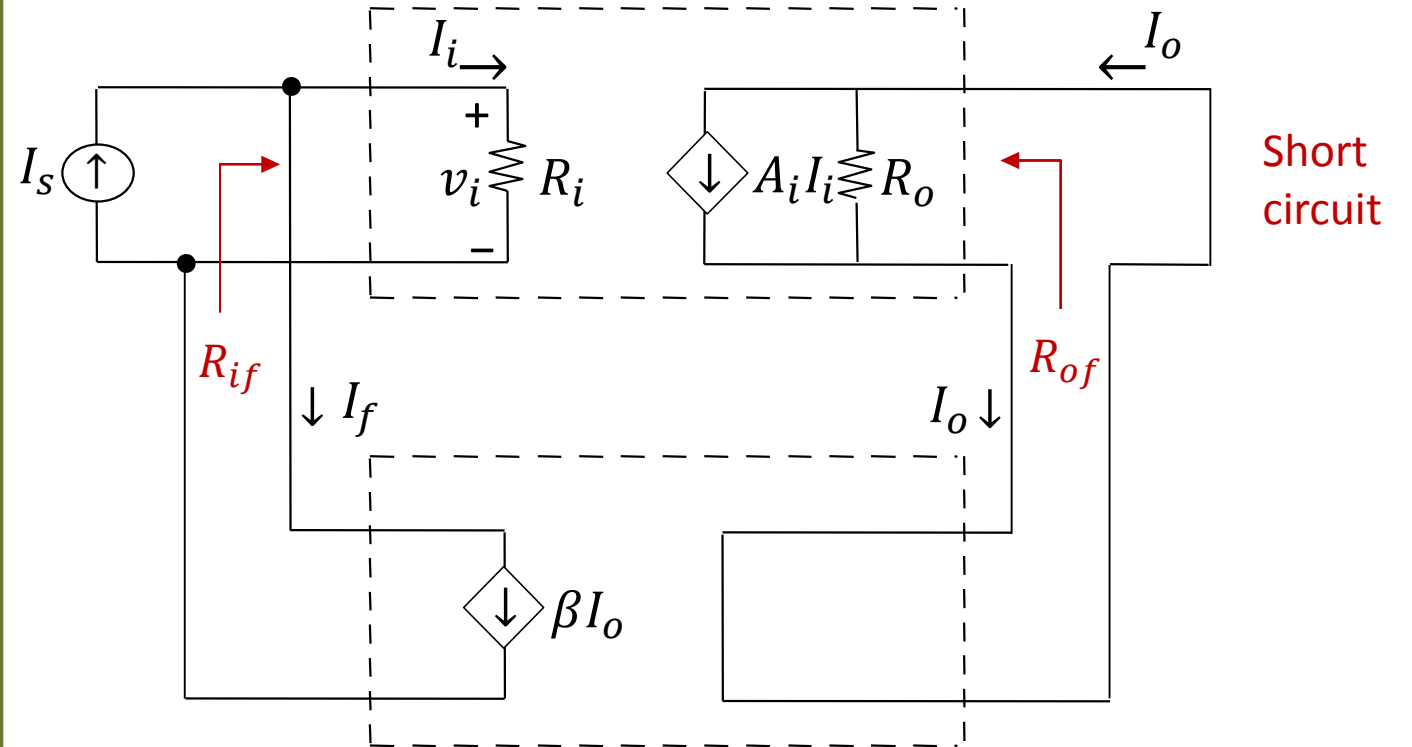

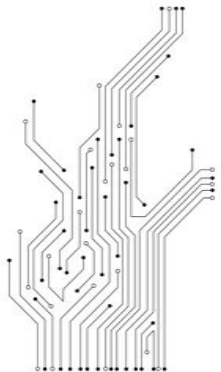Smaller R_{if} to extract more current from the source




Output Resistance, R_{of}

Open Circuit I_s and
Apply V_t at output

$$I_i = -\beta I_t$$


$$v_t = (I_t - A_i I_i) R_o$$

$$v_t = (I_t + A_i \beta I_t) R_o$$

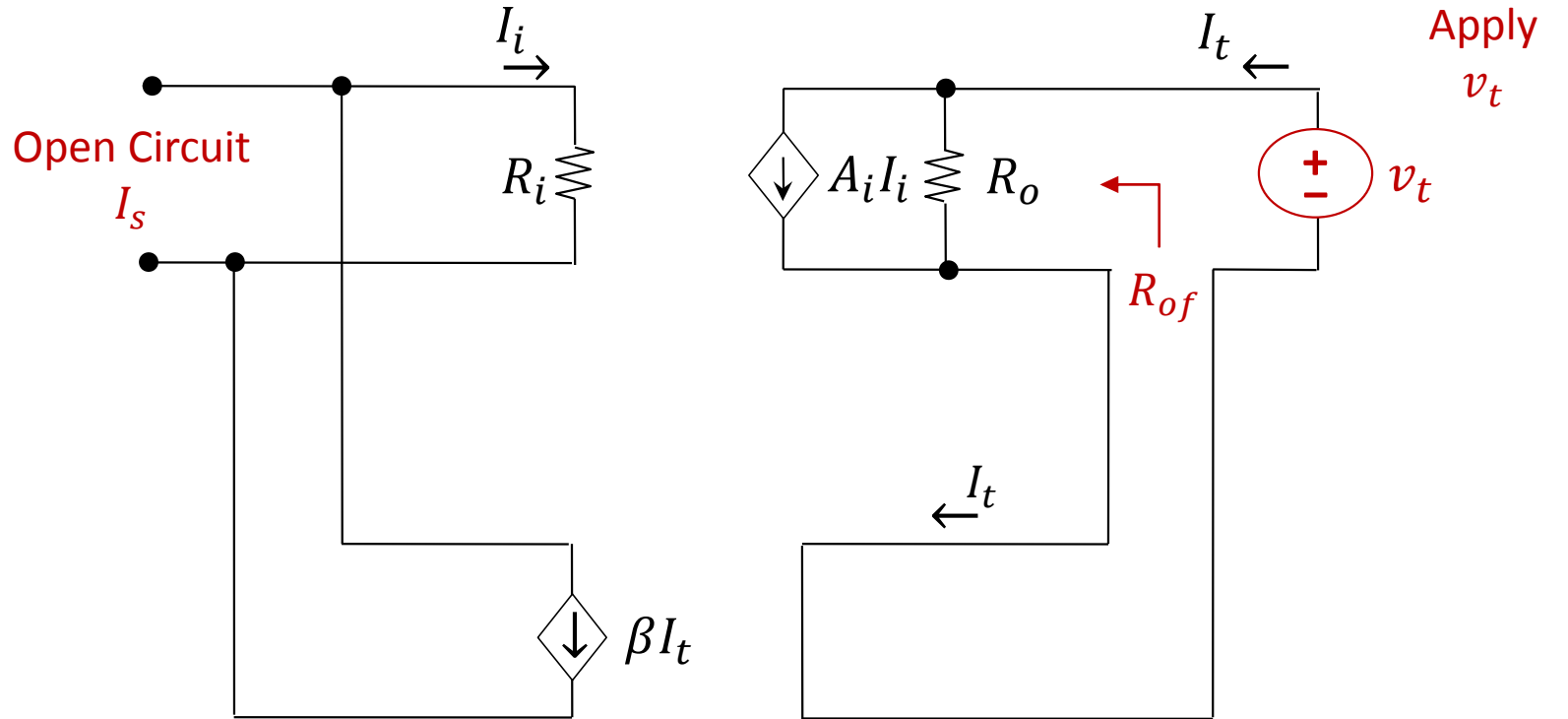


Hence
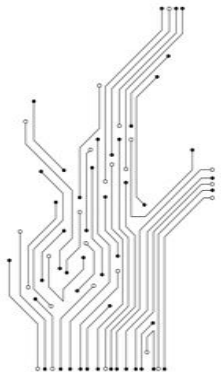
$$R_{of} = \frac{v_t}{I_t} = (1 + A_i \beta) R_o \quad (\text{Series-Sampling})$$



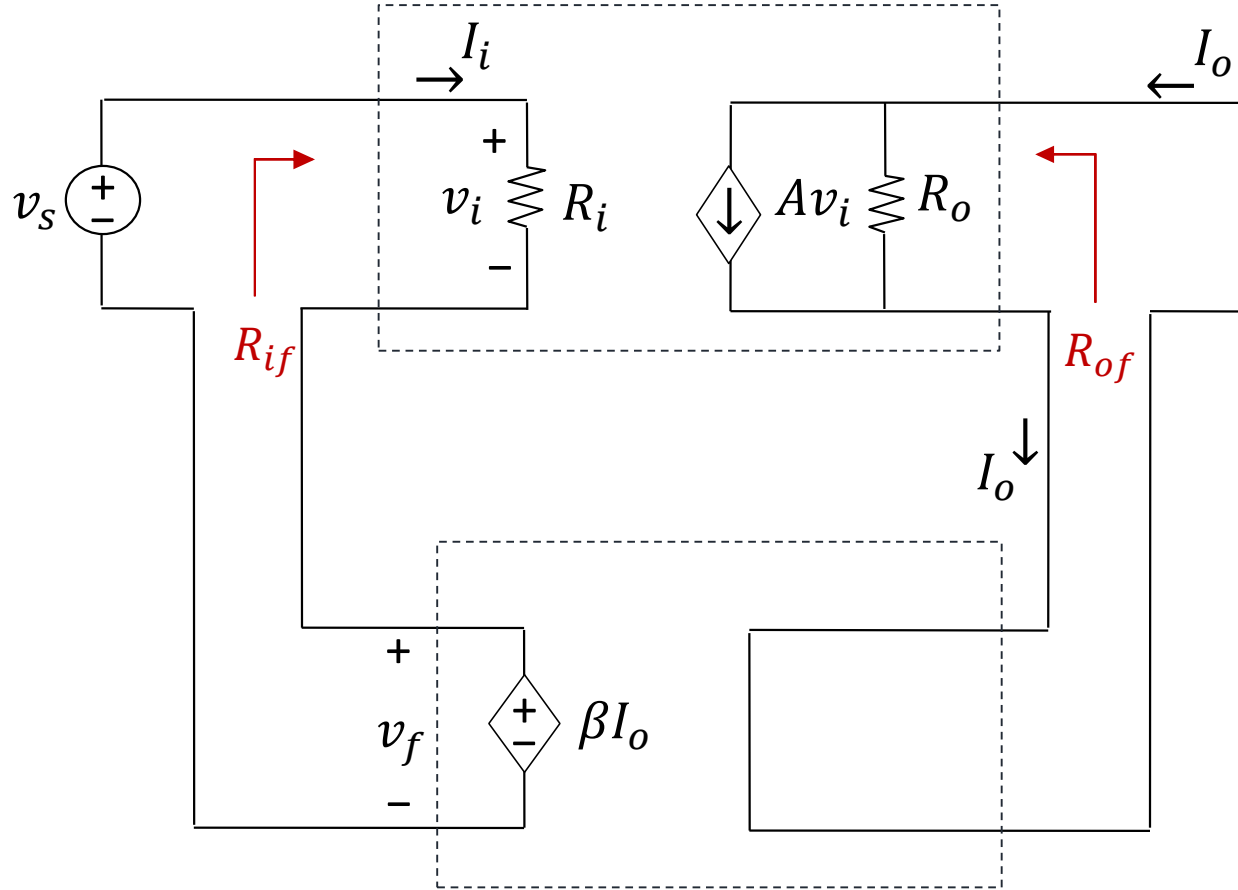R_{if} and R_{of} of the Series-Series Feedback Amplifier




$$\text{Series } R_f = R(1 + A\beta)$$


**Ideal Series-Series
Feedback Amplifier**

Input Resistance, $R_{if} = R_i(1 + A\beta)$

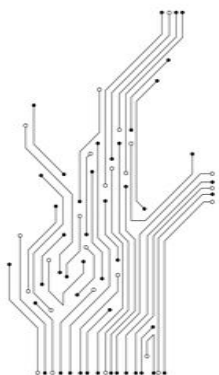Output Resistance, $R_{of} = R_o(1 + A\beta)$



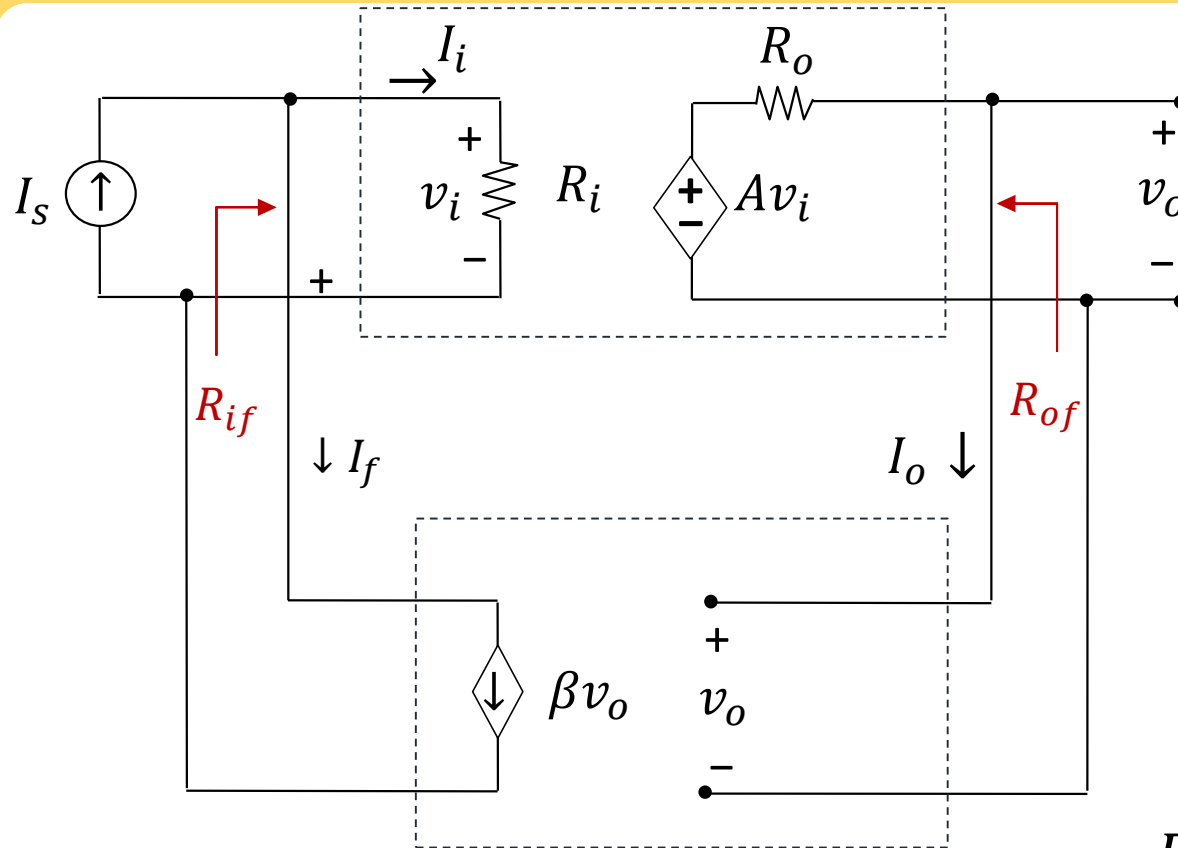R_{if} and R_{of} of the Shunt-Shunt Feedback Amplifier



Shunt (Parallel)

$$R_f = \frac{R}{(1 + A\beta)}$$


**Ideal Shunt-Shunt
Feedback Amplifier**

Input Resistance,

$$R_{if} = \frac{R_i}{(1 + A\beta)}$$

Output Resistance,

$$R_{of} = \frac{R_o}{(1 + A\beta)}$$

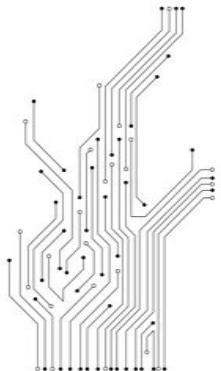

Summary of Feedback Topology


A_v : Voltage Gain

G_m : Trans-conductance

A_i : Current Gain

R_m : Trans-resistance

Type of Amplifier	Voltage Amplifier	Current Amplifier	Trans-conductance Amplifier	Trans-resistance Amplifier
Input Signal	v_i	I_i	v_i	I_i
Output Signal	v_o	I_o	I_o	v_o
Transfer Characteristics	$A_v v_s$	$A_i I_s$	$G_m v_s$	$R_m I_s$
Feedback Topology	Series-Shunt	Shunt-Series	Series-Series	Shunt-Shunt
Feedback Factor β	v_f/v_o	I_f/I_o	v_f/I_o	I_f/v_o
Input Resistance R_{if}	$R_i(1 + A\beta)$	$\frac{R_i}{(1 + A\beta)}$	$R_i(1 + A\beta)$	$\frac{R_i}{(1 + A\beta)}$
Output Resistance R_{of}	$\frac{R_o}{(1 + A\beta)}$	$R_o(1 + A\beta)$	$R_o(1 + A\beta)$	$\frac{R_o}{(1 + A\beta)}$

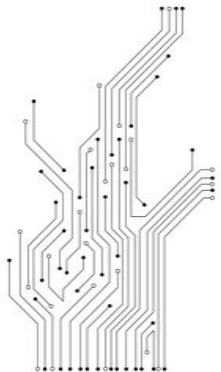

4. Procedures of Feedback Amplifier Analysis

1. Identify the Topology:

(Mixing)
↑

(a) Is the feedback signal X_f a **voltage** or a **current** signal? i.e., is X_f applied in **Series** or in **Shunt** with external excitation?

(b) Is the sampled signal X_o a **voltage** or a **current** signal? i.e., is X_o taken at the **output voltage node** or from the **output current loop**?

↓
(Sampling)

2. **Separate** feedback network from basic amplifier, A , and find Input and Output resistance, $R_{\beta i}$ and $R_{\beta o}$, of feedback circuit and also, feedback factor, β , from the feedback circuit.


(Contd.) →

4. Procedures of Feedback Amplifier Analysis (Contd.)


3. **Draw** the basic amplifier circuit without feedback network but with $R_{\beta i}$ and $R_{\beta o}$ obtained in step 2. This new basic amplifier is called A' .

4. Use a **Thevenin's** equivalent source input if the feedback signal X_f is a **voltage** or a **Norton's** equivalent source if X_f is a **current**.


Thevenin's
equivalent circuit

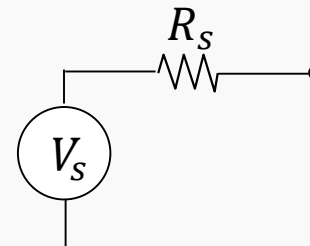

Norton's
equivalent circuit

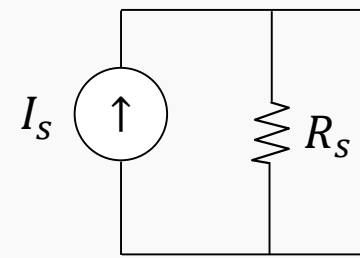

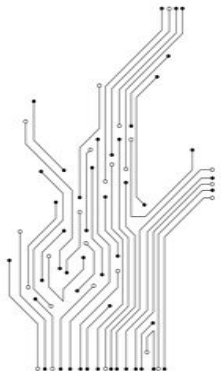5. Replace each active device in A' circuit by a proper model (i.e. h-parameter or hybrid- π model) and evaluate amplifier gain A' of the A' circuit with $R_{\beta i}$ and $R_{\beta o}$ included. Also, find the Input and Output resistance of the A' circuit (R'_i and R'_o).



4. Procedures of Feedback Amplifier Analysis (Contd.)

6. From amplifier gain, A' with $R_{\beta i}$ and $R_{\beta o}$ and feedback factor, β , find A_f , R_{if} and R_{of} .

$$A_f = \frac{A'}{1 + A'\beta}$$

New gain with $R_{\beta i}$ and $R_{\beta o}$
(Loading effect)

$$R_{if} = (1 + A'\beta)R'_i$$
$$R_{if} = R'_i / (1 + A'\beta)$$

New I/P
impedance

(Series mixing - Voltage)


(Shunt mixing - Current)

$$R_{of} = (1 + A'\beta)R'_o$$
$$R_{of} = R'_o / (1 + A'\beta)$$

New O/P
impedance

(Series sampling - Current)

(Shunt sampling - Voltage)

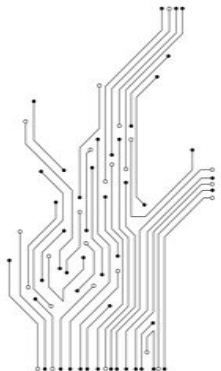


Feedback Network β

Input and Output Resistance ($R_{\beta i}$ and $R_{\beta o}$) of the Feedback Network β


First, separate the whole **Feedback** Amplifier into **TWO** blocks, the basic amp **A** and the **Feedback** network. Apply the following rules to find $R_{\beta i}$ and $R_{\beta o}$.

Input resistance of Feedback circuit, $R_{\beta i}$ Open circuit

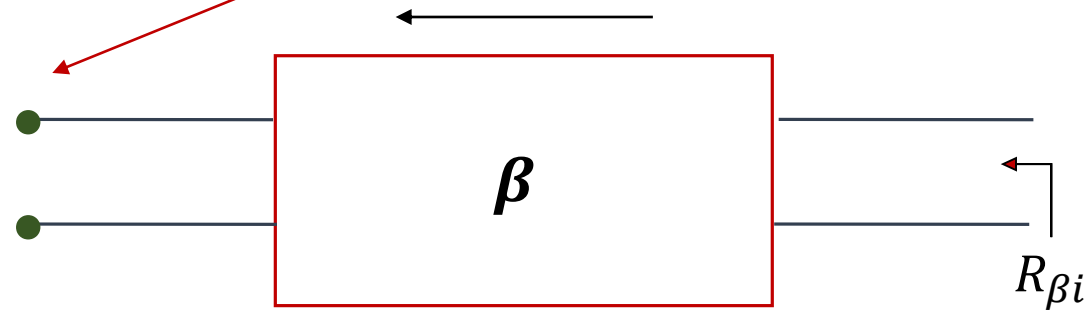1. For Voltage (Series) mixing, **SEVER** the output node of the **Feedback** circuit.




Series-Mixing

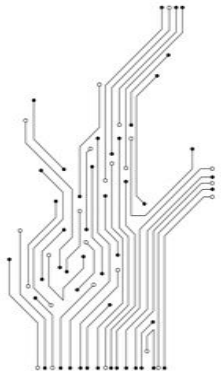


Feedback Network β

Input and Output Resistance ($R_{\beta i}$ and $R_{\beta o}$) of the Feedback Network β

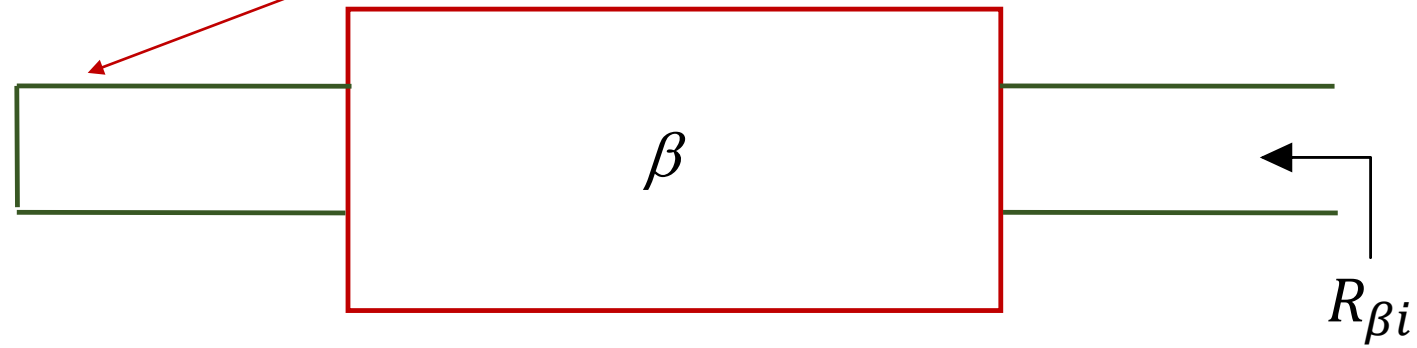2. For Current (Shunt) mixing, SHORT the output node of Feedback circuit.




Shunt-Mixing

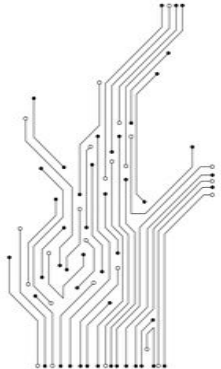


Output Resistance of Feedback Circuit, $R_{\beta o}$

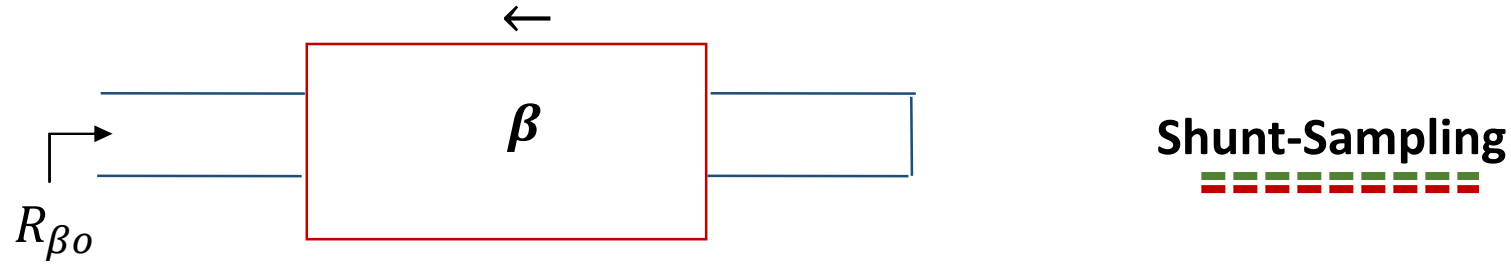1. For voltage (**Shunt**) sampling, **SHORT** the input node of **Feedback** circuit.



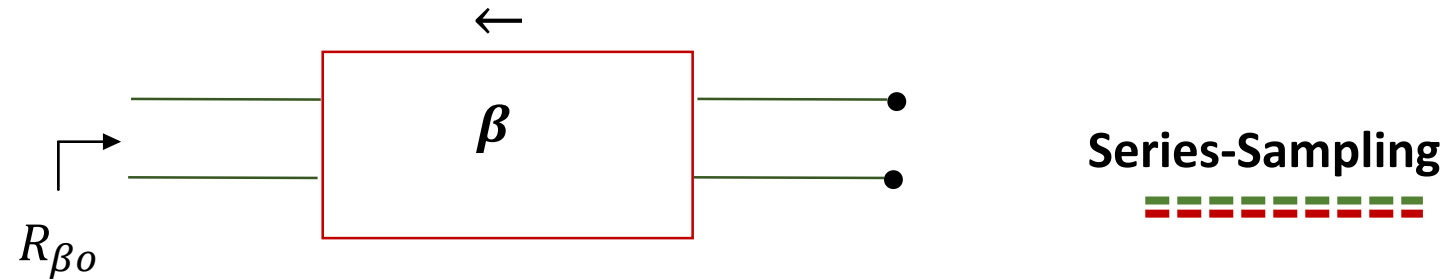2. For current (**Series**) sampling, **SEVER** the input node of **Feedback** circuit.




A simple rule to remember:

*"If connection is SHunt, SHort it,
if connection is SEries, SEver it."*


Practical Series-Shunt Feedback Amplifier

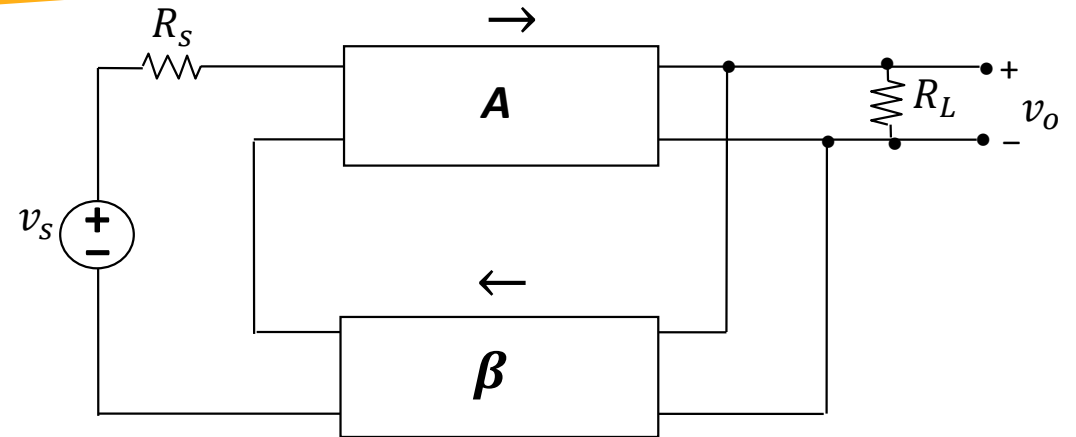Example 7:


1 Separate the **A** block and the **Feedback** block:



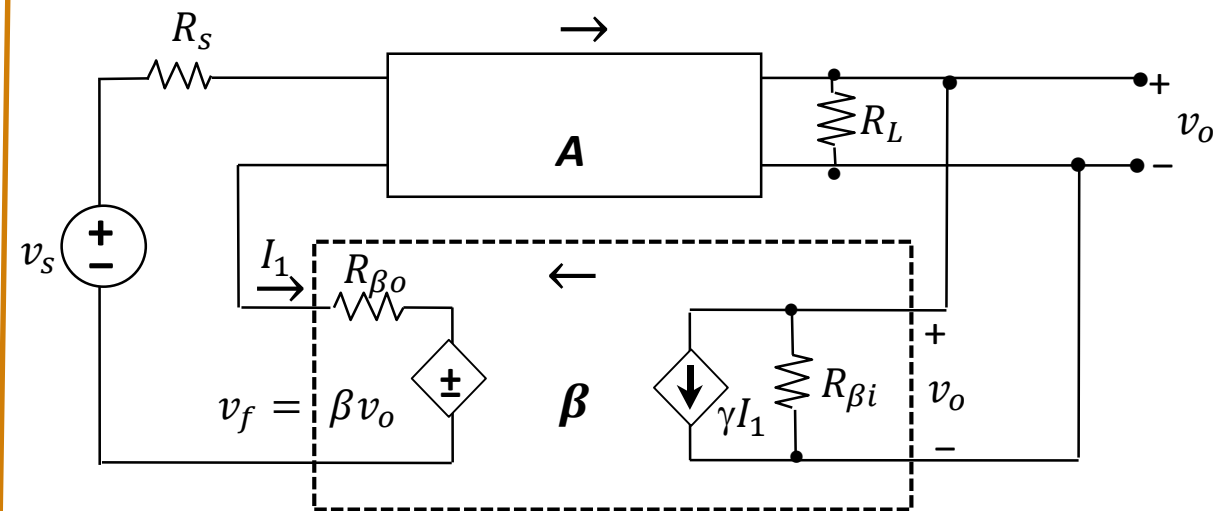2 Find $R_{\beta i}$ and $R_{\beta o}$ of **Feedback** block:



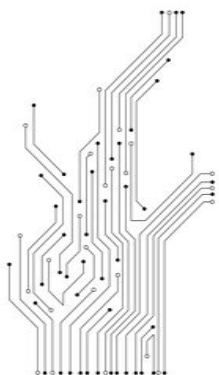*Compare this with the ideal **Series-Shunt Feedback** amplifier structure.




Practical Series-Shunt Feedback Amplifier (Contd.)

Example 7:

Include $R_{\beta i}$ and $R_{\beta o}$ with the **A** Block:

3

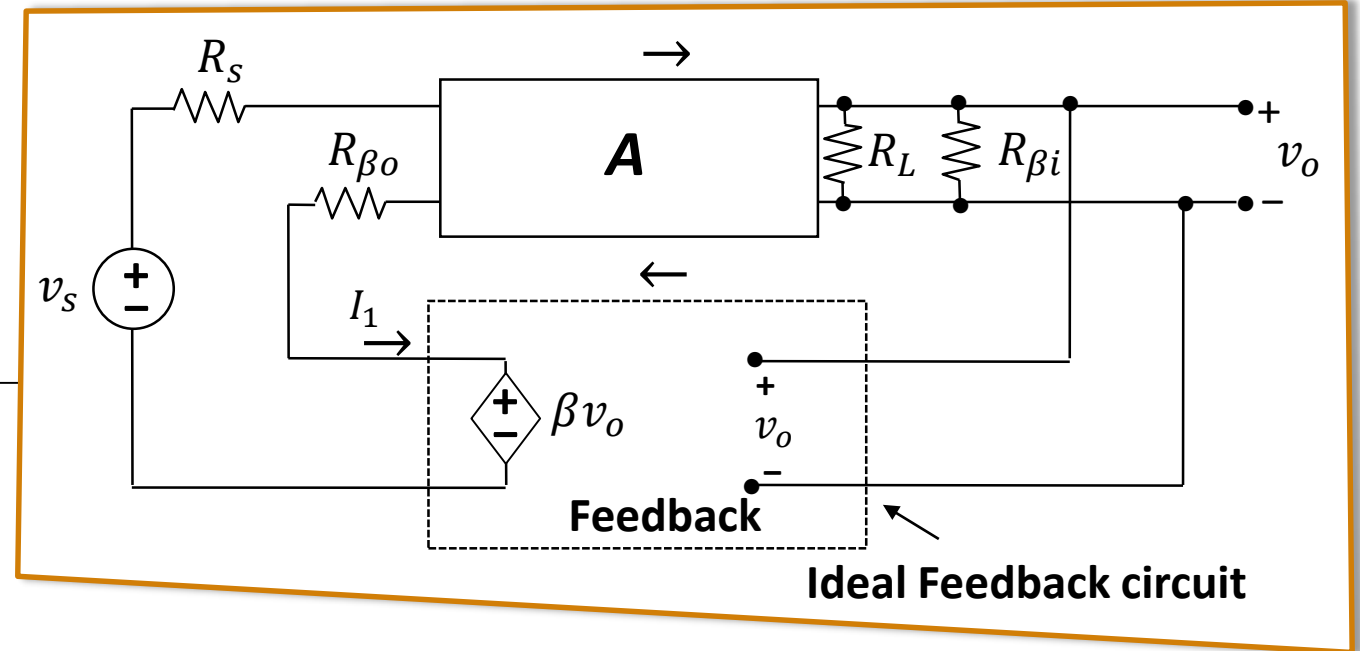


Note that the current dependent source γI_1 is neglected.

In fact, β is the forward transmission of the **Feedback** network and γ is the reverse transmission of the **Feedback** network.




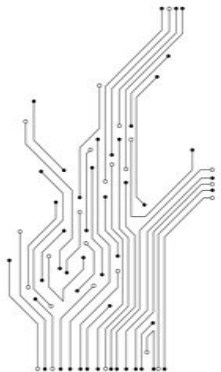This reverse transmission, in comparison to the much larger forward transmission of the basic amp **A**, is very negligible.




Practical Series-Shunt Feedback Amplifier (Contd.)

Example 7:

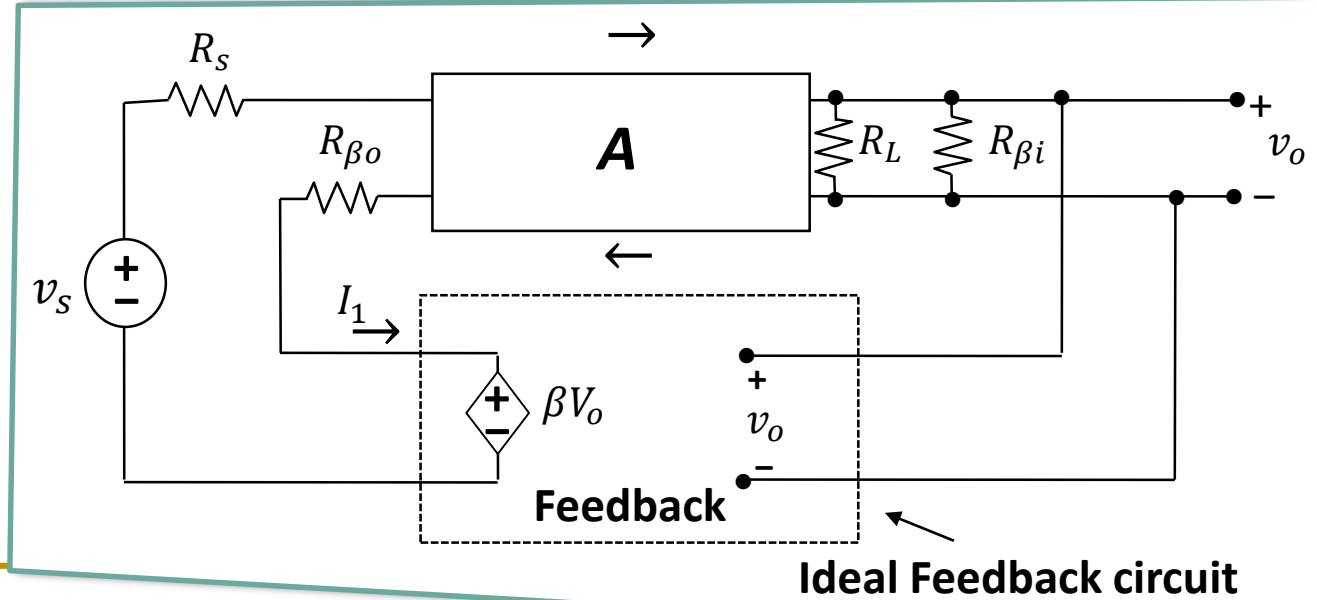

$R_{\beta i}$ and $R_{\beta o}$ are the loading effects of the feedback network **Feedback** on the basic amplifier A .

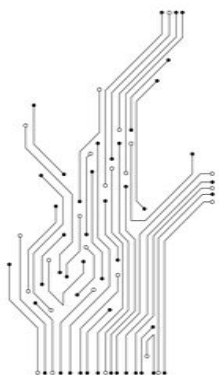They are obtained by destroying the feedback, i.e. while looking into the appropriate port (input port for $R_{\beta i}$ and output port for $R_{\beta o}$), the other port is either sever or short so as to destroy the feedback.




Equivalent Circuit of Feedback Network with $R_{\beta i}$ and $R_{\beta o}$

- 1 Output of **Feedback** circuit is **voltage**

Thevenin's equivalent circuit.


$$v_f = v_{R_{\beta o}} + \beta v_o$$

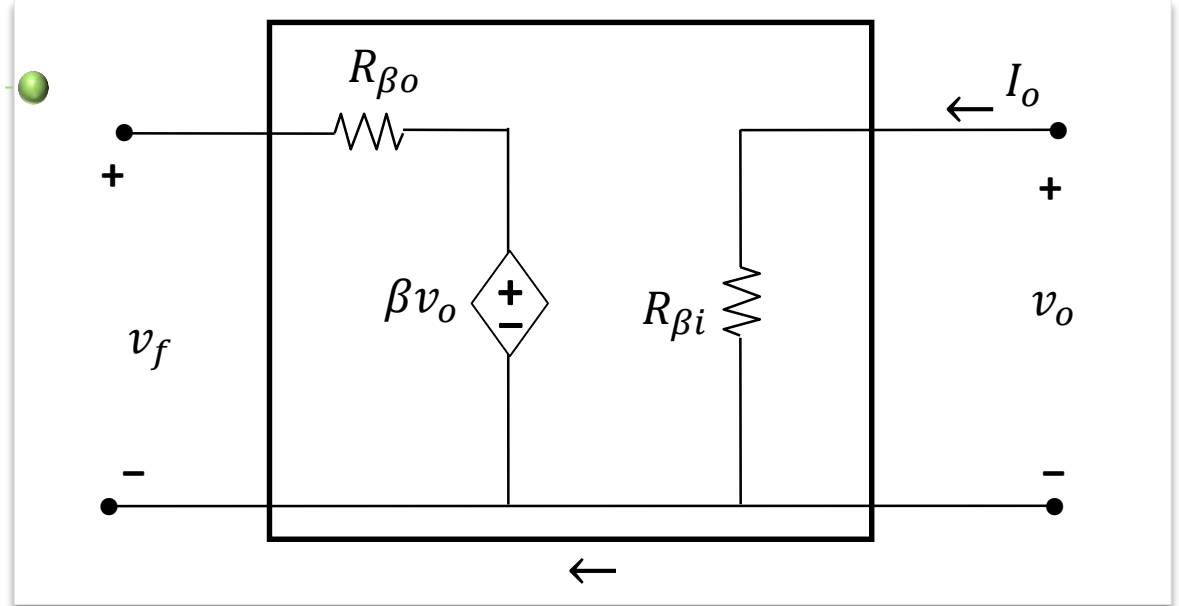

- 2 Output of **Feedback** circuit is **current**

Norton's equivalent circuit.

$$I_f = I_{R_{\beta o}} + \beta I_o$$

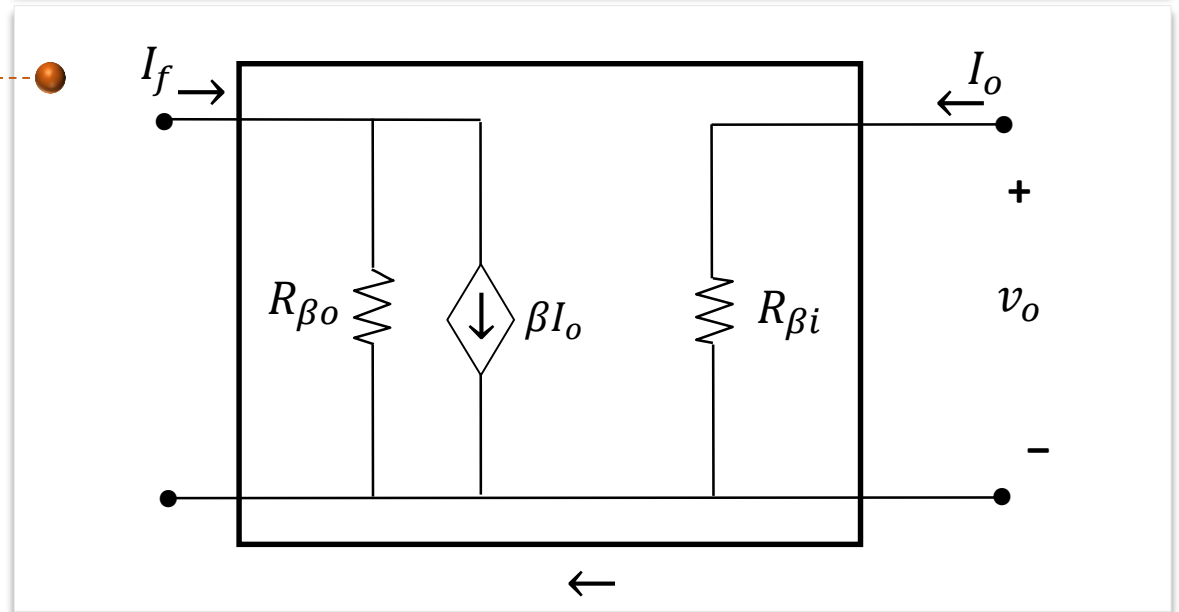


5. Loading Effect of Feedback Network on Basic Amplifier A



Basic Amplifier **A** with Feedback Network resistance $R_{\beta i}$ and $R_{\beta o}$

5.1 - Input of **A** circuit with $R_{\beta o}$

Shunt-mixing

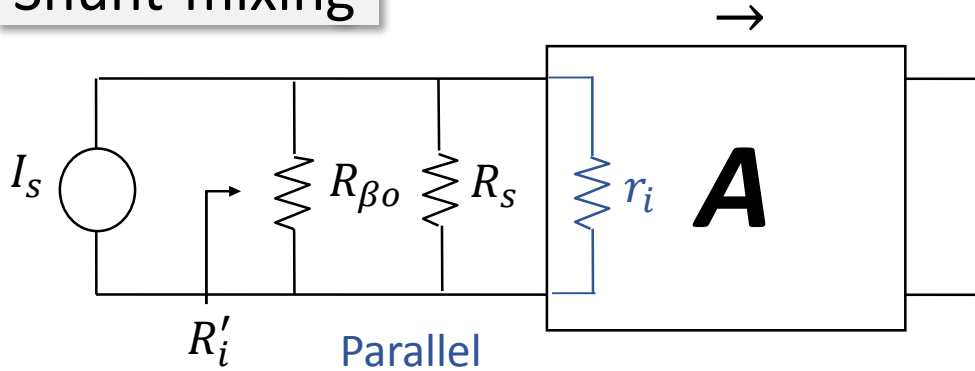

Series-mixing

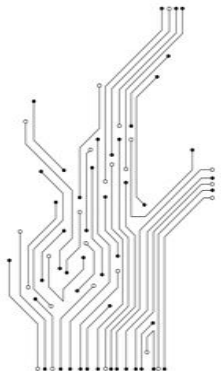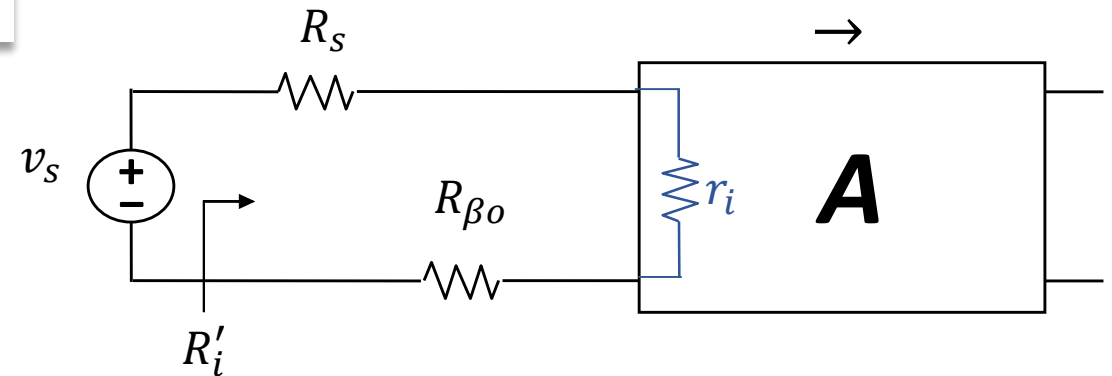


5. Loading Effect of Feedback Network on Basic Amplifier A


Basic Amplifier **A** with Feedback Network resistance $R_{\beta i}$ and $R_{\beta o}$

5.2 - Input of **A** circuit with $R_{\beta i}$

Shunt-sampling

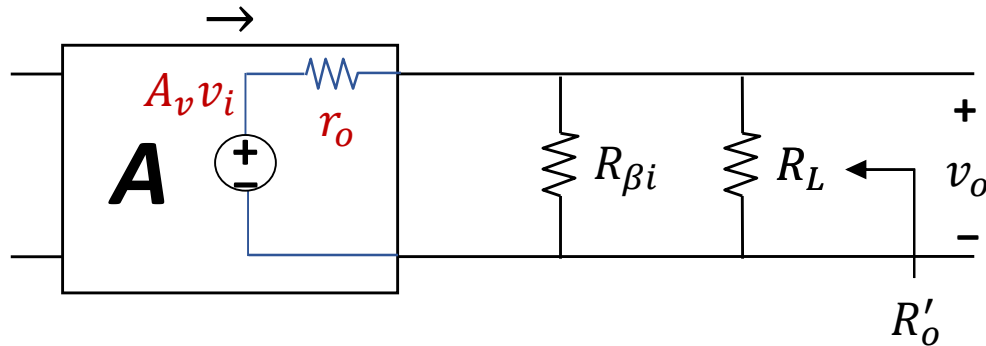


Series-sampling

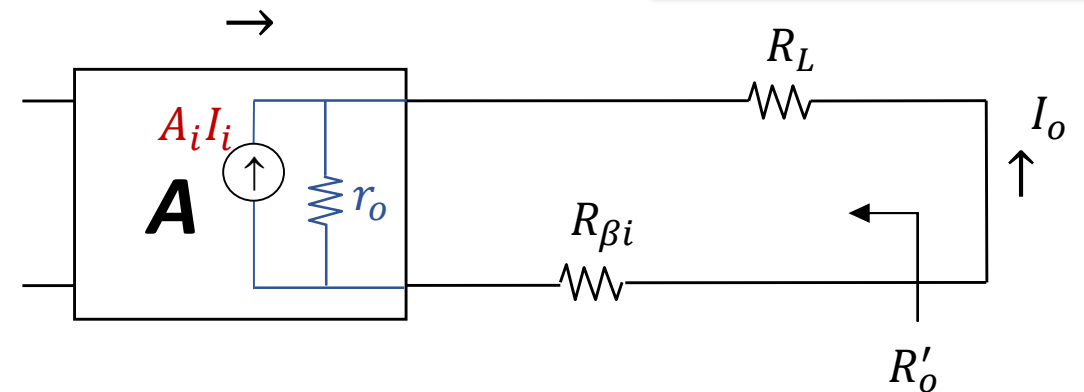

Series-Shunt Feedback Amplifier

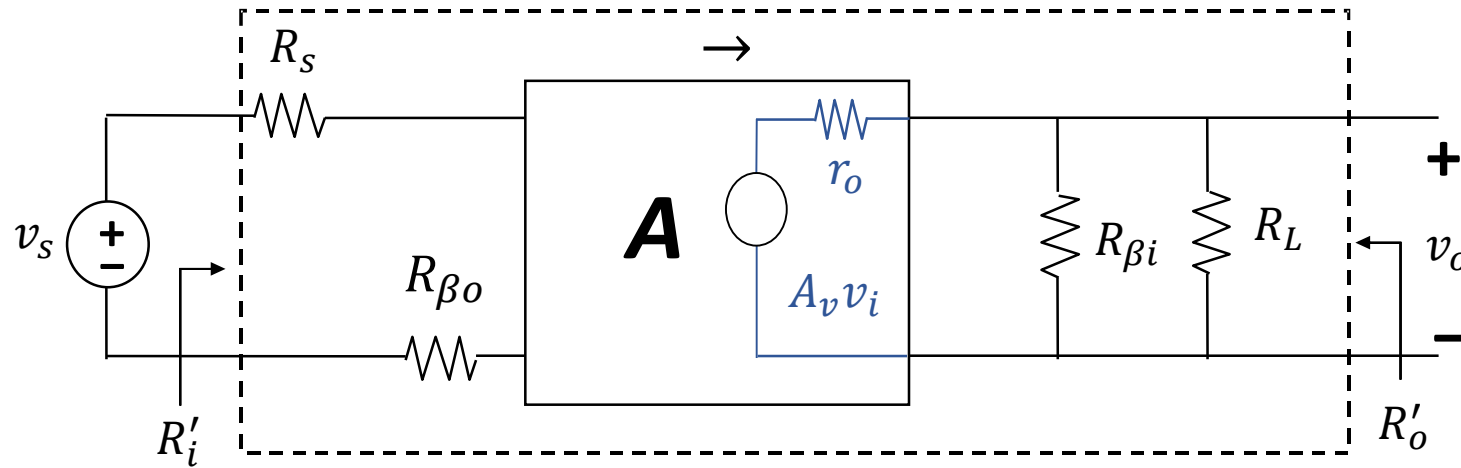
Basic Amplifier **A** with $R_{\beta i}$ and $R_{\beta o}$:



New gain, $A' = \frac{v_o}{v_s}$ New voltage gain with $R_{\beta o}$ and $R_{\beta i}$.

Loading effect

$$\beta = \frac{v_f}{v_o}$$

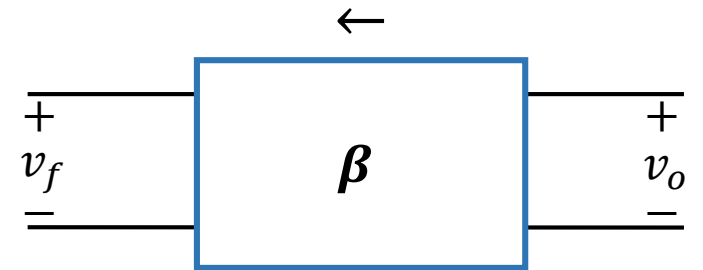

Feedback network β without $R_{\beta i}$ and $R_{\beta o}$

Series-Shunt Feedback Amplifier (Contd.)

New open-loop gain, A' , considering the loading effect ($R_{\beta i}, R_{\beta o}$)


Closed-loop gain:
$$A_f = \frac{A'}{1 + A'\beta}$$

Input-Output Resistance, R_{if} and R_{of}

$$R_{if} = (1 + A'\beta)R'_i \text{ (Series-mixing)}$$


$$R_{of} = \frac{R'_o}{(1 + A'\beta)} \text{ (Shunt-sampling)}$$

The amount of feedback = $(1 + A'\beta)$

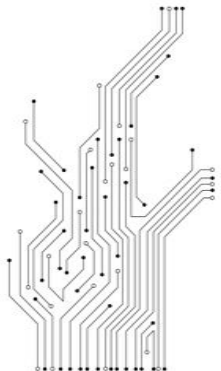

Analysis of a Feedback Amplifier

Example 8:

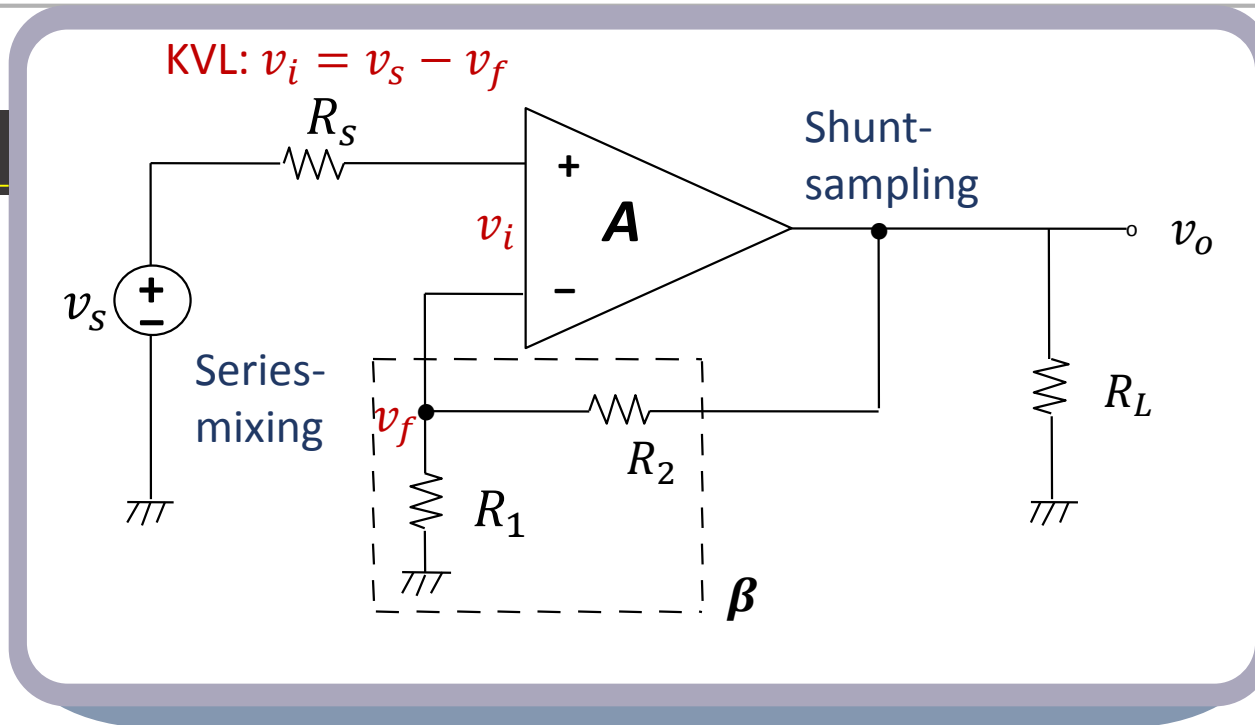

Topology check

1


From **Feedback** circuit, sampling is taken from output node (v_o) => Voltage sampling (Shunt-sampling).



Feedback signal is fed into Op-amp in series with external source, (v_s) => Voltage mixing (Series-mixing).




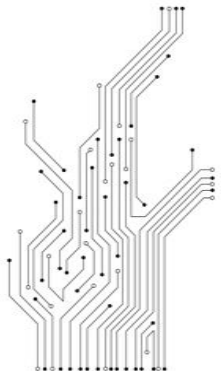\therefore This is a **Series-Shunt Feedback** amplifier.



Analysis of a Feedback Amplifier (Contd.)


Example 8:

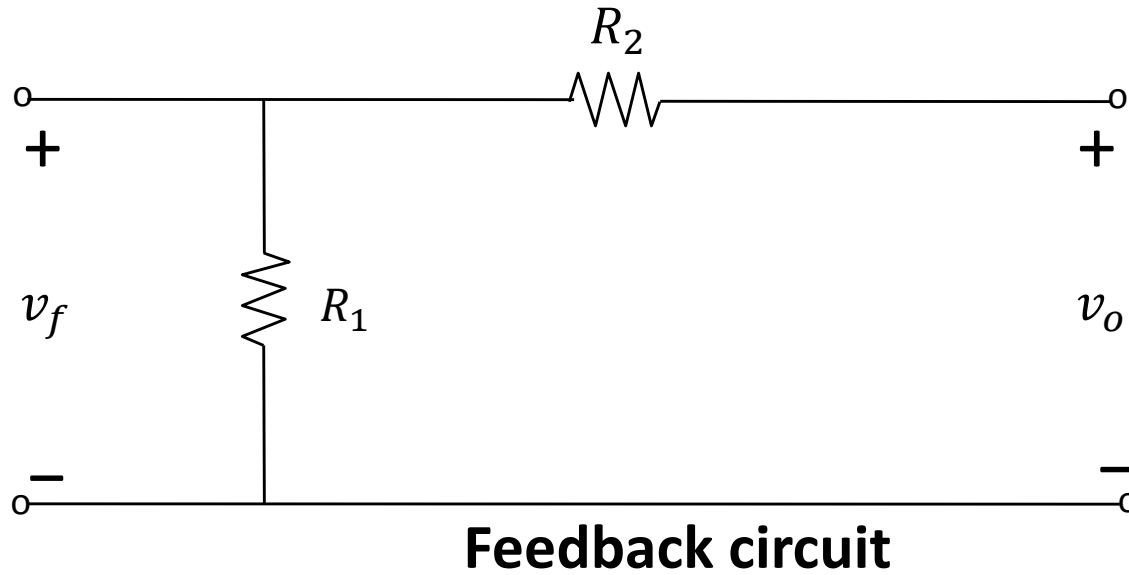


Separate feedback circuit and find β , $R_{\beta i}$ and $R_{\beta o}$.

2


$$v_f = \frac{R_1}{R_1 + R_2} v_o$$

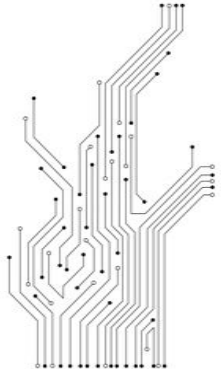
$$\beta = \frac{v_f}{v_o} = \frac{R_1}{R_1 + R_2}$$



Analysis of a Feedback Amplifier (Contd.)


Example 8:

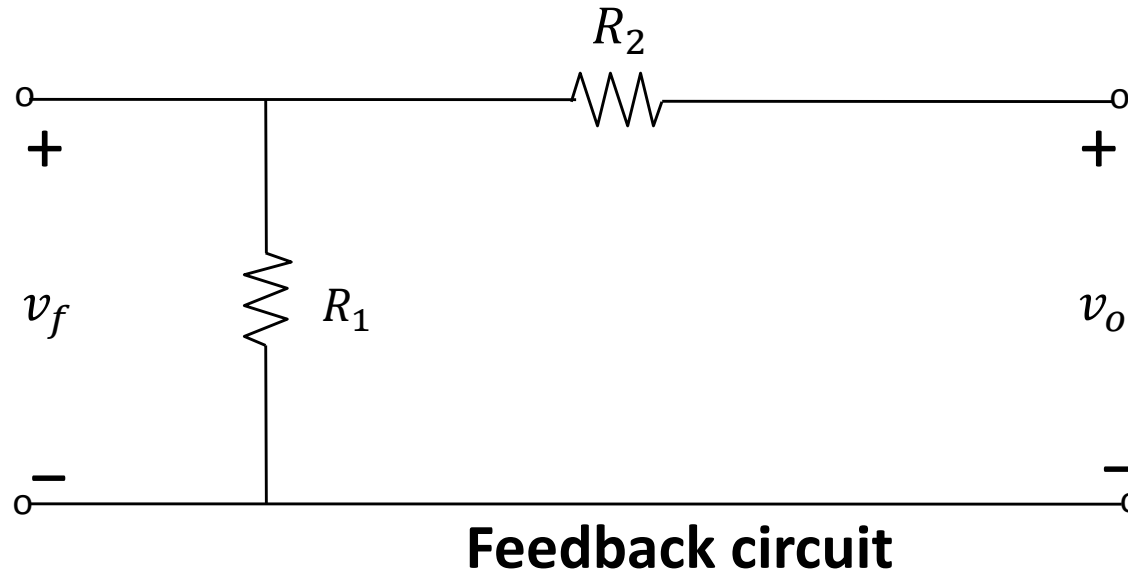


Separate feedback circuit and find β , $R_{\beta i}$ and $R_{\beta o}$.

2

Series-mixing
(Sever: Open Circuit)

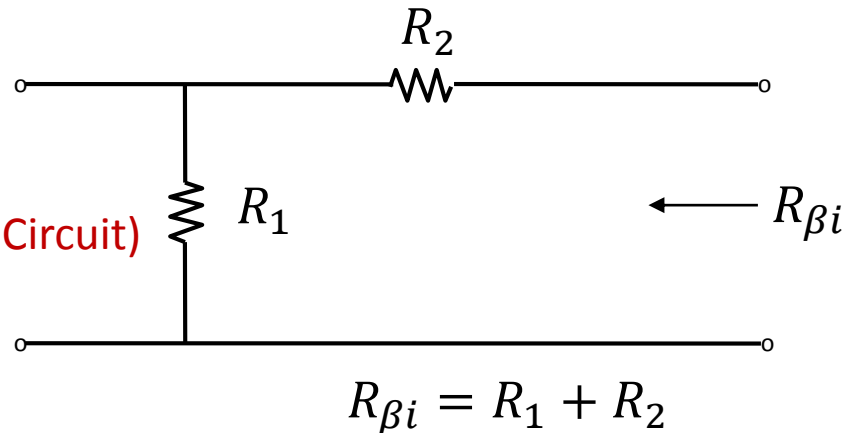


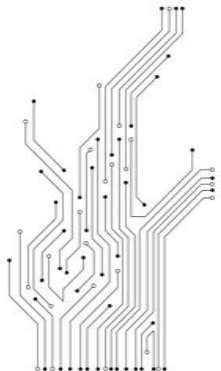To find $R_{\beta i}$, Sever O/P port of **Feedback** circuit (Series-mixing).




Analysis of a Feedback Amplifier (Contd.)

Example 8:

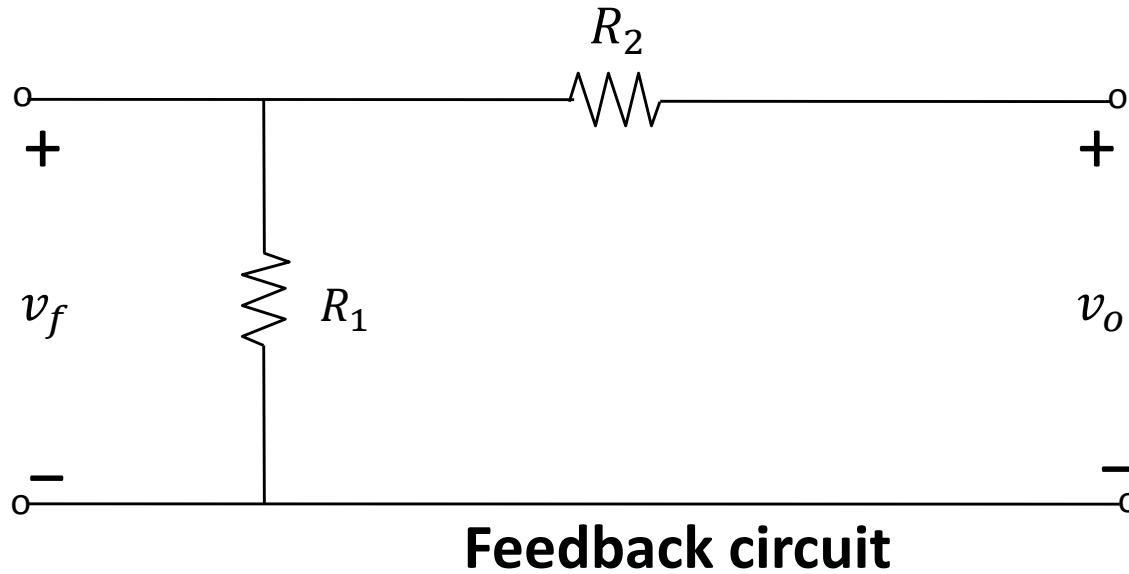


Separate feedback circuit and find β , $R_{\beta i}$ and $R_{\beta o}$.

2

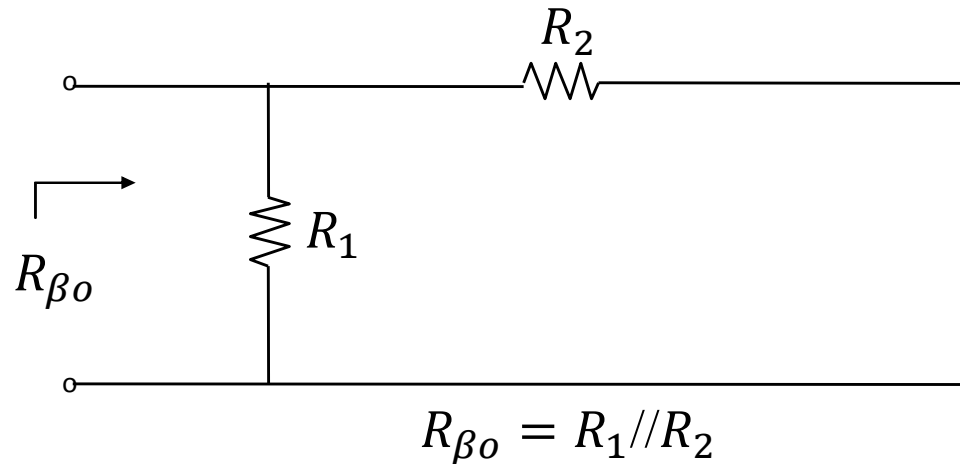


To find $R_{\beta o}$, Short I/P port of **Feedback** circuit (Shunt-Sampling).

Shunt-sampling
(Short: Short circuit)

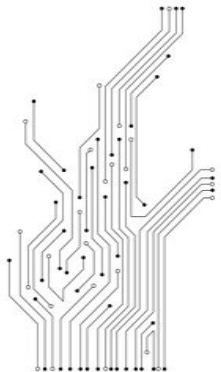

Analysis of a Feedback Amplifier (Contd.)


Example 8:

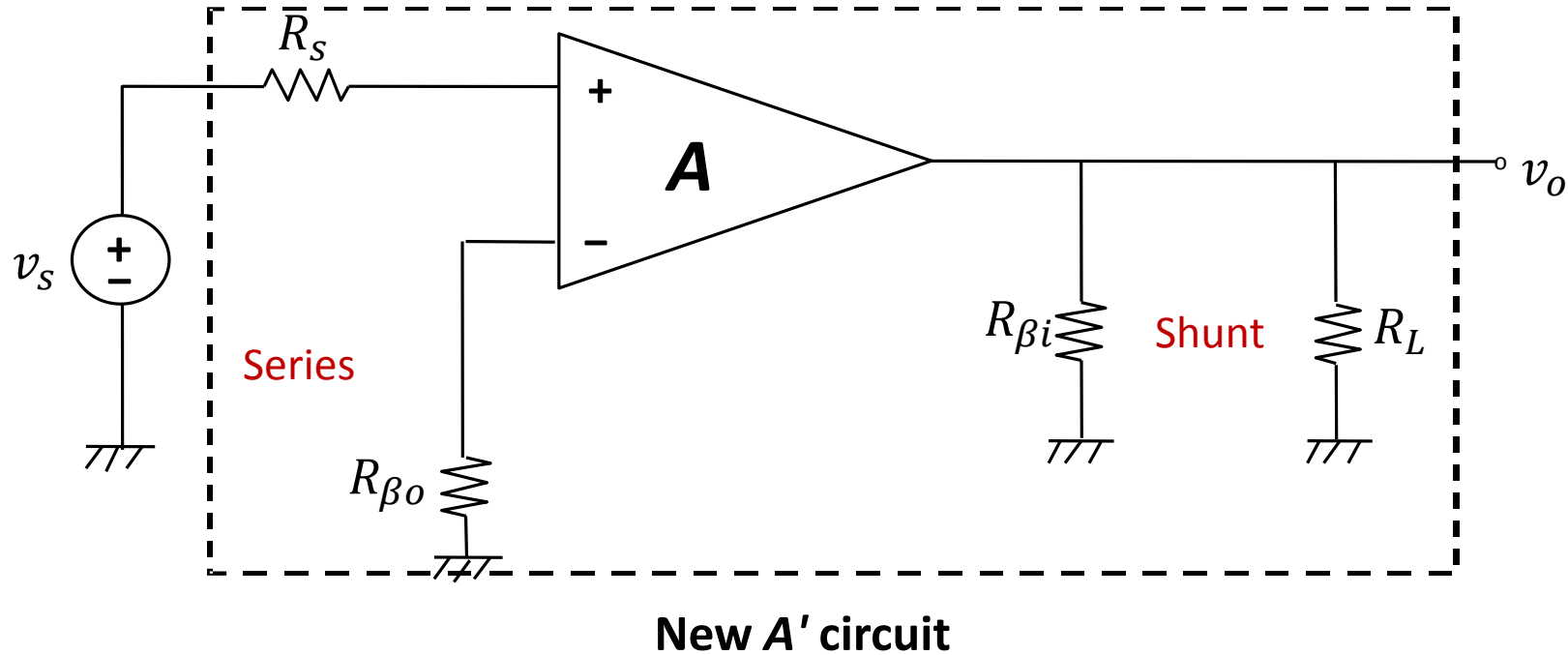

Redraw basic amplifier with Feedback network I/O resistances, and apply Thevenin's equivalent source

Analysis of a Feedback Amplifier (Contd.)

Example 8:


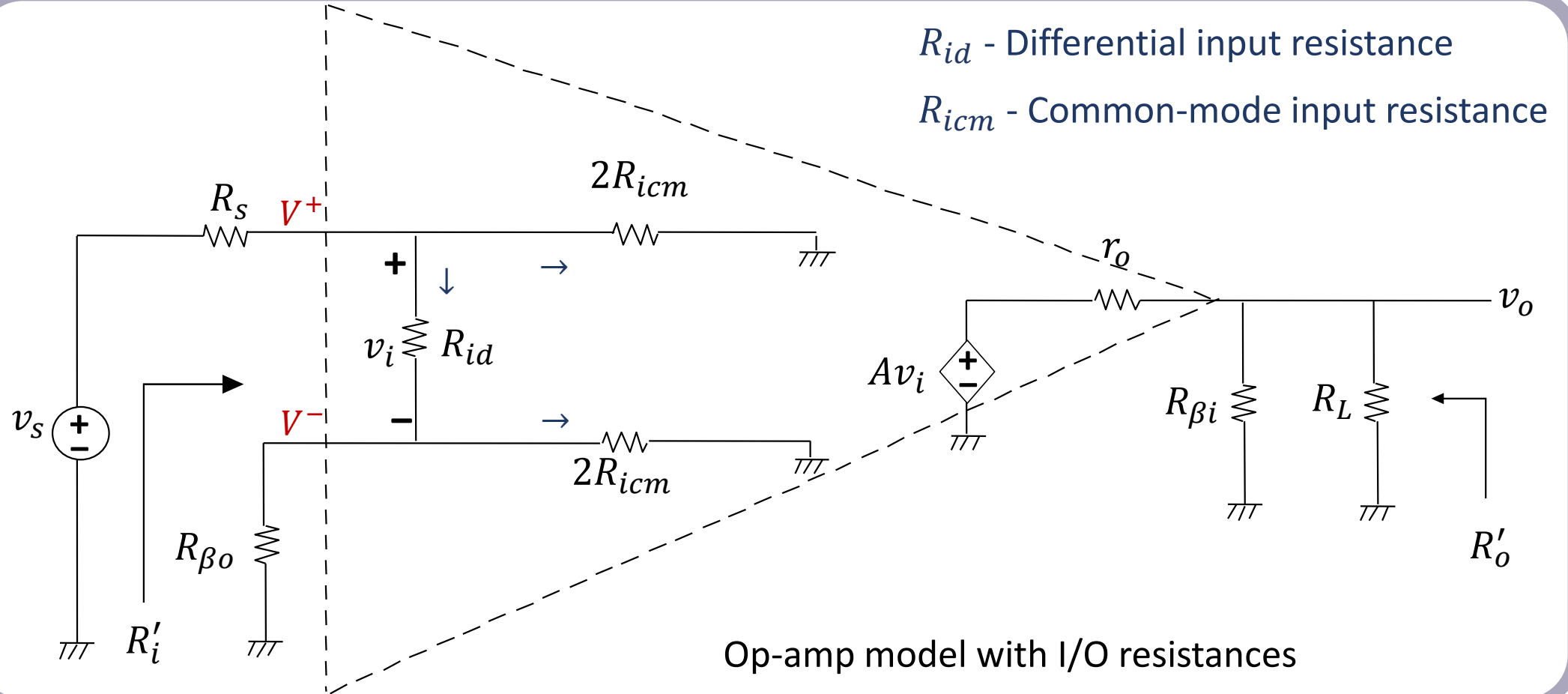


Find new gain A' and new I/O resistances R'_i and R'_o of new A' block.


Analysis of a Feedback Amplifier (Contd.)

Example 8:

Redraw
Circuit

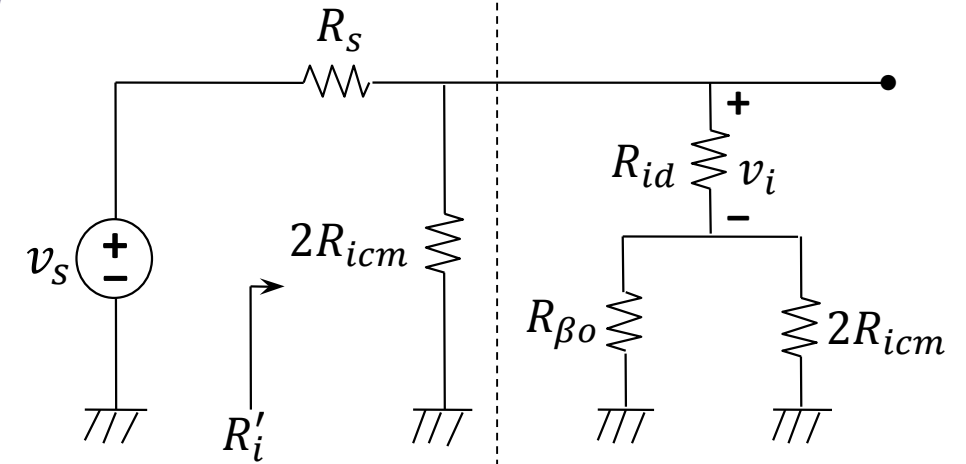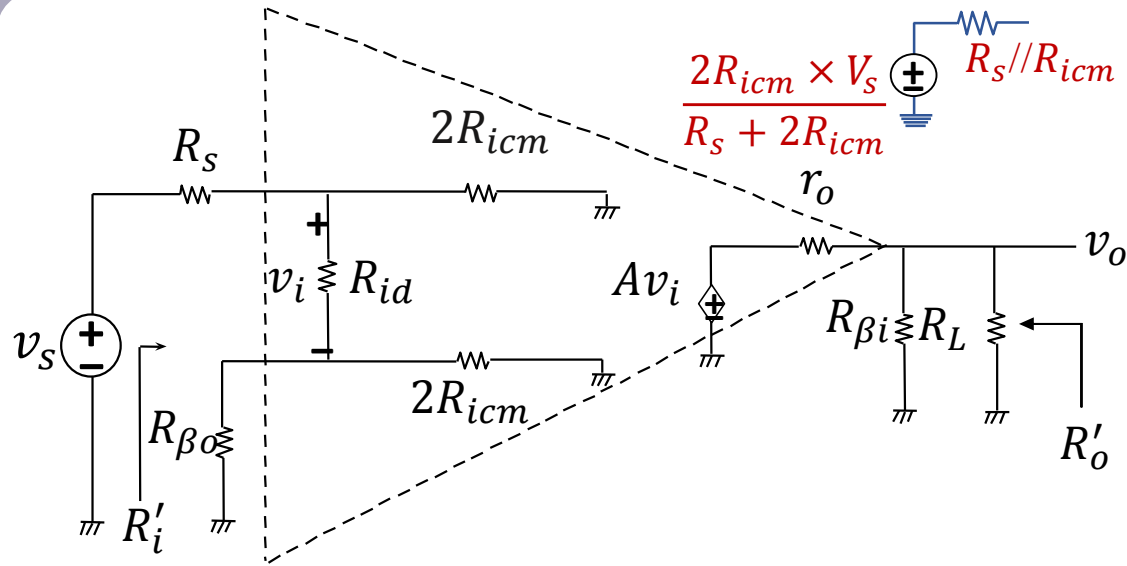

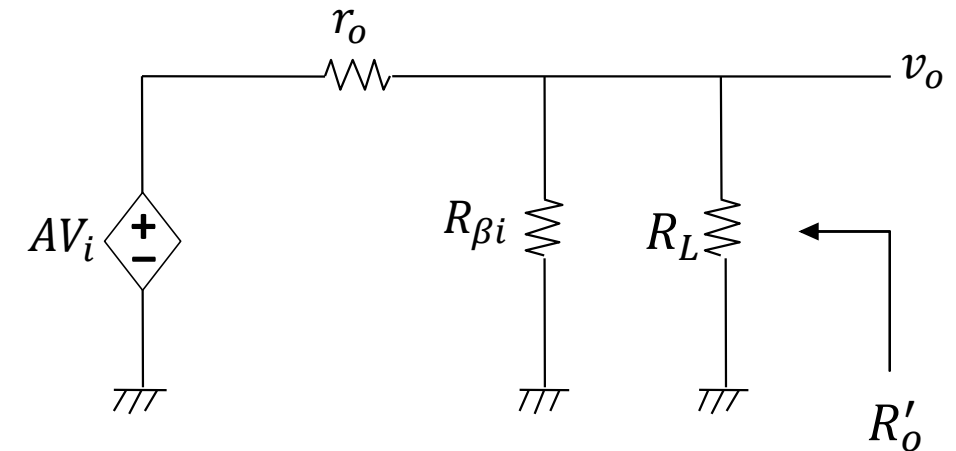
$$\frac{v_i}{v_s} = \frac{R_{id}}{(R_s // 2R_{icm}) + R_{id} + (R_{\beta o} // 2R_{icm})} \times \frac{2R_{icm}}{R_s + 2R_{icm}} \quad - (1)$$



Analysis of a Feedback Amplifier (Contd.)

Example 8:

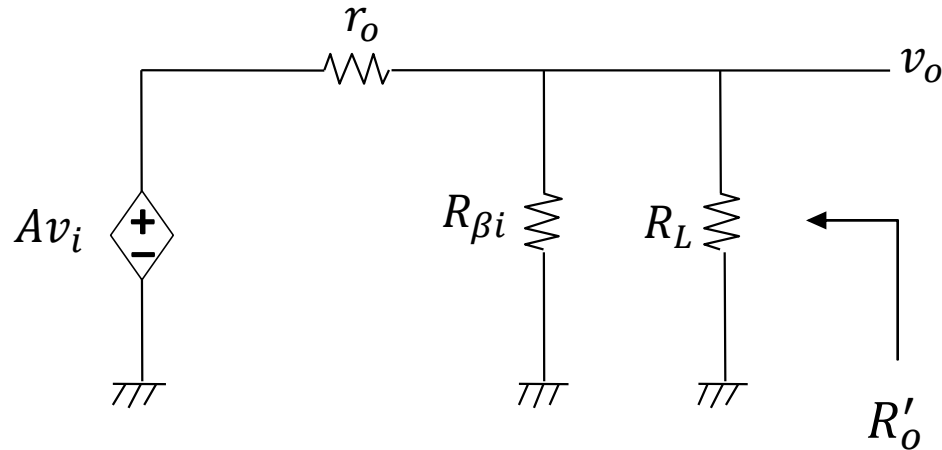

Redraw
Circuit


$$\frac{V_o}{V_i} = A \times \frac{(R_{\beta i} // R_L)}{r_o + (R_{\beta i} // R_L)} \quad - (2)$$



$$\therefore \text{New gain } A' = \frac{v_o}{v_s} = \frac{v_o}{v_i} \times \frac{v_i}{v_s}$$



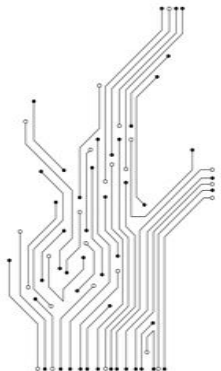
$$A' = \frac{A(R_{\beta i} // R_L)}{r_o + (R_{\beta i} // R_L)} \times \frac{R_{id}}{(R_s // 2R_{icm} + R_{id} + R_{\beta o} // 2R_{icm})} \times \frac{2R_{icm}}{(R_s + 2R_{icm})}$$




Analysis of a Feedback Amplifier (Contd.)

Example 8:

Redraw
Circuit

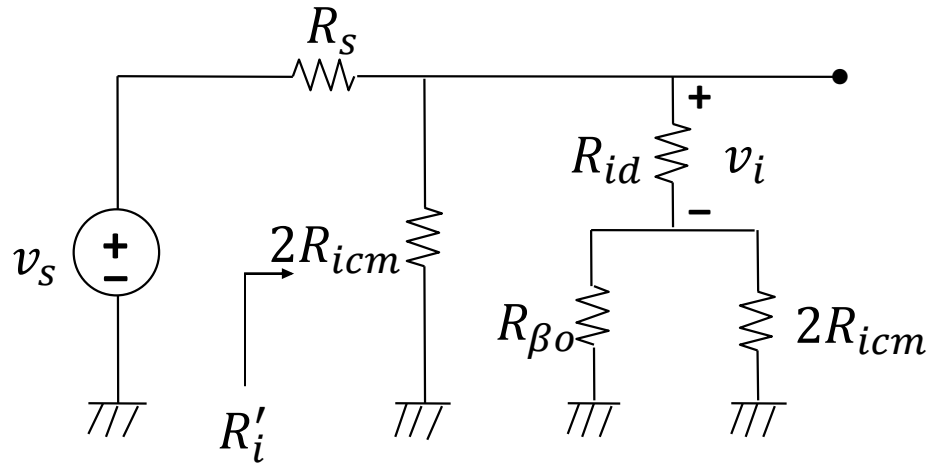

Kill the source

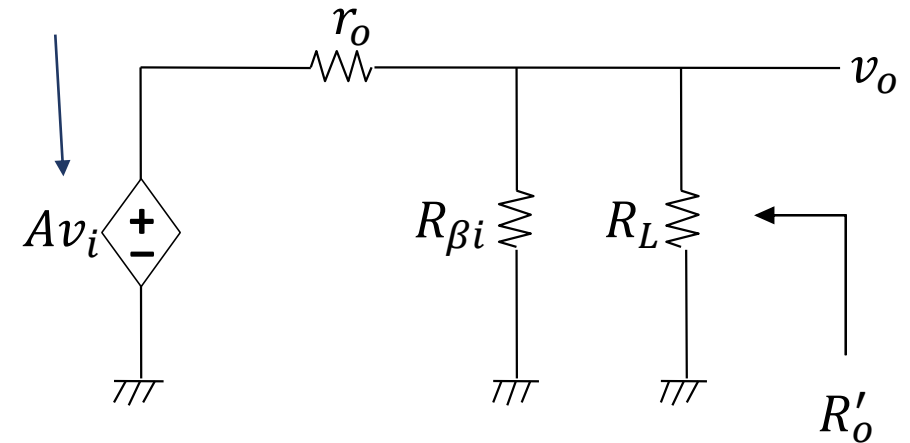


Input resistance, R'_i

$$R'_i = \left[(R_{id} + R_{\beta o} // 2R_{icm}) // 2R_{icm} \right] + R_s$$




Output resistance, R'_o


$$R'_o = r_o // R_{\beta i} // R_L$$

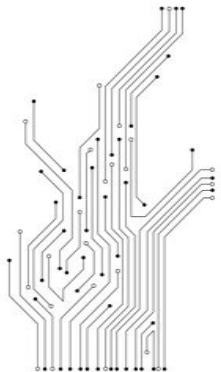


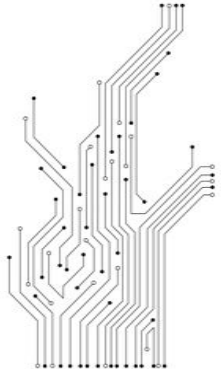
Analysis of a Feedback Amplifier (Contd.)

Find closed-loop gain A_f and Input-Output resistance R_{if} and R_{of} 6

$$A_f = \frac{A'}{1 + A'\beta}$$


$$R_{if} = (1 + A'\beta)R'_i \quad (\text{Series-mixing})$$


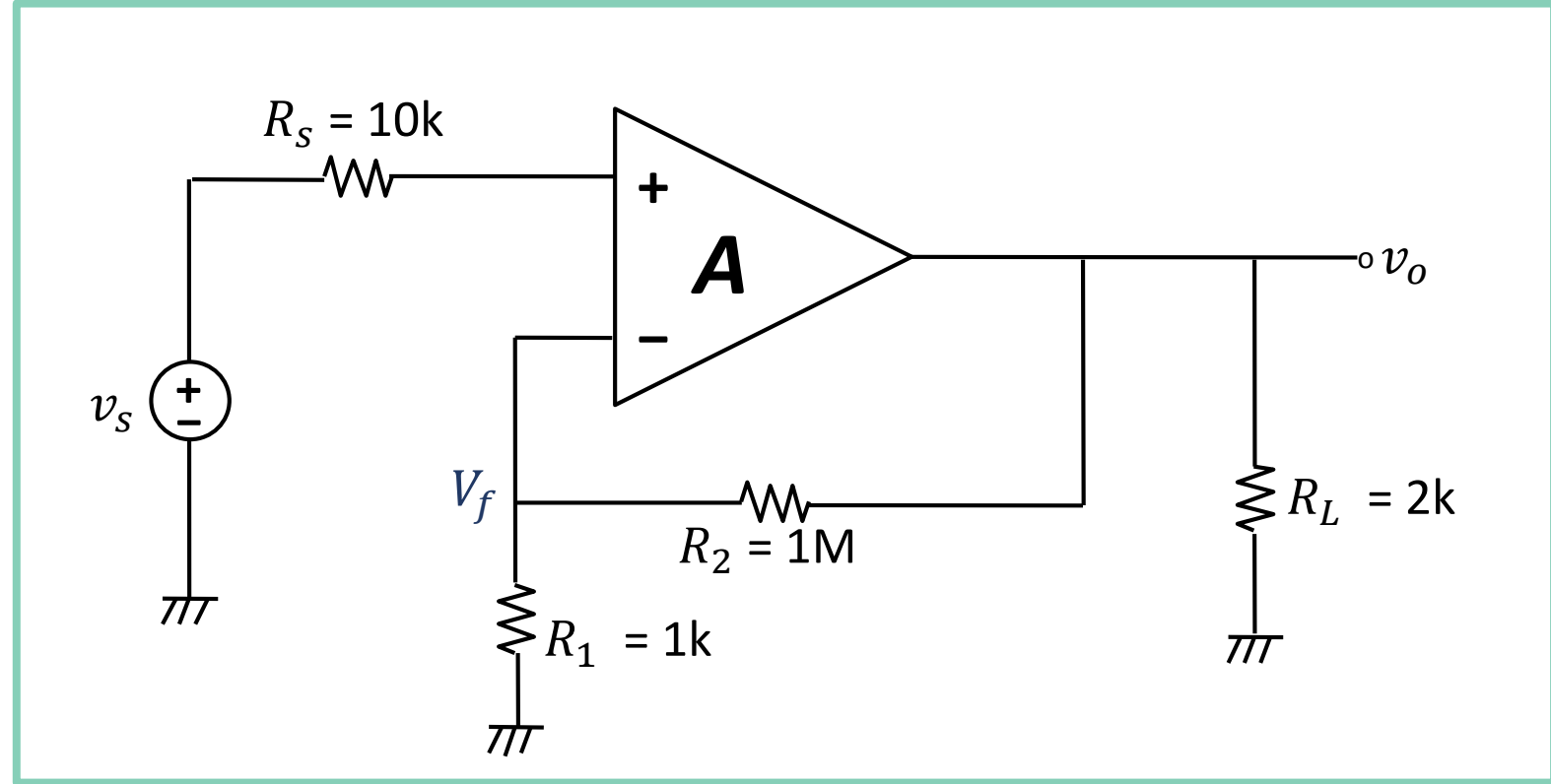
$$R_{of} = \frac{R'_o}{1 + A'\beta} \quad (\text{Shunt-sampling})$$




Analysis of a Feedback Amplifier (Contd.)

Example 8A:

With numerical values




$$A = 10^4$$

$$R_{id} = 100k\Omega$$

$$R_{icm} = 5k\Omega$$


$$r_o = 1k\Omega$$

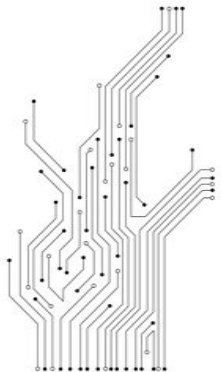

Analysis of a Feedback Amplifier (Contd.)

Example 8A:

With numerical values

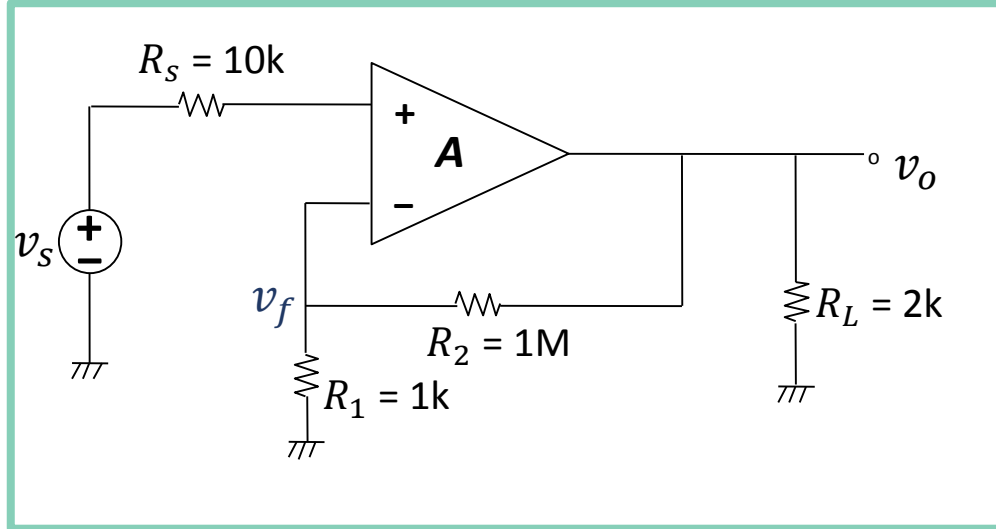

$$A = 10^4$$

$$R_{id} = 100\text{k}\Omega$$

$$R_{icm} = 5\text{k}\Omega$$

$$r_o = 1\text{k}\Omega$$


$$\beta = \frac{v_f}{v_o} = \frac{R_1}{R_1 + R_2} = \frac{1\text{k}}{1\text{k} + 1\text{M}} \approx 10^{-3}$$

$$R_{\beta i} = R_1 + R_2 = 1001\text{k}\Omega$$

$$R_{\beta o} = R_1 // R_2 = 1\text{k} // 1\text{M} \approx 1\text{k}\Omega$$

$$A' = \frac{A(R_{\beta i} // R_L)}{r_o + (R_{\beta i} // R_L)} \times \frac{R_{id}}{(R_s // 2R_{icm} + R_{id} + R_{\beta o} // 2R_{icm})} \times \frac{2R_{icm}}{(R_s + 2R_{icm})}$$


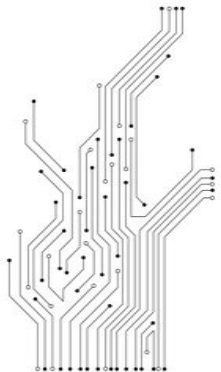
$$A' = \frac{10^4(1001\text{k} // 2\text{k})}{1\text{k} + (1001\text{k} // 2\text{k})} \times \frac{100\text{k}}{10\text{k} // 10\text{M} + 100\text{k} + 1\text{k} // 10\text{M}} \times \frac{10\text{M}}{10\text{k} + 10\text{M}} \approx 600\text{V/V}$$



Analysis of a Feedback Amplifier (Contd.)

Example 8A:

With numerical values

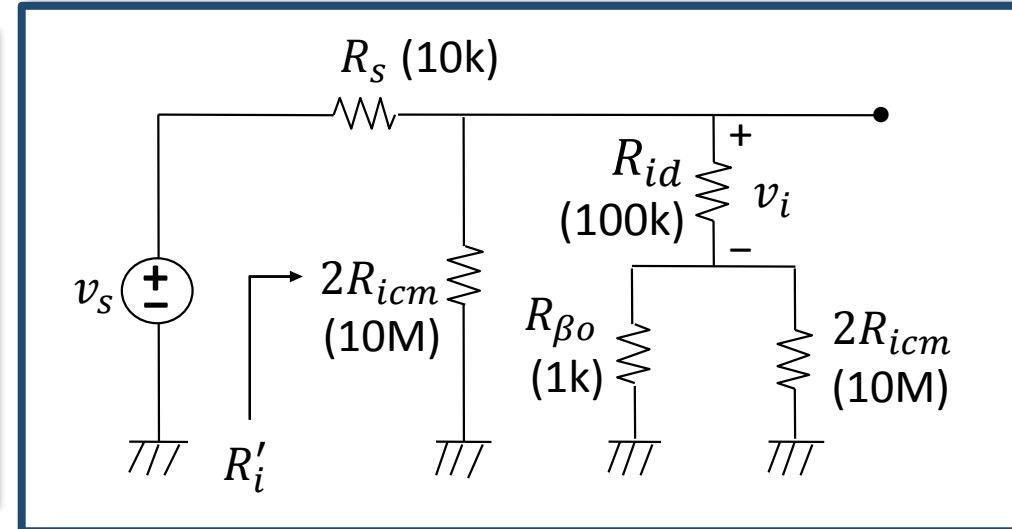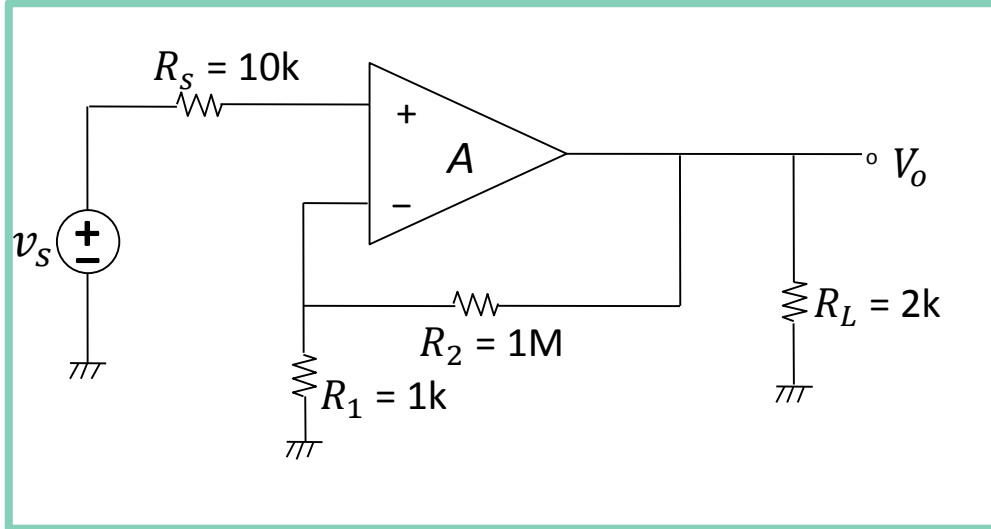


$$R'_i = (100k + 1k // 10M) // 10M + 10k \approx 111k\Omega$$

$$R'_o = 1k // 1001M // 2k \approx 0.67k\Omega$$


$$A_{f3} = \frac{A'}{1 + A'\beta} = \frac{6000}{1 + 6000 \times 10^{-3}} = 857V/V$$

$$R_{if} = R_i(1 + A'\beta) = 111k(1 + 6) = 777k\Omega$$
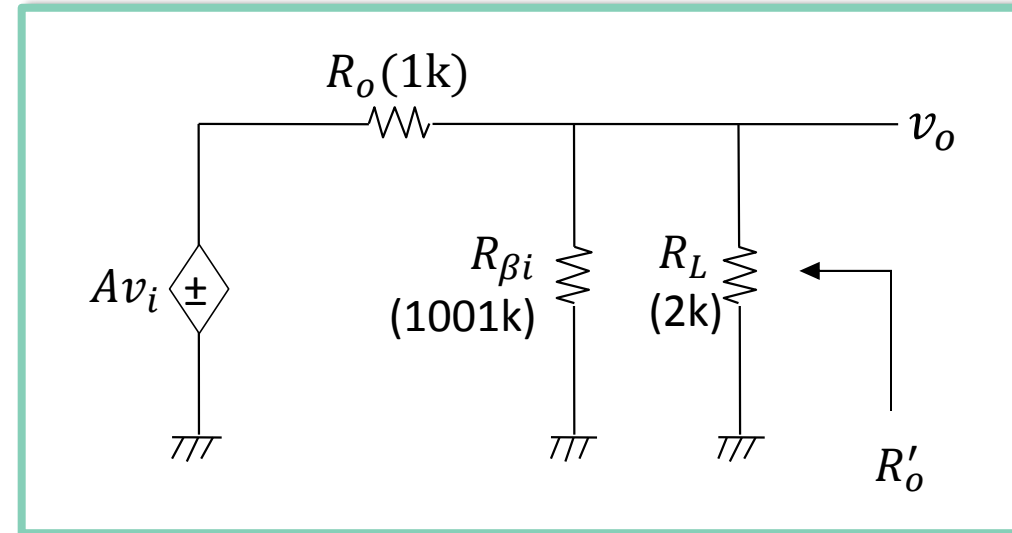
$$R_{of} = \frac{R_o}{(1 + A'\beta)} = \frac{0.67k}{1 + 6} = 95.7k\Omega$$



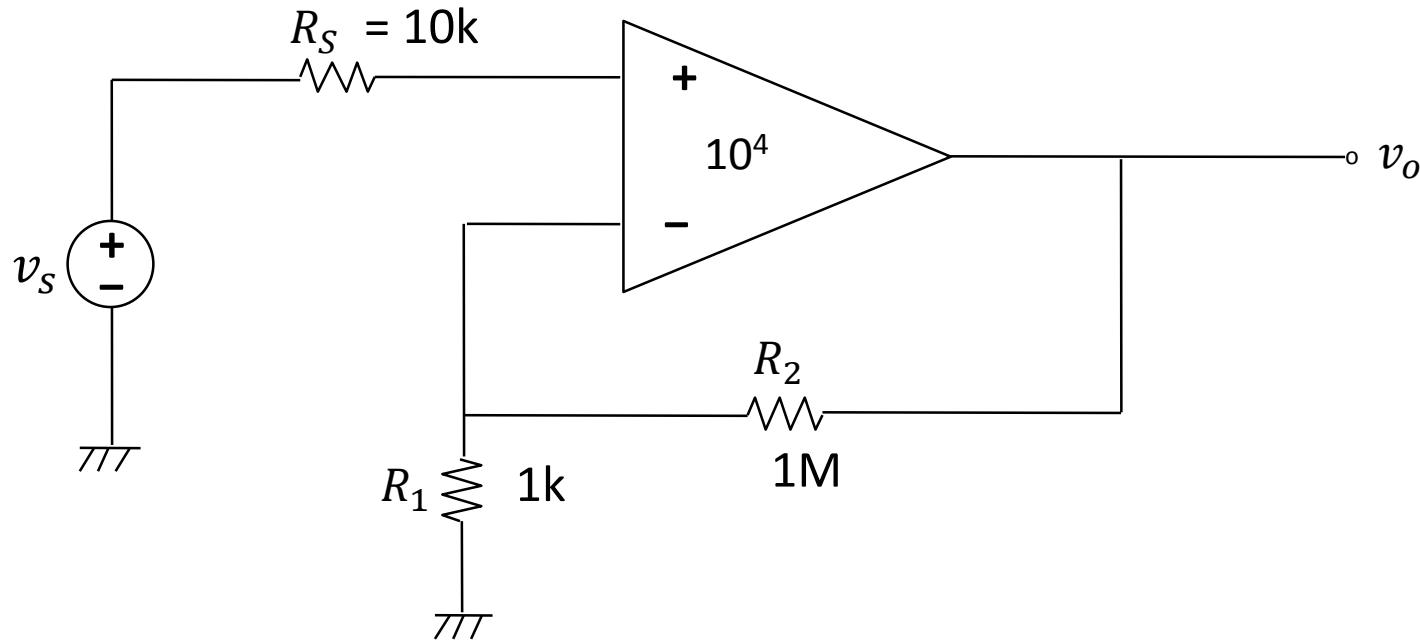Compare with Conventional Analysis of Op-amp



If $A = \infty$ (Ideal case)

$$A_{f1} = \frac{R_1 + R_2}{R_1} = 1 + \frac{1M}{1k} = 1001$$


Input R, $R_i \approx \infty$

Output R, $R_o \approx 0$

If $A = 10,000$


$$A_{f2} = \frac{A}{1 + A\beta} = \frac{10000}{1 + 10000 \left(\frac{1}{1001} \right)} = 909.9$$

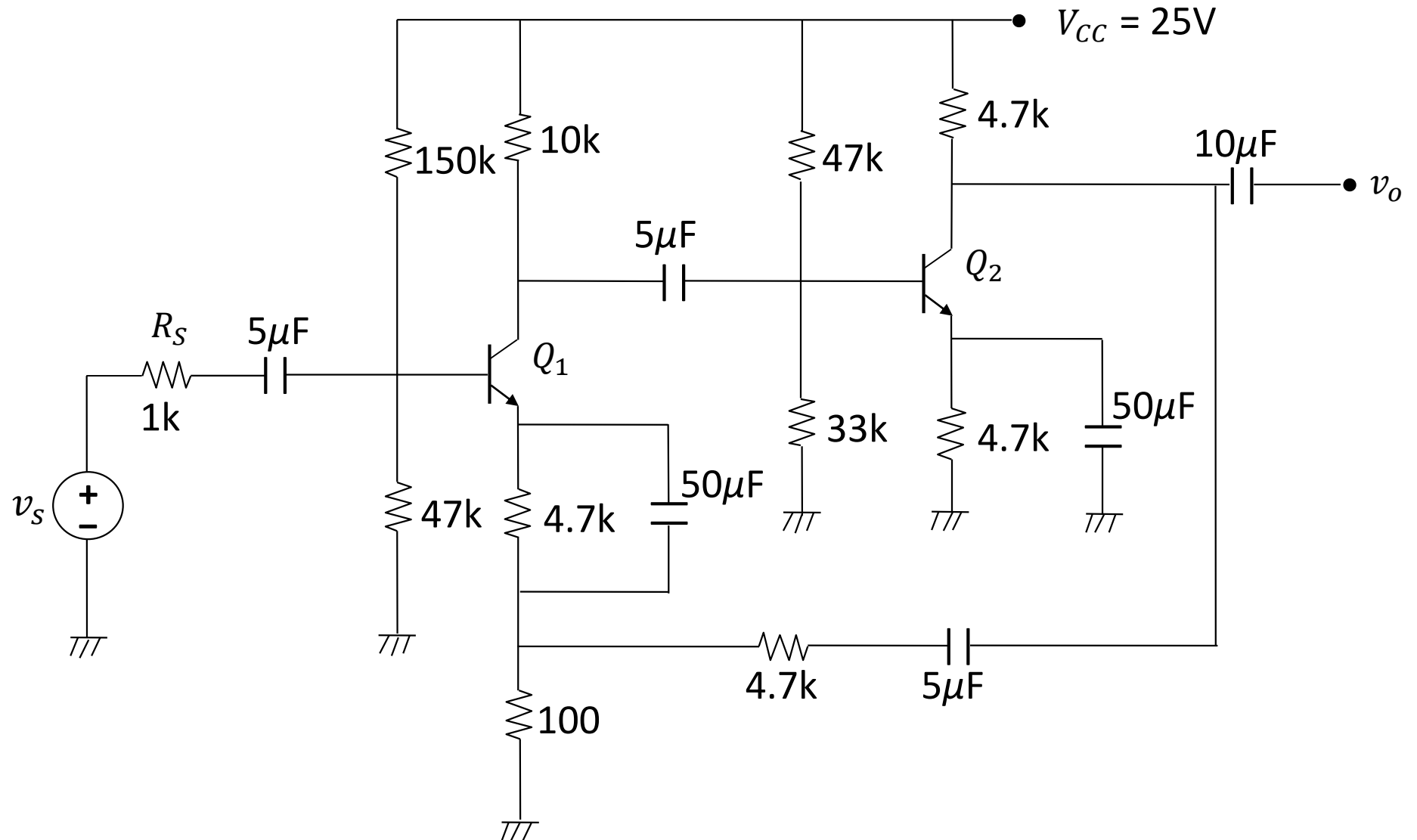Example of Series-Shunt Feedback Amplifier




6. Examples of Feedback Amplifier Analysis: Shunt-Series

New Basic Amplifier - A'

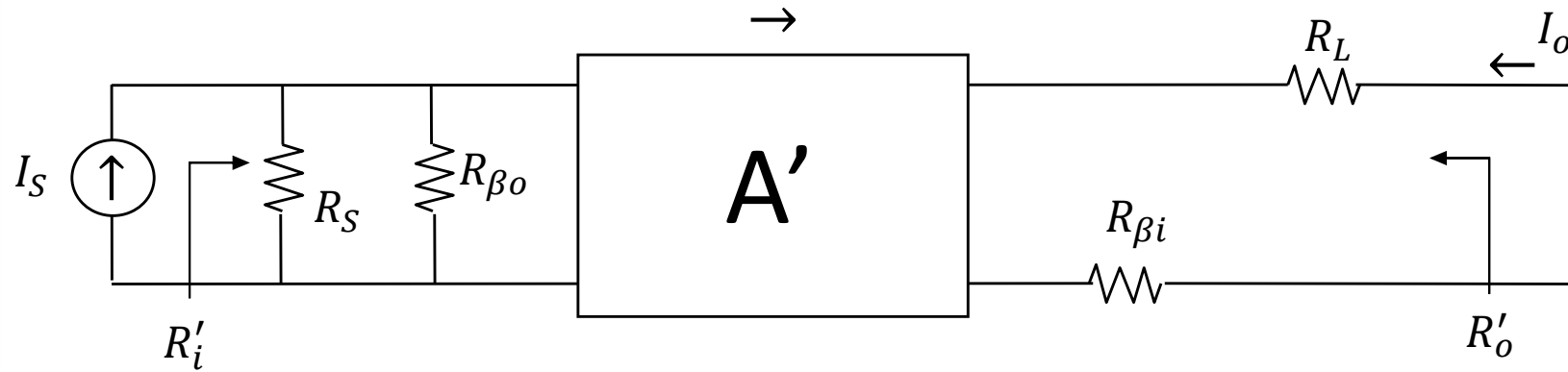


$$\text{New gain, } A' = \frac{I_o}{I_S}$$


$$\beta = \frac{I_f}{I_o}$$

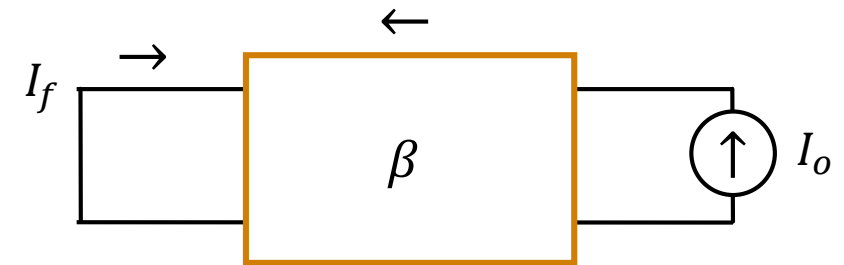

Feedback circuit - β

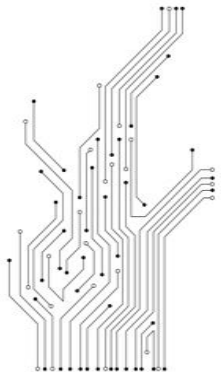

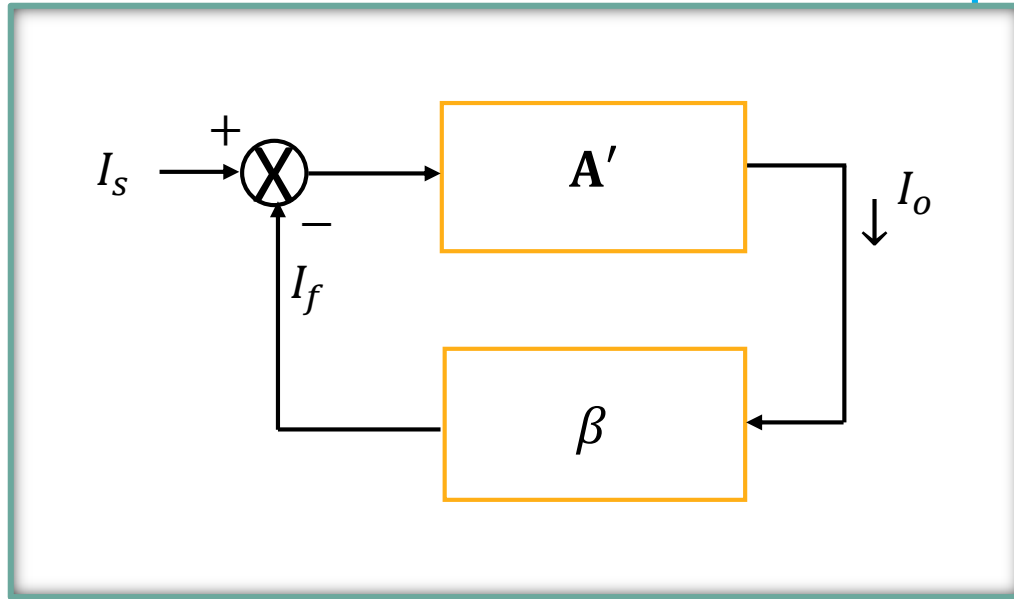
Closed-loop gain A_f and I/O Resistance R_{if} and R_{of}




$$A_f = \frac{A'}{1 + A'\beta}$$

$$R_{if} = \frac{R'_i}{1 + A'\beta} \quad (\text{Shunt-mixing})$$
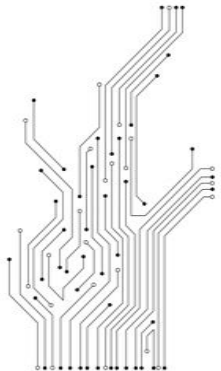
$$R_{of} = R'_o(1 + A'\beta) \quad (\text{Series-sampling})$$




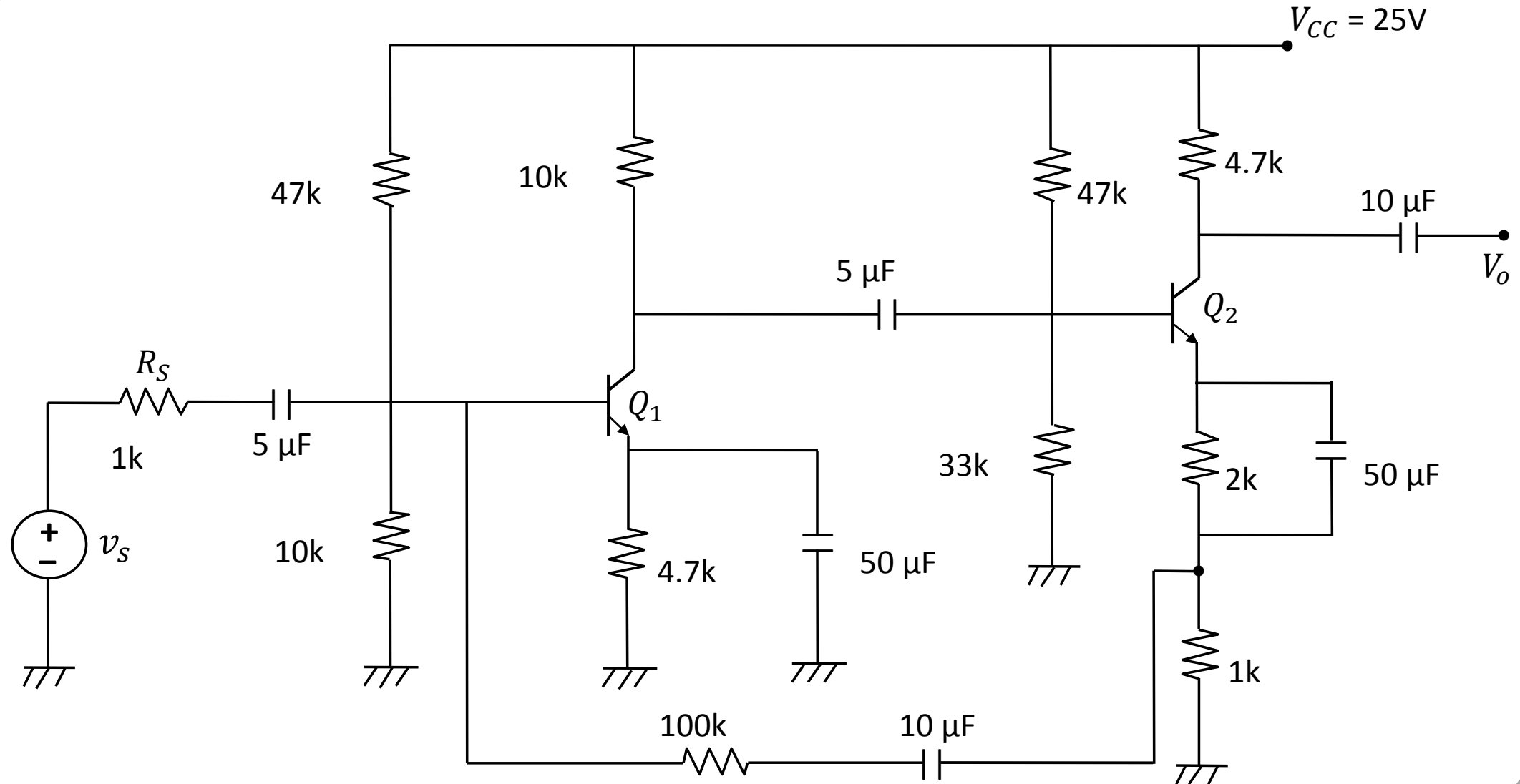Example of Shunt-Series Feedback Amplifier




6. Examples of Feedback Amplifier Analysis: Series-Series

New Basic
Amplifier - A'

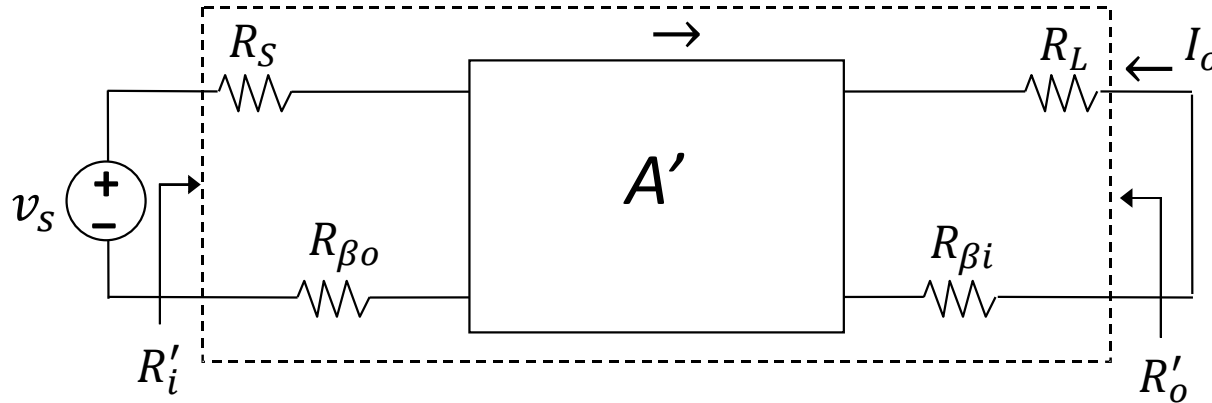


$$\text{New gain, } A' = \frac{I_o}{v_s}$$

$$\beta = \frac{v_f}{I_o}$$

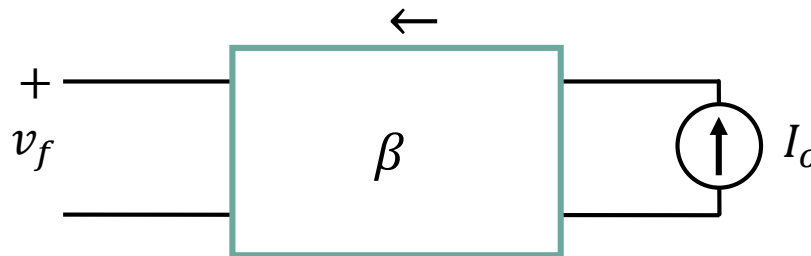

Feedback
circuit - β

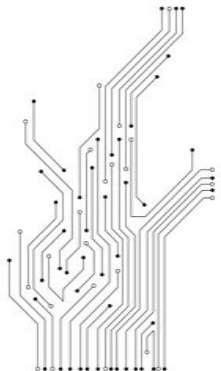


Closed-loop gain A_f and I/O Resistance R_{if} and R_{of}


$$A_f = \frac{A'}{1 + A'\beta}$$

$$R_{if} = R'_i(1 + A'\beta) \text{ (Series-mixing)}$$

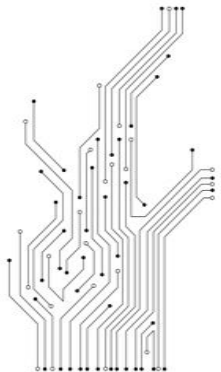
$$R_{of} = R'_o(1 + A'\beta) \text{ (Series-sampling)}$$



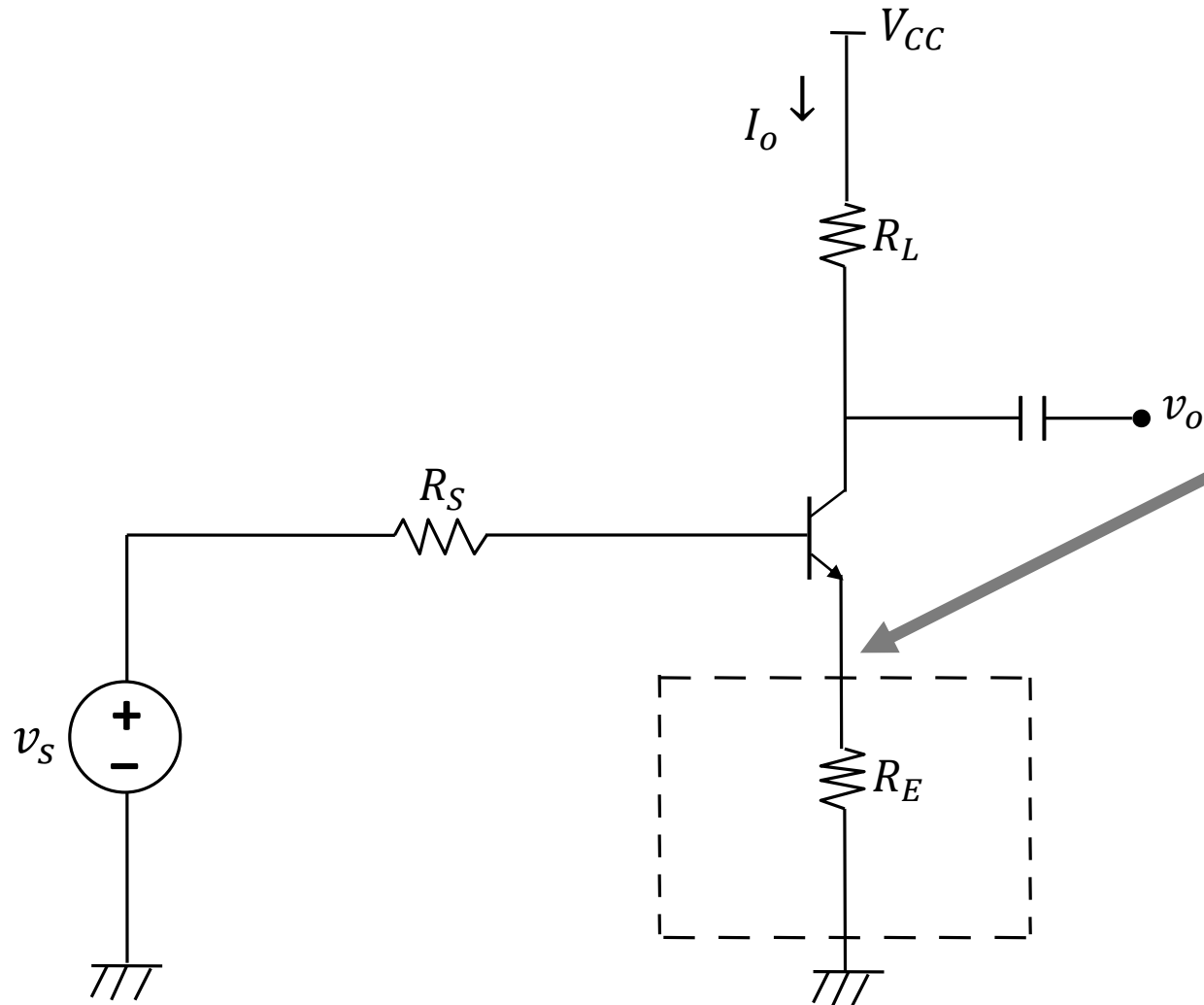Example of Series-Series Feedback Amplifier




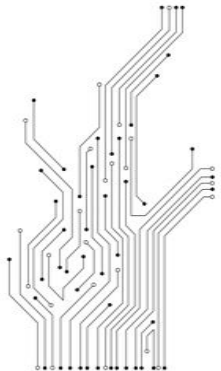The current sampled at output current loop and emitter voltage is connected in series with input source.




6. Examples of Feedback Amplifier Analysis: Shunt-Shunt


New Basic
Amplifier - A'

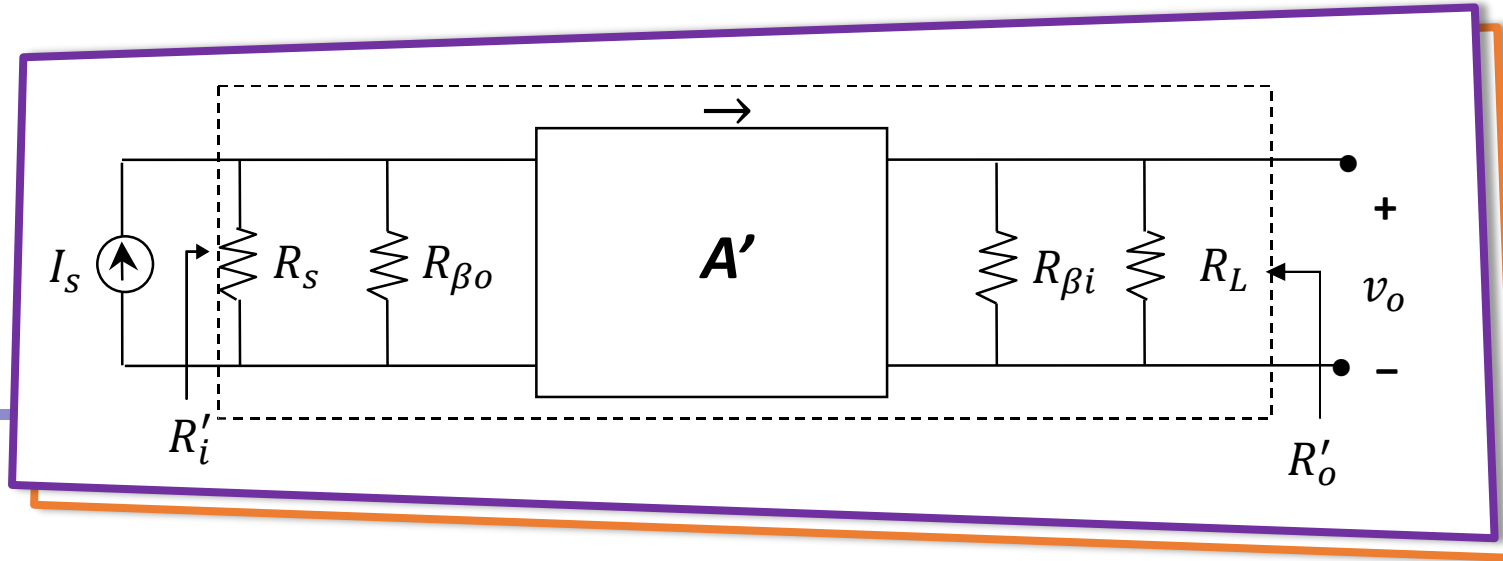
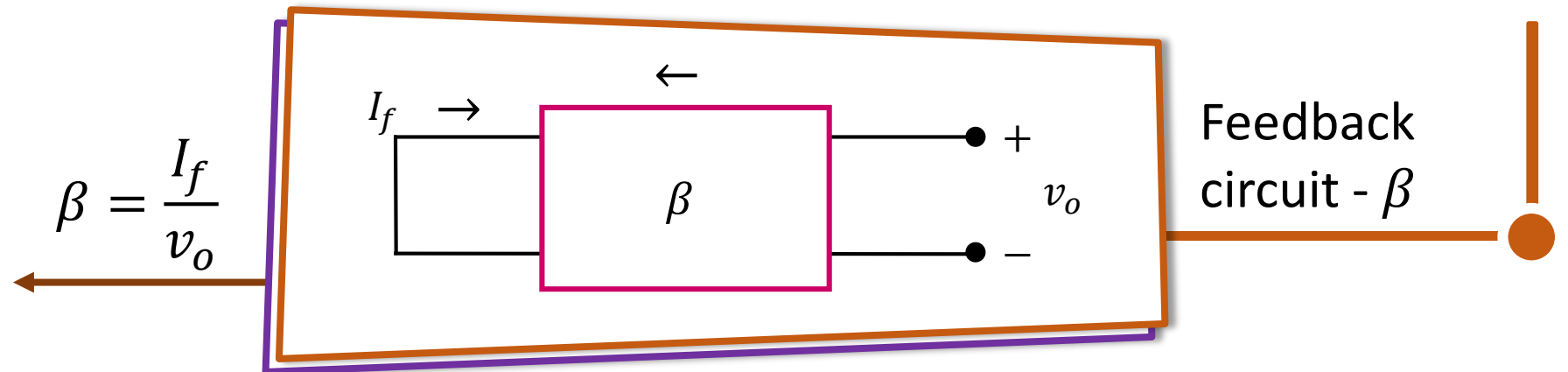
$$\text{New gain, } A' = \frac{v_o}{I_s}$$





Feedback
circuit - β

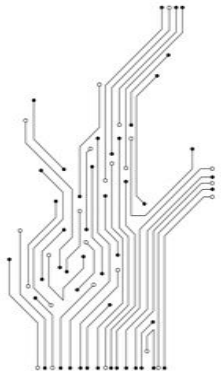


Closed-loop gain A_f and I/O Resistance R_{if} and R_{of}


$$A_f = \frac{A'}{1 + A'\beta}$$

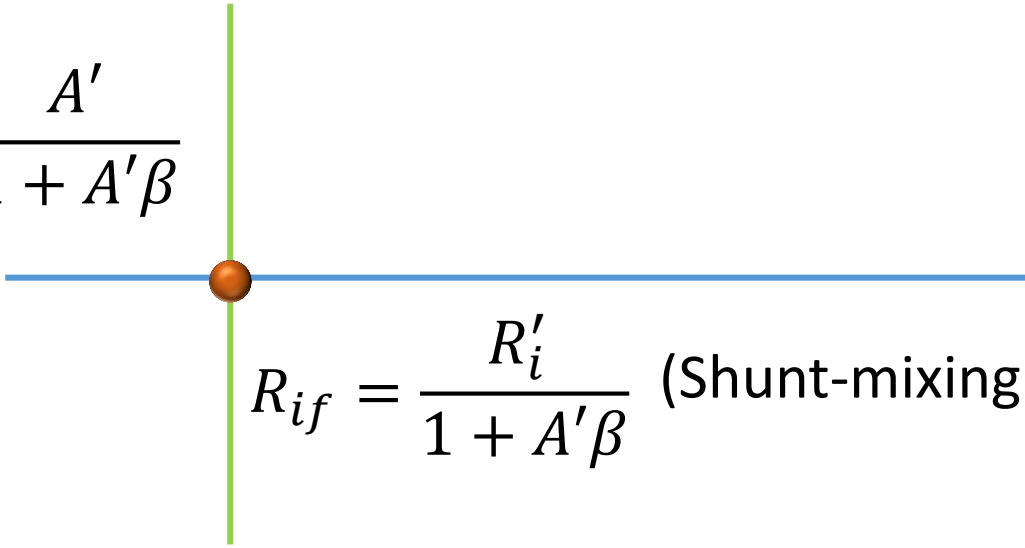
$$R_{if} = \frac{R'_i}{1 + A'\beta} \quad (\text{Shunt-mixing})$$

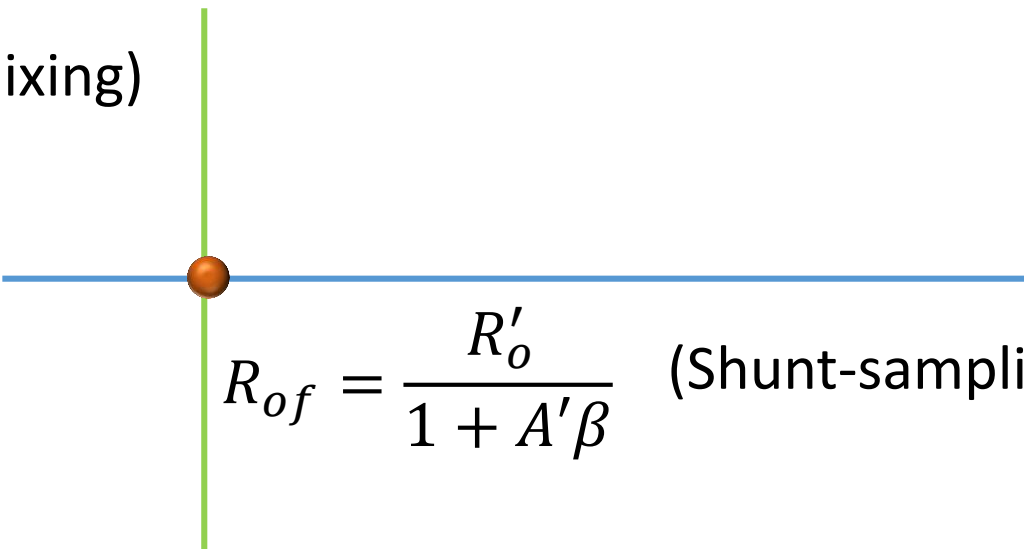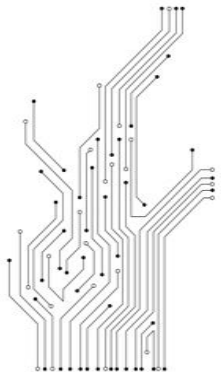
$$R_{of} = \frac{R'_o}{1 + A'\beta} \quad (\text{Shunt-sampling})$$




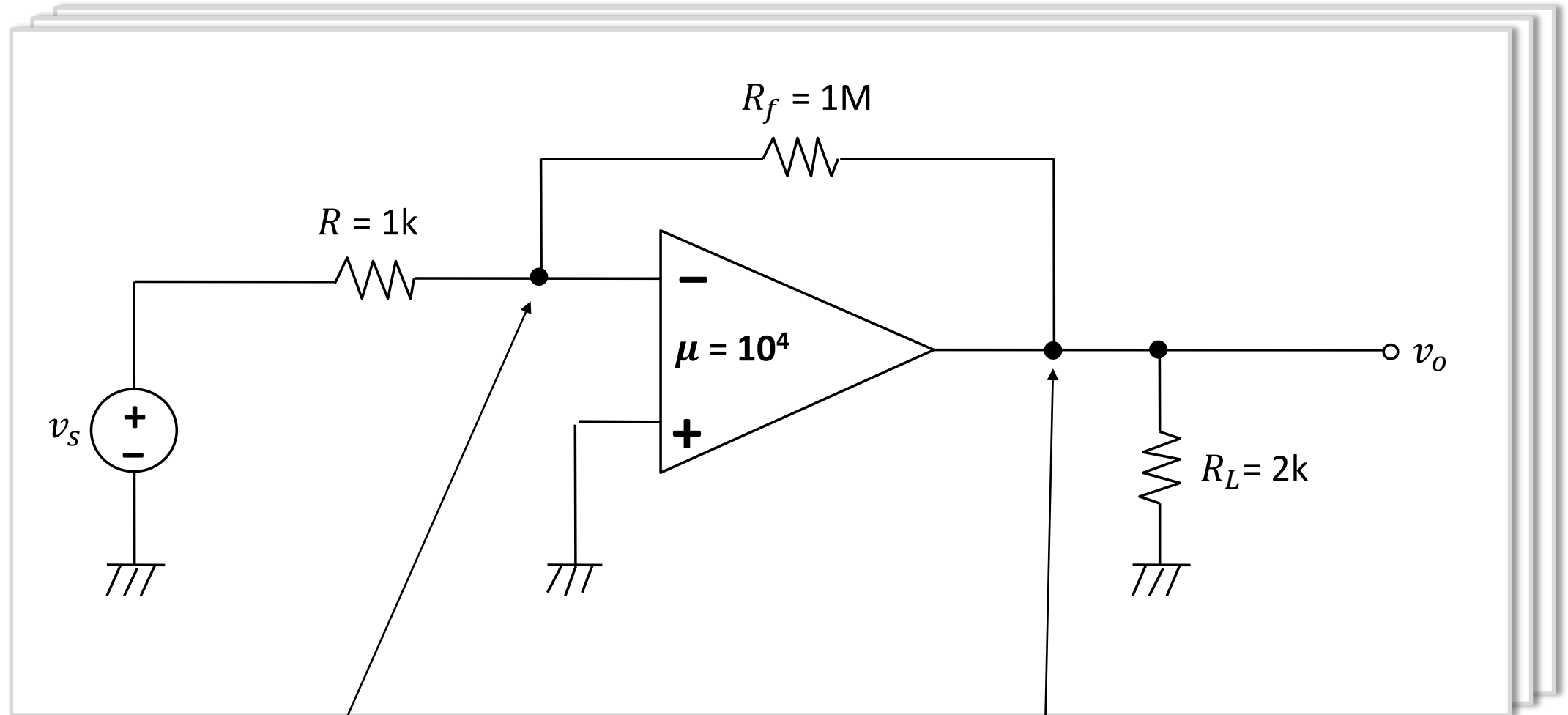Example of Shunt-Shunt Feedback Amplifier





Feedback signal is current \Rightarrow Shunt mixing



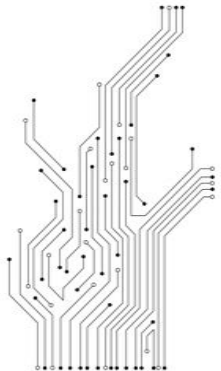
Voltage sampling taken at output node \Rightarrow Shunt-sampling





Case Study

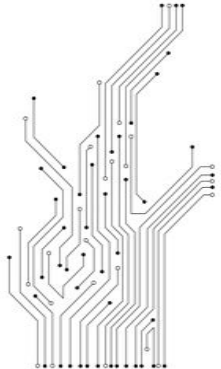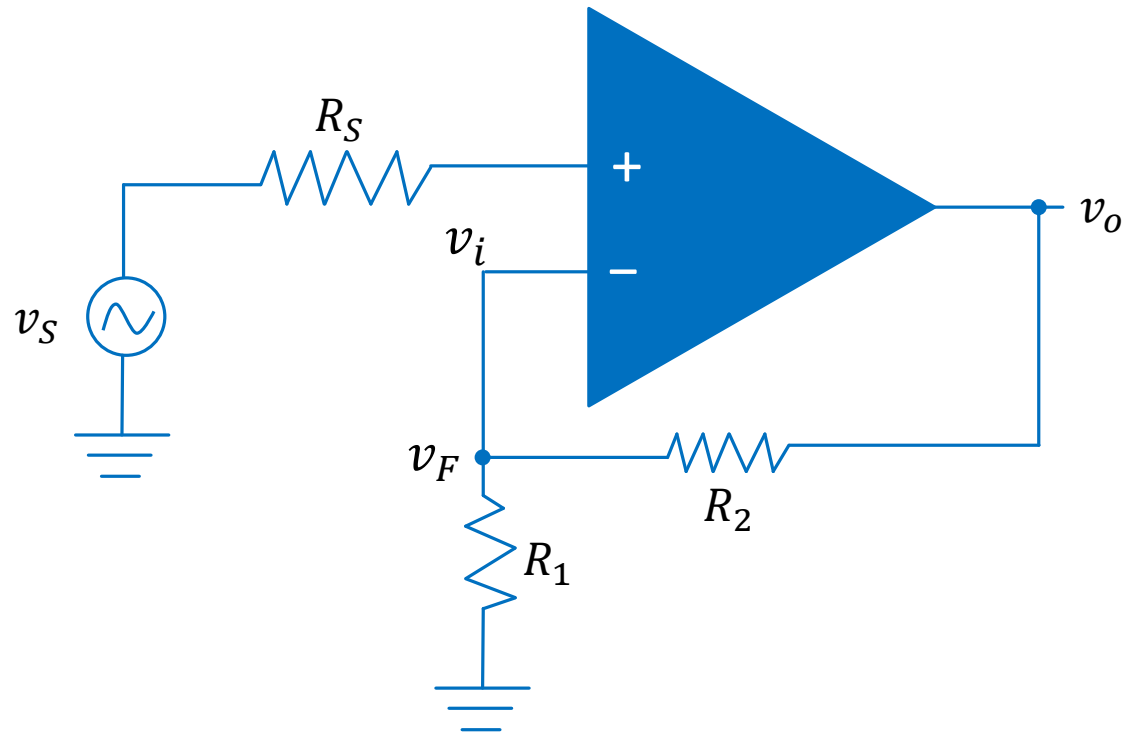


Case Study

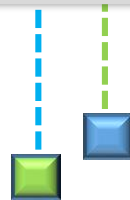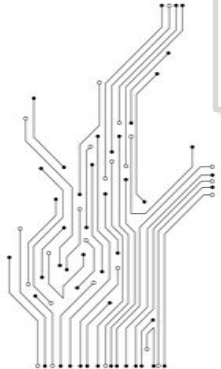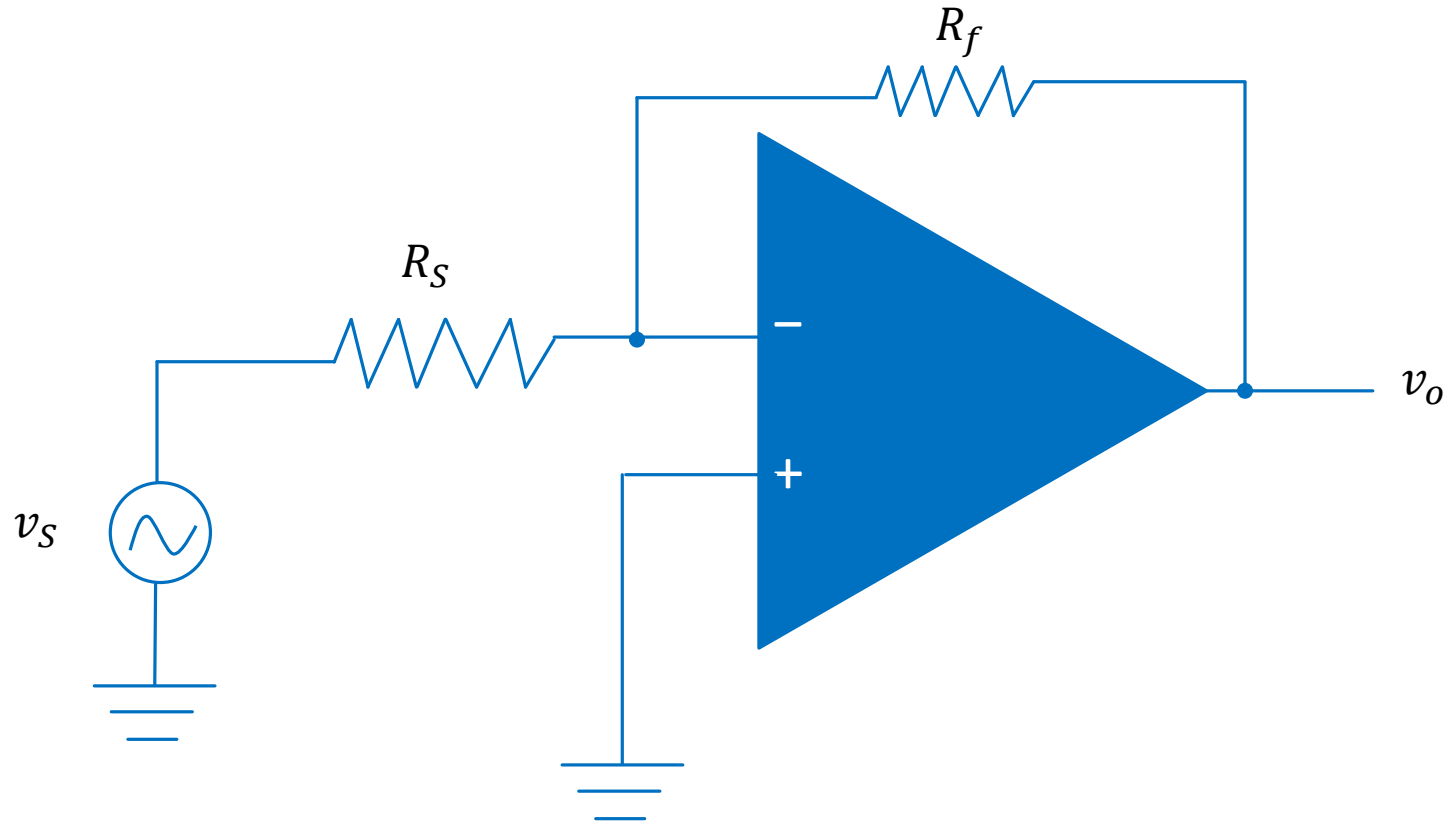

Case Study

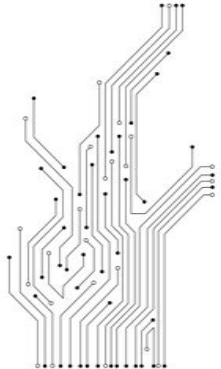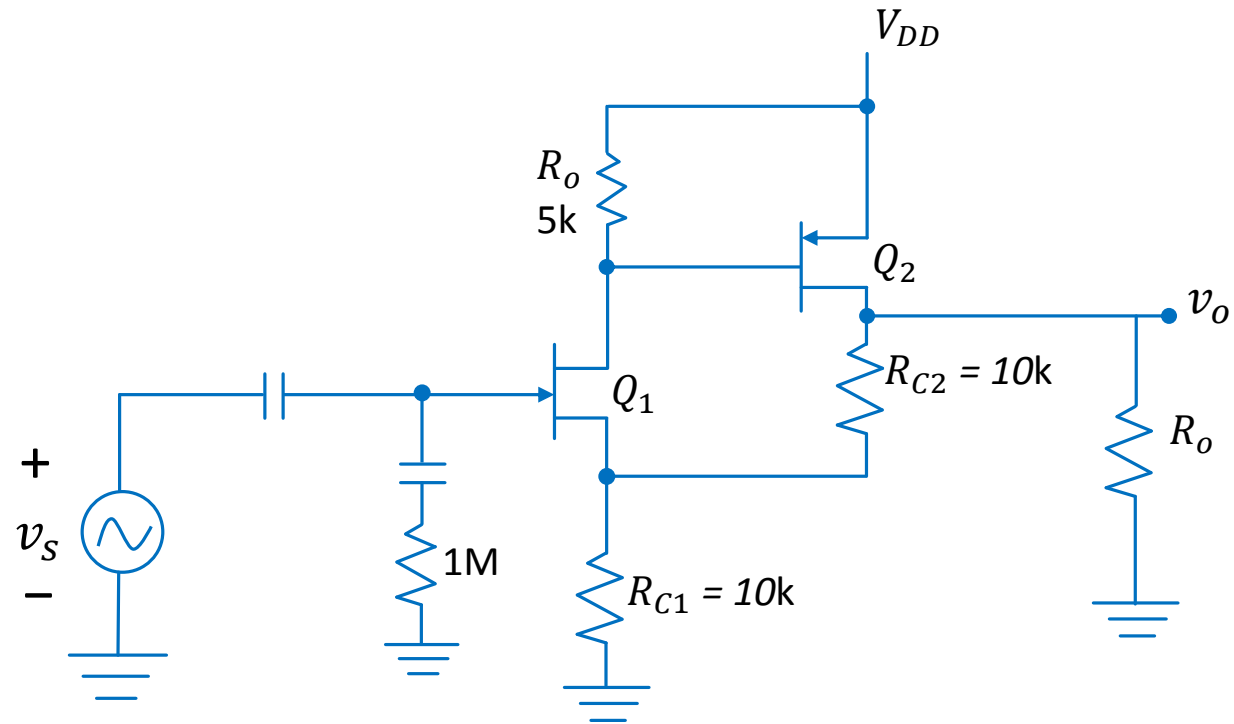

Case Study

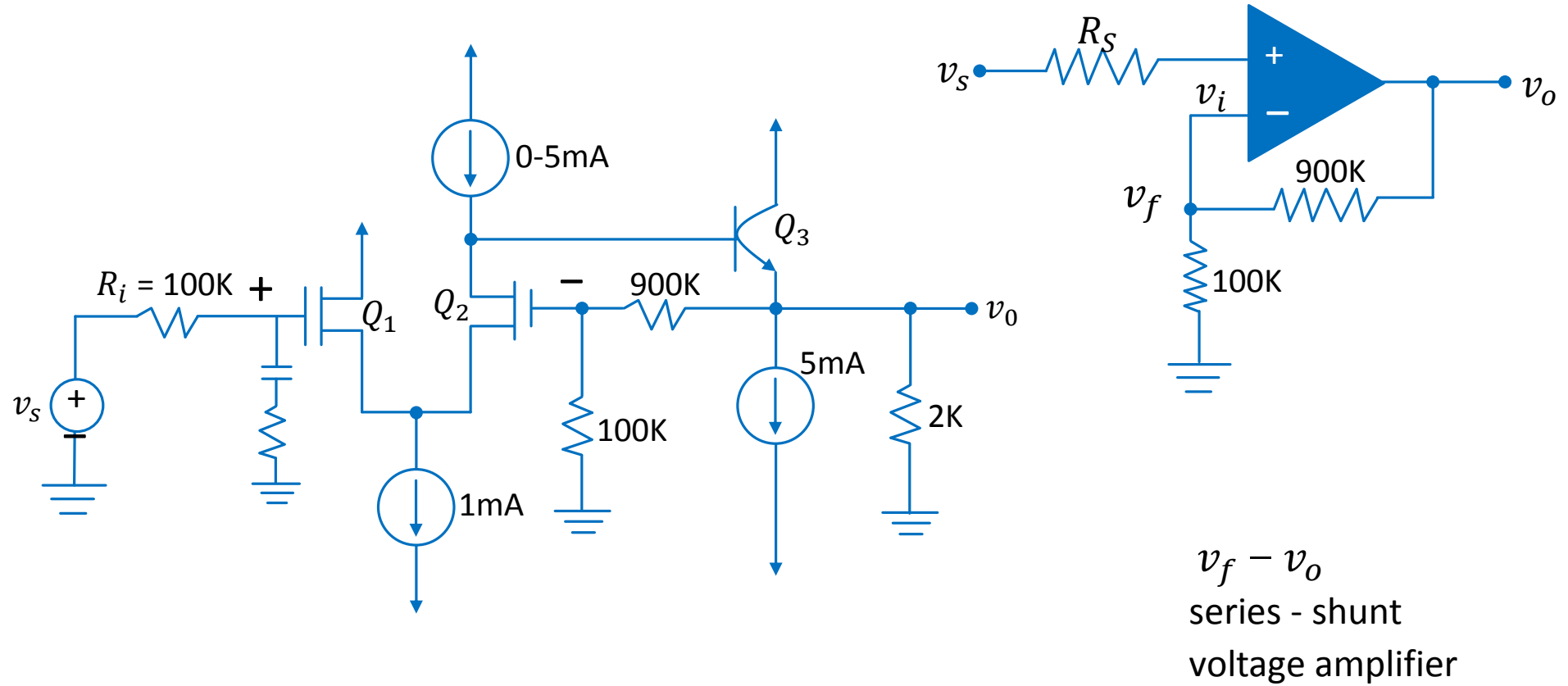

Summary

Here are the key takeaways from this lesson.

▶ The general feedback structure of the negative feedback amplifier consists of a basic amplifier A and a feedback network β .


▶ The characteristics of a negative feedback amplifier are gain de-sensitivity, reduced frequency distortion, noise reduction, reduced non-linear distortion, input and output impedance change which are obtained at the expense of gain reduction.

▶ There are four feedback topologies, Series-Shunt, Shunt-Series, Series-Series and Shunt-Shunt feedback topology.

▶ There are six steps to analyse the feedback amplifier with the loading effect of $R_{\beta i}$ and $R_{\beta o}$.

The steps are as follows:

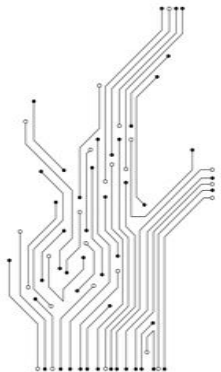- Identify the topology.
- Separate A and β .
- Find β , $R_{\beta i}$ and $R_{\beta o}$.
- Draw the basic amplifier with $R_{\beta i}$ and $R_{\beta o}$ to convert into a new basic amplifier A' .
- Find A' , R'_i and R'_o .
- Determine the Gain (A_f), Input Impedance (R_{if}) and Output Impedance (R_{of}) of a feedback amplifier.



Thank You

Feedback Circuits

