

Nanyang Technological University
School of Electrical & Electronic Engineering
E2002 Analog Electronics – Tutorial 8

- The DC operating point of the common-drain amplifier in Figure 1 has been calculated in Question 2 of Tutorial 7 to be $I_D = 1.87 \text{ mA}$ and $V_{DS} = 9.39 \text{ V}$. The n -MOS transistor M_1 has $K_n = 1 \text{ mA/V}^2$, $V_{TN} = 1 \text{ V}$ and $\lambda = 0.02 \text{ V}^{-1}$. Assume that the capacitors have infinite value, $R_I = 100 \Omega$, $R_1 = 1.2 \text{ M}\Omega$, $R_2 = 910 \text{ k}\Omega$, $R_S = 3 \text{ k}\Omega$, $R_L = 250 \Omega$ and $V_{DD} = 15 \text{ V}$, calculate the voltage gain, input resistance and output resistance of the amplifier.

(Ans: $A_v = 0.31$, $R_{in} = 517.54 \text{ k}\Omega$, $R_{out} = 434.6 \Omega$)

What is the maximum input signal amplitude for small signal operation?

(Ans: 556.52 mV)

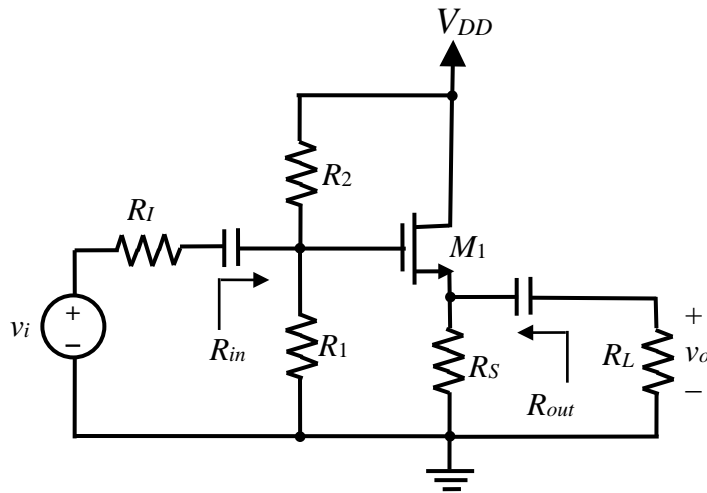


Figure 1

- What are the voltage gain, input resistance and output resistance for the amplifier in Figure 2. if $R_I = 250 \Omega$, $R_S = 68 \text{ k}\Omega$, $R_L = 200 \text{ k}\Omega$, $R_D = 43 \text{ k}\Omega$ and $V_{DD} = V_{SS} = 15 \text{ V}$? What is the maximum input signal for the amplifier that satisfies the small-signal limit? Use $K_p = 200 \mu\text{A/V}^2$ and $V_{TP} = -1 \text{ V}$ for your calculation.

(Ans: $A_v = 8.98$, $R_{in} = 3.47 \text{ k}\Omega$, $R_{out} = 43 \text{ k}\Omega$, $v_i \leq 0.292 \text{ V}$)

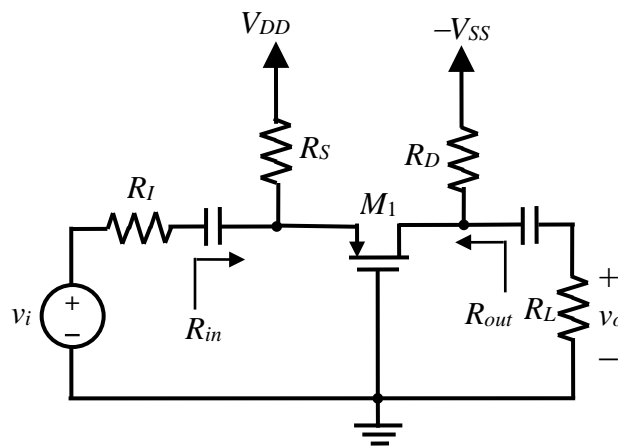


Figure 2

3. The gate resistor R_G in Figure 3 is said to be “bootstrapped” by the action of the source follower.
- a. Assume that the MOSFET is operating with $g_m = 3.54 \text{ mS}$ and r_o can be neglected. Draw the small signal model and find the voltage gain, input resistance and output resistance for the amplifier if $R_G = 1 \text{ M}\Omega$, $R_S = 2 \text{ k}\Omega$, $R_L = 100 \text{ k}\Omega$ and $V_{DD} = V_{SS} = 10 \text{ V}$.
(Ans: $A_v = 0.874$, $R_{in} = 7.94 \text{ M}\Omega$, $R_{out} = 247 \Omega$)
- b. What would R_{in} be if A_v were exactly +1?
(Ans: ∞)

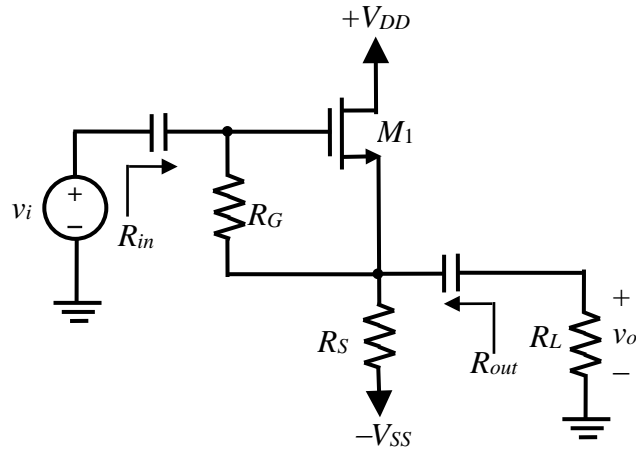


Figure 3