

## Lecture 3

---

### EE3010: Electrical Devices and Machines

School of Electrical and Electronic Engineering

Associate Professor Lee Peng Hin

Tel: +65 6790 4474 | Email: [ephlee@ntu.edu.sg](mailto:ephlee@ntu.edu.sg)

By the end of this lecture, you should be able to:

- ❖ Describe the respective powers, derive their relationships and equations for an induction motor.
- ❖ Explain the notions of developed torque and output torque and how to compute them.
- ❖ Use the induction motor equivalent circuit to study and predict the performance of the motor for a given operating condition.

From the per-phase equivalent circuit,

- ❖ The stator copper losses  $P_{SCL} = 3I_1^2 R_1$
- ❖ The air-gap power  $P_{AG} = P_{in} - P_{SCL}$
- ❖ Since  $X_2$  does not consume real power,  $P_{AG} = 3I_2^2 \left( \frac{R_2}{s} \right)$
- ❖ The rotor copper losses  $P_{RCL} = 3I_2^2 R_2$
- ❖ The converted power, also called developed power,

$$P_{dev} = P_{conv} = P_{AG} - P_{RCL} = 3I_2^2 \left( R_2 \left( \frac{1-s}{s} \right) \right)$$

- ❖ Also,  $P_{RCL} = sP_{AG}$ ,  $P_{conv} = (1-s)P_{AG}$ ,  $P_{out} = P_{conv} - P_{rot}$
- ❖ The induced torque  $T_{ind}$  is the torque generated by the internal electrical to mechanical power conversion. Also called developed torque  $T_{dev}$ .

$$T_{ind} = T_{dev} = \frac{P_{conv}}{\omega_m} = \frac{(1-s)P_{AG}}{(1-s)\omega_{sync}} = \frac{P_{AG}}{\omega_{sync}}$$

# Separating Rotor Cu Losses and the Power Converted


❖ The air-gap power  $P_{AG} = 3I_2^2 \left( \frac{R_2}{s} \right)$

❖ Rotor copper losses  $P_{RCL} = 3I_2^2 R_2$

❖ The converted power

$$P_{conv} = P_{AG} - P_{RCL} = 3I_2^2 \left\{ R_2 \left( \frac{1-s}{s} \right) \right\}$$

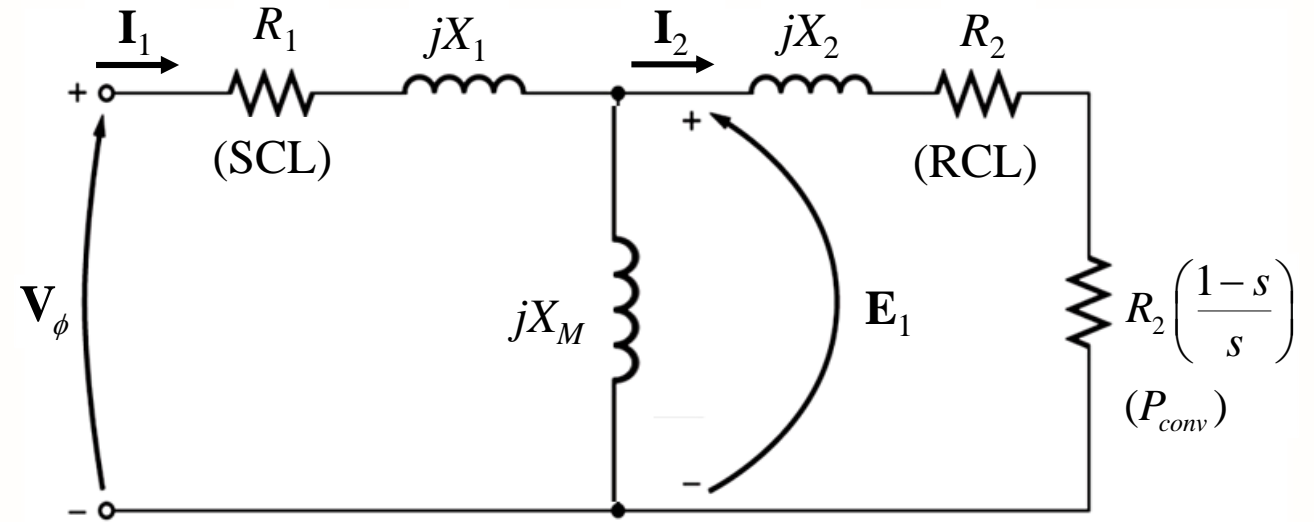❖ Thus,  $R_{conv} = R_2 \left( \frac{1-s}{s} \right)$



The per phase equivalent circuit with rotor copper losses and power converted separated.

## Example 1

A 460 V, 60 Hz, four-pole induction motor is wye-connected. The core losses are lumped together with the friction and windage losses and the stray losses to give the total rotational losses of 1100 W and they are assumed to be constant. The impedances per phase referred to the stator circuit are:

$$R_1 = 0.641\Omega, \quad R_2 = 0.332\Omega, \quad X_1 = 1.106\Omega, \\ X_2 = 0.464\Omega, \quad X_M = 26.3\Omega$$

For a rotor slip of 2.2% at the rated voltage and rated frequency, find the motor's

- |                         |                             |                             |
|-------------------------|-----------------------------|-----------------------------|
| a) Speed                | c) Input power factor       | e) $T_{ind}$ and $T_{load}$ |
| b) Input stator current | d) $P_{conv}$ and $P_{out}$ | f) Efficiency               |

(Solutions →)

## Example 1 – Solutions

a) 
$$n_{sync} = \frac{120 f_s}{p} = \frac{120(60)}{4} = 1800 \text{ r/min}$$

$$\Rightarrow n_m = (1 - s)n_{sync} = 1760 \text{ r/min}$$

b) The total impedance per phase is calculated as

$$\mathbf{Z}_{total} = 11.72 + j7.79 = 14.07 \angle 33.6^\circ \Omega$$

$$\Rightarrow \mathbf{I}_1 = \frac{\mathbf{V}_\phi}{\mathbf{Z}_{total}} = \frac{266 \angle 0^\circ}{14.07 \angle 33.6^\circ} = 18.88 \angle -33.6^\circ \text{ A}$$

c) The pf is  $\cos(33.6^\circ) = 0.833$  lagging.

## Example 1 – Solutions

$$\begin{aligned} \text{d) } P_{AG} &= P_{in} - P_{SCL} = \sqrt{3}V_{line}I_{line} \cos \theta - 3I_1^2 R_1 \\ &= \sqrt{3}(460)(18.88)0.833 - 3(18.88)^2 0.641 = 11845 \text{ W} \end{aligned}$$

$$P_{conv} = (1 - s)P_{AG} = 11585 \text{ W} \Rightarrow P_{out} = P_{conv} - P_{rot} = 10485 \text{ W}$$

$$\text{e) } T_{ind} = \frac{P_{conv}}{\omega_m} = \frac{P_{AG}}{\omega_{sync}} = 62.8 \text{ N.m.} \quad T_{load} = \frac{P_{out}}{\omega_m} = 56.9 \text{ N.m.}$$

$$\text{f) } \text{The efficiency of the motor } \eta = \frac{P_{out}}{P_{in}} \times 100\% = 83.7\%$$



## Example 2

A three-phase 230 V, 60 Hz, 100-hp (1 hp = 746 W), six-pole induction motor operating at rated conditions has an efficiency of 91 % and draws a line current of 248 A. The stator copper and rotor copper losses are 2803 W and 1549 W, respectively. Determine:

- |                  |                       |
|------------------|-----------------------|
| a) Power input   | d) Rotor speed        |
| b) Total losses  | e) Input power factor |
| c) Air-gap power | f) Rotational losses  |

(Solutions →)

## Example 2 – Solutions

a)  $\text{Eff } \eta = \frac{(P_{out} = 100 \times 746)}{P_{in}} \Rightarrow P_{in} = 81978 \text{ W}$

b)  $\text{Total losses} = P_{in} - P_{out} = 7378 \text{ W}$

c)  $P_{AG} = P_{in} - P_{SCL} = 79175 \text{ W}$

## Example 2 – Solutions

d) From  $P_{RCL} = sP_{AG} \Rightarrow s = 0.01956$

$$n_{sync} = 120 \frac{f_s}{p} = 1200 \text{ rpm}$$


$$n_m = (1 - s) n_{sync} = 1176 \text{ rpm}$$

e) From  $P_{in} = \sqrt{3}V_{line} I_{line} \cos \theta \Rightarrow \cos \theta = 0.83$

f)  $P_{rot} = \text{Total losses} - P_{SCL} - P_{RCL} = 3026 \text{ W}$

In this lecture, you have learnt:

- ❖ The equations that relate the respective powers and torques in an induction motor.
- ❖ The separation of air-gap power into the rotor copper loss and the power converted in an induction motor, and representing them as distinct elements in the equivalent circuit.
- ❖ The calculations of the various powers, torques and motor efficiency from the induction motor equivalent circuit for a given operating condition.

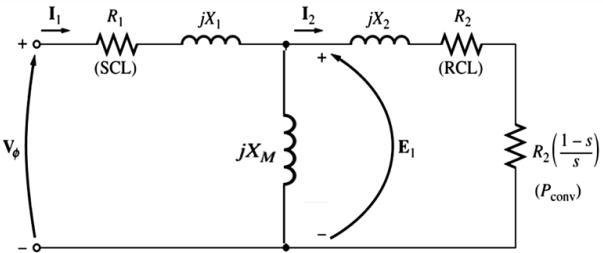No.	Slide No.	Image	Reference
1	5		<p>Adapted from <i>Electric Machinery Fundamentals, 5th ed.</i>, (p. 326), by S. J. Chapman, 2012, New York, NY: McGraw-Hill. Copyright 2012 by The McGraw-Hill Companies, Inc. Adapted with permission.</p>