



## Appendix A

### List of Formulae (with the usual notations)
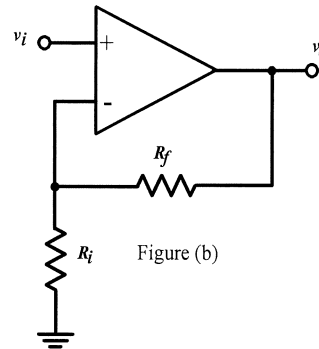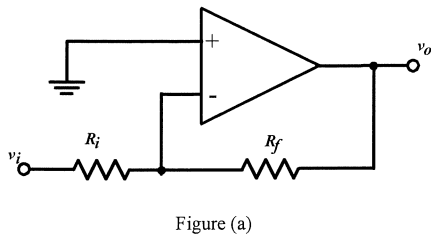
#### Op-Amps:

Closed-Loop Negative Feedback Inverting Gain,  $A_{VCL} = \frac{v_o}{v_i} = -\frac{R_f}{R_i}$  Figure (a)

Closed-Loop Negative Feedback Non-Inverting Gain,  $A_{VCL} = \frac{v_o}{v_i} = \left(1 + \frac{R_f}{R_i}\right)$  Figure (b)



Op-Amp's Slew Rate,  $SR \geq \left| \frac{dv_o}{dt} \right|_{\max} = A_{VCL} \omega a_m = A_{VCL} a_m 2\pi f$ ,


where  $v_i = a_m \sin(\omega t)$ ,  $v_o = A_{VCL} v_i$ ,  $v_o = A_{VCL} a_m \sin(\omega t)$  and  $\left| \frac{dv_o}{dt} \right| = A_{VCL} \omega a_m \cos(\omega t)$

Op-Amp's frequency response:  $A_{VOL}(jf) = \frac{A_o}{\left(1 + \frac{jf}{f_p}\right)}$

Gain-Bandwidth Product:  $A_o f_p = f_o = \frac{1}{\beta} (BW)_{CL}$

where  $\frac{1}{\beta} = \frac{R_f + R_i}{R_i}$

$t_r = \frac{0.35}{(BW)_{CL}}$

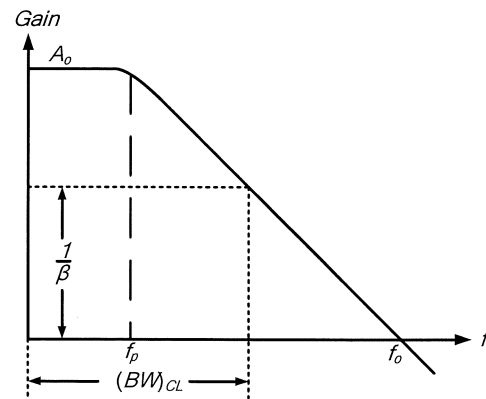

#### Diodes:

$v_D \approx nV_T \ln\left(\frac{i_D}{I_S}\right)$  or  $i_D \approx I_S e^{\left(\frac{v_D}{nV_T}\right)}$

where  $e^x = 1 + x + \frac{x^2}{2!} + \frac{x^3}{3!} + \frac{x^4}{4!} + \dots$

Diode conductance:  $g_D = \frac{1}{r_D} = \frac{I_D}{nV_T}$

### **BJT in Forward Active Region:**

Ignore early effect:  $i_C = I_S \exp\left(\frac{|v_{BE}|}{V_T}\right)$

With early effect:  $i_C = I_S \exp\left(\frac{|v_{BE}|}{V_T}\right) \left(1 + \frac{|v_{CE}|}{V_A}\right)$

where  $I_S$ : Saturation current,

$V_T$ : Thermal voltage, assume 25 mV at room temperature,

$V_A$ : Early voltage.

For npn transistor,  $|v_{BE}| = v_{BE}$  and  $|v_{CE}| = v_{CE}$ ;

For pnp transistor,  $|v_{BE}| = v_{EB}$  and  $|v_{CE}| = v_{EC}$ .

### **Small-signal model parameters of BJT:**

$$g_m = \frac{I_C}{V_T}, \quad r_\pi = \frac{\beta}{g_m} \quad \text{and} \quad r_o = \frac{V_A + |V_{CE}|}{I_C} \approx \frac{V_A}{I_C}$$

where  $I_C$ : DC collector current at Q-point

$V_{CE}$ : DC collector-emitter voltage at Q-point

Criterion for small-signal operation of BJT:  $|v_{be}| \leq 0.2V_T$

### **MOSFET in Saturation Region:**

Criterion:  $V_{DS} \geq V_{GS} - V_{TN}$  for NMOS;

$|V_{DS}| \geq |V_{GS}| - |V_{TP}|$  for PMOS

where  $V_{TN}, V_{TP}$ : Threshold voltage,

$V_{DS}$ : DC drain-source voltage,

$V_{GS}$ : DC gate-source voltage.

Ignore channel-length modulation effect:  $i_D = \frac{K_n}{2} (v_{GS} - V_{TN})^2$  for NMOS,

$$i_D = \frac{K_p}{2} (|v_{GS}| - |V_{TP}|)^2 \quad \text{for PMOS.}$$

With channel-length modulation effect:  $i_D = \frac{K_n}{2} (v_{GS} - V_{TN})^2 (1 + \lambda v_{DS})$  for NMOS,

$$i_D = \frac{K_p}{2} (|v_{GS}| - |V_{TP}|)^2 (1 + \lambda |v_{DS}|) \quad \text{for PMOS.}$$

where  $\lambda$ : channel length modulation parameter,

For NMOS  $K_n = K'_n \left(\frac{W}{L}\right)$  and  $K'_n = \mu_n C_{ox}$ ; For PMOS  $K_p = K'_p \left(\frac{W}{L}\right)$  and  $K'_p = \mu_p C_{ox}$ .

### MOSFET in Triode Region:

Criterion:  $V_{DS} < V_{GS} - V_{TN}$  for NMOS;  
 $|V_{DS}| < |V_{GS}| - |V_{TP}|$  for PMOS

Ignore channel-length modulation effect:

$$i_D = K_n \left( v_{GS} - V_{TN} - \frac{v_{DS}}{2} \right) v_{DS} \quad \text{for NMOS,}$$

$$i_D = K_p \left( |v_{GS}| - |V_{TP}| - \frac{|v_{DS}|}{2} \right) |v_{DS}| \quad \text{for PMOS.}$$

With channel-length modulation effect:  $i_D = K_n \left( v_{GS} - V_{TN} - \frac{v_{DS}}{2} \right) v_{DS} (1 + \lambda v_{DS})$  for NMOS,

$$i_D = K_p \left( |v_{GS}| - |V_{TP}| - \frac{|v_{DS}|}{2} \right) |v_{DS}| (1 + \lambda |v_{DS}|) \quad \text{for PMOS.}$$

### Small-signal model parameters of MOSFET

For NMOS:  $g_m = \sqrt{2K_n I_D (1 + \lambda V_{DS})} \approx \sqrt{2K_n I_D}$  and  $r_o = \frac{\frac{1}{\lambda} + V_{DS}}{I_D} \approx \frac{1}{\lambda I_D}$

For PMOS:  $g_m = \sqrt{2K_p I_D (1 + \lambda |V_{DS}|)} \approx \sqrt{2K_p I_D}$  and  $r_o = \frac{\frac{1}{\lambda} + |V_{DS}|}{I_D} \approx \frac{1}{\lambda I_D}$

where  $I_D$  : DC drain current at Q-point  
 $V_{DS}$  : DC drain-source voltage at Q-point


Criterion for small-signal operation:

For NMOS:  $|v_{gs}| \leq 0.2(V_{GS} - V_{TN})$

For PMOS:  $|v_{gs}| \leq 0.2(|V_{GS}| - |V_{TP}|)$

where  $V_{GS}$  : DC gate-source voltage at Q-point.

### Frequency Response: OCTC and SCTC

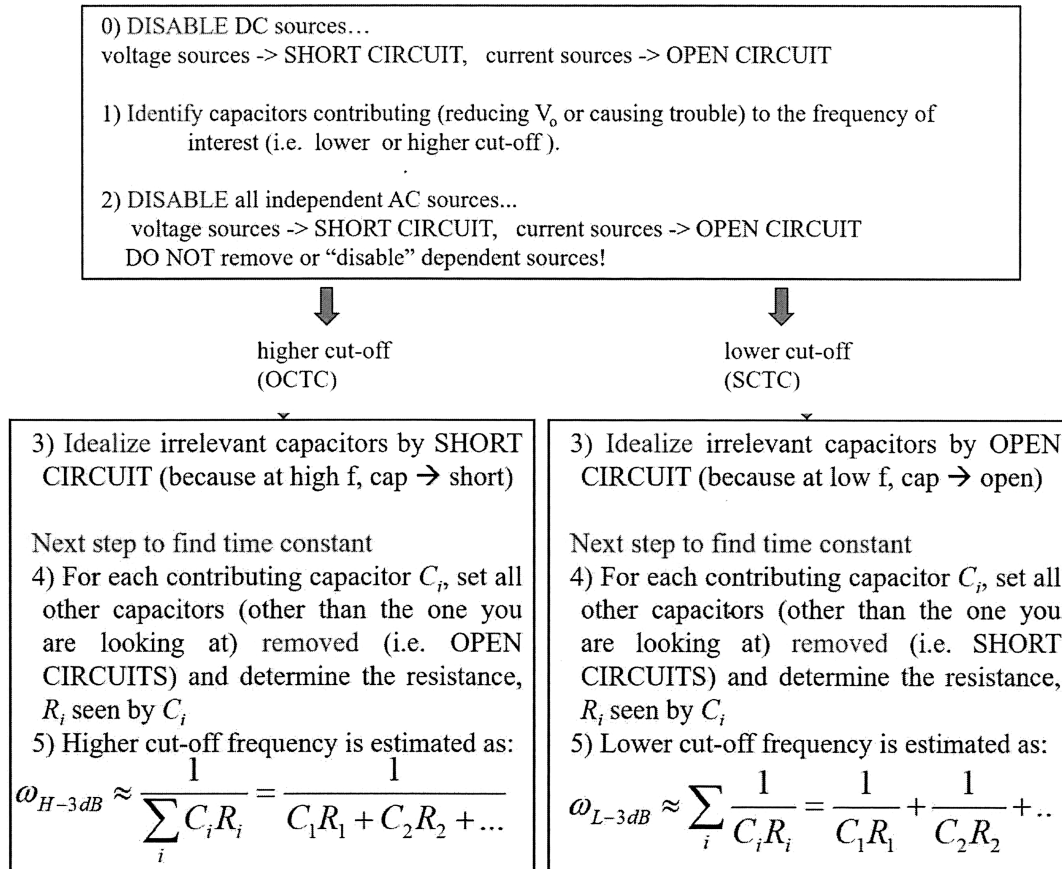

END OF PAPER