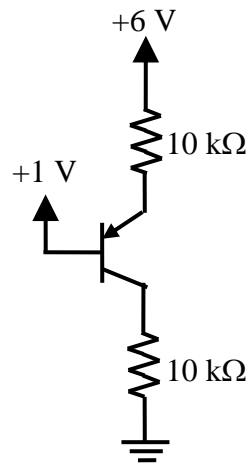



Nanyang Technological University
School of Electrical & Electronic Engineering
E2002 Analog Electronics – Tutorial 5

1. Identify the region of operation for the following circuits. What is the V_C , V_E , I_B , I_C and I_E in each case. If active, what is the collector voltage? Assume $|V_{BE}| = 0.7$ V and $\beta = 100$.

(Ans: (a) Saturation, $V_C = 1.4$ V, $V_E = 1.7$ V, $I_B = 0.29$ mA, $I_C = 0.14$ mA, $I_E = 0.43$ mA;
 (b) Active, $V_C = -13.68$ V, $V_E = -20.7$ V, $I_B = 18.4$ μ A, $I_C = 1.86$ mA, $I_E = 1.86$ mA)



(a)

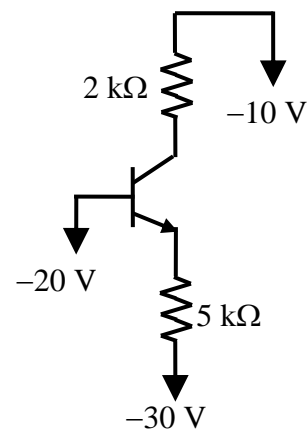

(b)

Figure 1

2. A common-emitter amplifier circuit is shown in Figure 2. Assume that the capacitors have infinite value, $\beta = 100$, $V_{CC} = V_{EE} = 15$ V, $R_I = 750$ Ω , $R_1 = R_2 = 200$ k Ω , $R_L = 100$ k Ω , $R_E = 280$ k Ω , and $R_C = 100$ k Ω . Calculate the DC operating point of the amplifier.
 (Ans: $I_C = 50$ μ A, $V_{EC} = 10.86$ V).

Calculate the dc power dissipation in each element in the amplifier circuit. Compare the result to the total power delivered by the sources.

(Ans: $P_{R1} = 1.125$ mW, $P_{R2} = 1.125$ mW, $P_{Rc} = 0.25$ mW, $P_{RE} = 0.71$ mW, $P_{BJT} = 0.54$ mW. $P_S = 3.76$ mW)

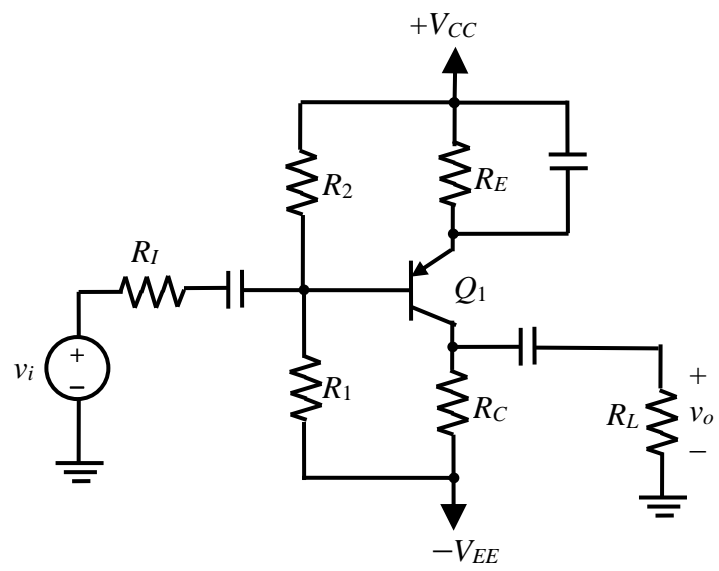


Figure 2