

EE2002

TUTORIAL 3 (with answers at the back)

1. The op-amp in Fig 1 has a slew rate of $0.50\text{V}/\mu\text{S}$. The amplifier must be capable of amplifying the following input signals:

$$v_1 = 0.01\sin(10^6 t)$$

$$v_2 = 0.05\sin(350 \times 10^3 t)$$

$$v_3 = 0.10\sin(200 \times 10^3 t)$$

$$v_4 = 0.20\sin(50 \times 10^3 t)$$

- a) Determine whether the output will be distorted due to slew-rate limitations on any input.
b) If so, find a remedy (other than changing the input signals).

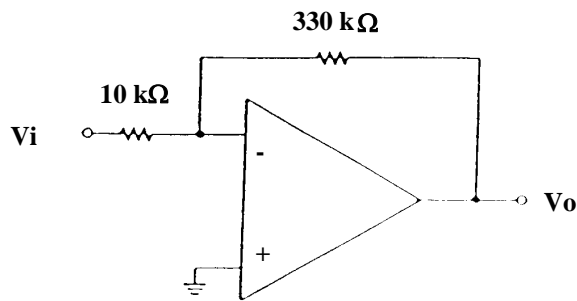


Fig. 1

- 2.a) What minimum SR is necessary for a unity-gain amplifier that must pass, without distortion, the input waveform shown in Fig 2.

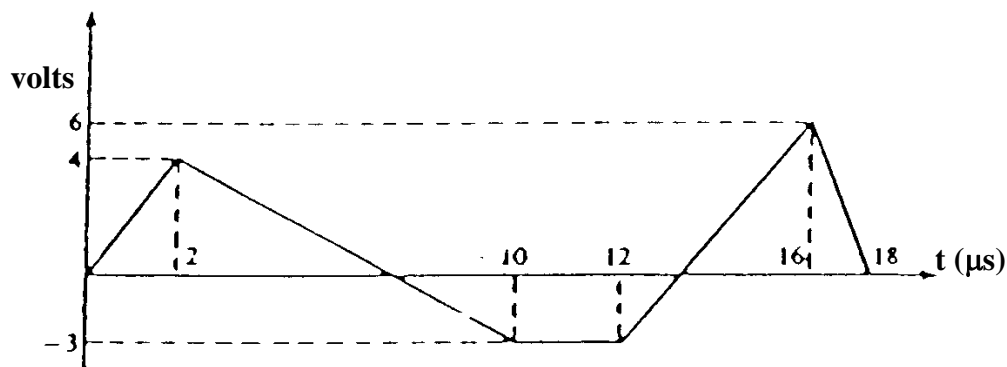


Fig. 2

- 2.b) Repeat (a), if the amplifier is in a noninverting configuration with $R_1=50\text{k}\Omega$ and $R_f=100\text{k}\Omega$.
3. In a certain application, a signal source having $60\text{k}\Omega$ of source resistance produces a 1-V-rms signal. The signal must be amplified to 2.5V rms and drive a $1\text{k}\Omega$ load. Assuming that the phase of the load voltage is of no concern, design an op-amp circuit for the application.

4.a) Determine the empirical diode junction equation for a 1N4005 diode given the following voltage and current values:

$$V_{D1} = 0.6\text{V} @ I_{D1} = 2.3\text{mA}$$

$$V_{D2} = 0.8\text{V} @ I_{D2} = 245\text{mA}$$

4.b) Use the empirical diode junction equation, obtained in 4(a), to calculate the diode voltage V_D for a 1N4005 diode when the diode current is

i) $I_D = 20\text{ mA}$

ii) $I_D = 300\text{ mA}$

4.c) A 1N4005 diode is used in the circuit shown in Fig. 3, determine the diode voltage and current by means of successive iteration method.

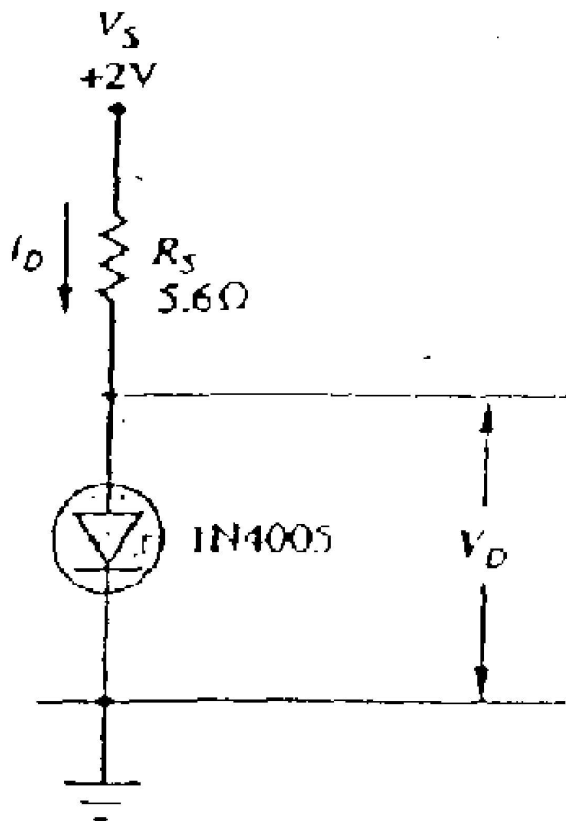


Fig. 3

5. Determine the AC component of the output voltage, v_{OUT} , for the circuit in Fig. 4 when $V_{SDC}=5V$ DC.

The data sheet for the 1N4305 diode has the following voltage and current values:

$$V_D = 0.50V \text{ at } I_D = 250\mu A$$

$$V_D = 0.70V \text{ at } I_D = 10mA$$

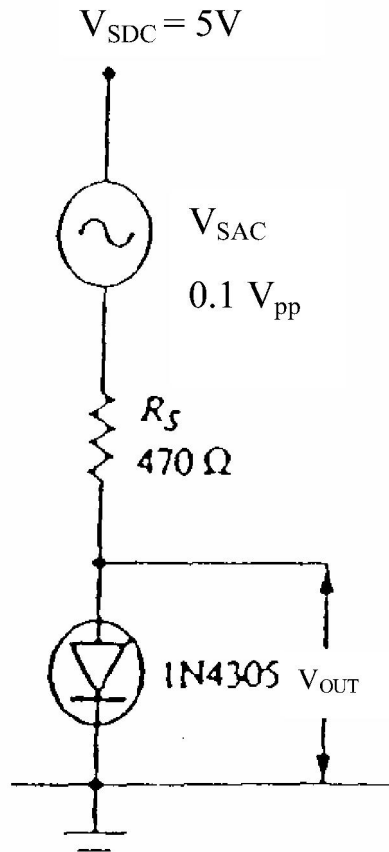


Fig. 4

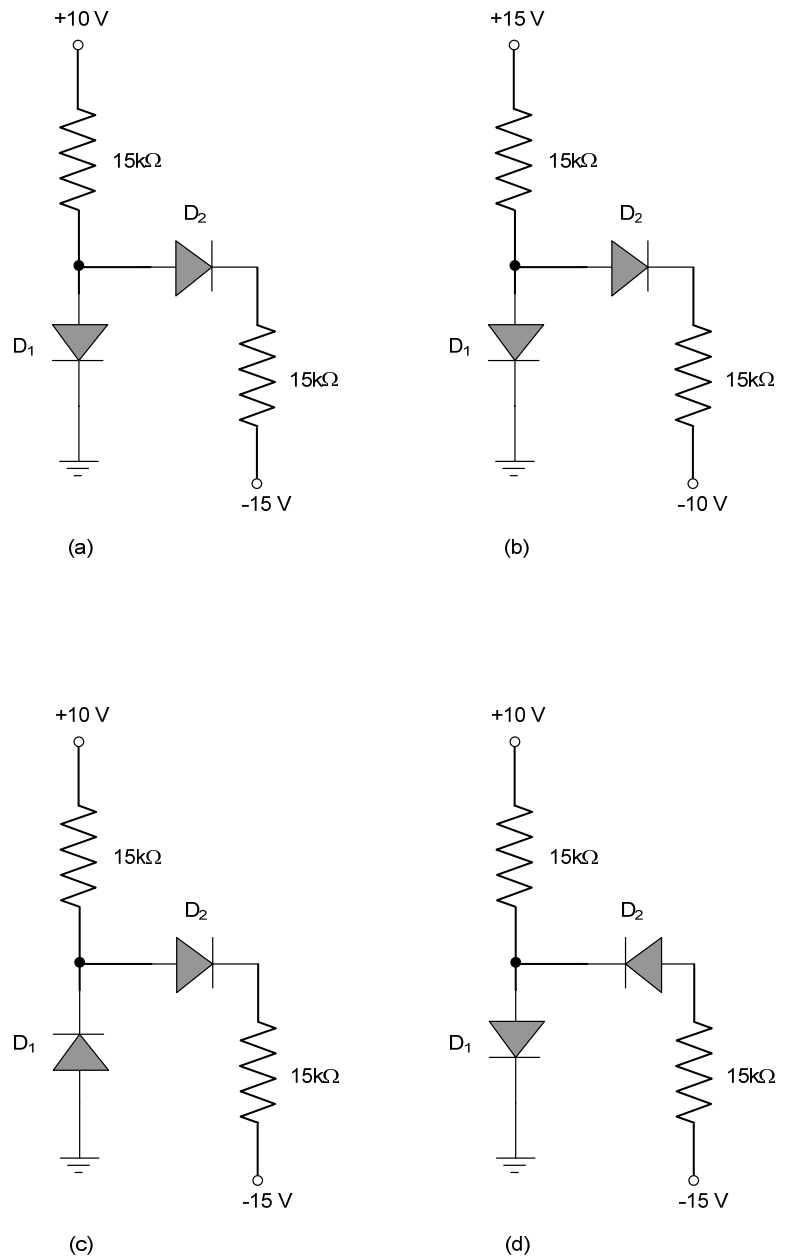


Fig. 5

6. Find the Q points of the diodes in the circuits of Fig. 5. For forward biased diode, the diode voltage is given as 0.75V.

Answers to Tutorial 3

1. (a) The output due to v_2 and v_3 will be distorted.
 (b) There are only two remedies:
 - (i) find an amp with greater SR, a SR of at least $0.66 \text{ V}/\mu\text{s}$
 - (ii) reduce the A_{CL} of the present amplifier to 25 V/V .
2. (a) The minimum SR is $3.0 \text{ V}/\mu\text{s}$
 (b) The $(SR)_{\min} = 9 \text{ V}/\mu\text{s}$
3. Many right answers.

4. (a) The empirical junction equation for the IN4005 diode is

$$i_D \approx (1.90 \text{ nA}) e^{v_D / 42.8 \text{ mV}}$$

$$\text{or } v_D = (42.8 \text{ mV}) \ln\left(\frac{i_D}{1.90 \text{ nA}}\right)$$

- (b)
 - (i) For $I_D = 20 \text{ mA}$, $V_D = 0.692 \text{ V}$
 - (ii) For $I_D = 300 \text{ mA}$, $V_D = 0.808 \text{ V}$

$$(c) \quad V_D = 0.794 \text{ V}$$

$$I_D = 215 \text{ mA}$$

5. $v_{OUT} = 1.24 \text{ mV}_{PP}$

6.

	D1	D2
(a)	-2.13V, 0A	0.75V, 0.808mA
(b)	0.75V, 0.283mA	0.75V, 0.667mA
(c)	0.75V, 0.183mA	0.75V, 0.9mA
(d)	0.75V, 0.617mA	-15.75V, 0A