

NANYANG
TECHNOLOGICAL
UNIVERSITY
SINGAPORE

EE3001 Engineering Electromagnetics

This session is about

35. Analysis and Design of Transmission Line


Learning Objectives

- Plot \hat{Z}_{in} - circle using $\hat{Z}_{in}(z)$ or $\Gamma(z)$ at any position z ;
- Plot \hat{Z}_{in} - circle using SWR on the transmission line; and
- Given \hat{Z}_L and ℓ/λ , determine $Z_{in}(z)$; and
- Given $\hat{Z}_{in}(z)$ and ℓ/λ , determine \hat{Z}_L (unknown load impedance); and
- Given \hat{Z}_{in} and \hat{Z}_L , determine ℓ/λ of a Transmission line.

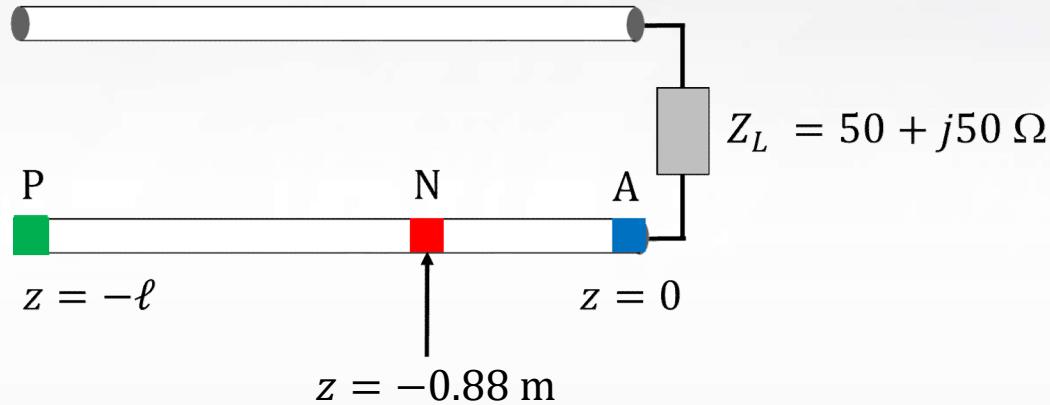Example 1


- $f = 30 \text{ MHz}, u_p = 3 \times 10^8 \text{ m/s}$ $[f\lambda = u_p]$
- Determine Z_{in} & Γ at A, P and N

$$Z_o = 50 \Omega, \ell = 2.13 \text{ m}$$



$$\square Z_o = 50 \Omega, \beta = \frac{\omega}{u_p} = \frac{2\pi \times 30 \times 10^6}{3 \times 10^8} = 0.2\pi \text{ rad/m} \quad [\lambda = 10 \text{ m}]$$

Example 1


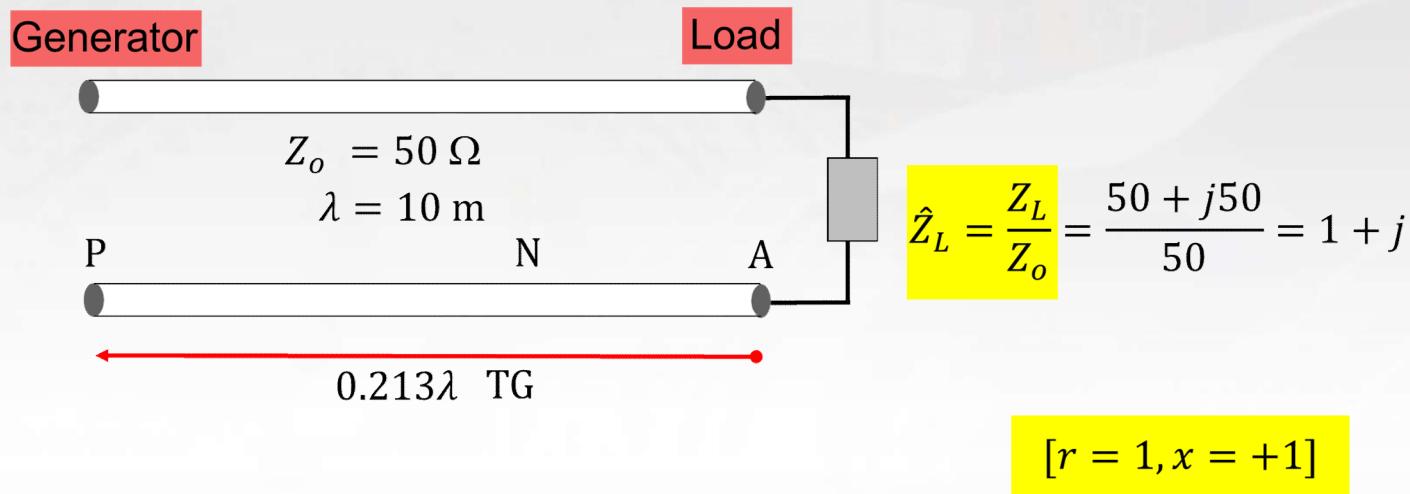


Note: All impedance divide by Z_o and distance divide by λ

$$\frac{AP}{\lambda} = \frac{2.13}{10\text{m}} = 0.213 \rightarrow \text{A to P} = 0.213\lambda \text{ Towards Generator} \\ = 0.213 \text{ WTG}$$

$$\frac{AN}{\lambda} = \frac{0.88\text{m}}{10} = 0.088 \rightarrow \text{A to N} = 0.088 \text{ WTG}$$


Example 1

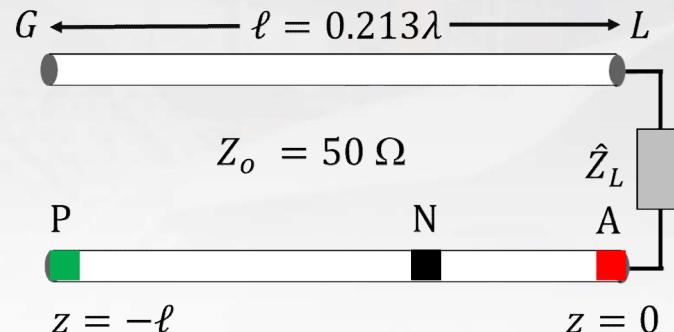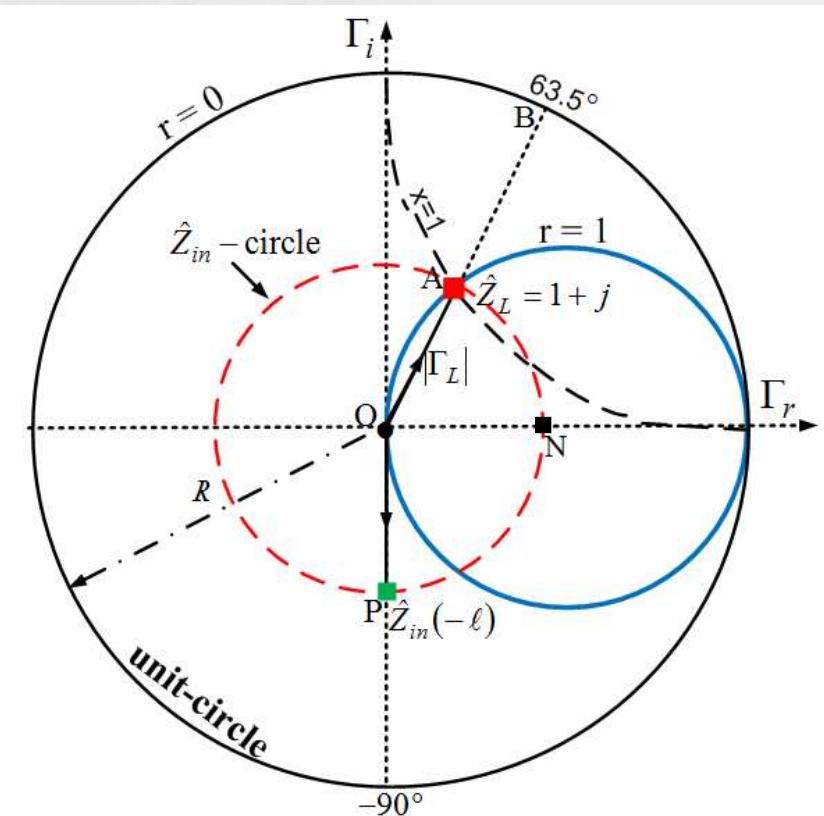


$\hat{Z}_L = 1 + j \Rightarrow r = 1, x = +1$
Plot point A on Smith Chart

- @A: $|\Gamma_L| = \frac{OA}{OB} = 0.45$; $\theta_\Gamma = 63.5^\circ$
- Plot \hat{Z}_{in} -circle: radius = OA center at O
- P TG A

Example 1

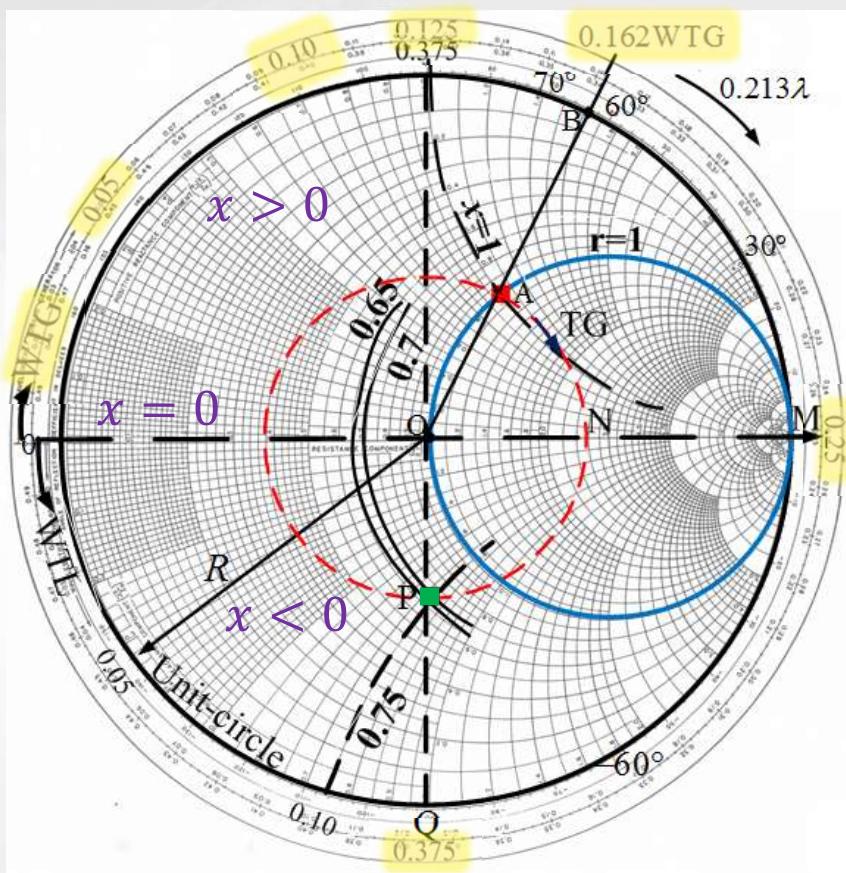

Page 35-6 of 35-30

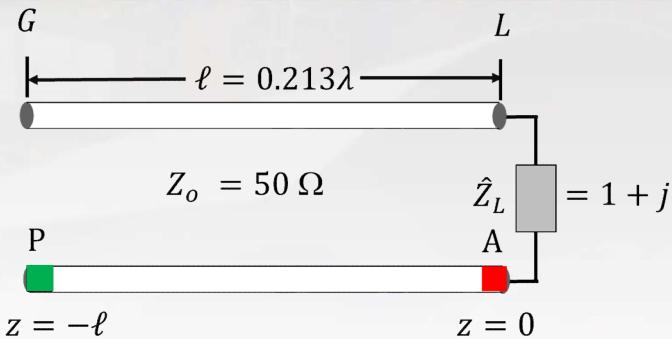

$$@A: \hat{Z}_L = 1 + j \\ r = 1, x = +1$$

$$A@ 0.162 \text{ WTG} \\ P@ 0.162 \text{ WTG} \\ + \frac{0.213}{0.375} \text{ WTG}$$


$$@P: |\Gamma| = 0.45, \theta_\Gamma = -90^\circ$$

$$\Gamma = 0.45 \angle -90^\circ$$

$$r = 0.675, x = -0.75$$

$$\hat{Z}_{in} = 0.675 - j0.75$$
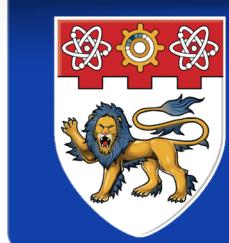
$$Z_{in} = \hat{Z}_{in} Z_o = 33.8 - j37.5 \Omega$$



NANYANG
TECHNOLOGICAL
UNIVERSITY
SINGAPORE

EE3001 Engineering Electromagnetics

This session is about

35. Analysis and Design of Transmission Line (2)

Example 1

- Use of Smith Chart to determine $\hat{Z}_{in}(z)$
- All $\hat{Z}_{in}(z)$ along the transmission line $-\ell \leq z \leq 0$ lie on the \hat{Z}_{in} -circle, to find \hat{Z}_{in} at a specific point such as point P, we need a **reference point on the line** e.g. $\hat{Z}_L \equiv$ point A can be used as the reference.
- To determine \hat{Z}_{in} @ point P, we move from the reference point, A, to P, a distance of 0.213 **Wavelength Towards Generator(WTG)**.
NOTE: **WTG scale** starts at extreme left and increases from 0 to 0.5 in a **clockwise direction**.
- The **initial position** of \hat{Z}_L [Point A] can be obtained from the **WTG scale** i.e.
A @ 0.162 WTG

Example 1

- P on WTG scale: $(0.162 + 0.213) = 0.375$ [along straight line OQ].
- The intersection between the straight line OQ and the \hat{Z}_{in} -circle gives Point P.
- @ Point P

$$r = 0.675, \quad x = -0.75 \quad ; \quad |\Gamma| = \frac{OP}{OQ} = 0.45$$

$$\hat{Z}_{in} = r + jx = 0.675 - j0.75 \quad ; \quad \theta_\Gamma = -90^\circ$$

$$Z_{in} = \hat{Z}_{in} Z_o = 33.8 - j37.5 \Omega \quad ; \quad \Gamma = 0.45\angle - 90^\circ$$

Example 1

□ To obtain \hat{Z}_{in} & Γ at point N [AN = 0.088 WTG], we may start from A @ 0.162 WTG, moves 0.088 WTG i.e. N is located at $(0.162 + 0.088) = 0.25$ WTG [along straight line OM].

□ Intersection between \hat{Z}_{in} -circle and OM gives Point N.

□ @ Point N

$$r = 2.62, x = 0;$$


$$\Gamma = 0.45\angle 0^\circ;$$

$$\hat{Z}_{in} = 2.62 + j0 \rightarrow Z_{in} = \hat{Z}_{in} Z_o = 131 \Omega = R_{max} + j0 @ \theta_\Gamma = 0^\circ$$


□ **Exercise:** Find \hat{Z}_{in} and Γ @ $z_1 = -1$ m $Az_1 = 0.1$ WTG [A @ 0.162 WTG]

□ **Ans:** $\hat{Z}_{in} = 2.54 - j0.42$, $Z_{in} = 127 - j21 \Omega$ $\Gamma = 0.45\angle - 9^\circ$ [z_1 @ 0.262 WTG]

Example 1

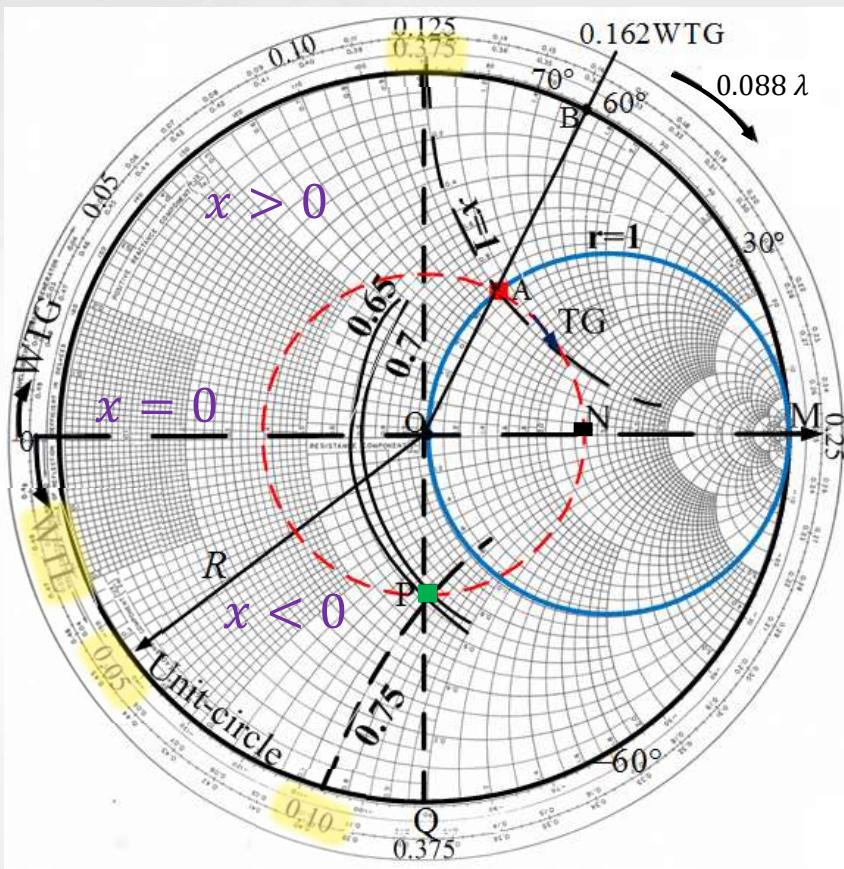

Page 35-10 of 35-30

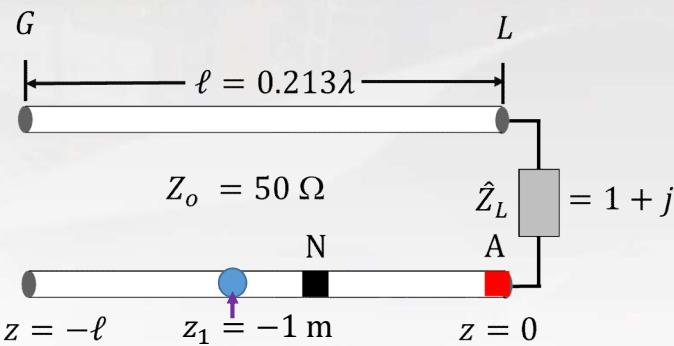

$$@A: \hat{Z}_L = 1 + j$$

$$r = 1, x = +1$$

$$A @ 0.162 \text{ WTG}$$

$$N @ 0.162 \text{ WTG}$$

$$+ 0.088$$

$$0.25 \text{ WTG}$$


$$@N: |\Gamma| = 0.45, \theta_\Gamma = 0^\circ$$

$$\Gamma = 0.45 \angle 0^\circ$$

$$r = 2.62, x = 0$$

$$\hat{Z}_{in} = 2.62 - j0$$
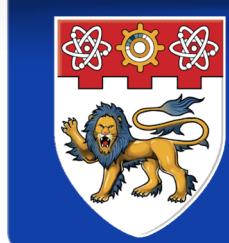
$$Z_{in} = \hat{Z}_{in} Z_o = 131 \Omega$$



NANYANG
TECHNOLOGICAL
UNIVERSITY
SINGAPORE

EE3001 Engineering Electromagnetics

This session is about

35. Analysis and Design of Transmission Line (3)



Example 1

- Use of Smith Chart to determine positions of Voltage maximum and minimum along Transmission Line $-\ell \leq z \leq 0$ [$\ell = 0.213\lambda$]

- Find the distance from the load [Point A] to the first voltage maximum.

@ $z_{max}, \theta_\Gamma = 0^\circ$ [i.e. $z_{max} \equiv$ Point N]

$$\therefore d_{max} = |A \rightarrow N| = (0.25 - 0.162)\lambda = 0.088\lambda. \quad [z_{max} = -0.088\lambda]$$



- Find the position of voltage minimum on the transmission line.

$$\therefore d_{min} = (d_{max} + 0.25)\lambda = 0.338\lambda > \ell = 0.213\lambda \quad [z_{min} = -0.338\lambda]$$

The position of voltage minimum is the point nearest to Point V ($\theta_\Gamma = \pm 180^\circ$).

Since Point V is nearest to Point P, $z_{min} \equiv$ Point P.

Example 1

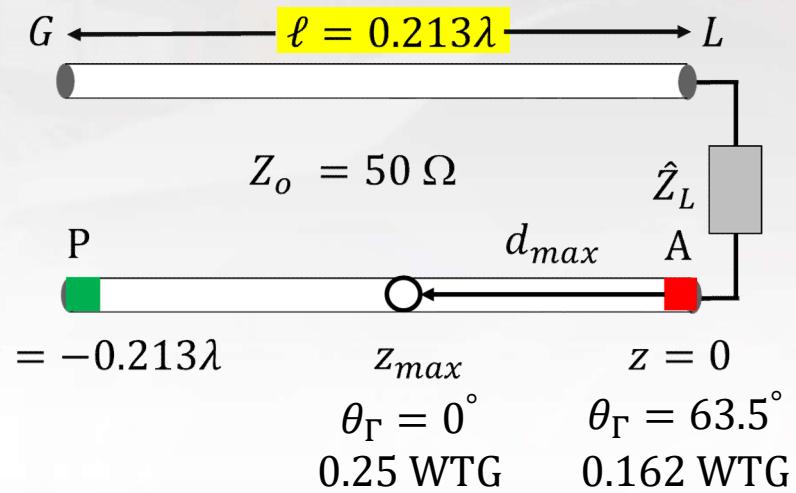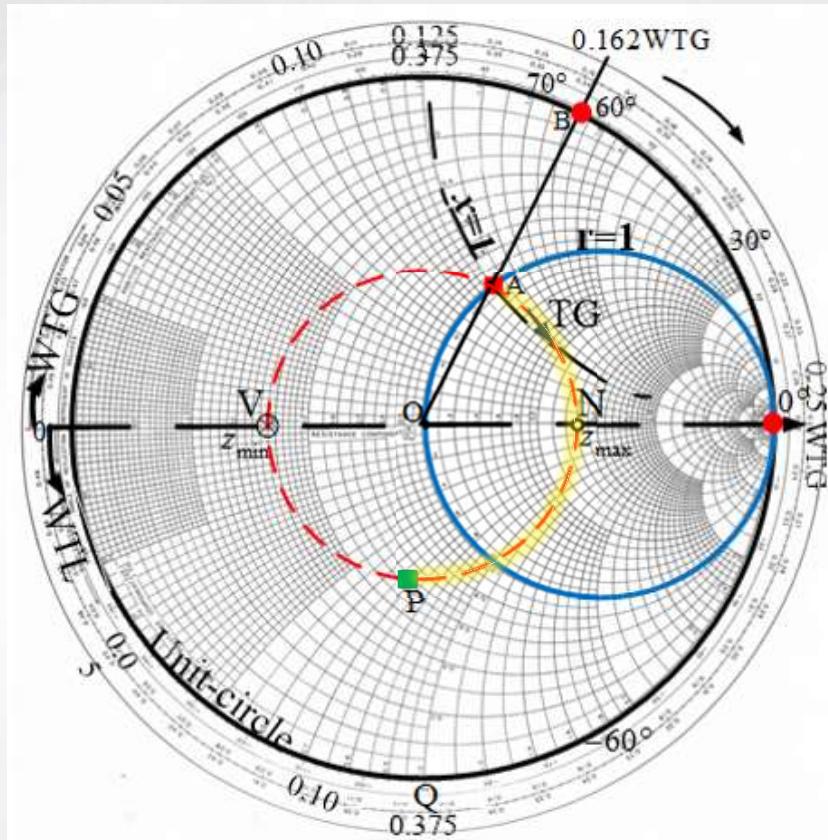


$$d_{max} = (0.25 - 0.162)\lambda = 0.088\lambda$$

$$z_{max} = -d_{max} = -0.088\lambda$$

$$z_{min} = -(d_{max} + 0.25) = -0.338\lambda$$

Example 1

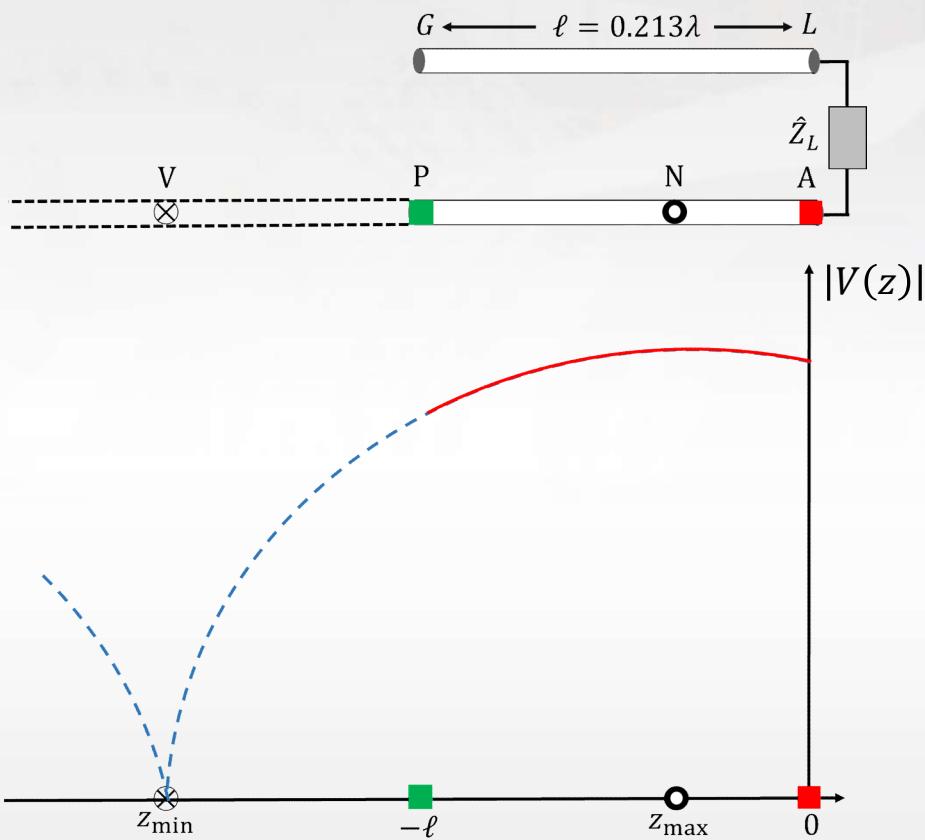

Example 1


- $\text{SWR} = \frac{|V|_{max}}{|V|_{min}} = \frac{1+|\Gamma_L|}{1-|\Gamma_L|} = \frac{1+0.45}{1-0.45} = 2.62$
- SWR can also be read directly from the \hat{Z}_{in} -circle:

$$\hat{Z}_{in} = \frac{1+|\Gamma_L|\angle\theta_\Gamma}{1-|\Gamma_L|\angle\theta_\Gamma} = \frac{1+|\Gamma_L|}{1-|\Gamma_L|} = \text{SWR} @ \theta_\Gamma = 0$$

$$@ \theta_\Gamma = 0^\circ: r = 2.62, x = 0 \rightarrow \hat{Z}_{in} = 2.62 + j0 = \text{SWR} + j0$$

- REMARKS: Knowing SWR of a transmission line e.g. $|V|_{max} = 6V$ and $|V|_{min} = 2V$, we have $\text{SWR} = 3$ and $\hat{Z}_{in} = 3 + j0 @ \theta_\Gamma = 0^\circ [r = 3, x = 0]$ can be plotted on the Smith Chart and \hat{Z}_{in} -circle can be drawn.

Example 1

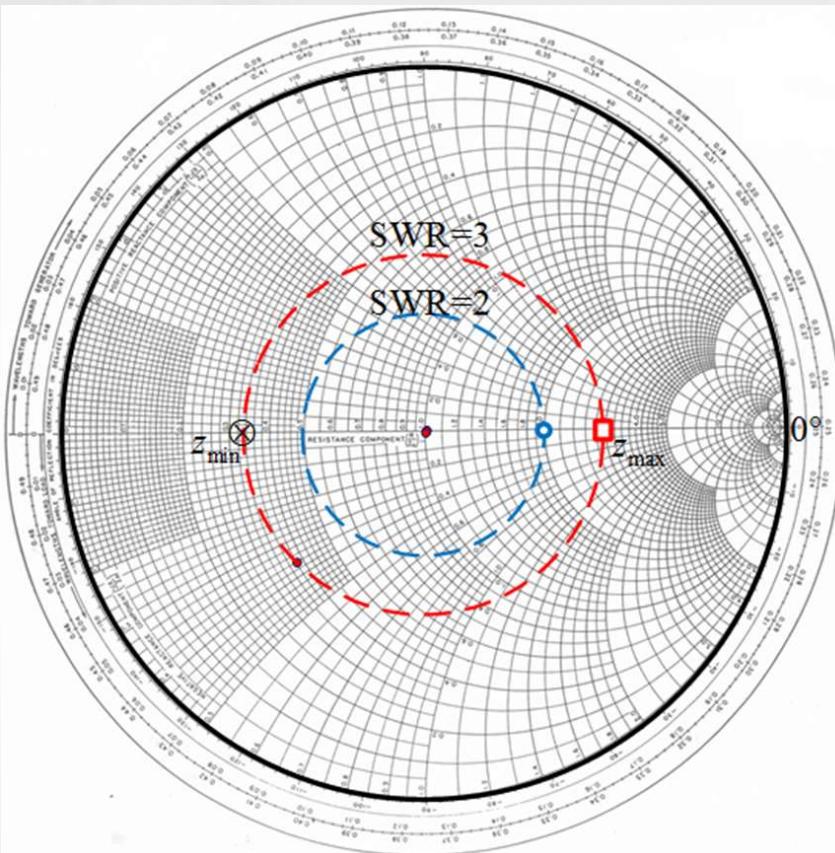

$$SWR = 2: \hat{Z}_{in} = 2 + j0 @ \theta_\Gamma = 0 \quad \text{blue circle}$$

$$SWR = 3: \hat{Z}_{in} = 3 + j0 @ \theta_\Gamma = 0 \quad \text{red square}$$

Example 2

- $|V|_{\max} = 57 \text{ V} @ z_{\max} = -10 \text{ cm}, |V|_{\min} = 15 \text{ V} @ z_{mi} = -21 \text{ cm}, Z_o = 100 \Omega$
 $\ell = 44 \text{ cm}$ find λ and $Z_{in}(-\ell)$.

(i) $\frac{\lambda}{4} = |z_{\max} - z_{\min}| \rightarrow \lambda = 44 \text{ cm}$

$$\text{SWR} = \frac{|V|_{\max}}{|V|_{\min}} = \frac{57}{15} = 3.8$$

(ii) $V @ 0 \text{ WTG}$


$$VP = 44 - 21 = 23 \text{ cm} = 0.523\lambda$$


$$P @ (0 + 0.523) = 0.523 \equiv 0.023 \text{ WTG}$$

$$\hat{Z}_{in} = 0.28 + j0.13$$

$$Z_{in}(-\ell) = \hat{Z}_{in} Z_o = 28 + j13 \Omega$$

$$Z_o = 100 \Omega$$

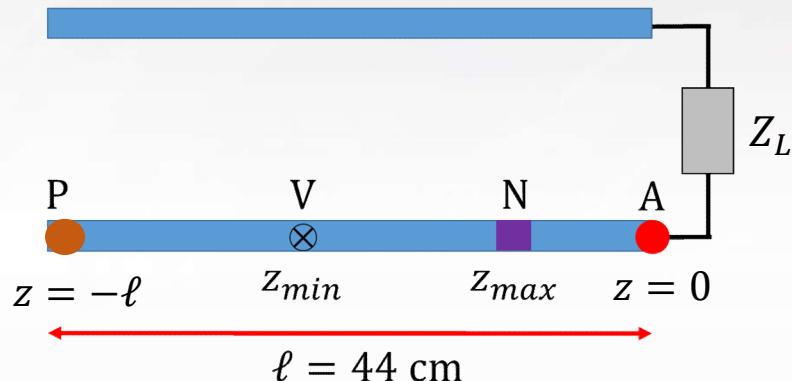

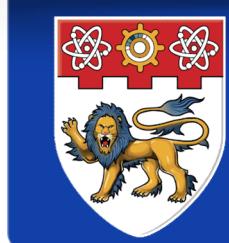

NANYANG
TECHNOLOGICAL
UNIVERSITY
SINGAPORE


EE3001 Engineering Electromagnetics

This session is about

35. Analysis and Design of Transmission Line (4)

Example 3

- Consider the transmission line as shown below, find $P_{in}(z)$ and $|V(z)|$ at points P, z_1 , N and A.

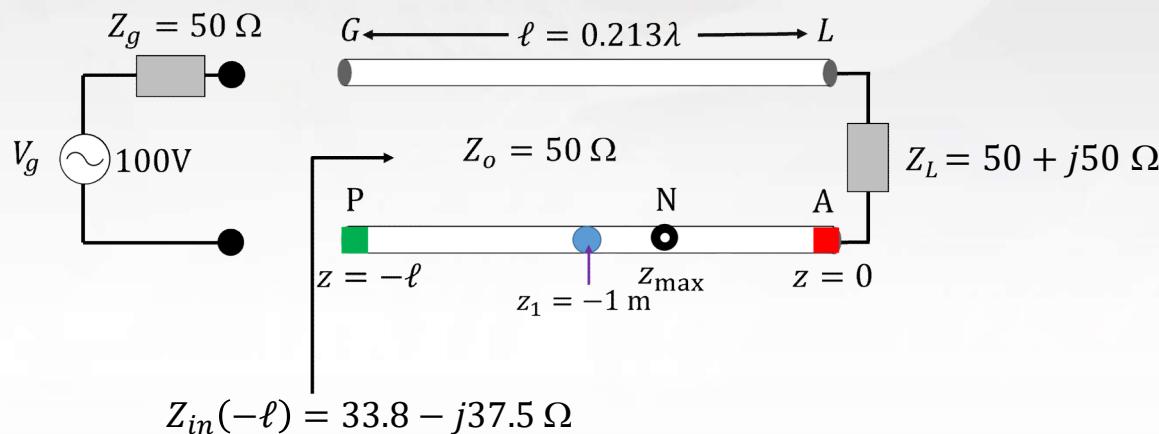

Given: $V_g = 100 \text{ V}$, $Z_g = 50 \Omega$, $Z_o = 50 \Omega$, $\ell = 0.213\lambda$, $Z_L = 50 + j50 \Omega$


The input impedance @P : $Z_{in}(-\ell) = 33.8 - j37.5 \Omega$ [Page 35-8]

@N : $Z_{in}(z_{\max}) = 131 \Omega$ [Page 35-10]

@ z_1 : $Z_{in}(z_1) = 127 - j21 \Omega$

Example 3

$|V(z)|$ and $P_{in}(z)$ @ Point P can be found using equivalent circuit at $z = -\ell$

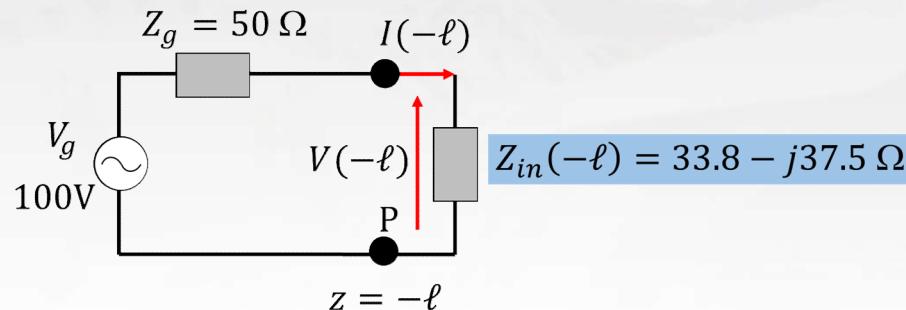

$$V(-\ell) = \frac{Z_{in}}{Z_g + Z_{in}} \times V_g = 50 - j22.4 = 54.8 \angle -24^\circ \quad [\text{Point P}]$$

$$\begin{aligned} P_{in}(-\ell) &= \frac{1}{2} |I(-\ell)|^2 \operatorname{Re}(Z_{in}) = \frac{1}{2} \left| \frac{V_g}{Z_g + Z_{in}} \right|^2 \operatorname{Re}(Z_{in}) \\ &= \frac{1}{2} \left| \frac{100}{50 + (33.8 - j37.5)} \right|^2 \times (33.8) = 20 \text{ W} = P_{in}(z) = P_L \end{aligned}$$



Example 3

$$P_{in}(z) = \frac{1}{2} \left| \frac{V(z)}{Z_{in}(z)} \right|^2 \operatorname{Re}(Z_{in}(z)) \rightarrow |V(z)| = \sqrt{\frac{2P_{in}(z) \times |Z_{in}(z)|^2}{\operatorname{Re}(Z_{in})}} \quad (5.8)$$

- At z_1 , $Z_{in}(z_1) = 127 - j21 \Omega$; $P_{in}(z_1) = 20 \text{ W}$

$$|V(z_1)| = \sqrt{\frac{2(20) \times (127^2 + 21^2)}{127}} = 72.2 \text{ V}$$

- At N: $z = z_{\max}$, $Z_{in}(z_{\max}) = 131 \Omega$; $P_{in}(z_{\max}) = 20 \text{ W}$

$$P_{in}(z_{\max}) = \frac{|V|_{\max}^2}{2R_{\max}} = 20 \text{ W} \rightarrow |V|_{\max} = 72.4 \text{ V}$$

- At A: $z = 0$, $Z_L = 50 + j50 \Omega$, $P_{in}(0) = P_L = 20 \text{ W}$, $|V_L| = 63.2 \text{ V}$

Example 3

REMARKS: Using (3) to obtain $V(z)$ and $V(z, t) = \text{Re}[V(z)e^{j\omega t}]$

$$V(z) = V_o^+ e^{-j\beta z} [1 + \Gamma_L e^{+j2\beta z}] \quad (3) \quad [\text{Page 28-8}]$$


$\Gamma_L = 0.45\angle 63.5^\circ$ can be found using Smith Chart or equation (5)

V_o^+ can be determined by substituting $V(-\ell) = 54.8\angle -24^\circ$ V,

$\Gamma_L = 0.45\angle 63.5^\circ$ and $\beta\ell = 2\pi \frac{\ell}{\lambda} = 2\pi(0.213)$ into (3):

$$V(-\ell) = V_o^+ e^{+j\beta\ell} [1 + \Gamma_L e^{-j2\beta\ell}] \quad (7) \quad [\text{Page 28-13}]$$

$$V_o^+ = 50\angle -76.7^\circ$$

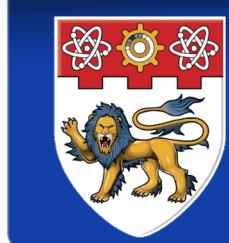

NANYANG
TECHNOLOGICAL
UNIVERSITY
SINGAPORE


EE3001 Engineering Electromagnetics

This session is about


35. Analysis and Design of Transmission Line (5)

Example 4

- Use of Smith Chart to determine unknown load Z_L
- Given $Z_{in} = 67.5 - j75 \Omega$, $Z_o = 100 \Omega$ and $\ell = 0.425\lambda$, find Z_L and Γ_L .

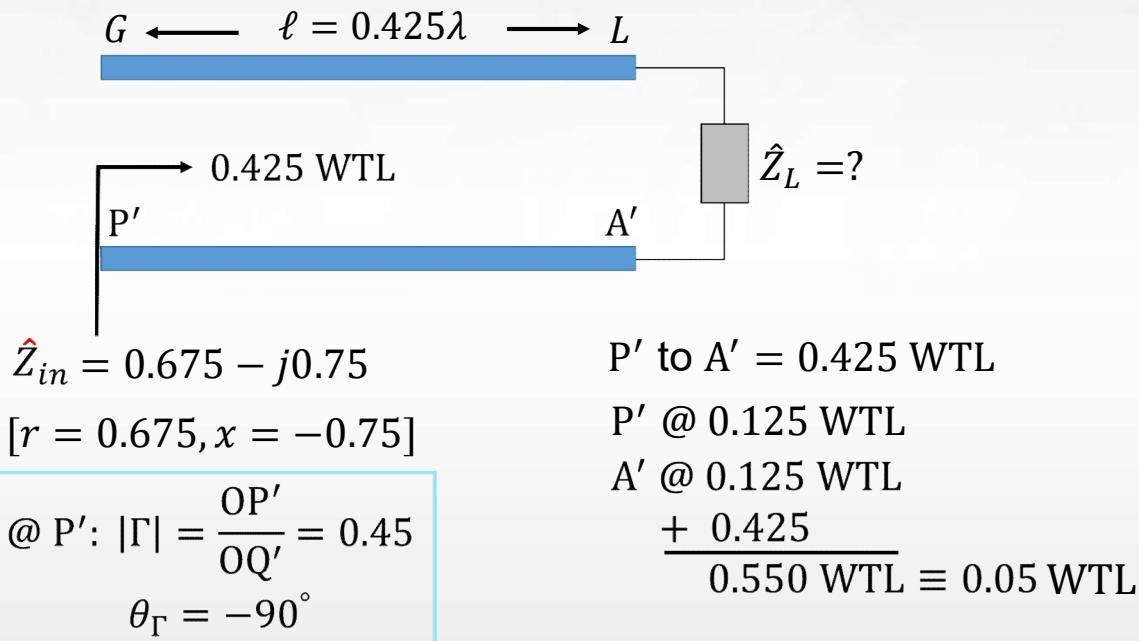

Example 4

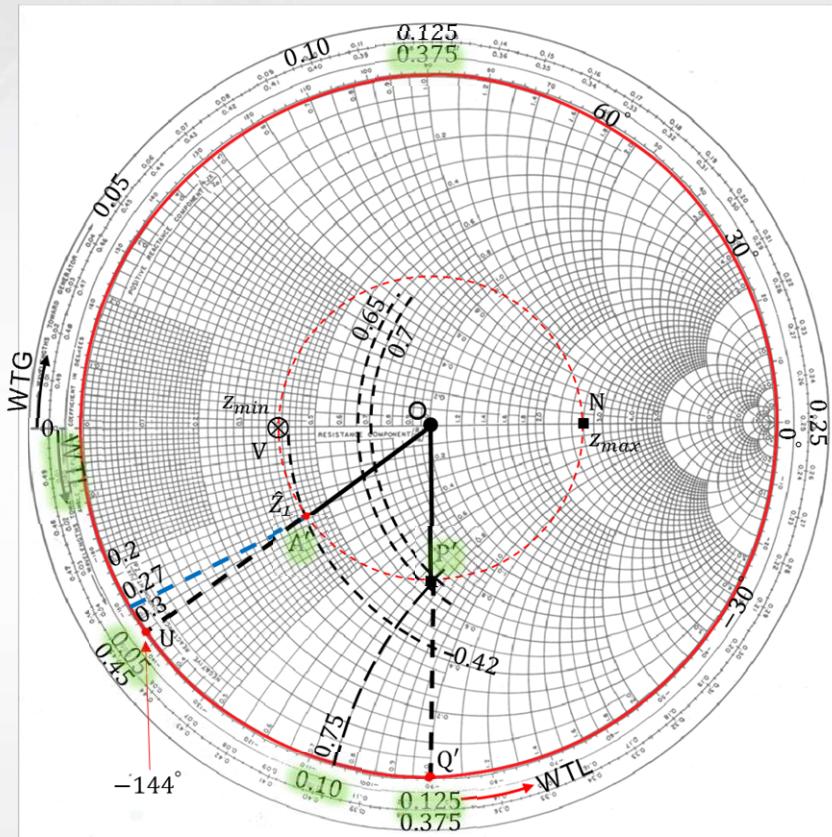

$r = 0.675$ and $x = -0.75$ @ P'
 P' @ 0.125 WTL, $\ell = 0.425\lambda$
 A' @ 0.550 WTL $\equiv 0.05$ WTL

@ A' : $\Gamma_L = 0.45 \angle -144^\circ$

$$r = 0.42, x = -0.27$$

$$\hat{Z}_L = 0.42 - j0.27$$

$$Z_L = \hat{Z}_L Z_0 = 42 - j27 \Omega$$

Example 4

- $\hat{Z}_{in} = Z_{in}/Z_o = 0.675 - j0.75$ (Plot Point P')
- Once P' is plotted on the chart, \hat{Z}_{in} -circle can be drawn.
- To find \hat{Z}_L , we need to move $P' \rightarrow A'$, 0.425 **Wavelength Towards Load (WTL)**.
- **NOTE:** Wavelength Towards Load (**WTL**) scale starts from 0 to 0.5 in **anti-clockwise direction**.
- The **initial position** of \hat{Z}_{in} [Point P'] on the **WTL scale** can be obtained i.e.
 $P' @ 0.125 \text{ WTL}$
- A' on WTL: $(0.125 + 0.425) = 0.55 \equiv 0.05 \text{ WTL}$ [along OU].
- The intersection between OU and \hat{Z}_{in} -circle gives Point A'.


Example 4

- Q: Find the position of voltage minimum, z_{min} , on the transmission line.
- From Point A' ($z = 0$) move TG: $A' \xrightarrow{\text{TG}} V \rightarrow N \rightarrow P'$
 $A' @ 0.45 \text{ WTG}, V @ 0 \text{ WTG} \equiv 0.5 \text{ WTG} \rightarrow A'V = (0.5 - 0.45)\lambda = 0.05\lambda$
 Point V is located 0.05λ from Point A'($z = 0$):

$$z_{min} = -0.05\lambda$$
- From Point P' ($z = -0.425\lambda$) move TL: $P' \xrightarrow{\text{TL}} N \rightarrow V \rightarrow A'$
 $P' @ 0.125 \text{ WTL}, V @ 0.5 \text{ WTL} \rightarrow P'V = (0.5 - 0.125)\lambda = 0.375\lambda$
 Point V is located 0.375λ from Point P'($z = -0.425\lambda$):

$$z_{min} = -(0.425 - 0.375)\lambda = -0.05\lambda$$

Example 4

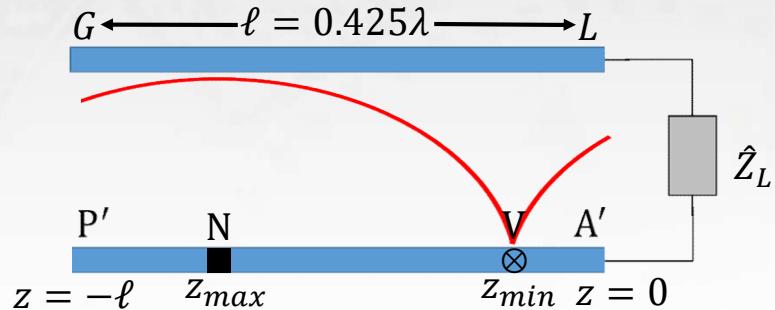

$A' @ 0.45 \text{ WTG}$

$P' @ 0.125 \text{ WTL}$

$V @ 0.5 \text{ WTG}$


$V @ 0.5 \text{ WTL}$


$$A'V = 0.05\lambda$$

$$P'V @ 0.375\lambda$$

$$z = -0.05\lambda$$
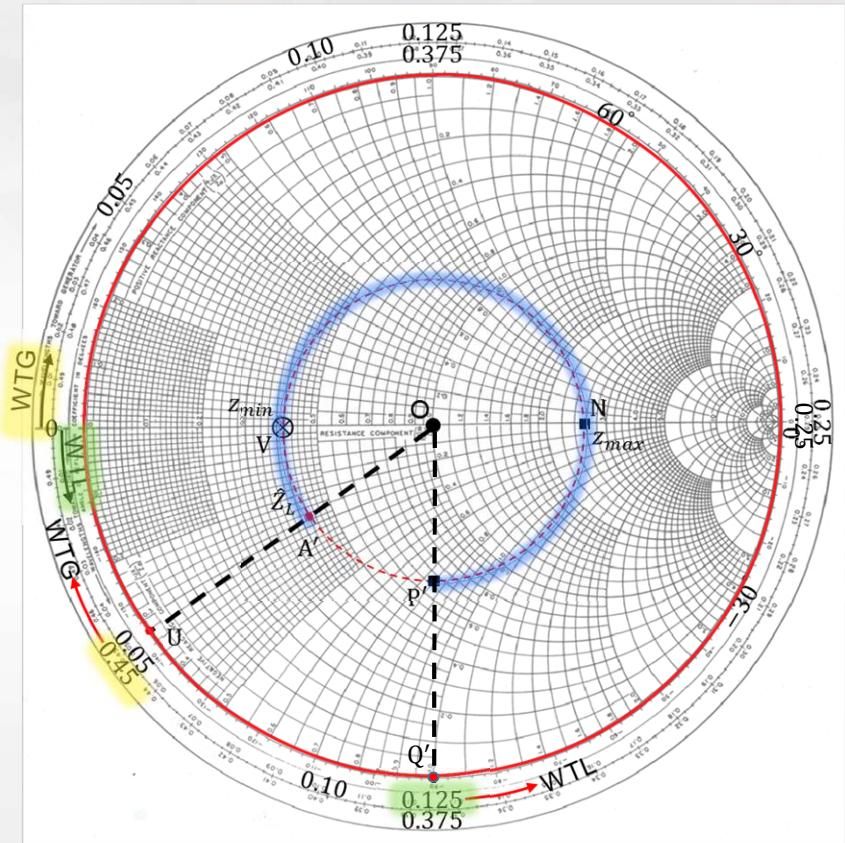
$$\begin{aligned} z &= -(0.425 - 0.375)\lambda \\ &= -0.05\lambda \end{aligned}$$



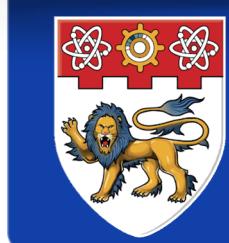

NANYANG
TECHNOLOGICAL
UNIVERSITY
SINGAPORE


EE3001 Engineering Electromagnetics

This session is about


35. Analysis and Design of Transmission Line (6)

Example 5

- Use of Smith Chart to determine ℓ/λ
- Given $\hat{Z}_{in} = 0.42 - j0.27$ and $\hat{Z}_L = 1 + j1$, determine the electrical length ℓ/λ of the transmission line.

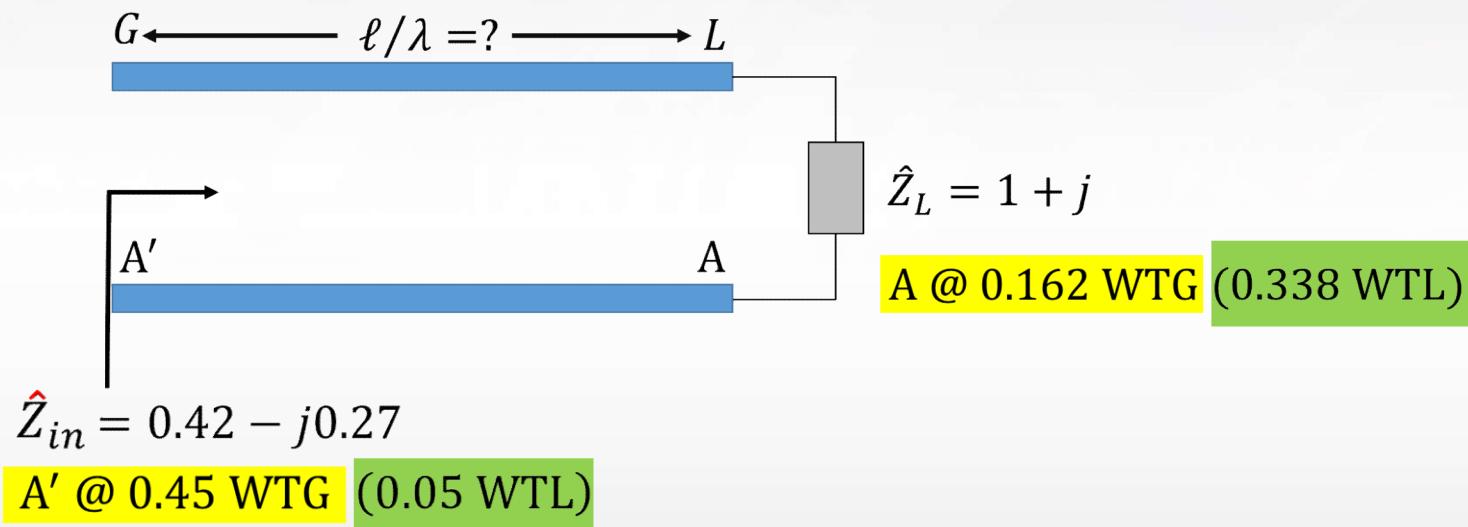

Example 5

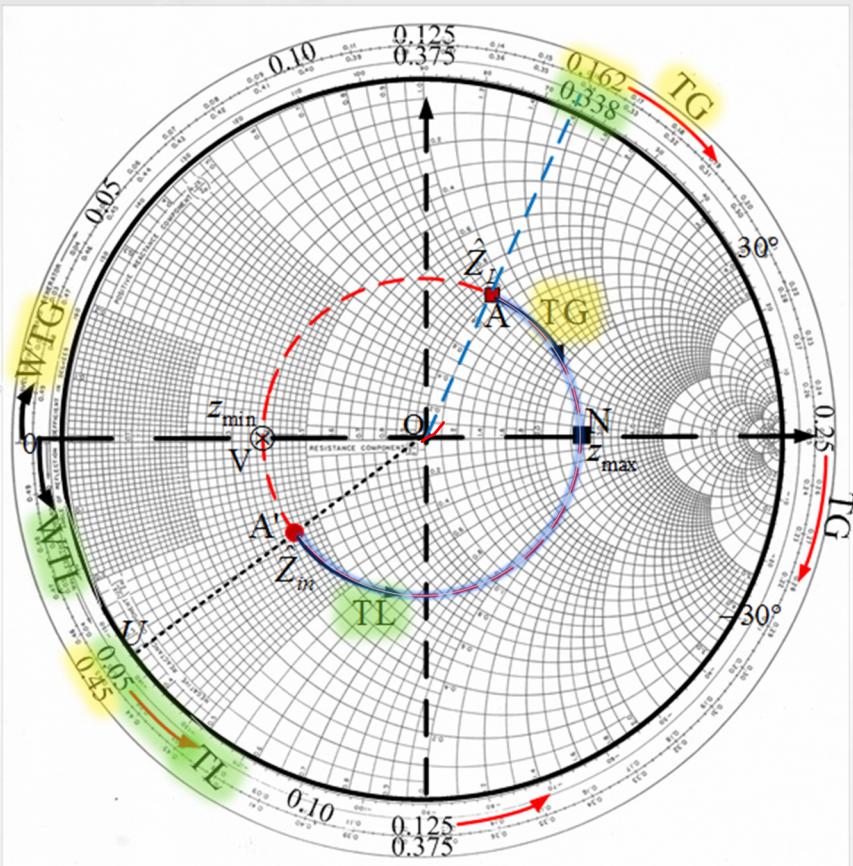

WTG: A ■ A'

0.162 WTG

$$\frac{\ell}{\lambda} = (0.45 - 0.162) \\ = 0.288$$

A'

0.45 WTG

WTL: A' ■ A

0.05 WTL

0.338 WTL

$$\frac{\ell}{\lambda} = (0.338 - 0.05) \\ = 0.288$$

Summary

□ Plot \hat{Z}_{in} - circle using

i. $\hat{Z}_{in}(z) = r + jx$ e.g. $\hat{Z}_{in}(0) = \hat{Z}_L = 1 + j1$ [P₁ ■]

P₁ @ 0.162 WTG

ii. $\Gamma(z) = |\Gamma| \angle \theta_\Gamma$ e.g. $\Gamma(-\ell) = 0.45 \angle -90^\circ$ [P₂ ●]

P₂ @ 0.125 WTL


iii. $\text{SWR} = \frac{|V|_{\max}}{|V|_{mi}} = 2.62 \rightarrow \hat{Z}_{in} = 2.62 @ \theta_\Gamma = 0$ [P₃ ■]

$$r = 2.62, x = 0$$

P₃ @ 0.25 WTL, 0.25 WTG

Summary

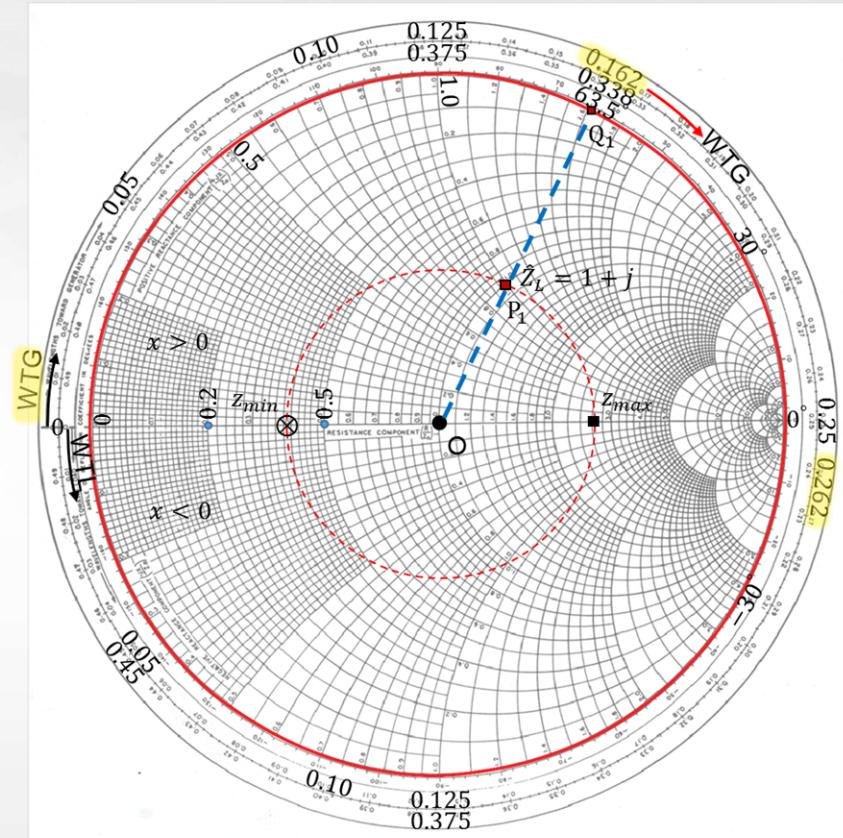- i. $\hat{Z}_{in}(z) = r + jx$ e.g. $\hat{Z}_{in}(0) = \hat{Z}_L = 1 + j1$ [P₁ ■]
- P₁ @ 0.162 WTG




Summary

ii. $\Gamma(z) = |\Gamma| \angle \theta_\Gamma$ e.g. $\Gamma(-\ell) = 0.45 \angle -90^\circ$

P_2 @ 0.125 WTL

[P_2 ●]

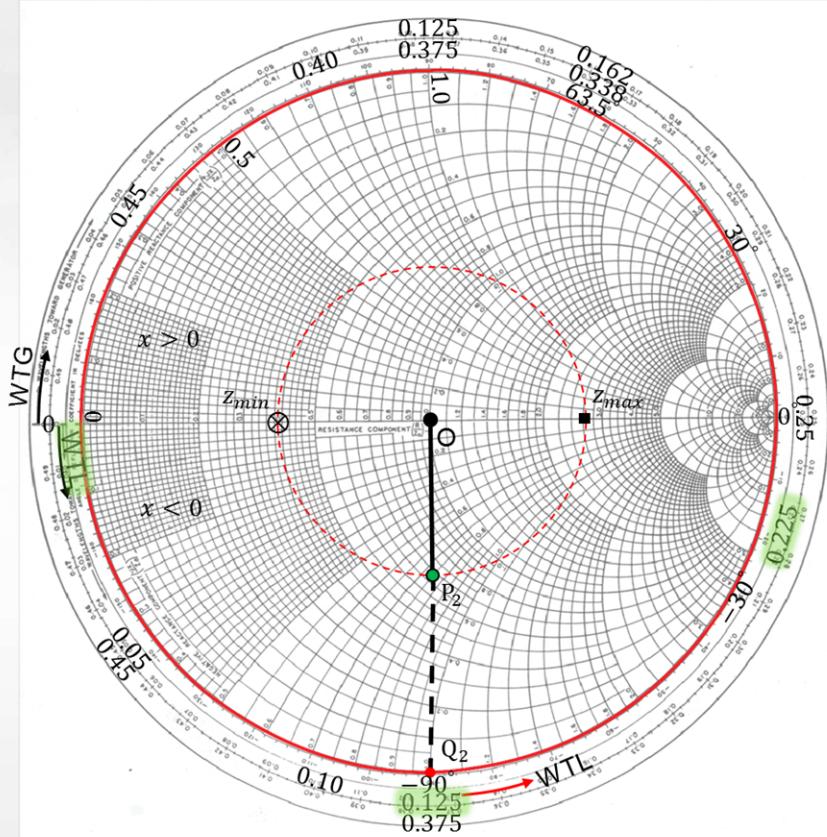


Summary

iii. $\text{SWR} = \frac{|V|_{\max}}{|V|_{\min}} = 2.62 \rightarrow \hat{Z}_{in} = 2.62 @ \theta_{\Gamma} = 0$ [P₃ ■]

$$r = 2.62, x = 0$$

P₃ @ 0.25 WTL, 0.25 WTG

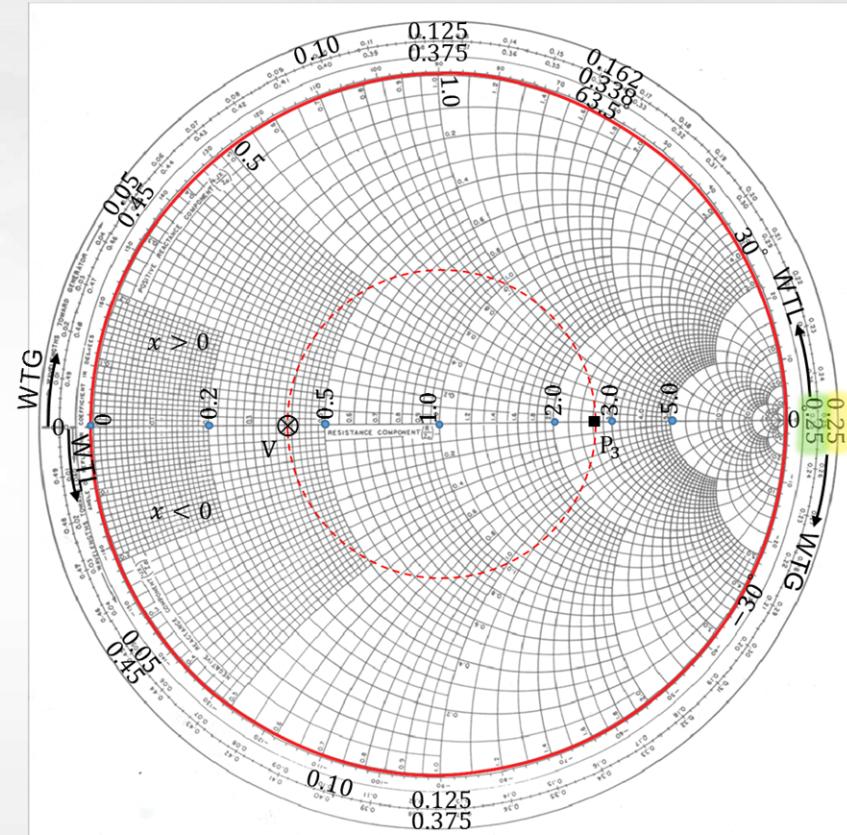


Summary

- Smith chart relates the following 3 variables: $\hat{Z}_{in}(z)$, \hat{Z}_L and ℓ/λ .

Given any two, the 3rd variable can be determined quickly.

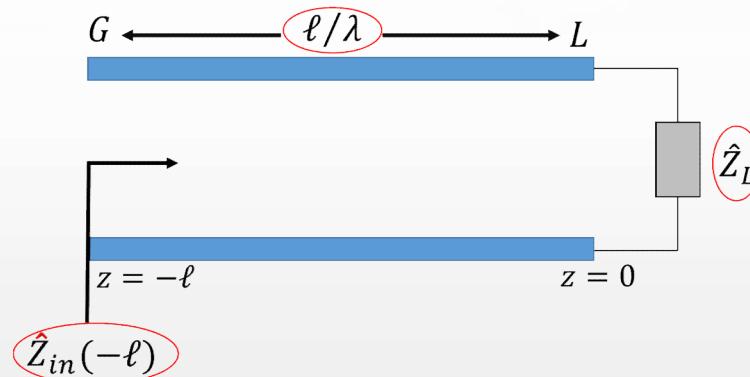1. Given \hat{Z}_L and ℓ/λ , determine $\hat{Z}_{in}(-\ell)$ at the source end.
2. Given $\hat{Z}_{in}(z)$ and ℓ/λ , determine \hat{Z}_L (unknown load impedance)
3. Given $\hat{Z}_{in}(-\ell)$ and \hat{Z}_L , determine ℓ/λ of a Transmission line.






NANYANG
TECHNOLOGICAL
UNIVERSITY
SINGAPORE

EE3001 Engineering Electromagnetics

This session is about

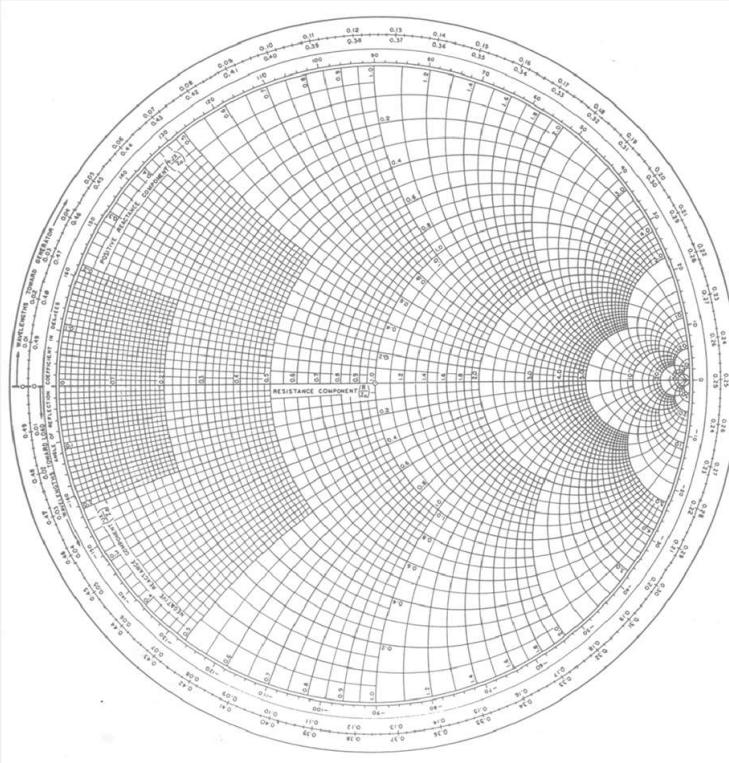36. Summary of Smith Chart


Smith Chart: Γ –Plane and $\hat{Z}_{in}(z)$ –Plane




Smith Chart: Γ –Plane and $\hat{Z}_{in}(z)$ –Plane

Γ –Plane

$$\Gamma(z) = |\Gamma| \angle \theta_\Gamma$$

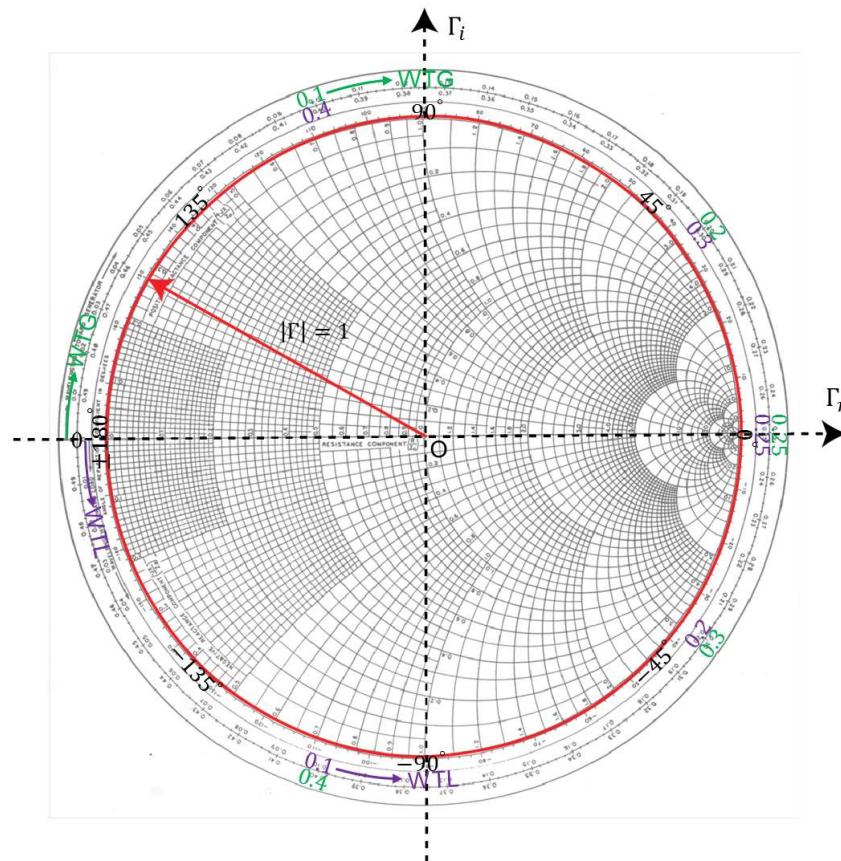


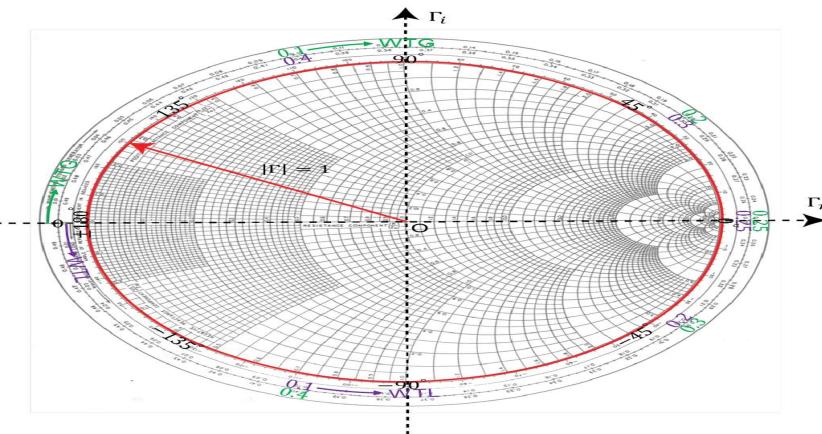Smith Chart: Γ –Plane and $\hat{Z}_{in}(z)$ –Plane





\hat{Z}_{in} –Plane

$$\hat{Z}_{in}(z) = r + jx$$

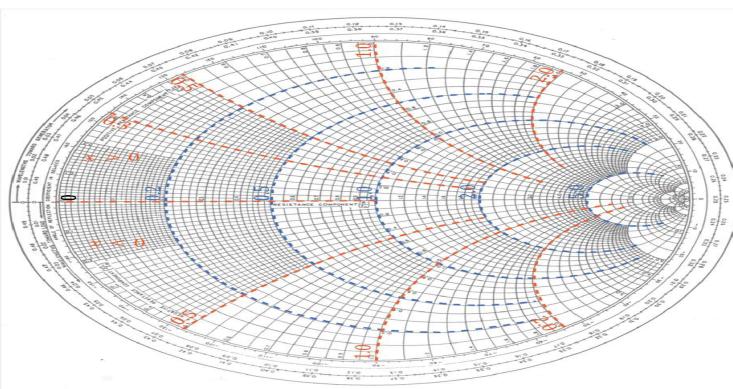


Smith Chart: Γ –Plane and $\hat{Z}_{in}(z)$ –Plane

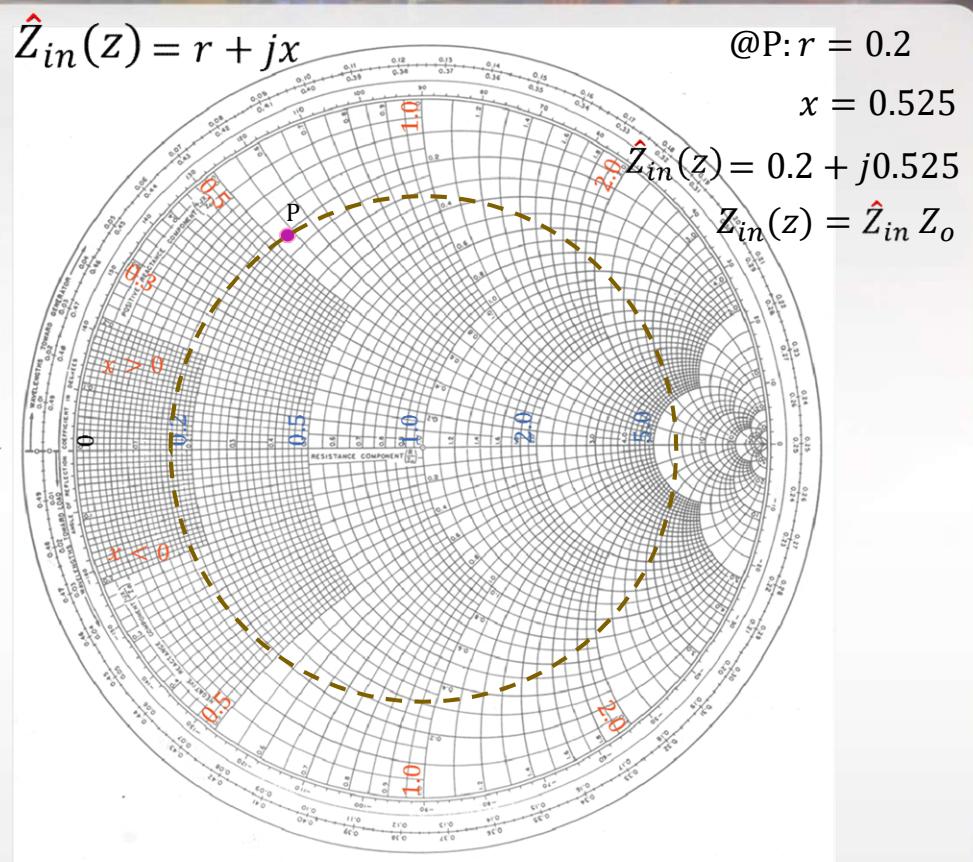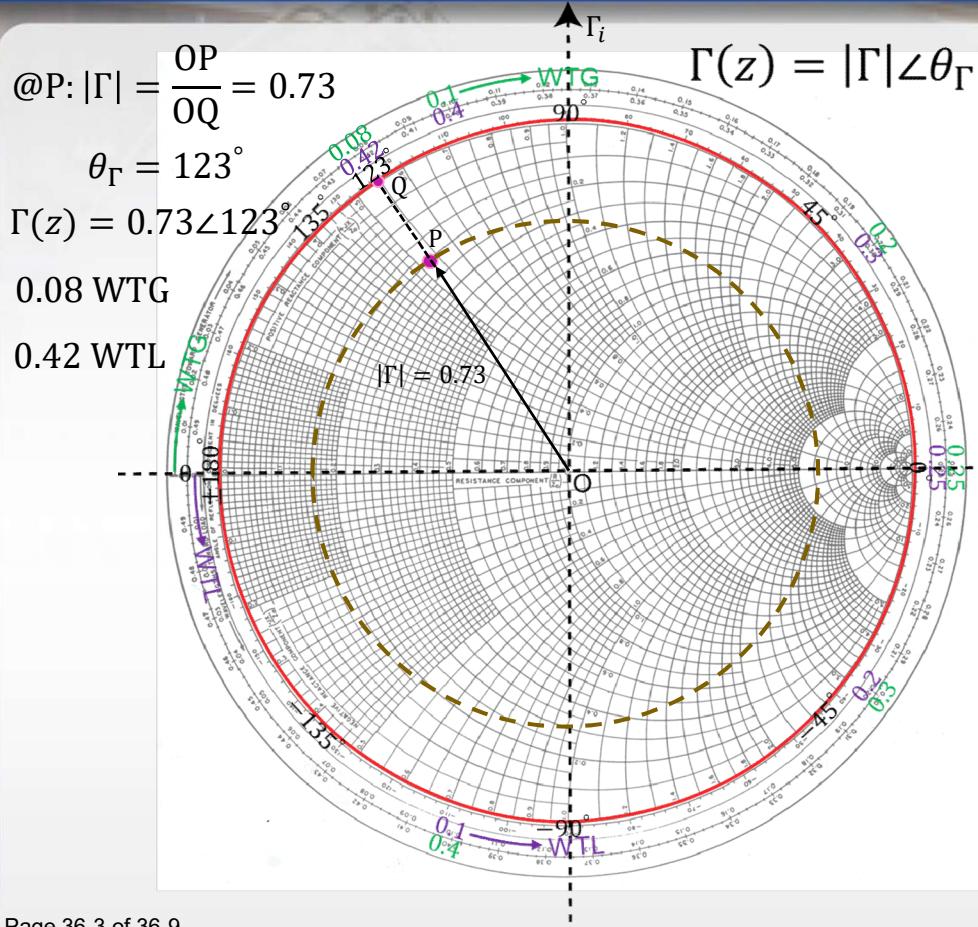


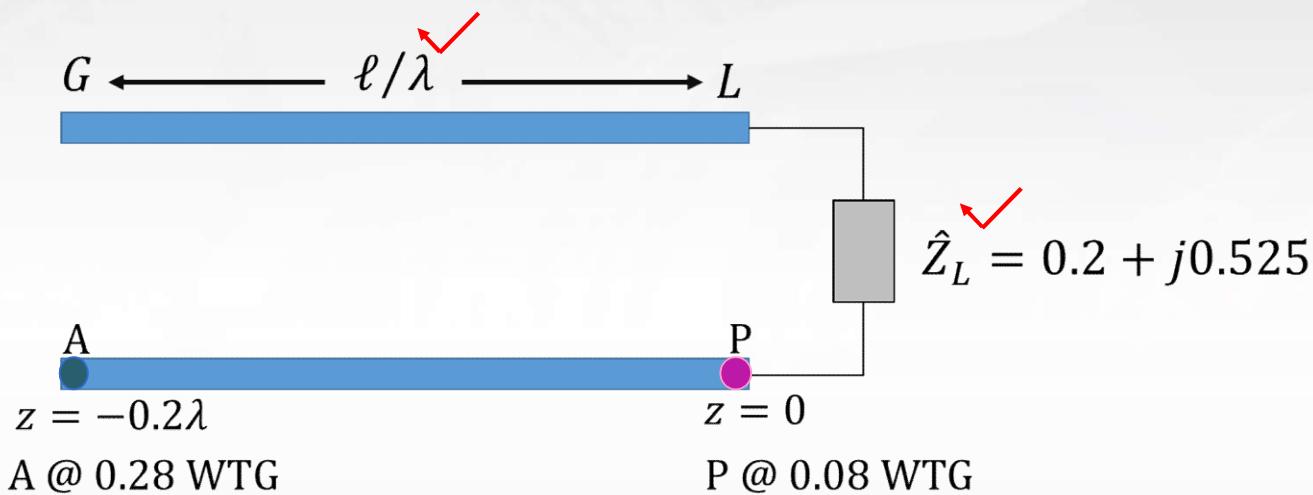
Example 1

- Given $Z_L = 20 + j52.5 \Omega$, $Z_o = 100 \Omega$, $\ell = 0.2\lambda$, find $\Gamma(-\ell)$ and $Z_{in}(-\ell)$.




- Ans: $\Gamma(-\ell) = 0.73 \angle -20.9^\circ$, $Z_{in}(-\ell) = 276 - j309 \Omega$

Example 1

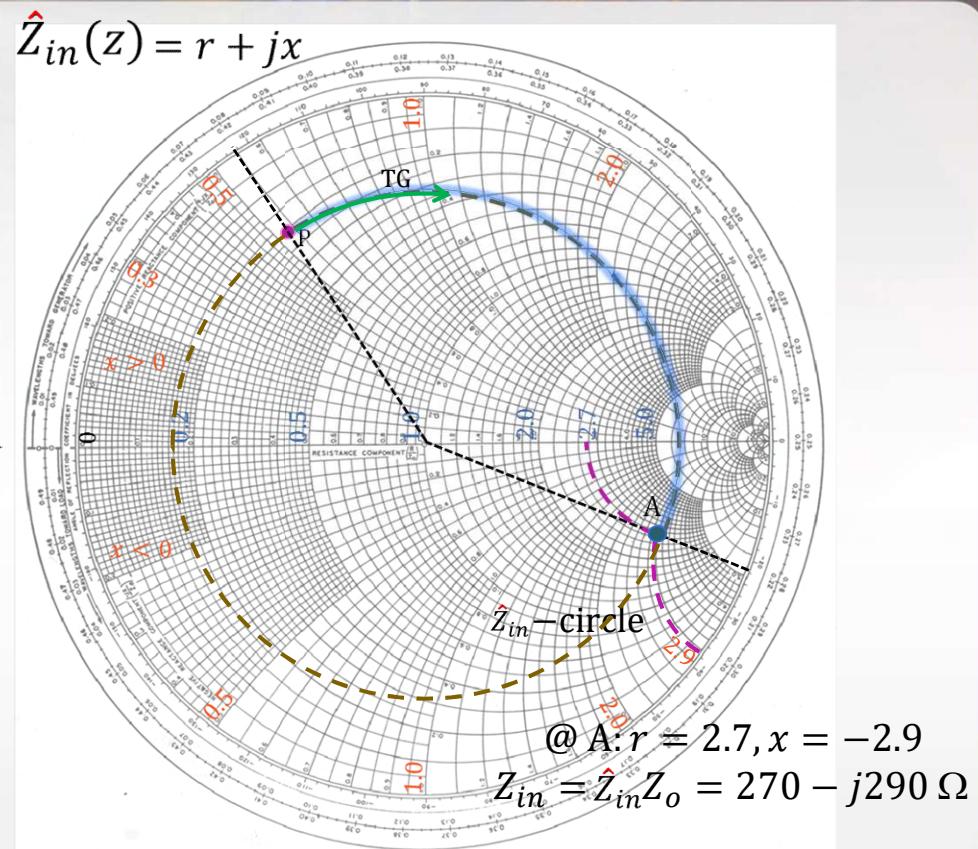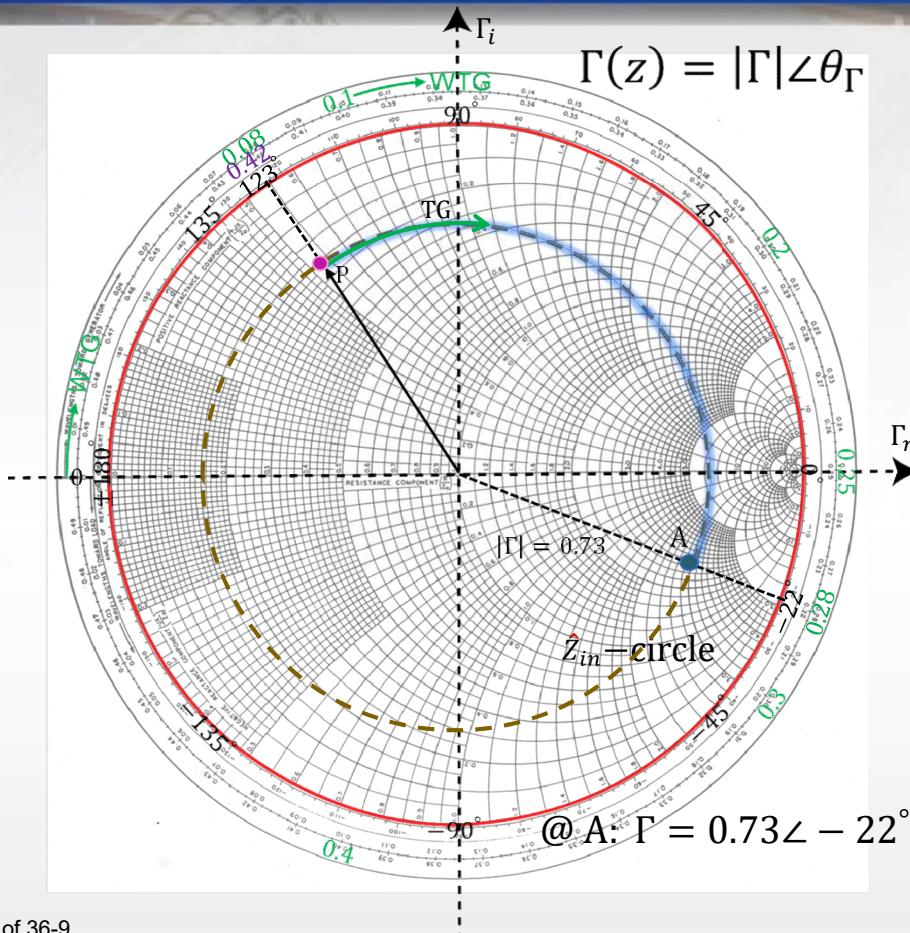


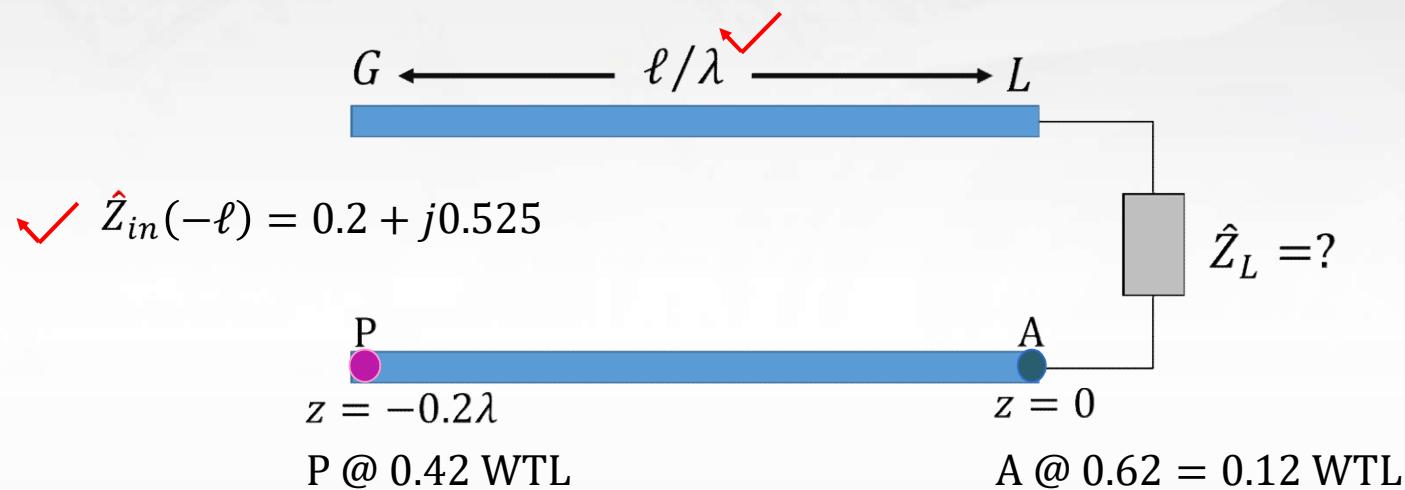
Example 2

- Given $Z_{in}(-\ell) = 20 + j52.5 \Omega$, $Z_o = 100 \Omega$, $\ell = 0.2\lambda$, find Γ_L and Z_L .




- Ans: $\Gamma_L = 0.73 \angle -93^\circ$, $Z_L = 29 - j90.6 \Omega$

Example 2

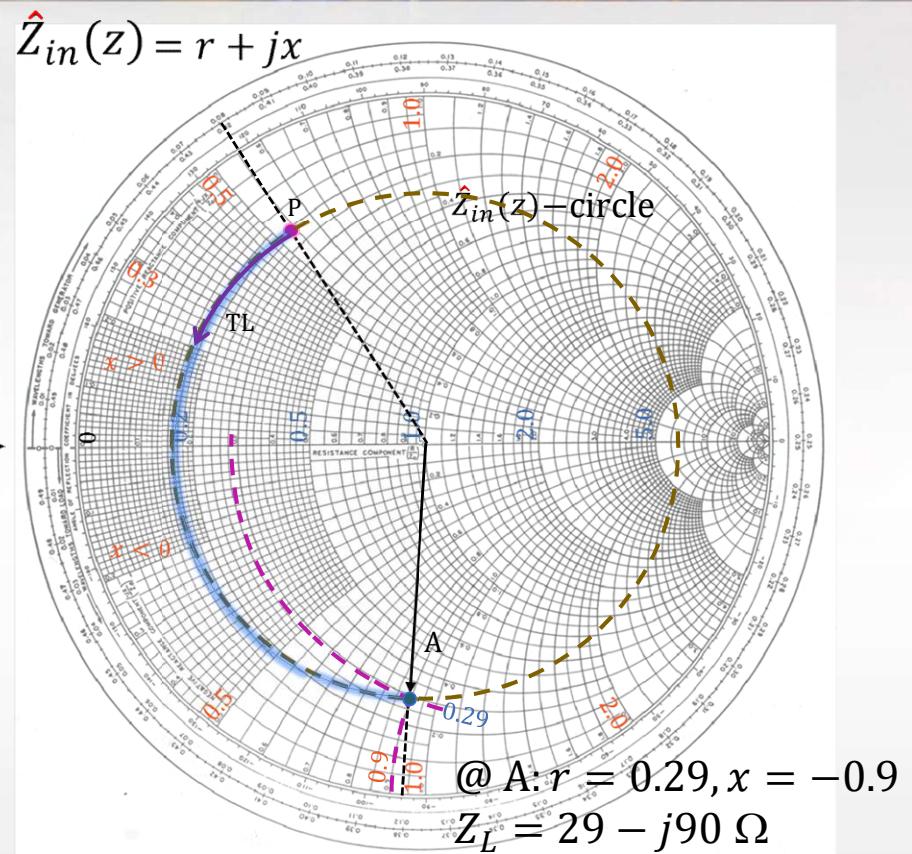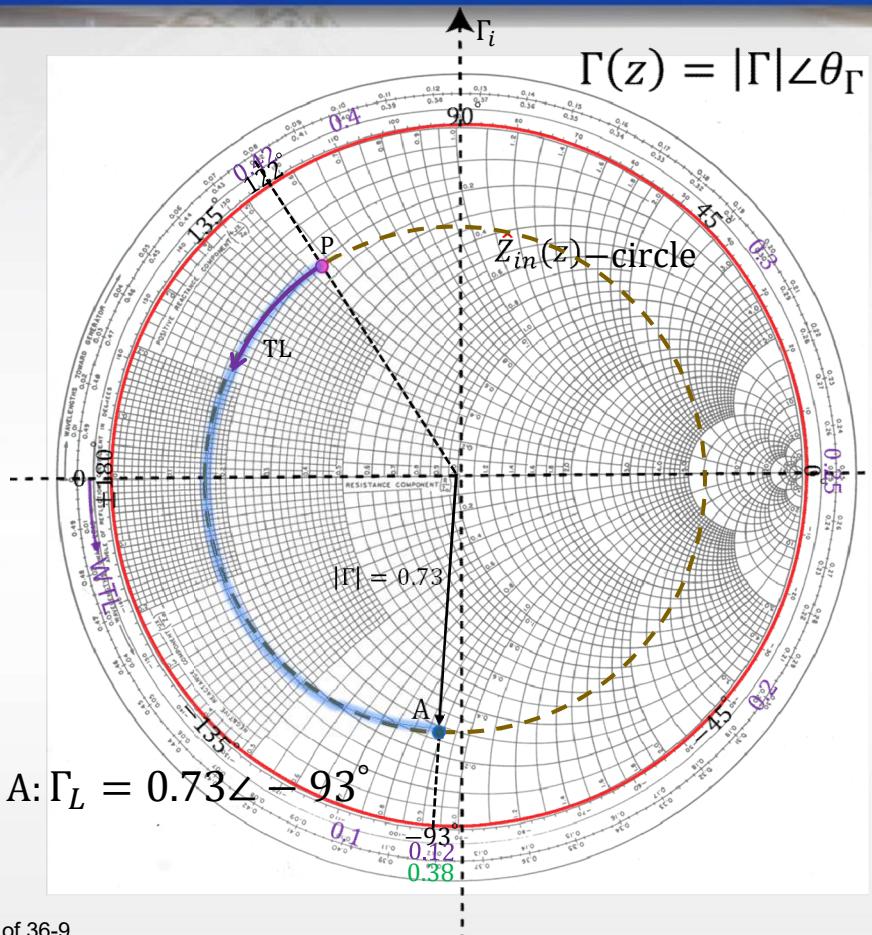


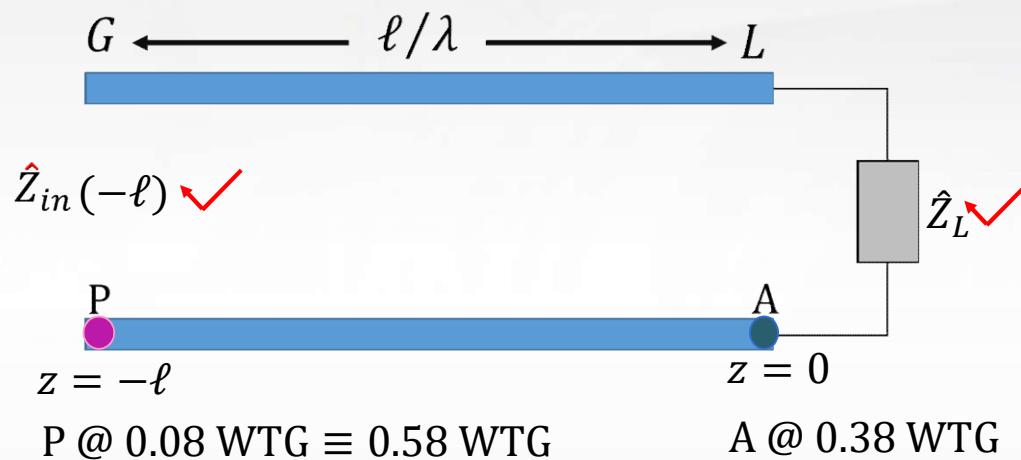
Example 3

- Given $\hat{Z}_{in}(-\ell) = 0.2 + j0.525$, $\hat{Z}_L = 0.29 - j0.91$, find ℓ/λ .



- Ans: $\ell/\lambda = 0.2$

Example 3

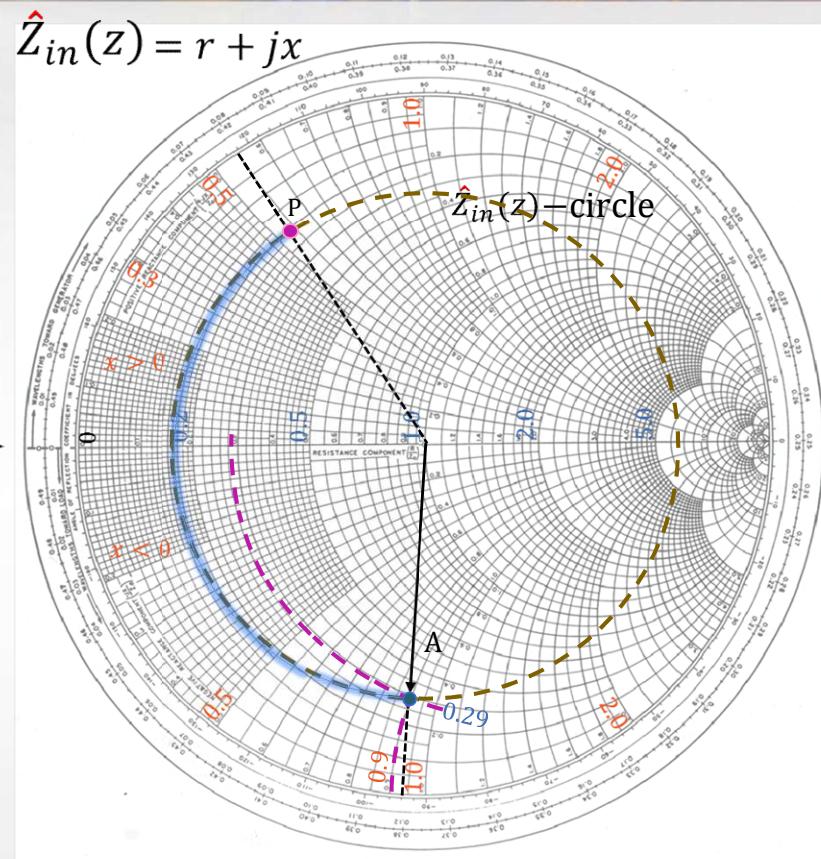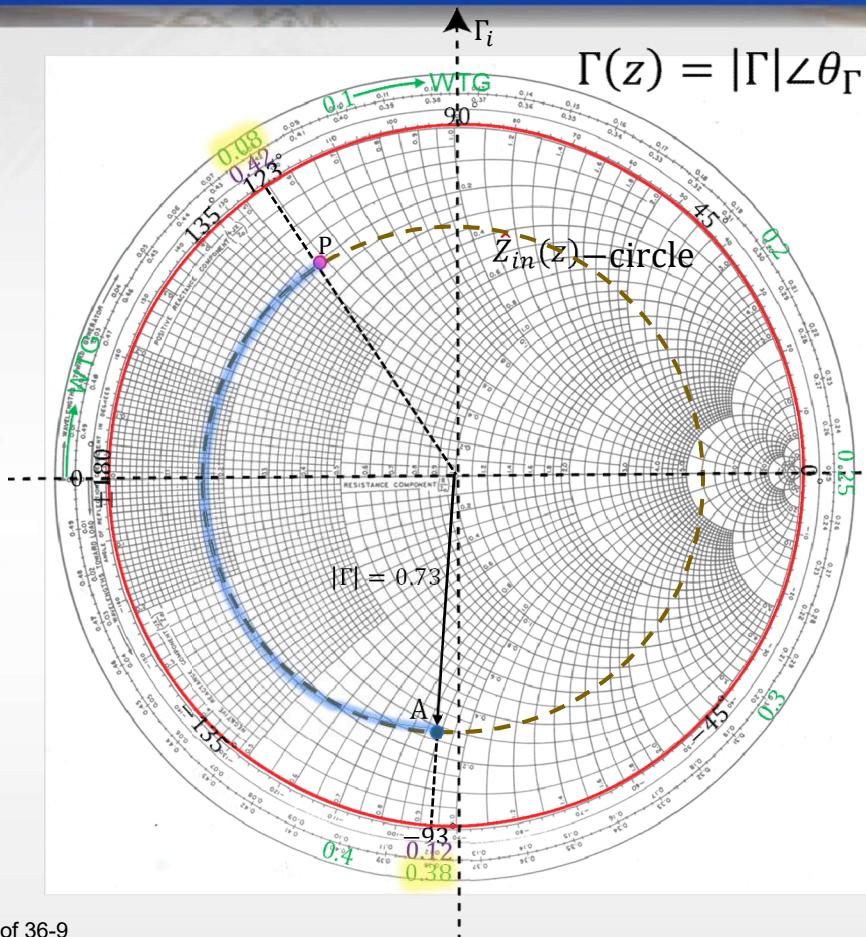



EE3001 Engineering Electromagnetics

This session is about

37. Appendix for Part II

Appendix for Part II

□ Reflection and Transmission of Electromagnetic Wave:

$$\Gamma_{\parallel} = \frac{\eta_2 \cos \theta_t - \eta_1 \cos \theta_i}{\eta_2 \cos \theta_t + \eta_1 \cos \theta_i};$$

$$\Gamma_{\perp} = \frac{\eta_2 \cos \theta_i - \eta_1 \cos \theta_t}{\eta_2 \cos \theta_i + \eta_1 \cos \theta_t};$$

$$\tau_{\parallel} = \frac{2\eta_2 \cos \theta_i}{\eta_2 \cos \theta_t + \eta_1 \cos \theta_i}$$

$$\tau_{\perp} = \frac{2\eta_2 \cos \theta_i}{\eta_2 \cos \theta_i + \eta_1 \cos \theta_t}$$

$$\frac{\sin \theta_t}{\sin \theta_i} = \sqrt{\frac{\mu_1 \varepsilon_1}{\mu_2 \varepsilon_2}}; \quad \tan \theta_{B\parallel} = \sqrt{\frac{\varepsilon_2}{\varepsilon_1}}; \quad \sin \theta_c = \sqrt{\frac{\varepsilon_2}{\varepsilon_1}}$$

Appendix for Part II

□ Transmission Line Equations:

$$V(z) = V_o^+ e^{-j\beta z} + V_o^- e^{+j\beta z}$$

$$I(z) = \frac{V_o^+}{Z_o} e^{-j\beta z} - \frac{V_o^-}{Z_o} e^{+j\beta z}$$

$$\Gamma_L = \frac{Z_L - Z_o}{Z_L + Z_o}$$

$$\Gamma(z) = \Gamma_L e^{+j2\beta z} \quad -\ell \leq z \leq 0$$

$$Z_{in}(-\ell) = \frac{Z_L + jZ_o \tan(\beta\ell)}{Z_o + jZ_L \tan(\beta\ell)} Z_o$$