

# EE3019 – Integrated Electronics


## Latches and Flip Flops

# Learning Objectives

---



By the end of this lesson, you should be able to:

 - Explain latches and flip-flops.
- Discuss Set Reset latch (SR) – circuit and parasitic.
- Explain clocked JK latch.


 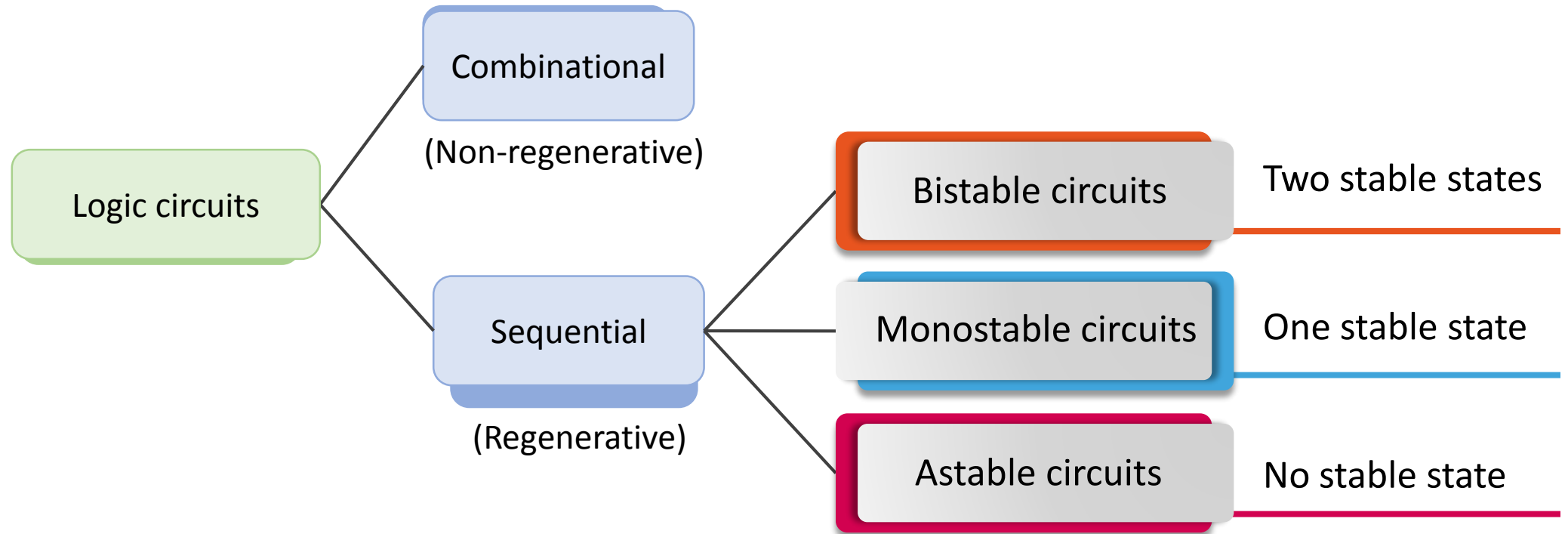
# Latches and Flip-Flops

There are three critical components in sequential circuits:




# Latches and Flip-Flops

There are three critical components in sequential circuits:

Bistable circuits

Monostable circuits

Astable circuits

 

# Latches and Flip-Flops

There are three critical components in sequential circuits:



Bistable circuits

Monostable circuits

Astable circuits

They have two stable states or operation modes, each of which can be obtained under certain current input and previous output conditions.

Flip flop

  

# Latches and Flip-Flops

There are three critical components in sequential circuits:



Bistable circuits

Monostable circuits

Astable circuits

They only have one stable operating point (state). The output eventually returns to the single stable state after a certain time duration.

555 Timer circuit  
(e.g. door bell)

  

# Latches and Flip-Flops

There are three critical components in sequential circuits:



Bistable circuits

Monostable circuits

Astable circuits

There is no stable operating point (state) which the circuit can preserve for a certain time period.


Ring oscillator

  




# Behaviour of Bistable Elements – Cross-coupled Inverters


a Gate-level schematic

 

b Transistor-level schematic

 

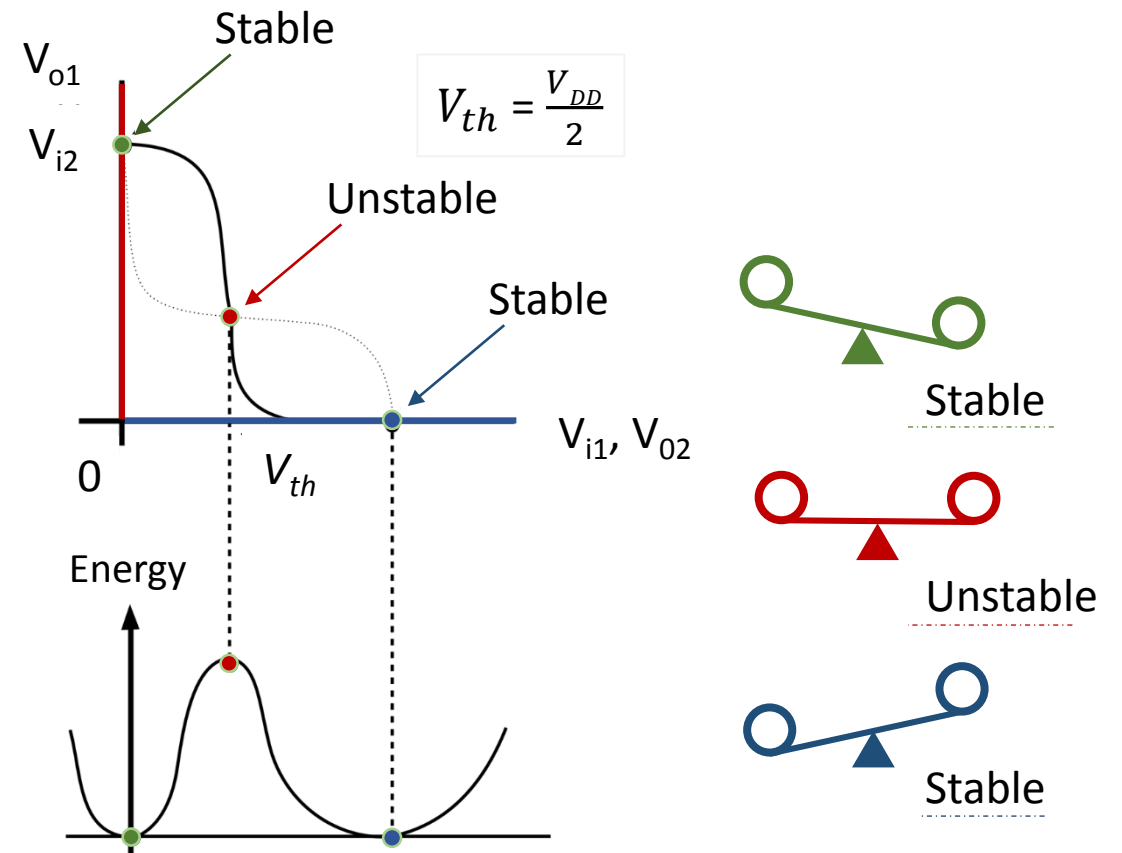c Intersecting voltage transfer curves of the two inverters






d Qualitative view of the potential energy levels corresponding to the three operating points




# CMOS SR Latch Based on NOR Gates

SR: Set - Reset

 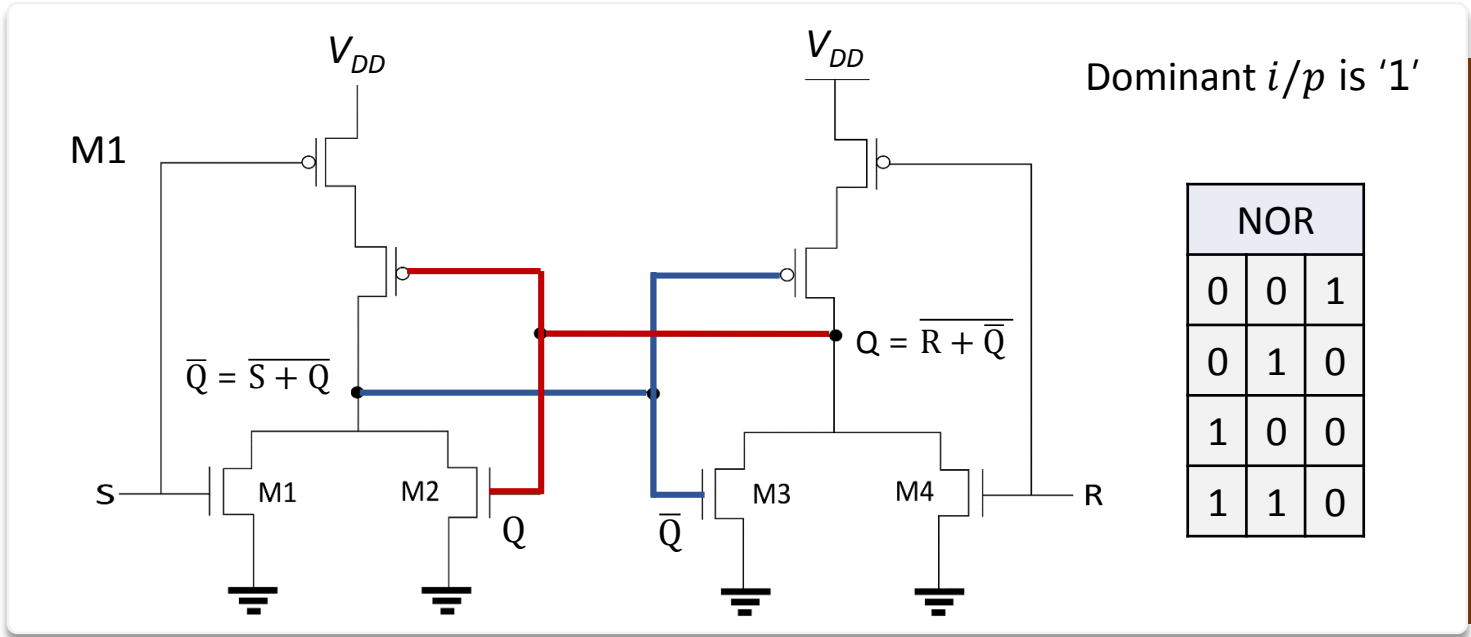 


Dominant *i/p* is '1'

SR Flip-flop			
Inputs		Next state ( $Q_{n+1}$ )	Action
S	R		
0	0	$Q_n$	Hold
0	1	0	Reset
1	0	1	Set
1	1	?	Not allowed

 


# SR Latch - Parasitic Capacitance

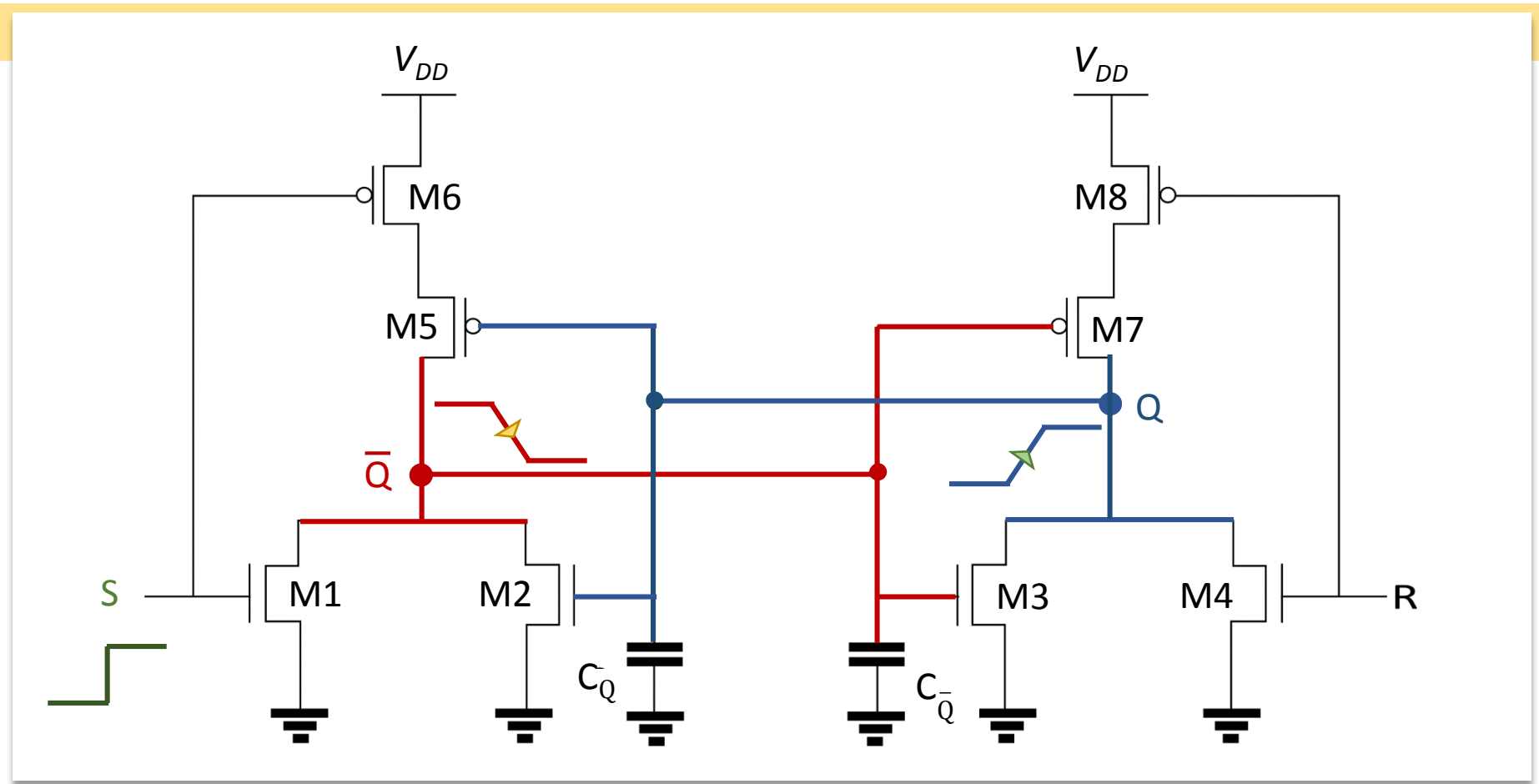


CMOS SR Latch with lumped load capacitance at both output nodes.

# SR Latch - Parasitic Capacitance (Contd.)

Assume RESET  $\rightarrow$  SET

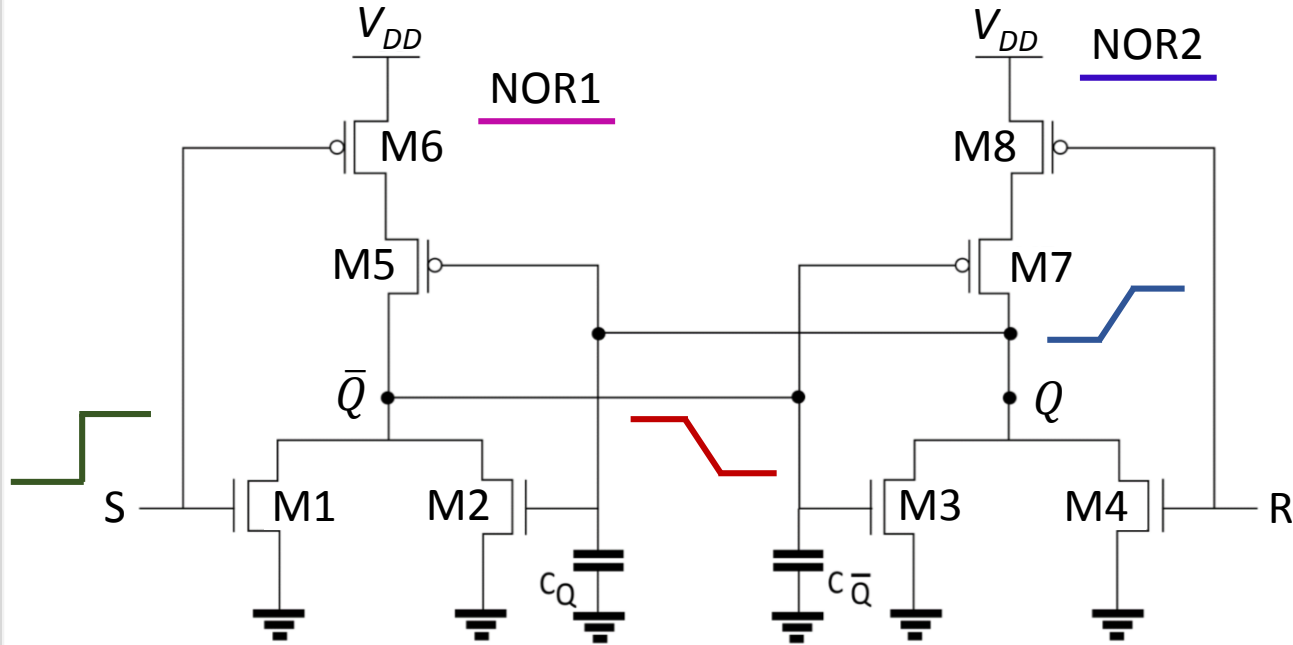
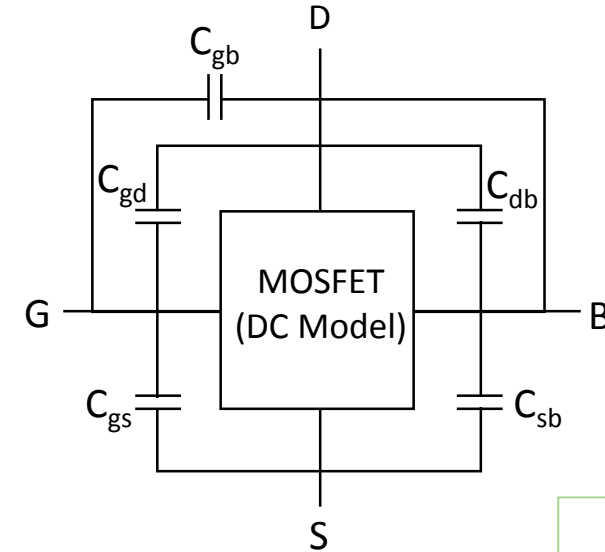
$$\tau_{\text{rise}Q(\text{Latch})} = \tau_{\text{fall } \bar{Q}(\text{NOR1})} + \tau_{\text{rise}Q(\text{NOR2})}$$




$$\tau = \frac{C\Delta V}{i}$$

Total parasitic capacitance at  $\bar{Q}$  and  $Q$ :


$$C_{\bar{Q}} = C_{gb3} + C_{gb7} + C_{db1} + C_{db2} + C_{db5} + C_{sb5} + C_{db6}$$
 
$$C_Q = C_{gb2} + C_{gb5} + C_{db3} + C_{db4} + C_{db7} + C_{sb7} + C_{db8}$$




# Clocked SR Latch based on NOR Gates


CLK: Enable signal

 



(a) Gate-level schematic

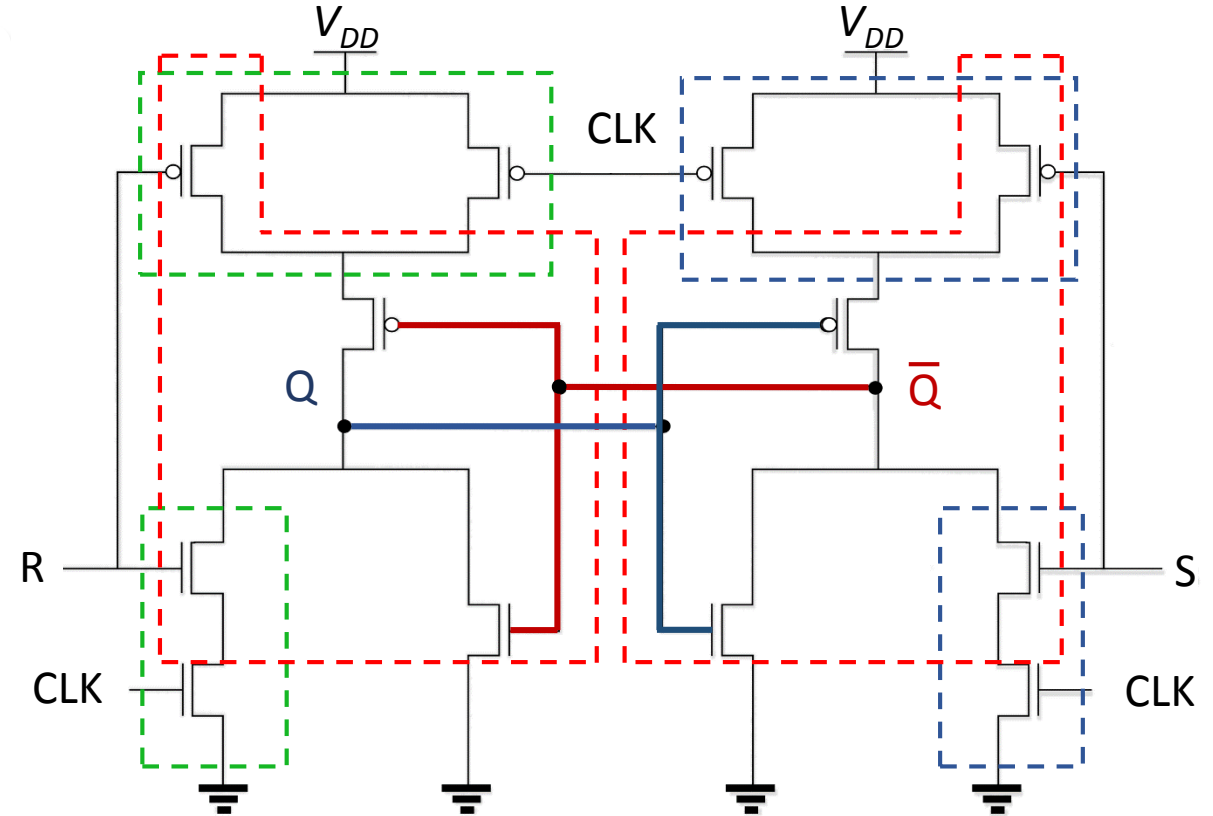



(b) Transistor-level schematic

 

## 8 - Transistor Clocked SR Latch

 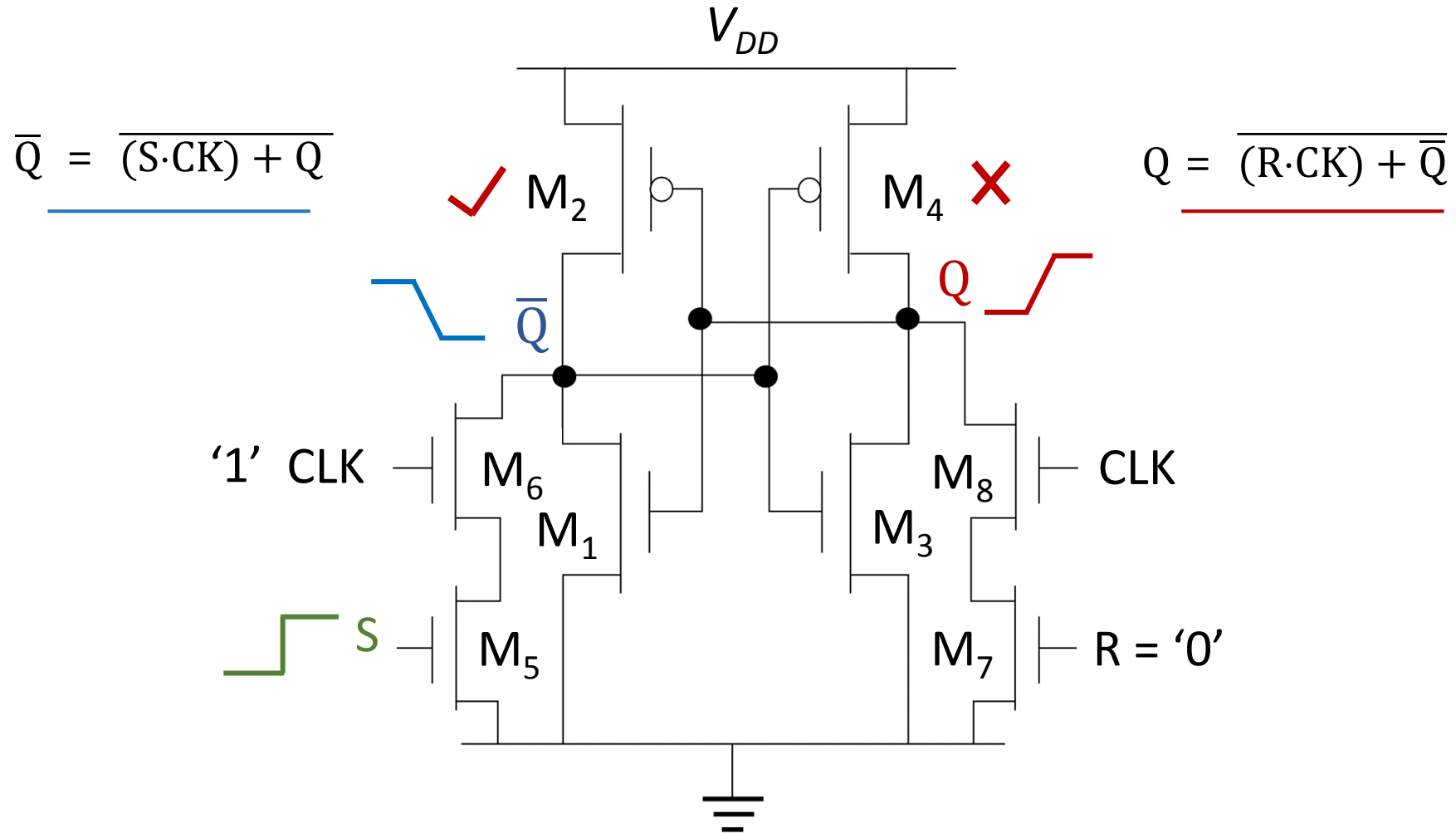

# 6 - Transistor Clocked SR Latch

  

# Transistor Sizing the SR Flip Flop

**Example:**  $\mu_n C_{ox} = 50 \mu A/V^2$ ;  $\mu_p C_{ox} = 20 \mu A/V^2$


$$V_{tn} = 0.6V; V_{tp} = -0.8V; V_{DD} = 5V$$

Assuming  $0.25 \mu m$  CMOS technology,  $Q=0$ :

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right)_3 = \left(\frac{0.5 \mu m}{0.25 \mu m}\right) \quad \left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right)_4 = \left(\frac{1.5 \mu m}{0.25 \mu m}\right)$$

Determine the minimum size of  $M_5$ ,  $M_6$ ,  $M_7$  and  $M_8$  to make the SR latch switchable.

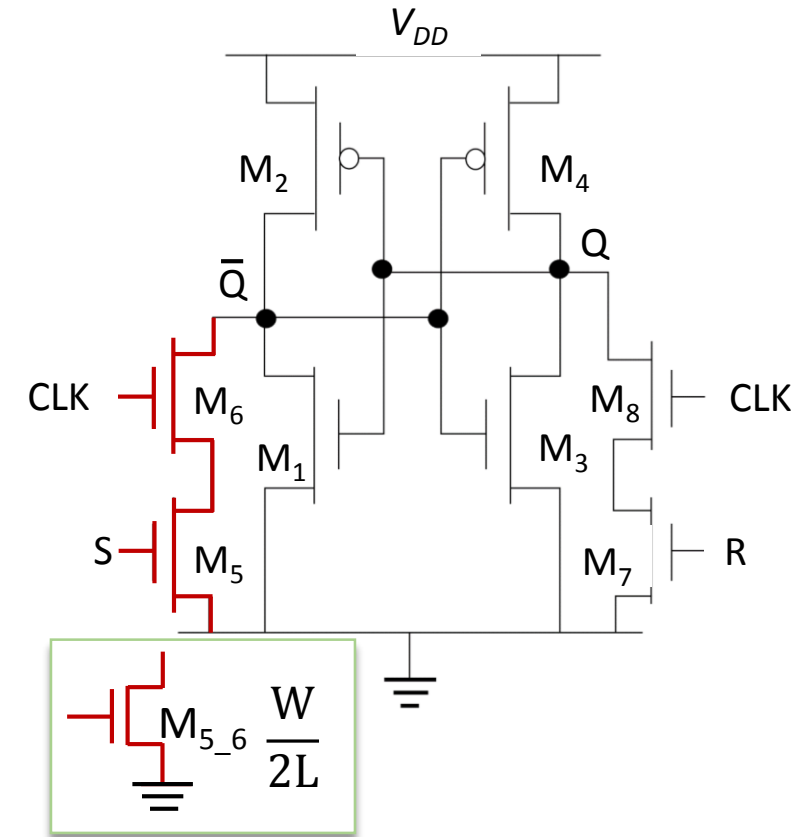Assume  $M_5$  is identical to  $M_6$ , i.e.  $M_5 = \frac{W}{L}$  and  $M_6 = \frac{W}{L}$ ;  $M_{5\_6} = \frac{W}{2L}$



Under this condition, the pull-down network can be modelled by a single transistor  $M_{5\_6}$ , whose width is half the width of the individual devices,  $M_5$  and  $M_6$ .

Contd.



# Transistor Sizing the SR Flip Flop (Contd.)

**Example:**  $\mu_n C_{ox} = 50 \mu A/V^2$ ;  $\mu_p C_{ox} = 20 \mu A/V^2$


$$V_{tn} = 0.6V; V_{tp} = -0.8V; V_{DD} = 5V$$

To switch latch from  $Q = 0$  to  $Q = 1$ ,  
we equate the current in the inverter  
for  $V_{\bar{Q}} = \frac{V_{DD}}{2}$  as given below:

$M_{5\_6}$  and  $M_2$  are in  
linear region.

$$|V_{DS}| < |V_{GS}| - |V_t|$$


$\frac{V_{DD}}{2}$        $V_{DD}$

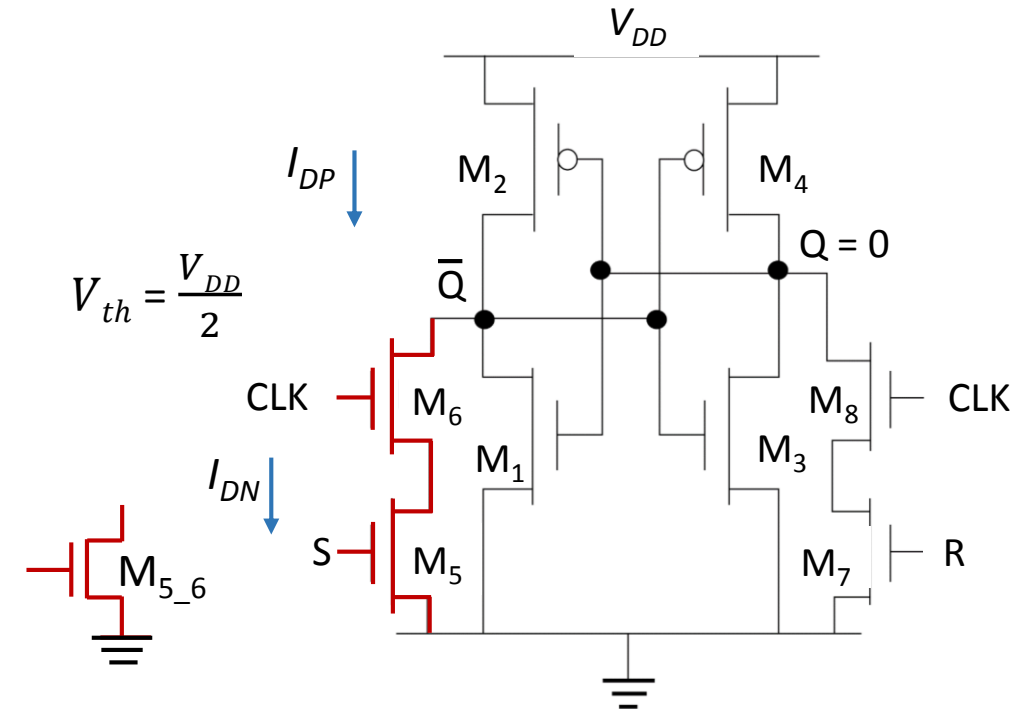

$$I_{DN} = I_{DP}$$

$$k'_n \left( \frac{W}{L} \right)_{5\_6} \left( (V_{DD} - V_{t_n}) V_{DSn} - \frac{V_{DSn}^2}{2} \right) = k'_p \left( \frac{W}{L} \right)_2 \left( (-V_{DD} - V_{t_p}) V_{DSp} - \frac{V_{DSp}^2}{2} \right)$$

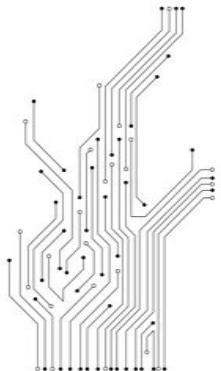
This implies that  $\left( \frac{W}{L} \right)_{5\_6} \geq 2.25$  and  $\left( \frac{W}{L} \right)_5$  and  $\left( \frac{W}{L} \right)_6 \geq 4.5$




# Clocked JK Latch based on NOR Gates

CLK: Enable


JK Latch  
↑↑  
SR

 

J	K	$Q_{n+1}$
0	0	$Q_n$
0	1	0
1	0	1
1	1	$\bar{Q}_n$

 

Gate-level schematic

 


Input output graph of JK latch
 
# Summary

Here are the key takeaways from this lesson.

- There are three critical components in sequential circuits, bistable circuits, monostable circuits and astable circuits.
- The behaviour of cross-coupled inverters is such that it switches the output from one stable state to another stable state through an unstable state.
- The CMOS SR Latch is based on NOR Gates where the delay of the latch is the total delay of NOR 1 and NOR 2 can be calculated based on the lump capacitance,  $C_{\bar{Q}}$  and  $C_Q$ .
- The lump capacitance of  $C_{\bar{Q}}$  and  $C_Q$  are the total parasitic capacitance of all the transistors connected to  $\bar{Q}$  and  $Q$ .
- The number of transistors are reduced from 20 to 12 to 8 and finally to 6 in clocked NOR based SR latch.
- The transistor sizing of the transistors can be calculated in the 6-transistor clocked SR latch.



# Thank You

Latches and Flip Flops

