

Nanyang Technological University
School of Electrical & Electronic Engineering
EE2002 Analog Electronics

Tutorial 10

1. In the AC model of the common-base circuit shown in Figure 1, the transistor Q_1 has $\beta = 100$, $V_A = \infty$, $C_\mu = 1\text{pF}$ and $C_\pi = 10\text{pF}$. AC coupling capacitors $C_{c1} = C_{c2} = 1\mu\text{F}$. Assume $V_T = 25\text{ mV}$ and DC collector current $I_C = 0.5\text{ mA}$. Using the OCTC and SCTC methods, determine the upper and lower 3-dB frequency of the amplifier, ω_H and ω_L respectively, and hence the amplifier bandwidth.

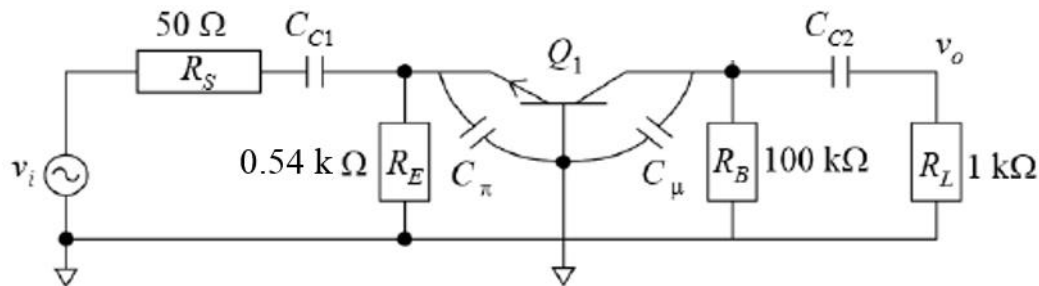


Figure 1

(Ans: $\omega_H = 813\text{ Mrad/s}$; $\omega_L = 10.5\text{ krad/s}$; $BW = \omega_H - \omega_L = 813\text{ Mrad/s}$)

2. Using the short-circuit time constant method, determine the lower -3dB frequency (ω_L) for the amplifier circuit shown in Figure 2. M2 is a PMOS while M1 is a NMOS. A signal source v_s with a series resistance $R_S = 1\text{ M}\Omega$ is connected to the input at G through a coupling capacitor $C_1 = 1\mu\text{F}$, while a load resistor $R_L = 10\text{ k}\Omega$ is connected to the output at D through a coupling capacitor $C_2 = 1\mu\text{F}$. The resistance $R_I = 5\text{ M}\Omega$. For the transistors M_1 and M_2 , $\mu_n C_{ox1}(W_1/L_1) = \mu_p C_{ox2}(W_2/L_2) = 50\text{ }\mu\text{A/V}^2$, $|V_{TP}| = V_{TN} = 2\text{V}$, and $\lambda = 0.005\text{ V}^{-1}$.

Ans: 34.9 rad/s

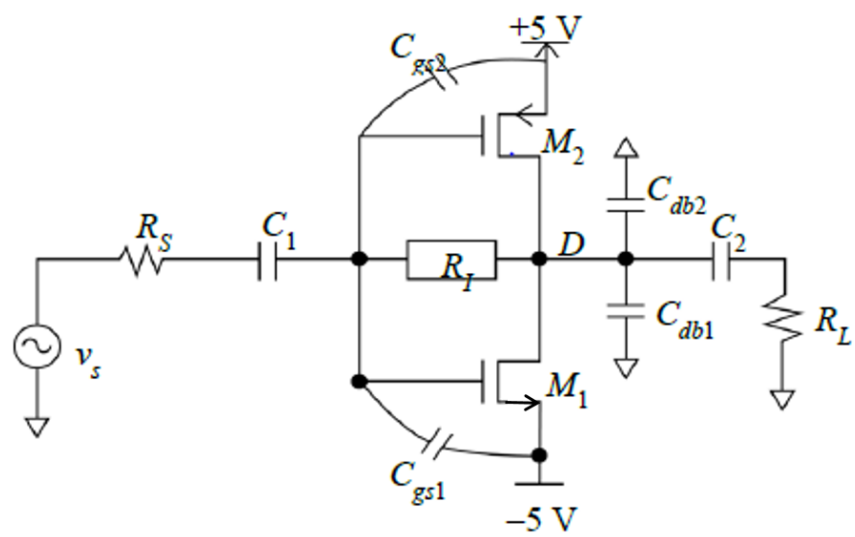


Figure 2