



AC Analysis of BJT and MOSFET Inverting Amplifiers

Assoc Prof Chang Chip Hong

email: echchang@ntu.edu.sg

EE2002 Analog Electronics




Lesson Objectives

At the end of this lesson, you should be able to:

- Draw small signal model for BJT and MOSFET
- Calculate the small signal parameters of BJT and MOSFET
- Construct AC equivalent circuit of BJT and MOSFET inverting amplifiers
- Calculate the following performance characteristics of C-E and C-S amplifiers
 - Voltage gain
 - Input resistance
 - Output resistance

Hybrid-Pi Model of BJT

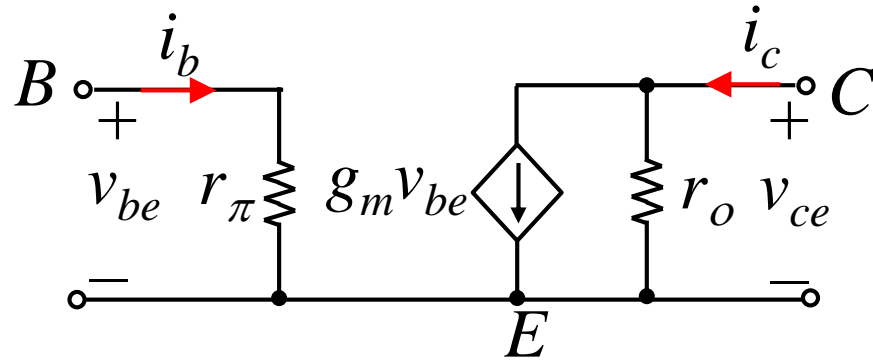

- This hybrid-pi small-signal model is the intrinsic low-frequency representation of the BJT.
- Small-signal parameters are controlled by the Q-point and are independent of geometry of BJT.

Transconductance:

$$g_m = \frac{I_C}{V_T} \approx 40 I_C$$

where $V_T = \frac{kT}{q} \approx 25 \text{ mV} @ 25^\circ\text{C}$

Input resistance:


$$r_\pi = \frac{\beta}{g_m}$$

Output resistance:

$$r_o = \frac{V_A + V_{CE}}{I_C} \approx \frac{V_A}{I_C} \text{ if } V_A \gg V_{CE}$$

Equivalent Forms of Small-Signal Model for BJT

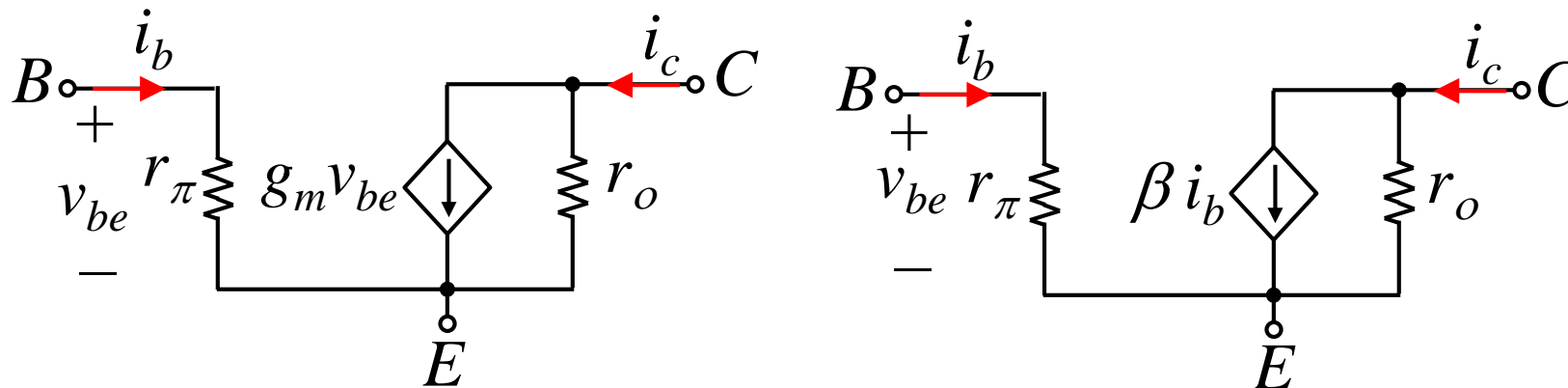Voltage-controlled current source $g_m v_{be}$ can be transformed into current-controlled current source.





$$v_{be} = i_b r_\pi$$

$$g_m v_{be} = g_m i_b r_\pi = \beta i_b$$

$$i_c = \beta i_b + \frac{v_{ce}}{r_o} \approx \beta i_b$$


Basic relationship $i_c = \beta i_b$ is useful for both dc and ac analysis when BJT is in forward-active region.

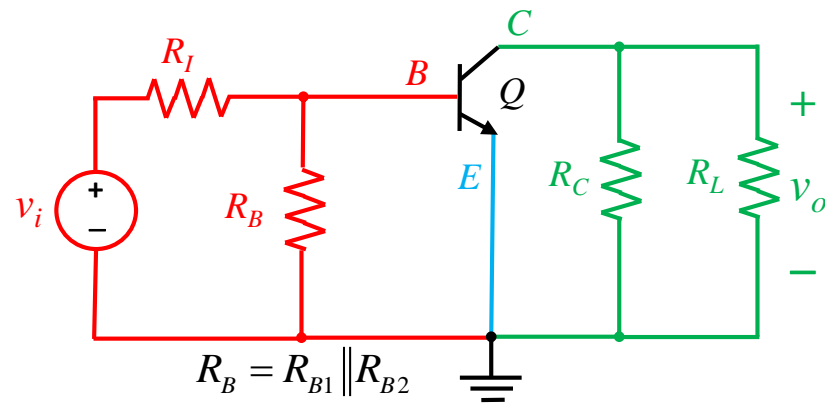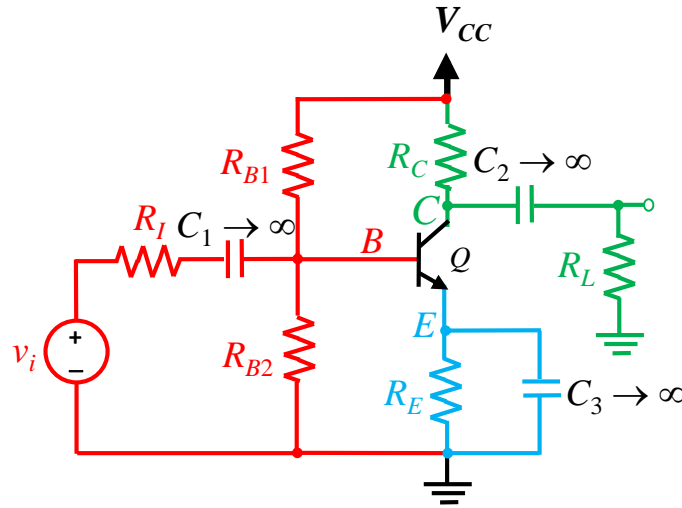Small Signal Analysis of C-E Amplifier with Fully Bypass R_E



- The ac equivalent circuit is constructed by assuming that all capacitances have zero impedance at signal frequency and dc voltage source is ac ground.
- Assume that Q-point has already been calculated from DC analysis. Hence, g_m , r_π , and r_o of BJT can be calculated.

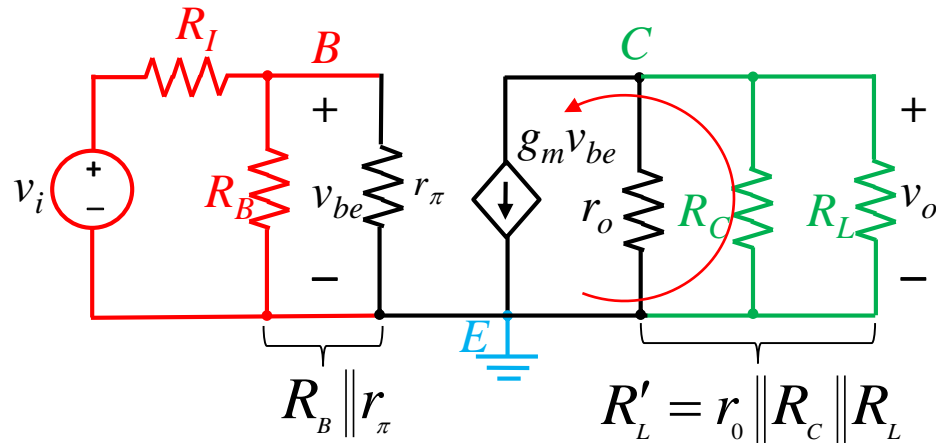C-E Amplifier with Fully Bypass R_E : Voltage Gain



Overall voltage gain from source v_i to output voltage v_o across R_L is:


$$A_v = \frac{v_o}{v_i} = \frac{v_c}{v_b} \times \frac{v_b}{v_i} = A_{vt} \times \frac{v_b}{v_i}$$

Terminal voltage gain between base and collector is:

$$A_{vt} = \frac{v_c}{v_b} = \frac{v_o}{v_{be}} = \frac{-g_m v_{be} R'_L}{v_{be}} = -g_m R'_L$$

$$\therefore A_v = -g_m R'_L \left(\frac{R_B \parallel r_\pi}{R_I + R_B \parallel r_\pi} \right)$$

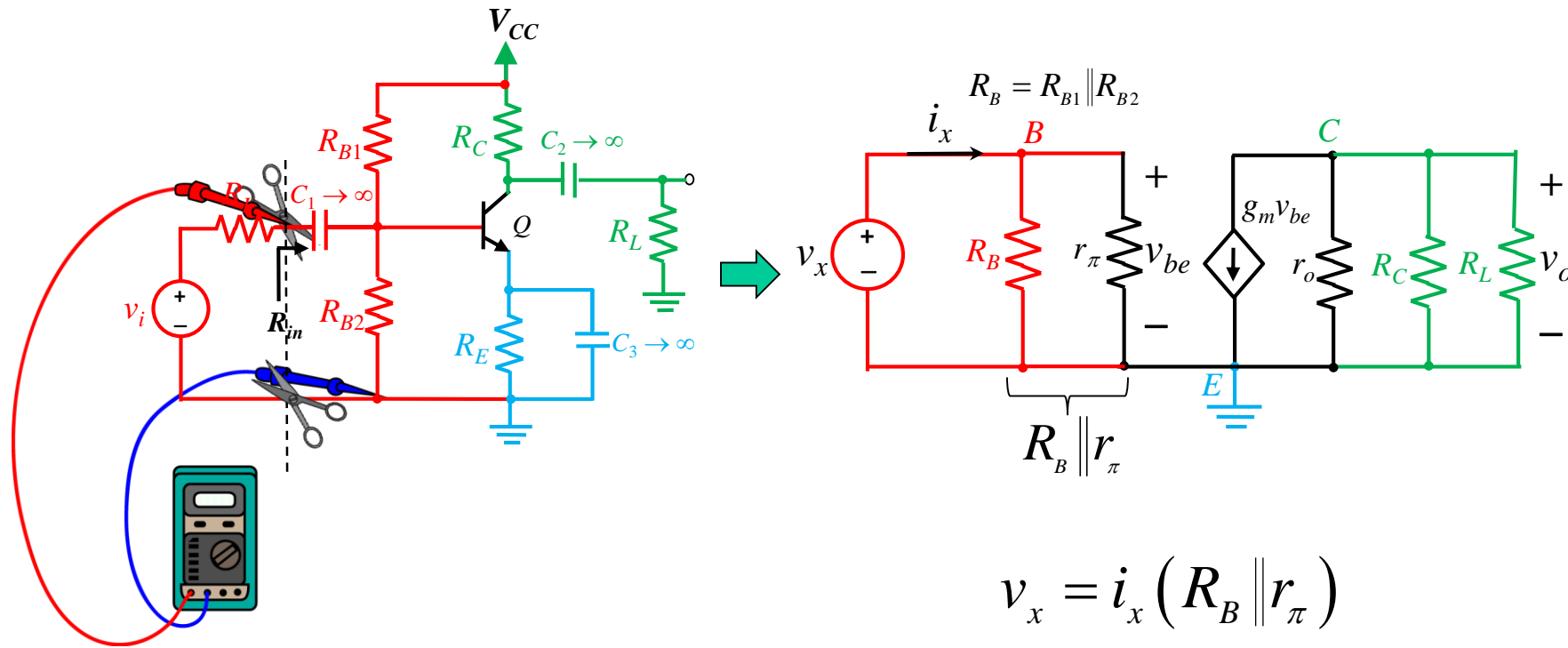C-E Amplifier with Fully Bypass R_E : Input Resistance




$$v_x = i_x (R_B \parallel r_\pi)$$

$$R_{in} = \frac{v_x}{i_x}$$

$$= R_B \parallel r_\pi$$

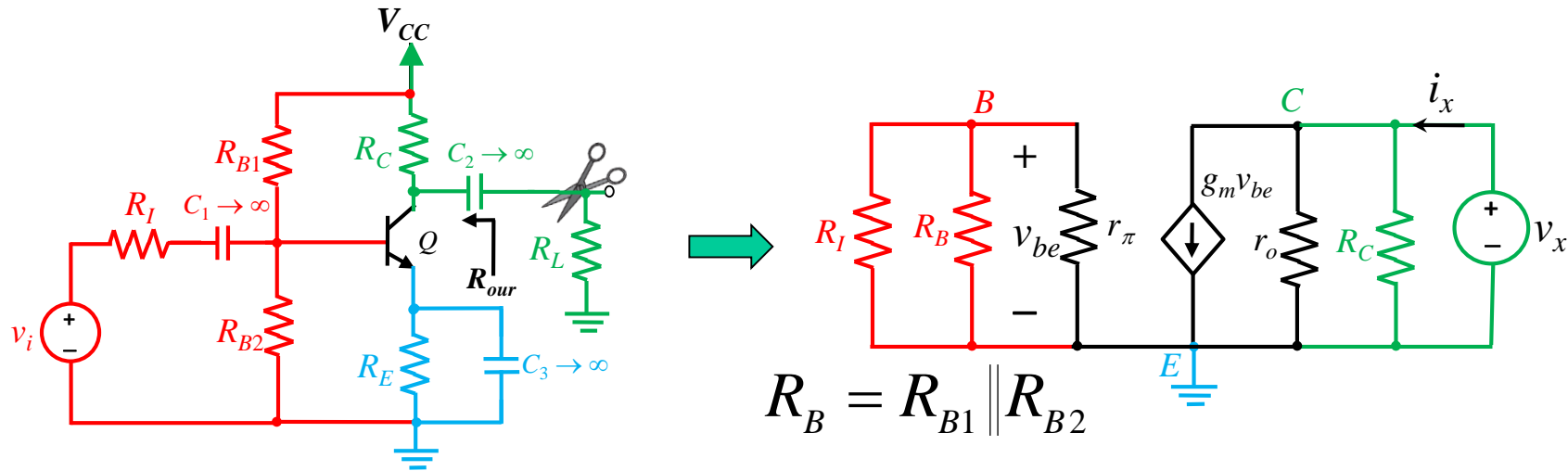C-E Amplifier with Fully Bypass R_E : Output Resistance



$$i_x = \frac{v_x}{R_C} + \frac{v_x}{r_o} + g_m v_{be}$$

$$v_{be} = 0 \Rightarrow i_x = \frac{v_x}{R_C} + \frac{v_x}{r_o}$$


$$R_{out} = \frac{v_x}{i_x} = \left(\frac{1}{R_C} + \frac{1}{r_o} \right)^{-1} = R_C \parallel r_o$$

$$R_{out} \approx R_C \text{ if } r_o \gg R_C$$

C-E Amplifier with Fully Bypass R_E : Example


Problem: Find voltage gain, input and output resistances.

Given: $\beta = 65$, $V_A = 50$ V

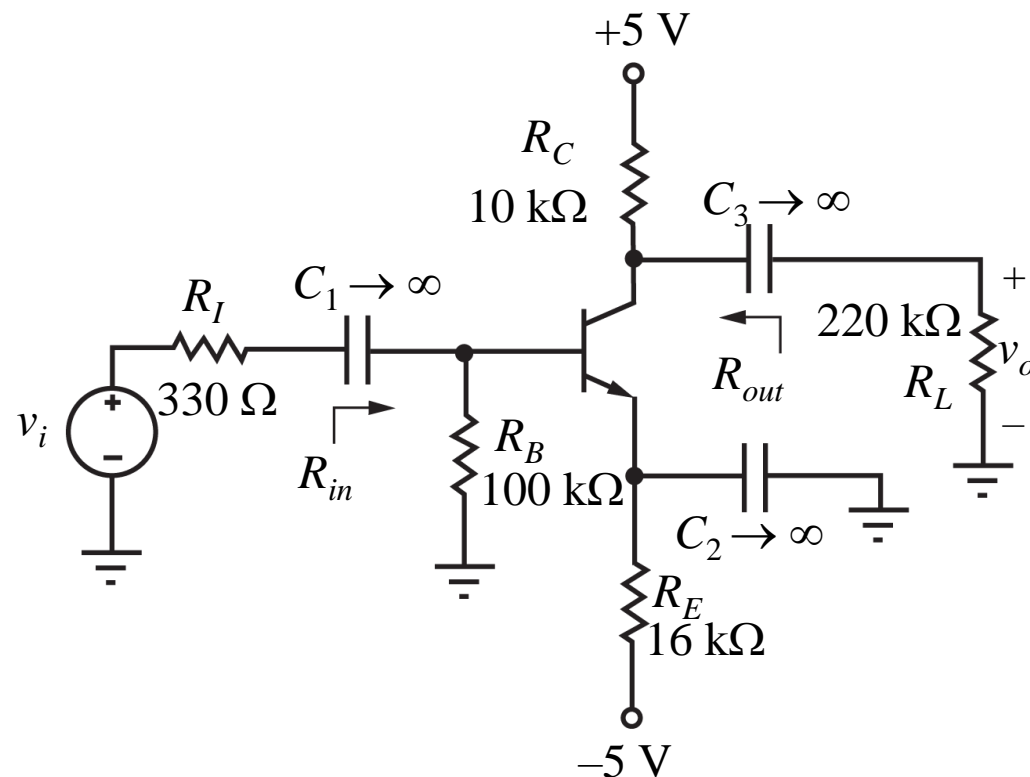

Find the Q-point from dc equivalent circuit:
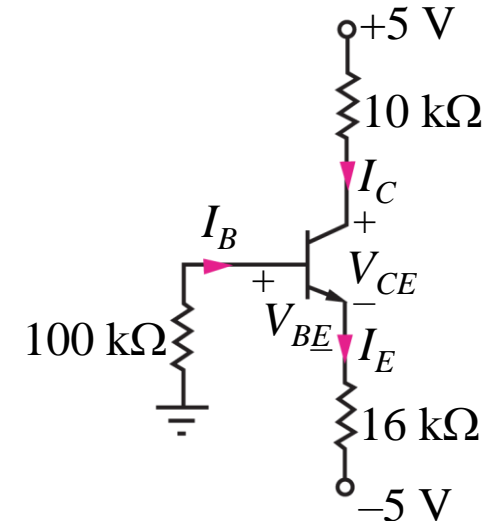
$$100 \times 10^3 I_B + 0.7 + 66 I_B (16 \times 10^3) + (-5) = 0$$



$$I_B = 3.71 \mu\text{A}$$

$$I_C = 65 I_B = 241 \mu\text{A}$$



$$I_E = 66 I_B = 245 \mu\text{A}$$

$$5 - 10 \text{ k} \times 241 \mu - V_{CE} - 16 \text{ k} \times 245 \mu - (-5) = 0$$

$$V_{CE} = 3.67 \text{ V}$$

AC Analysis of C-E Amplifier with Fully Bypass R_E

Small signal equivalent

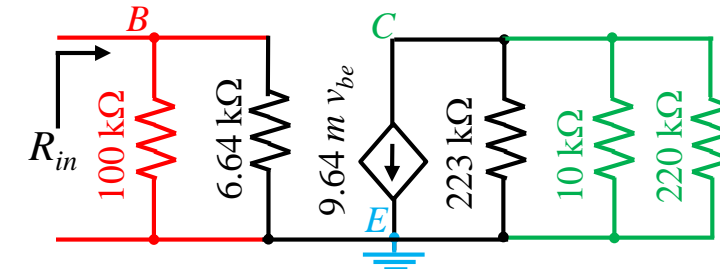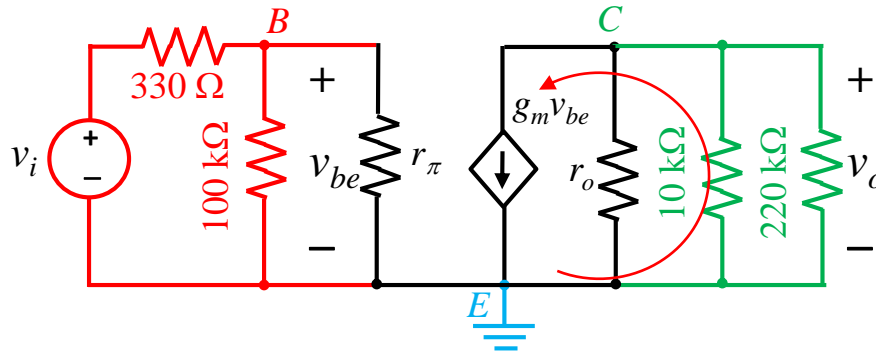


$$R_{in} = 100 \text{ k} \parallel 6.64 \text{ k} = 6.23 \text{ k}\Omega$$

$$g_m \approx 40 \times 241 \mu = 9.64 \text{ mS}$$

$$r_\pi = \frac{65}{9.64 \text{ m}} = 6.64 \text{ k}\Omega$$

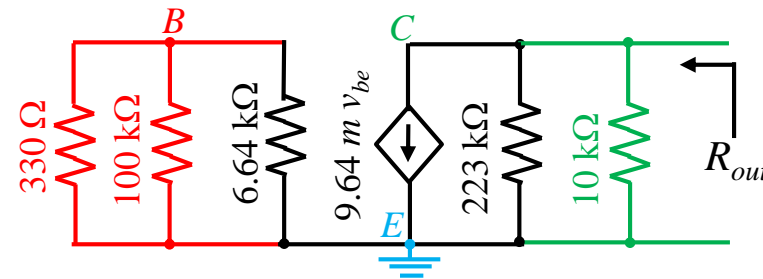
$$r_o = \frac{50 + 3.67}{241 \mu} = 223 \text{ k}\Omega$$



$$R_{out} = 223 \text{ k} \parallel 10 \text{ k} = 9.57 \text{ k}\Omega$$

$$A_v = A_{vt} \left(\frac{R_{in}}{R_I + R_{in}} \right) = \left(\frac{-9.64 \times v_{be} \times (223 \parallel 10 \parallel 220)}{v_{be}} \right) \left(\frac{6.23 \text{ k}}{330 + 6.23 \text{ k}} \right) = -84.0$$

Small Signal Parameters of MOSFET

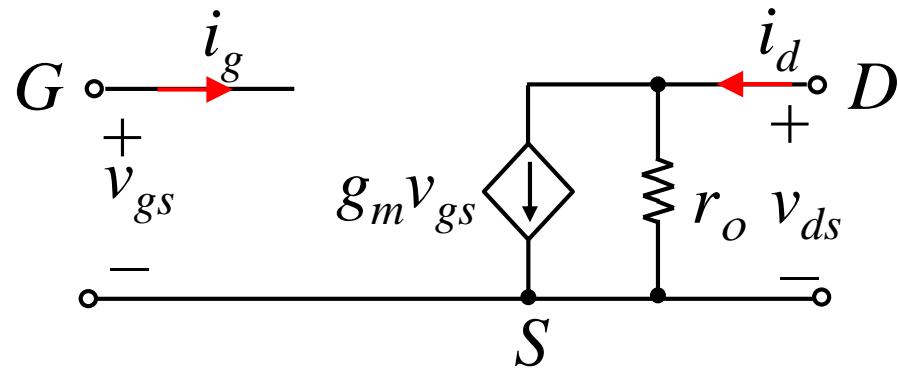

- Since gate is insulated from channel by gate-oxide, input resistance = ∞ .
- Small-signal parameters are controlled by the Q-point.
- MOSFET transconductance is geometry dependent.

$$i_D = \frac{K_n}{2} (v_{GS} - V_{TN})^2 (1 + \lambda v_{DS})$$

$$g_m = \left. \frac{\partial i_D}{\partial v_{GS}} \right|_{Q-pt} = K_n (V_{GS} - V_{TN}) (1 + \lambda V_{DS})$$


$$\text{where } K_n = \mu_n C_{ox} \left(\frac{W}{L} \right)$$

$$g_m = \frac{I_D}{V_{GS} - V_{TN}} \approx \sqrt{2K_n I_D}$$


$$r_o = \frac{1}{\lambda} + \frac{V_{DS}}{I_D} \approx \frac{1}{\lambda I_D} \text{ if } \frac{1}{\lambda} \gg V_{DS}$$

Small Signal Analysis of C-S Amplifier with Fully Bypass R_S

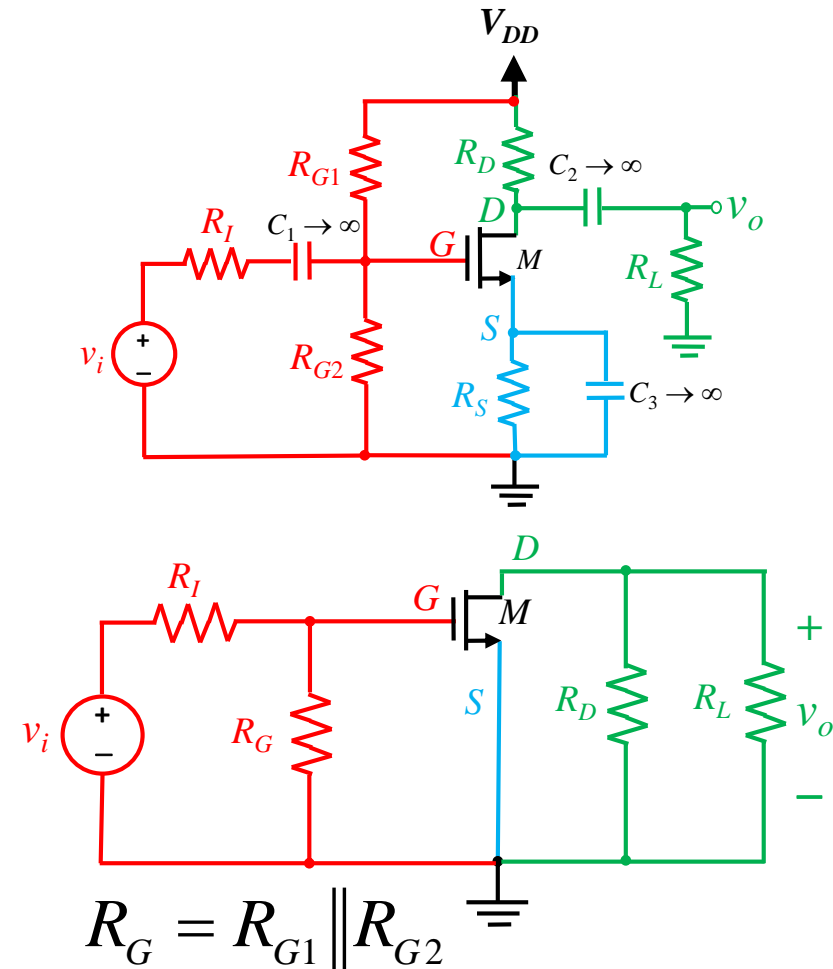- AC equivalent circuit is constructed by assuming that all capacitances have zero impedance at signal frequency and dc voltage sources represent ac grounds.
- The small signal parameters, g_m and r_o of the MOSFET is calculated at the Q-point, I_D and V_{DS} .



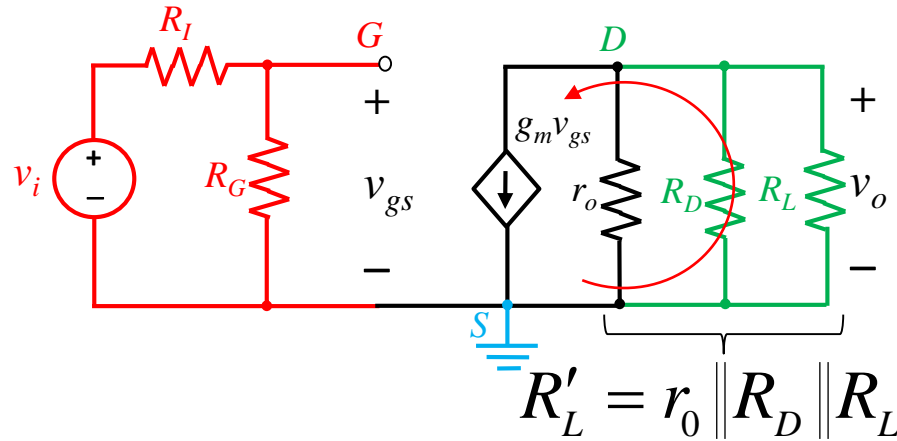C-S Amplifier with Fully Bypass R_S : Voltage Gain





Terminal voltage gain between gate and drain is:

$$A_{vt} = \frac{v_d}{v_g} = \frac{-g_m v_{gs} R'_L}{v_{gs}} = -g_m R'_L$$

Overall voltage gain from source v_i to output voltage v_o across R_L is:

$$\begin{aligned} A_v &= \frac{v_o}{v_i} = \frac{v_o}{v_g} \times \frac{v_g}{v_i} = A_{vt} \times \frac{v_g}{v_i} \\ &= -g_m R'_L \left(\frac{R_G}{R_I + R_G} \right) \end{aligned}$$

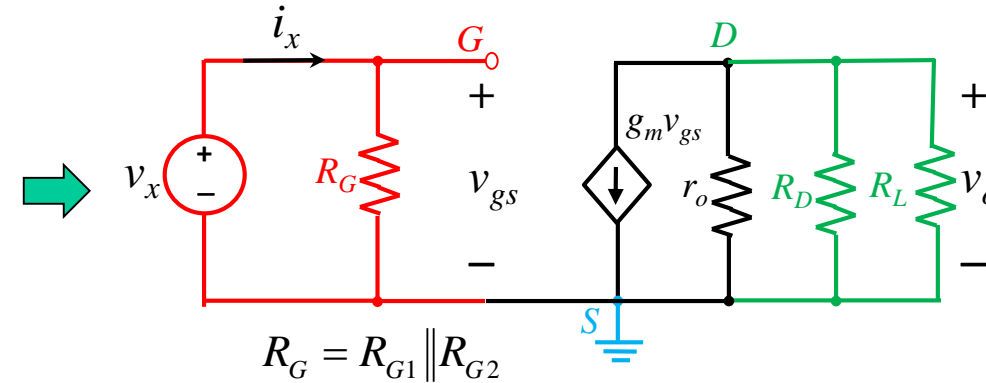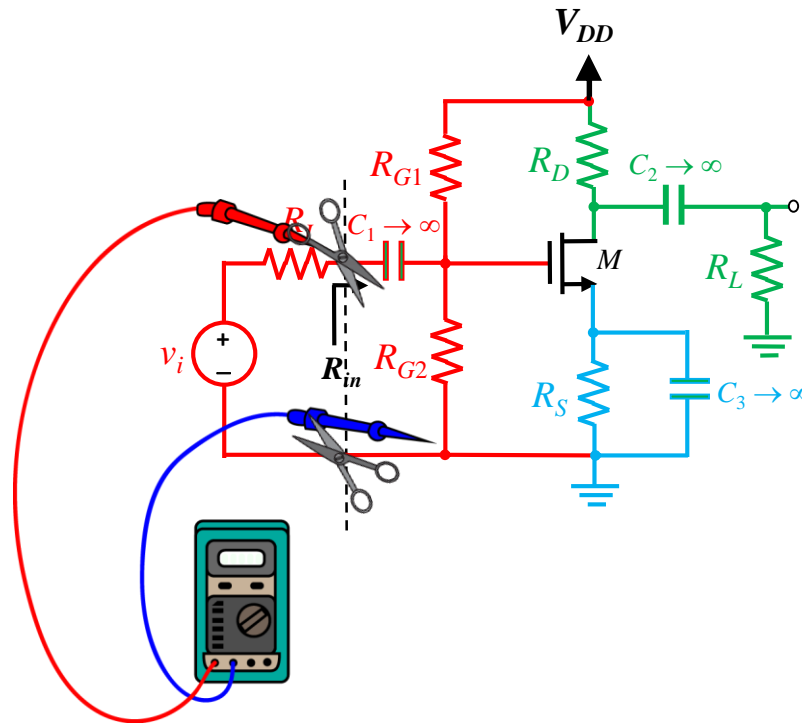C-S Amplifier with Fully Bypass R_S : Input Resistance




$$v_x = i_x R_G$$

$$R_{in} = \frac{v_x}{i_x}$$

$$= R_G$$

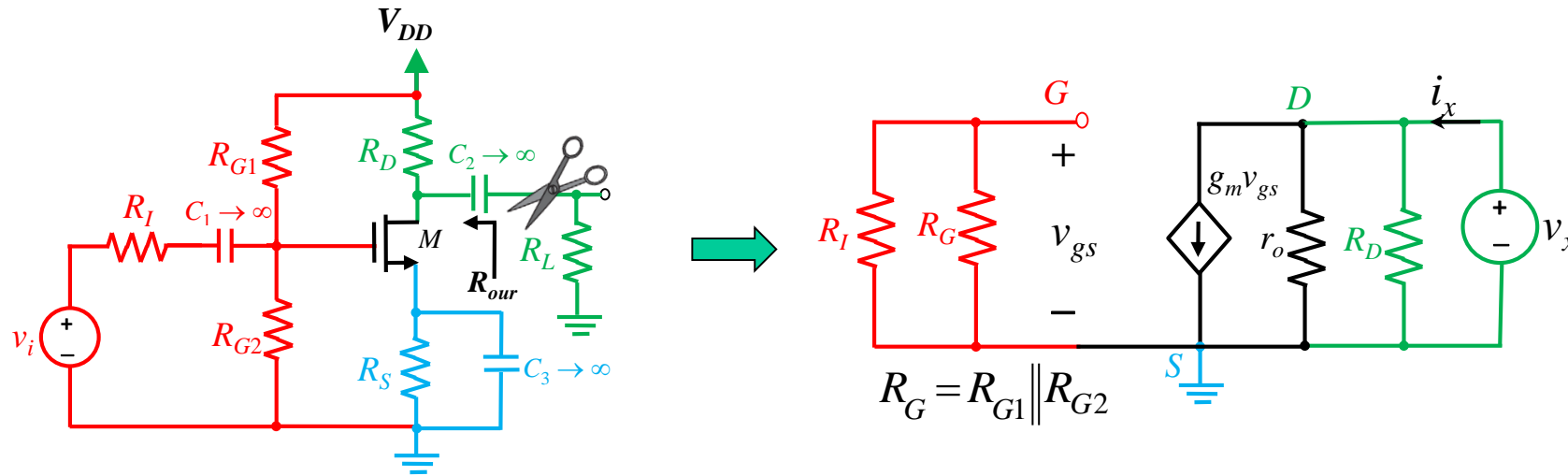C-S Amplifier with Fully Bypass R_S : Output Resistance




Since $v_{gs} = 0$, $g_m v_{gs} = 0$.

$$v_x = i_x (R_D \parallel r_o)$$

$$R_{out} = \frac{v_x}{i_x} = R_D \parallel r_o$$


$$R_{out} \approx R_D \text{ if } r_o \gg R_D$$

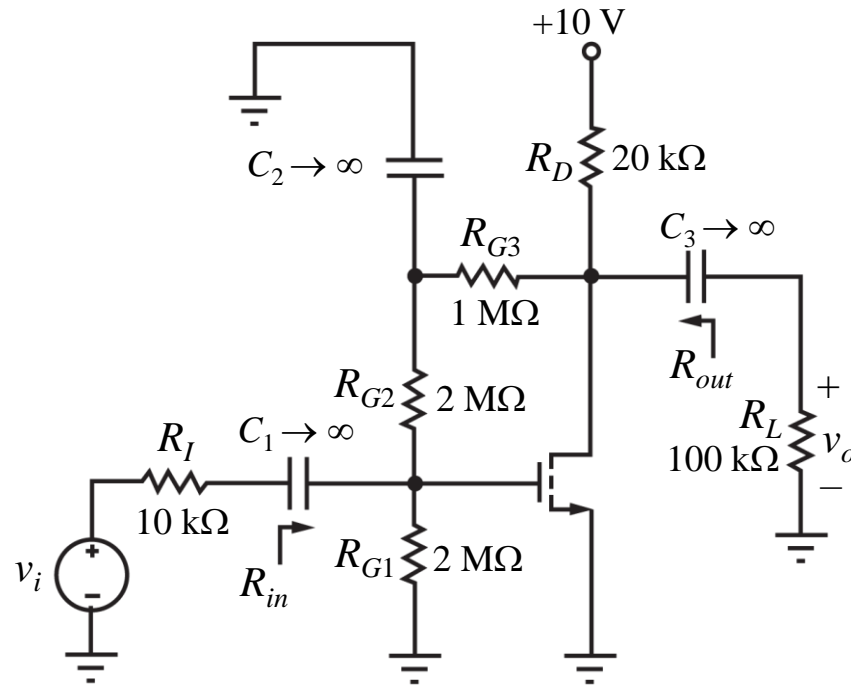C-S Amplifier with Fully Bypass R_S : Example



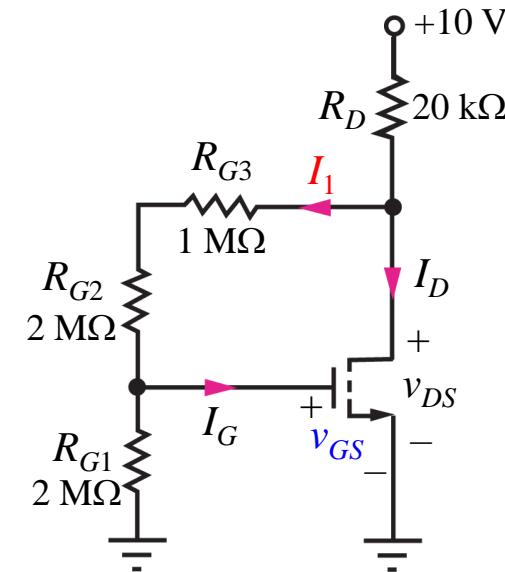Problem: Find voltage gain, input and output resistances.

Given: $K_n = 500 \mu\text{A}/\text{V}^2$, $V_{TN} = 1\text{V}$,
 $\lambda = 0.0167 \text{ V}^{-1}$



DC Analysis:

$$I_1 = \frac{V_{DS}}{5 \times 10^6}$$

$$V_{GS} = I_1 \times 2 \times 10^6 = 0.4V_{DS}$$


$$I_D = \frac{500 \mu}{2} (V_{GS} - 1)^2 \quad \text{--- (1)}$$

$$V_{DS} = 10 - 20 \times 10^3 (I_D + I_1) \quad \text{--- (2)}$$

$$\therefore V_{DS} = 5\text{V}, V_{GS} = 2\text{V}, I_D = 250 \mu\text{A}$$

C-S Amplifier with Fully Bypass R_S : Example


Small Signal Equivalent Circuit:

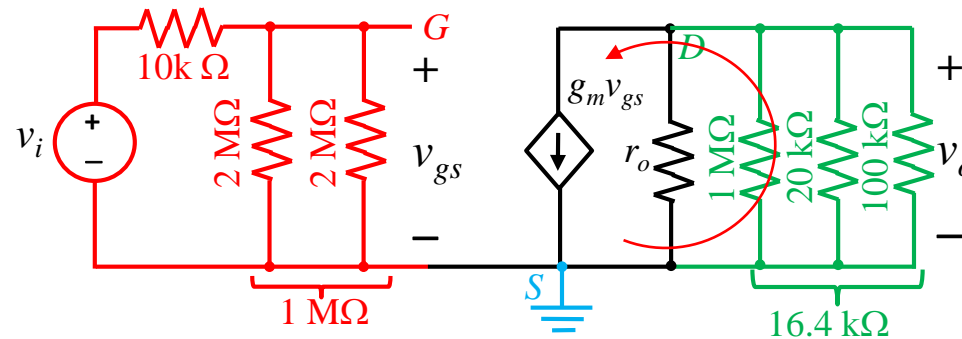


$$g_m \approx \sqrt{2 \times 500 \mu \times 250 \mu} = 0.5 \text{ mS}$$

$$r_o = \frac{1}{\frac{0.0167}{250 \mu} + 5} = 260 \text{ k}\Omega$$
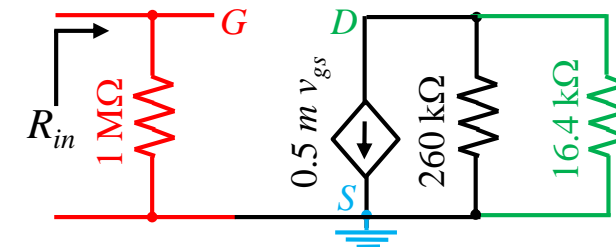
$$A_v = A_{vt} \left(\frac{R_{in}}{R_I + R_{in}} \right) = \frac{-(0.5 \text{ m}) v_{gs} (260 \text{ k} \parallel 1 \text{ M} \parallel 20 \text{ k} \parallel 100 \text{ k})}{v_{gs}} \left(\frac{1 \text{ M}}{10 \text{ k} + 1 \text{ M}} \right) = -7.93$$



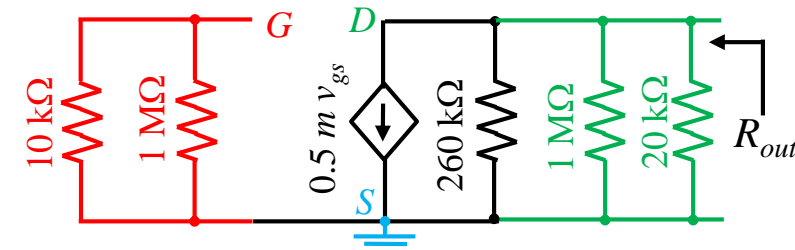
$$R_{in} = 2 \text{ M} \parallel 2 \text{ M} = 1 \text{ M}\Omega$$



$$R_{out} = 260 \text{ k} \parallel 1 \text{ M} \parallel 20 \text{ k} = 18.2 \text{ k}\Omega$$

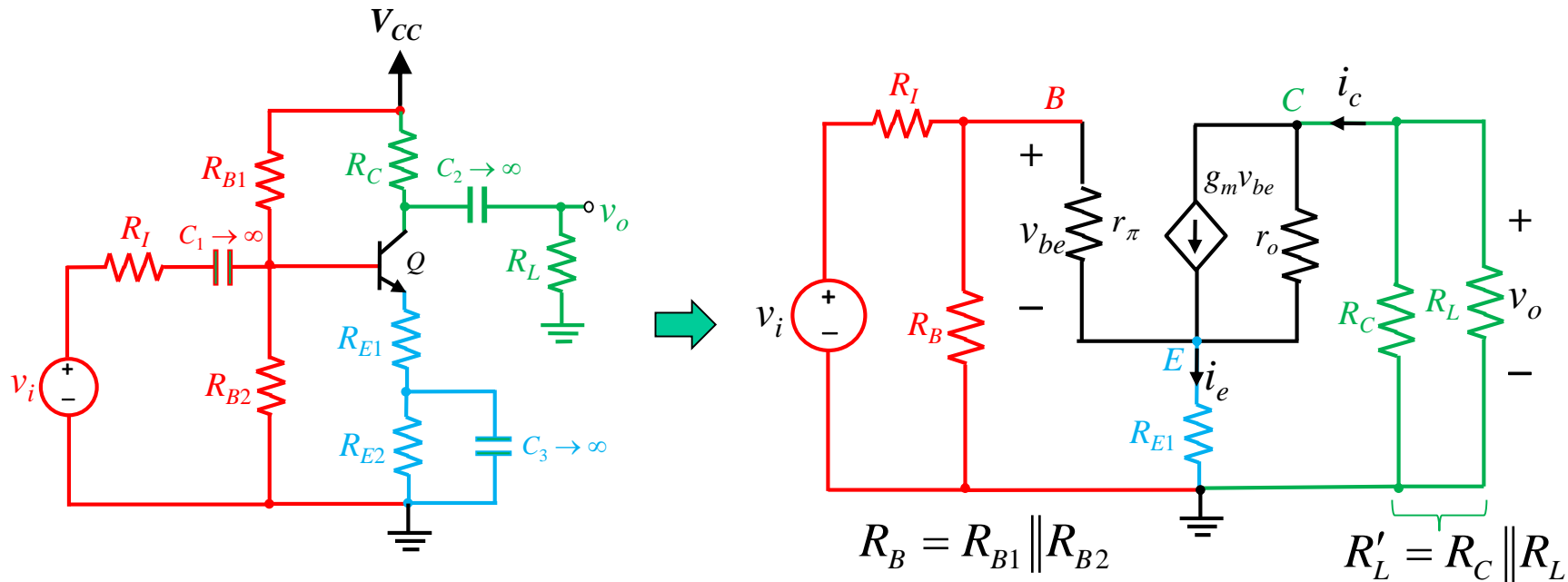
C-E Amplifier with Unbypassed R_E : Terminal Voltage Gain



$$\because i_{r_o} \ll g_m v_{be}, i_c \approx g_m v_{be} \approx i_e$$

$$A_{vt} = \frac{v_c}{v_b} = \frac{-i_c R'_L}{v_{be} + i_e R_{E1}} \approx \frac{-g_m v_{be} R'_L}{v_{be} + g_m v_{be} R_{E1}} = \frac{-g_m R'_L}{1 + g_m R_{E1}}$$

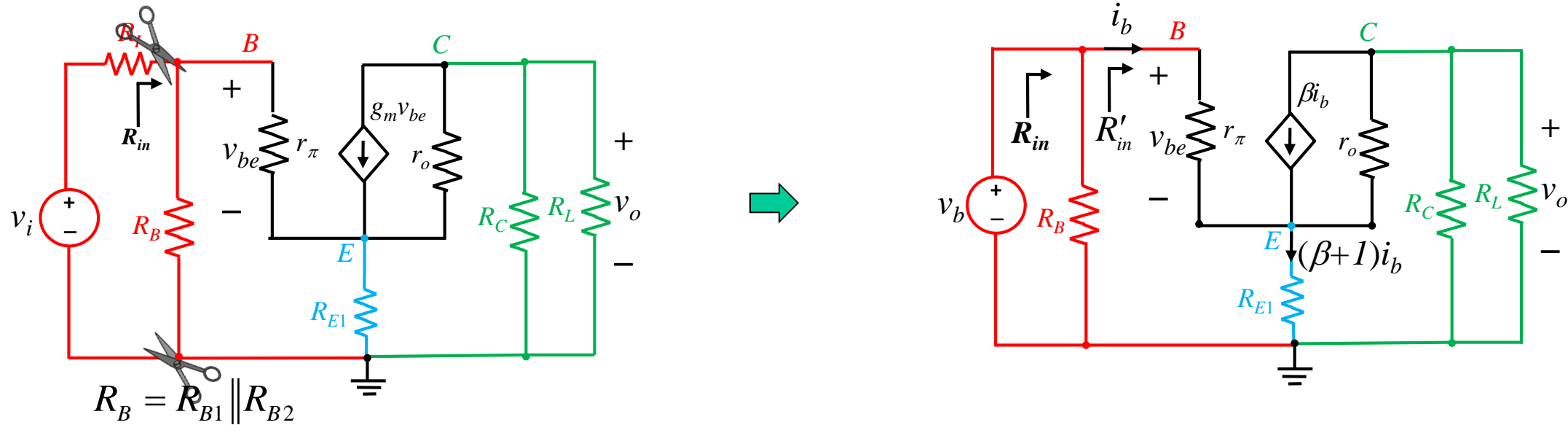
C-E Amplifier with Unbypass R_E : Input Resistance





$$v_b = i_b r_\pi + (\beta + 1) i_b R_{E1}$$

$$R'_{in} = \frac{v_b}{i_b} = r_\pi + (\beta + 1) R_{E1} \quad \Rightarrow \quad R_{in} = R'_{in} \parallel R_B$$

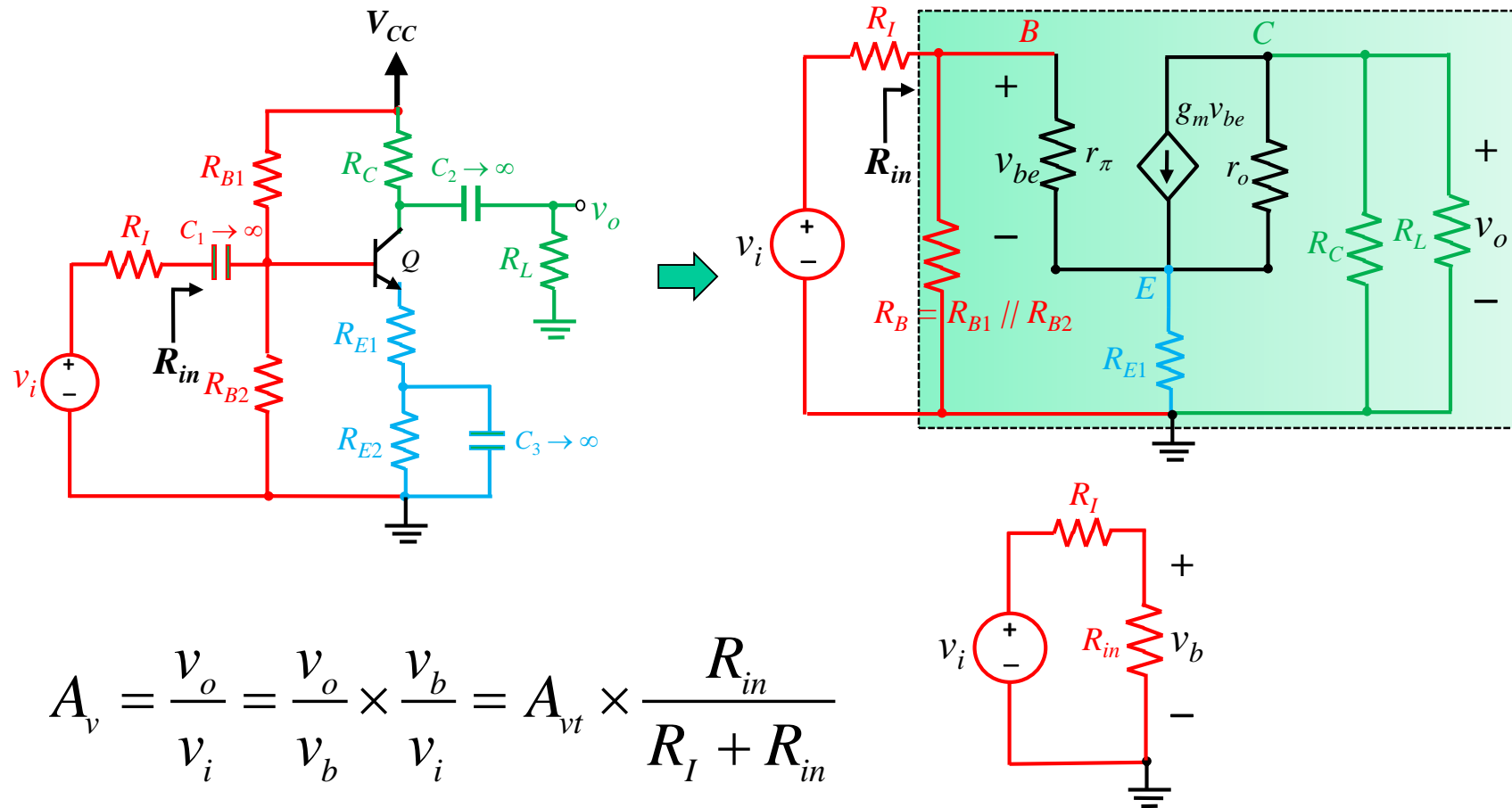C-E Amplifier with Unbypass R_E : Overall Voltage Gain



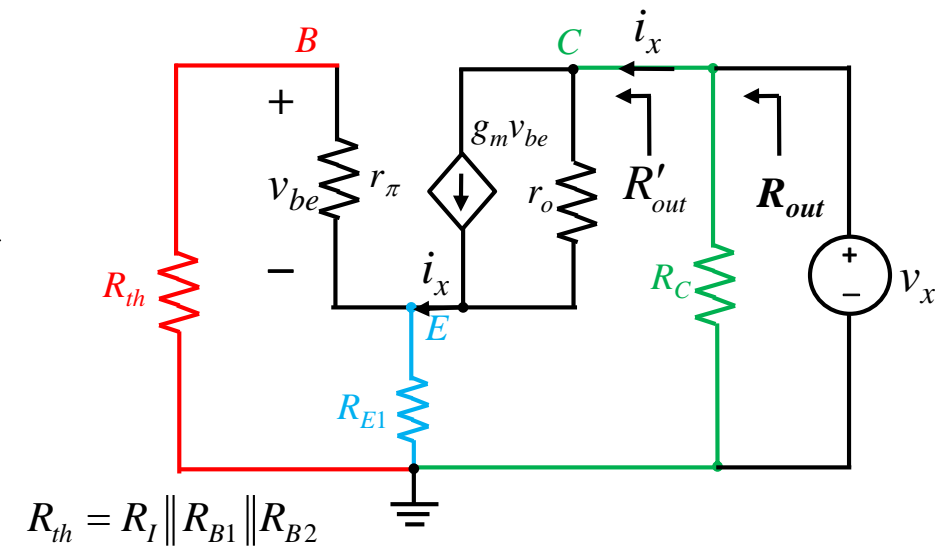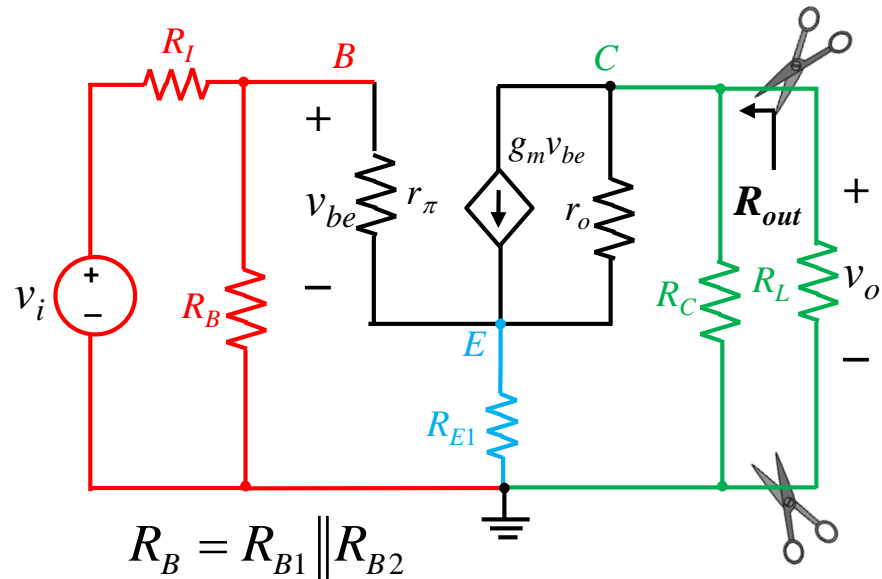C-E Amplifier with Unbypass R_E : Output Resistance




$$v_x = \underbrace{\left(i_x - g_m v_{be} \right)}_{\text{current through } r_o} r_o + v_e$$

$$v_e = i_x \left\{ (r_\pi + R_{th}) \parallel R_{E1} \right\}$$

$$v_{be} = - \left(\frac{r_\pi}{r_\pi + R_{th}} \right) v_e$$

$$= - \left(\frac{r_\pi}{r_\pi + R_{th}} \right) i_x \left\{ (r_\pi + R_{th}) \parallel R_{E1} \right\}$$

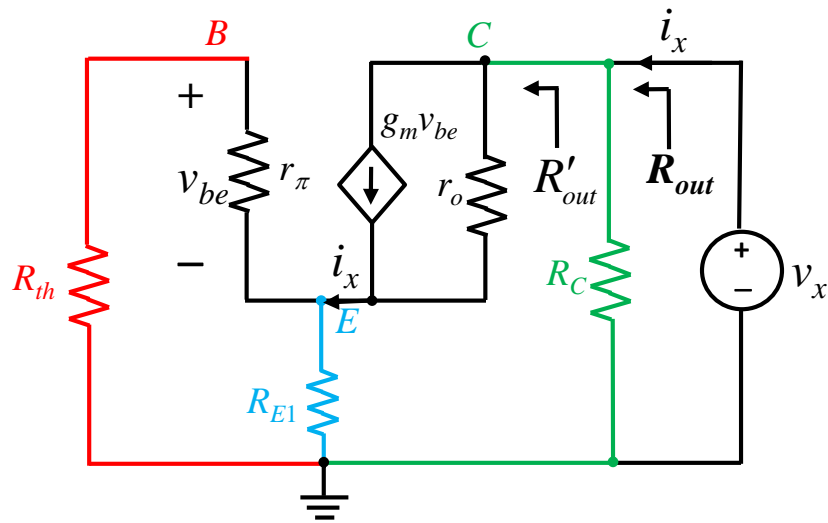C-E Amplifier with Unbypass R_E : Output Resistance




$$\begin{aligned}
 v_x &= (i_x - g_m v_{be}) r_o + v_e \\
 &= \left(i_x + g_m \left(\frac{r_\pi}{r_\pi + R_{th}} \right) i_x \left\{ (r_\pi + R_{th}) \parallel R_{E1} \right\} \right) r_o \\
 &\quad + i_x \left\{ (r_\pi + R_{th}) \parallel R_{E1} \right\}
 \end{aligned}$$

$$R'_{out} = \frac{v_x}{i_x} \approx \left(1 + g_m \left(\frac{r_\pi}{r_\pi + R_{th}} \right) \left\{ (r_\pi + R_{th}) \parallel R_{E1} \right\} \right) r_o$$

$$R_{out} = R'_{out} \parallel R_C$$

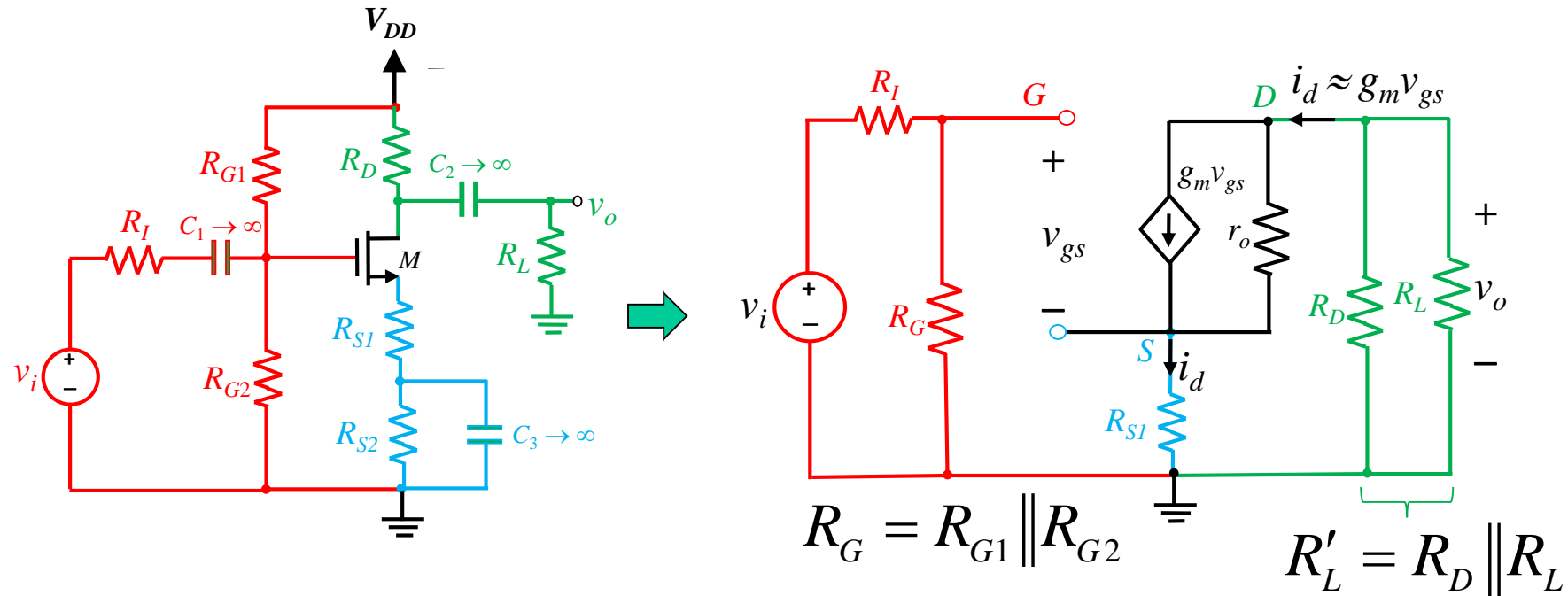
C-S Amplifier with Unbypass R_S : Terminal Voltage Gain



$$\because i_{r_o} \ll g_m v_{gs}, i_d \approx g_m v_{gs}$$


$$A_{vt} = \frac{v_d}{v_g} = \frac{-i_d R'_L}{v_{gs} + i_d R_{S1}} \approx \frac{-g_m v_{gs} R'_L}{v_{gs} + g_m v_{gs} R_{S1}} = \frac{-g_m R'_L}{1 + g_m R_{S1}}$$

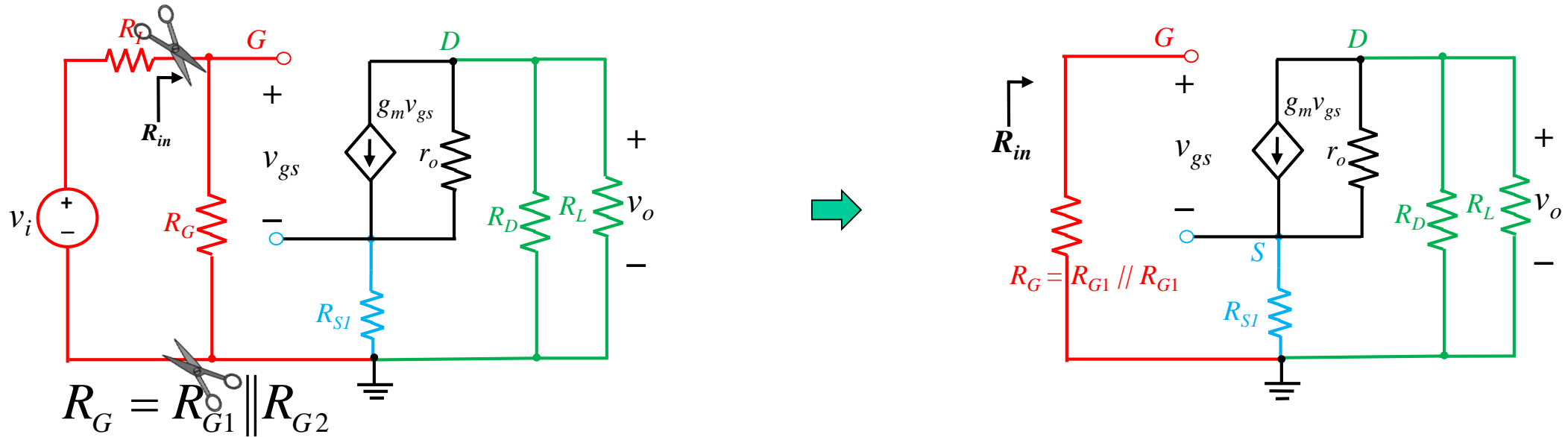C-S Amplifier with Unbypassed R_S : Input Resistance





$$R_{in} = R_G$$

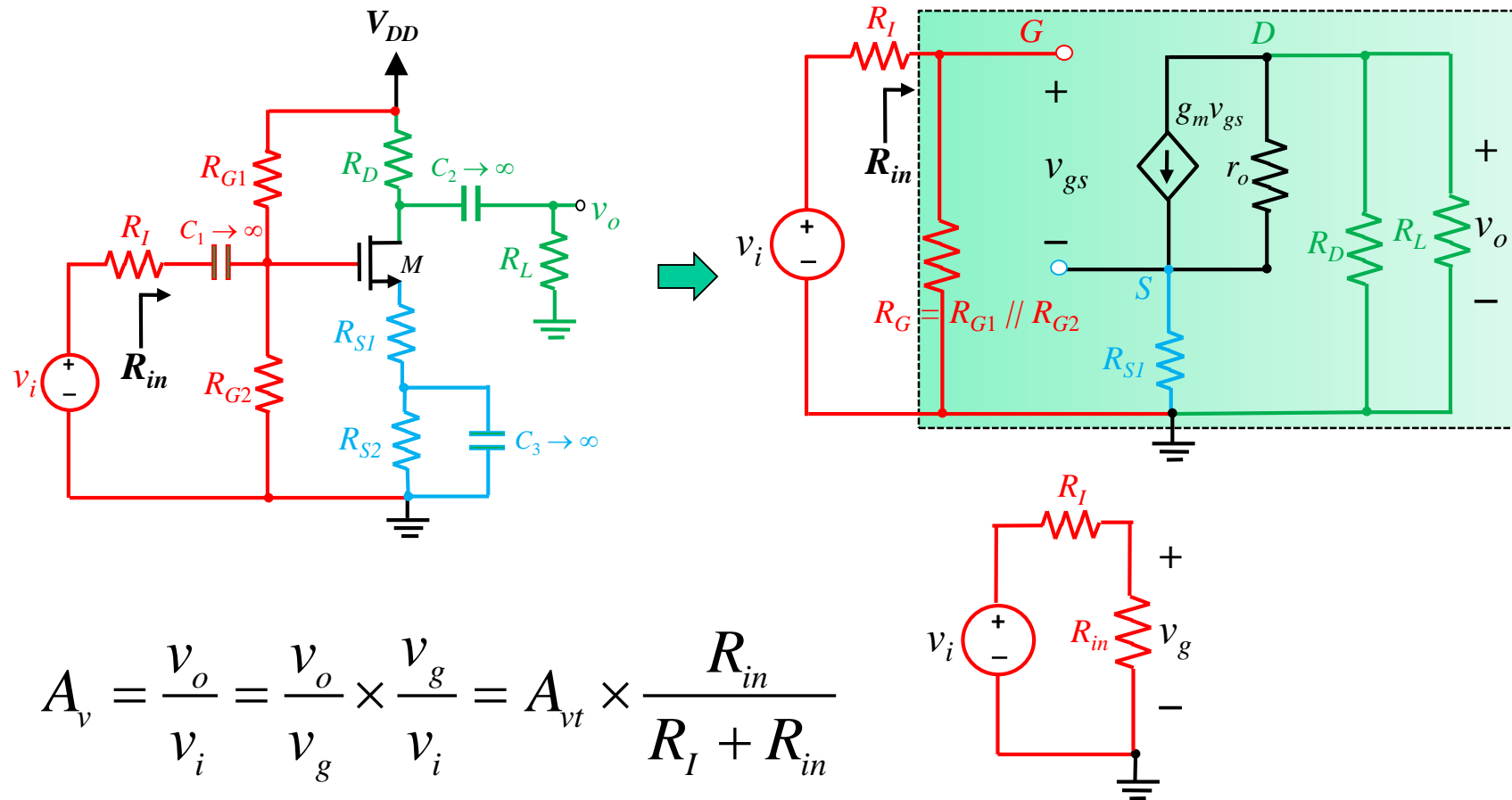C-S Amplifier with Unbypass R_S : Overall Voltage Gain



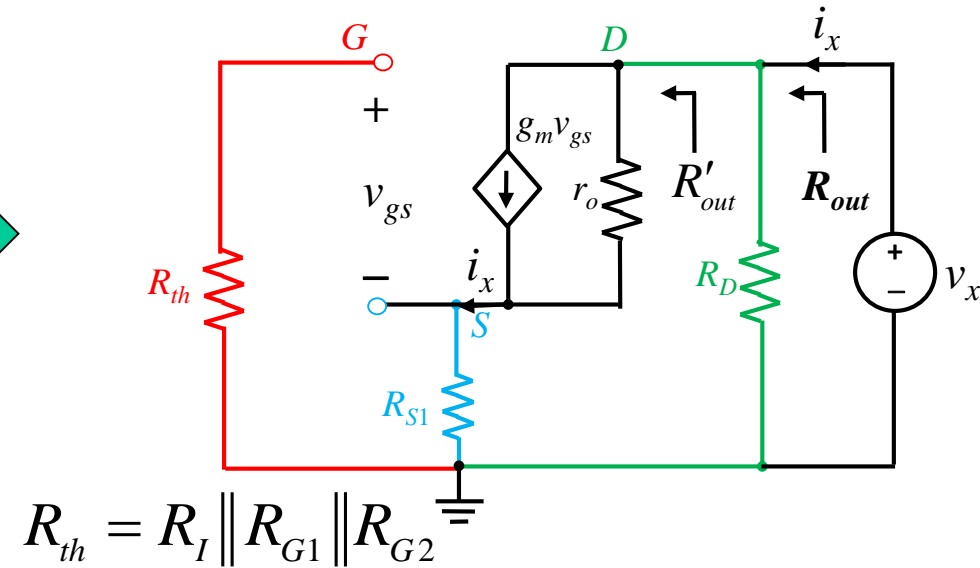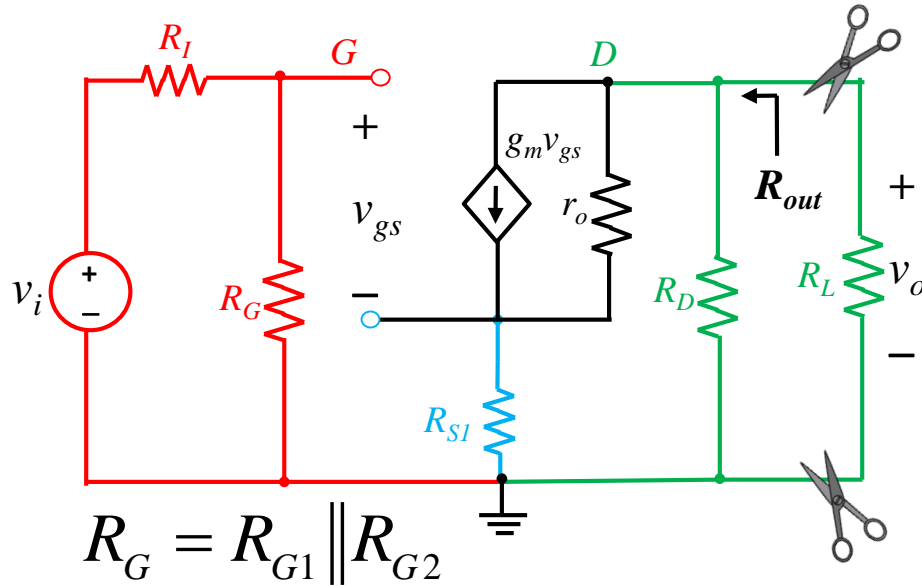C-S Amplifier with Unbypass R_S : Output Resistance



$$v_x = \underbrace{(i_x - g_m v_{gs})}_{\text{current through } r_o} r_o + v_s$$

$$v_s = i_x R_{S1}$$

$$\because v_g = 0, v_{gs} = -v_s = -i_x R_{S1}$$

$$v_x = (i_x + g_m i_x R_{S1}) r_o + i_x R_{S1}$$

$$R'_{out} = \frac{v_x}{i_x} \approx (1 + g_m R_{S1}) r_o$$

$$R_{out} = R'_{out} \parallel R_D$$