

NANYANG TECHNOLOGICAL UNIVERSITY**SEMESTER 2 EXAMINATION 2018-2019****EE2002 – ANALOG ELECTRONICS**

April / May 2019

Time Allowed: 2½ hours


INSTRUCTIONS

1. This paper contains 5 questions and comprises 9 pages.
 2. Answer ALL questions.
 3. All questions carry equal marks.
 4. This is a closed book examination.
 5. Unless specifically stated, all symbols have their usual meanings.
 6. A List of Formulae is provided in Appendix A on pages 7 to 9.
-
1. (a) For the non-ideal Op-Amp in negative feedback shown in Figure 1(a) on page 2, derive the expression for the output voltage v_{OUT} in terms of all or some of the following variables v_1 , v_2 , V_{IO} , I_+ , I_- , R_1 , R_2 , R_3 , R_4 , R_5 , R_6 and R_7 , assuming that the output is in the linear range of operation.

Note: Parallel resistance of R_a and R_b can be written as $R_a // R_b$ without expanding it.

(11 Marks)

Note: Question No. 1 continues on page 2.

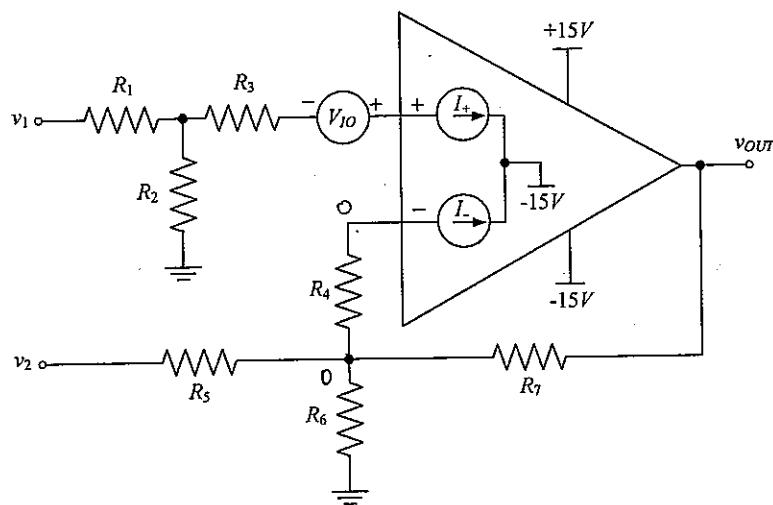
**Figure 1(a)**

- (b) In Figure 1(b), the empirical junction diode equation is:

$$V_D = n V_T \ln [I_D / I_S]$$

for the identical diodes D_1 and D_2 where $n = 1$, $V_T = 26 \text{ mV}$ and $I_S = 6 \times 10^{-17} \text{ A}$ at room temperature. The resistors $R_1 = R_2 = 8 \text{ k}\Omega$, $R_4 = 5 \text{ k}\Omega$, $R_3 = 20 \text{ k}\Omega$ and the DC voltage source $V_S = 10 \text{ V}$. Find the DC quiescent operating point or Q-point (I_D , V_D) of the diodes D_1 and D_2 (to 3 decimal places in μA and V, respectively).

(9 Marks)

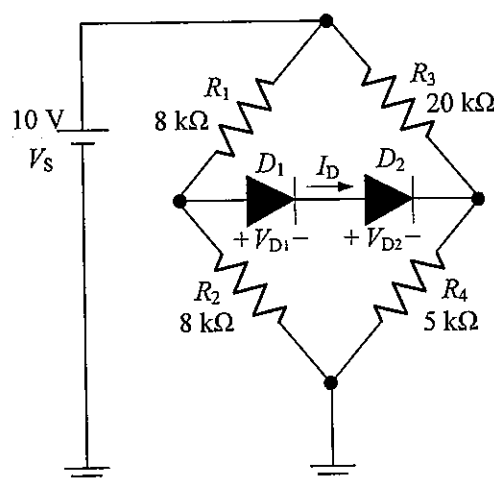**Figure 1(b)**

2. For the amplifier shown in Figure 2, the MOSFET transistor has $V_{TN} = 1$ V, $K_n = 200 \mu\text{A}/\text{V}^2$ and $\lambda = 0.01 \text{ V}^{-1}$. All the capacitors C_G , C_D and C_S in the circuit are assumed to have infinite capacitance.

(a) Find the Q-point of the transistor. (6 Marks)

(b) Draw the small signal equivalent circuit. Determine the voltage gain $A_v = \frac{v_o}{v_i}$ and current gain $A_i = \frac{i_o}{i_i}$ of the amplifier. (10 Marks)

(c) Determine the maximum amplitude of the input signal v_i for small-signal operation. (4 Marks)

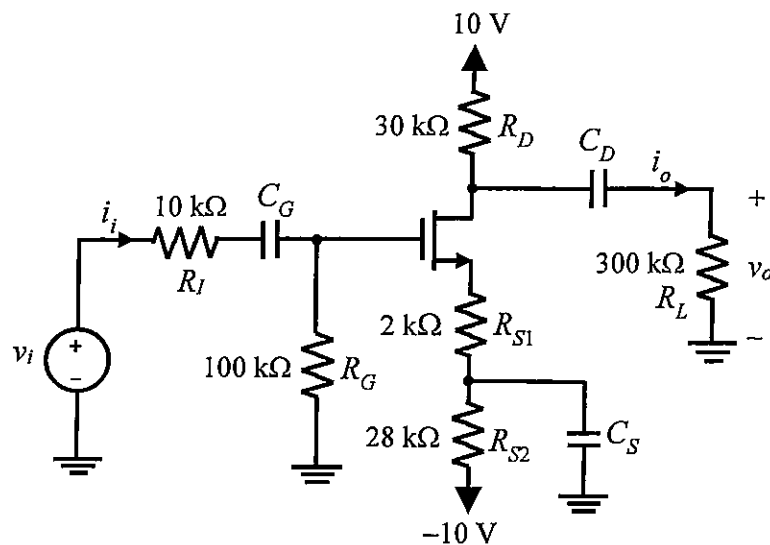


Figure 2

3. In Figure 3, the DC operating point for BJT Q_1 is $I_{C1} = 170 \mu\text{A}$ and $V_{CE1} = 4 \text{ V}$, and the DC operating point for BJT Q_2 is $I_{C2} = 240 \mu\text{A}$ and $V_{CE2} = 3 \text{ V}$. Both Q_1 and Q_2 have $\beta = 100$, $V_A = 75 \text{ V}$ at the room temperature. Assume that all the capacitors have infinite values, and all the resistors have the values as indicated in Figure 3.

- Determine the voltage gain $A_v = \frac{v_o}{v_i}$ (9 Marks)
- Determine the input resistance R_{in} and output resistance R_{out} of the amplifier. (6 Marks)
- Determine the small-signal input signal range for v_i of this amplifier. (5 Marks)

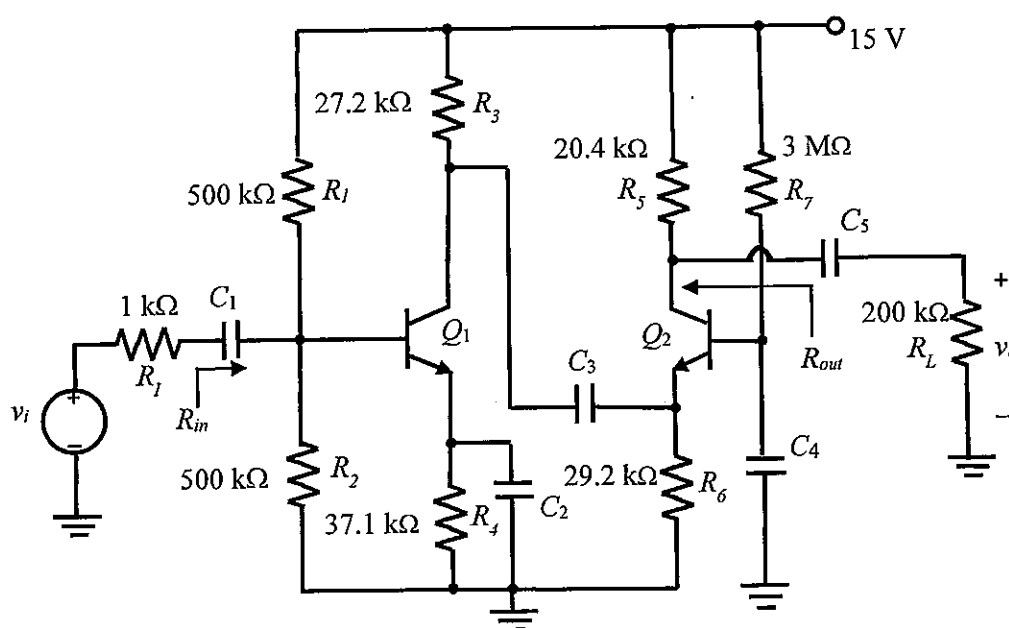


Figure 3

4. Consider the cascode current mirror circuit comprising PMOS transistors M_1 - M_4 as shown in Figure 4. Assume all the transistors are identical and in saturation. Perform small-signal analysis, indicating clearly the g_m and r_o of the i -th transistor as $g_{m,i}$ and $r_{o,i}$. For example, the g_m and r_o for transistor M_1 should be written as $g_{m,1}$ and $r_{o,1}$, respectively.

- (a) Draw the AC small signal model of the circuit and derive the expression for the output resistance R_{out} in terms of the small signal parameters g_m and r_o of the MOSFET.

(10 Marks)

- (b) Given that $I_{REF} = 200 \mu A$, K_p for the MOSFET is $100 \mu A/V^2$, $|V_{TP}| = 0.5 V$ and $\lambda = 0.01 V^{-1}$, find the value of the output resistance R_{out} based on the expression in part (a) if the drain of M_2 is connected to 0 V.

(5 Marks)

- (c) Using the same MOSFET parameter values given in part (b), find the value of the maximum voltage on the drain of M_2 such that all the transistors are in the saturation region.

(5 Marks)

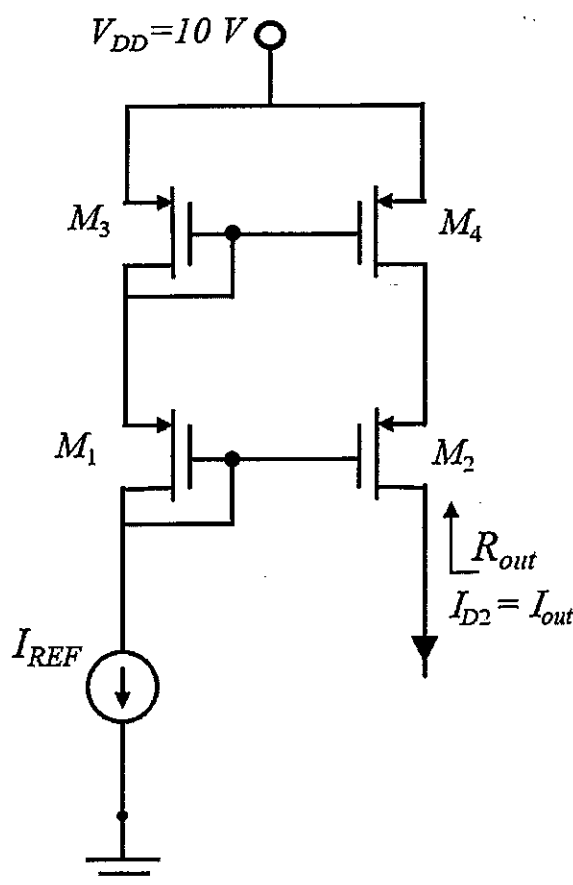


Figure 4

5. Observe that the circuit shown in Figure 5 is a cascade of two identical Op-Amp gain stages. Assume the Op-Amps are ideal.

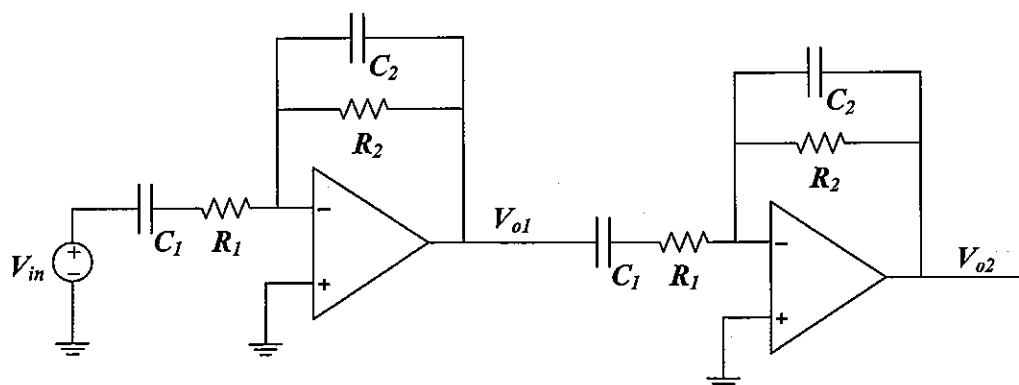


Figure 5

- (a) Considering only the first stage in this part, derive the first stage transfer function V_{o1} / V_{in} , in terms of R_2 , C_2 , R_1 and C_1 . (6 Marks)
- (b) Given that $R_2 = 10 \text{ k}\Omega$, $C_2 = 10 \text{ nF}$, $R_1 = 1 \text{ k}\Omega$, $C_1 = 10 \text{ }\mu\text{F}$, draw the Bode plot for the transfer function $|V_{o1} / V_{in}|$ derived in part (a). Clearly mark the slopes (in dB/decade) for all the regions in the plot, and indicate the lower cut-off angular frequency ω_L , upper cut-off angular frequency ω_H , and the maximum gain A_0 achieved at angular frequency $\omega = 1000 \text{ rad/sec}$. (8 Marks)
- (c) Now, consider the cascade of both stages in Figure 5, with a transfer function $|V_{o2} / V_{in}|$. Use the SCTC and OCTC methods to find the new values of ω_L and ω_H for the cascade $V_{o2} / V_{in} = (V_{o1} / V_{in})^2$. (6 Marks)

Appendix A**List of Selected Formulae (with the usual notations)****Op-Amps:**

Closed-Loop Negative Feedback Inverting Gain, $A_{vCL} = \frac{v_o}{v_i} = -\frac{R_f}{R_i}$ Figure (a)

Closed-Loop Negative Feedback Non-Inverting Gain, $A_{vCL} = \frac{v_o}{v_i} = \left(1 + \frac{R_f}{R_i}\right)$ Figure (b)

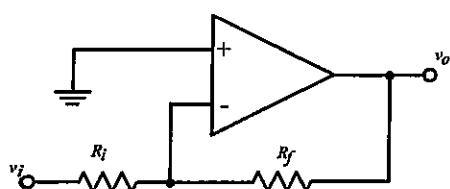


Figure (a)

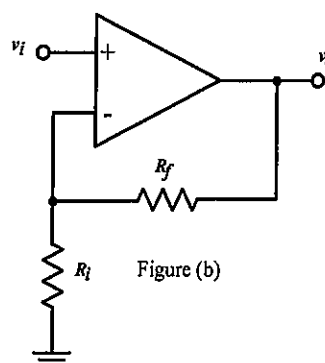


Figure (b)

Op-Amp's Slew Rate, $SR \geq \left| \frac{dv_o}{dt} \right|_{\max} = A_{vCL} \omega a_m = A_{vCL} a_m 2\pi f$,


where $v_i = a_m \sin(\omega t)$, $v_o = A_{vCL} v_i$, $v_o = A_{vCL} a_m \sin(\omega t)$ and $\left| \frac{dv_o}{dt} \right| = A_{vCL} \omega a_m \cos(\omega t)$

Op-Amp's frequency response: $A_{VOL}(jf) = \frac{A_o}{\left(1 + \frac{jf}{f_p}\right)}$

Gain-Bandwidth Product: $A_o f_p = f_o = \frac{1}{\beta} (BW)_{CL}$

where $\frac{1}{\beta} = \frac{R_f + R_i}{R_i}$

$t_r = \frac{0.35}{(BW)_{CL}}$

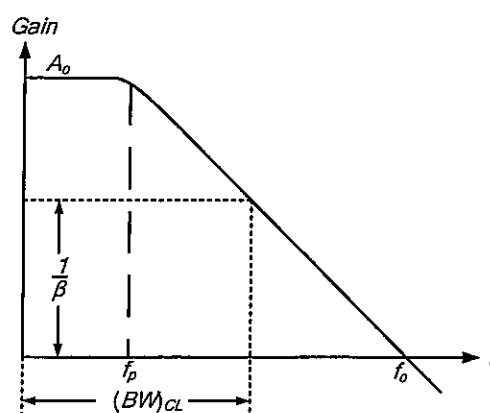**Diodes:**

$v_D \approx nV_T \ln\left(\frac{i_D}{I_S}\right)$ or $i_D \approx I_S e^{\left(\frac{v_D}{nV_T}\right)}$

where $e^x = 1 + x + \frac{x^2}{2!} + \frac{x^3}{3!} + \frac{x^4}{4!} + \dots$

Diode conductance: $g_D = \frac{1}{r_D} = \frac{I_D}{nV_T}$

BJT in Forward Active Region:

Ignore early effect: $i_C = I_s \exp\left(\frac{|v_{BE}|}{V_T}\right)$

With early effect: $i_C = I_s \exp\left(\frac{|v_{BE}|}{V_T}\right) \left(1 + \frac{|v_{CE}|}{V_A}\right)$

where I_s : Saturation current,

V_T : Thermal voltage, assume 25 mV at room temperature,

V_A : Early voltage.

For npn transistor, $|v_{BE}| = v_{BE}$ and $|v_{CE}| = v_{CE}$;

For pnp transistor, $|v_{BE}| = v_{EB}$ and $|v_{CE}| = v_{EC}$.

Small-signal model parameters of BJT:

$$g_m = \frac{I_C}{V_T}, \quad r_\pi = \frac{\beta}{g_m} \quad \text{and} \quad r_o = \frac{V_A + |V_{CE}|}{I_C} \approx \frac{V_A}{I_C}$$

where I_C : DC collector current at Q-point

V_{CE} : DC collector-emitter voltage at Q-point

Criterion for small-signal operation of BJT: $|v_{be}| \leq 0.2V_T$

MOSFET in Saturation Region:

Criterion: $V_{DS} \geq V_{GS} - V_{TN}$ for NMOS;

$|V_{DS}| \geq |V_{GS}| - |V_{TP}|$ for PMOS

where V_{TN}, V_{TP} : Threshold voltage,

V_{DS} : DC drain-source voltage,

V_{GS} : DC gate-source voltage.

Ignore channel-length modulation effect:

$$i_D = \frac{K_n}{2} (v_{GS} - V_{TN})^2 \quad \text{for NMOS,}$$

$$i_D = \frac{K_p}{2} (|v_{GS}| - |V_{TP}|)^2 \quad \text{for PMOS.}$$

With channel-length modulation effect:

$$i_D = \frac{K_n}{2} (v_{GS} - V_{TN})^2 (1 + \lambda v_{DS}) \quad \text{for NMOS,}$$

$$i_D = \frac{K_p}{2} (|v_{GS}| - |V_{TP}|)^2 (1 + \lambda |v_{DS}|) \quad \text{for PMOS.}$$

where λ : channel length modulation parameter,

For NMOS $K_n = K'_n \left(\frac{W}{L}\right)$ and $K'_n = \mu_n C_{ox}$; For PMOS $K_p = K'_p \left(\frac{W}{L}\right)$ and $K'_p = \mu_p C_{ox}$.

MOSFET in Triode Region:

Criterion: $V_{DS} < V_{GS} - V_{TN}$ for NMOS;
 $|V_{DS}| < |V_{GS}| - |V_{TP}|$ for PMOS

Ignore channel-length modulation effect:

$$i_D = K_n \left(v_{GS} - V_{TN} - \frac{v_{DS}}{2} \right) v_{DS} \text{ for NMOS,}$$

$$i_D = K_p \left(|v_{GS}| - |V_{TP}| - \frac{|v_{DS}|}{2} \right) |v_{DS}| \text{ for PMOS.}$$

With channel-length modulation effect:

$$i_D = K_n \left(v_{GS} - V_{TN} - \frac{v_{DS}}{2} \right) v_{DS} (1 + \lambda v_{DS}) \text{ for NMOS,}$$

$$i_D = K_p \left(|v_{GS}| - |V_{TP}| - \frac{|v_{DS}|}{2} \right) |v_{DS}| (1 + \lambda |v_{DS}|) \text{ for PMOS.}$$

Small-signal model parameters of MOSFET

For NMOS: $g_m = \sqrt{2K_n I_D (1 + \lambda V_{DS})} \approx \sqrt{2K_n I_D}$ and $r_o = \frac{\frac{1}{\lambda} + V_{DS}}{I_D} \approx \frac{1}{\lambda I_D}$

For PMOS: $g_m = \sqrt{2K_p I_D (1 + \lambda |V_{DS}|)} \approx \sqrt{2K_p I_D}$ and $r_o = \frac{\frac{1}{\lambda} + |V_{DS}|}{I_D} \approx \frac{1}{\lambda I_D}$

where I_D : DC drain current at Q-point

V_{DS} : DC drain-source voltage at Q-point

Criterion for small-signal operation:

For NMOS: $|v_{gs}| \leq 0.2(V_{GS} - V_{TN})$

For PMOS: $|v_{gs}| \leq 0.2(|V_{GS}| - |V_{TP}|)$

where V_{GS} : DC gate-source voltage at Q-point.

Frequency Response: OCTC and SCTC

1. **Disable** all independent sources (voltage sources \rightarrow Short Circuit; current sources \rightarrow Open Circuit); **Do not** remove or "disable" dependent sources!
2. **Identify** capacitors contributing to the frequency of interest, i.e., lower of higher cut-off.

higher cut-off \downarrow

3. **Idealise** irrelevant capacitors by **short circuit** (because at high f, cap \rightarrow short)
4. For each contributing capacitor C_i , set all other capacitors (other than the one you are looking at) **removed** (i.e. **Open Circuits**) and determine the resistance, R_i , seen by C_i
5. Higher cut-off frequency is estimated as:

$$\omega_{H-3dB} \approx \frac{1}{\sum_i C_i R_i}$$

\downarrow lower cut-off

3. **Idealise** irrelevant capacitors by **open circuit** (because at low f, cap \rightarrow open)
4. For each contributing capacitor C_i , set all other capacitors (other than the one you are looking at) **removed** (i.e. **Short Circuits**) and determine the resistance, R_i , seen by C_i
5. Lower cut-off frequency is estimated as:

$$\omega_{L-3dB} \approx \frac{1}{\sum_i C_i R_i}$$

END OF PAPER



EE2002 PYP Solution

2018/2019 S2

Date

No.

1a.

$$\begin{aligned}
 V_{out} &= V_{out}|_{V_1} + V_{out}|_{V_2} + V_{out}|_{V_{I0}} + V_{out}|_{I_+} + V_{out}|_{I_-} \\
 &= V_1 \left(1 + \frac{R_7}{R_5 \parallel R_6} \right) \left(\frac{R_2}{R_1 + R_2} \right) + V_2 \left(-\frac{R_7}{R_5} \right) + V_{I0} \left(1 + \frac{R_7}{R_5 \parallel R_6} \right) \\
 &\quad + I_+ \left(-\left((R_2 \parallel R_1) + R_3 \right) \right) \left(1 + \frac{R_7}{R_5 \parallel R_6} \right) + I_- (R_4 + R_7) \\
 &= \left(1 + \frac{R_7}{R_5 \parallel R_6} \right) \left(V_1 \left(\frac{R_2}{R_1 + R_2} \right) + V_{I0} - I_+ \left((R_2 \parallel R_1) + R_3 \right) \right) - V_2 \left(\frac{R_7}{R_5} \right) \\
 &\quad + I_- (R_4 + R_7)
 \end{aligned}$$

1b. Finding V_{TH} ,

At node A,


$$V_A = V_S \left(\frac{R_2}{R_1 + R_2} \right) = \frac{1}{2} \cdot 10V = 5V$$

At node B,

$$V_B = V_S \left(\frac{R_4}{R_3 + R_4} \right) = \frac{5}{25} \cdot 10V = 2V$$

$$V_{TH} = V_A - V_B = 3V$$

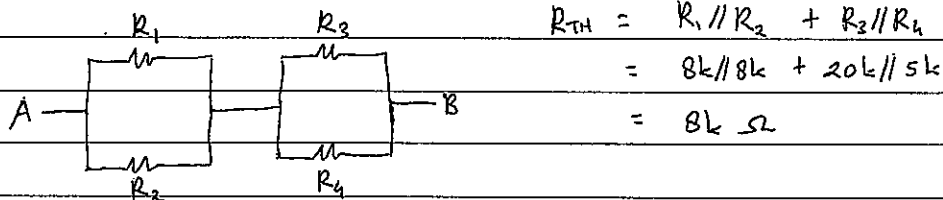Finding R_{TH} , voltage source becomes short circuit, then the circuit can be seen this way:



$$\begin{aligned}
 V_{01} &= V_{02} = V_0 \\
 I_D &= \frac{V_{TH} - 2V_0}{R_{TH}} \\
 I_D &= \frac{3 - 2V_0}{8k} \quad \dots (1)
 \end{aligned}$$

$$V_0 = nV_T \ln \left(\frac{I_D}{I_S} \right) = 26 \times 10^{-3} \ln \left(\frac{I_D}{6 \times 10^{-17}} \right) \quad \dots (2)$$

V_0	0.7	0.7497	0.7480	0.7481	0.7481	0.7481
I_D (in μA)	200	187.5725	187.9895	187.9751	187.9756	187.9756

DC quiescent operating point:

$I_D = 187.976 \mu A$
$V_0 = 0.748 V$




Date

No.

2a.

Assume the NMOS is in saturation region,

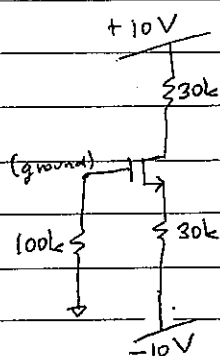

$$10 = V_{GS} + I_D (30k)$$

$$V_{GS} = 10 - (30k)(I_D) \dots (1)$$

$$I_D = \frac{K_n}{2} (V_{GS} - V_{TN})^2 \dots (2)$$

Substitute (1) into (2),

$$I_D = 100\mu \left(10 - (30k)I_D - 1 \right)^2$$

$$0 = 9 \times 10^4 I_D^2 - 55 I_D + 8.1 \times 10^{-3}$$

$$I_D = 0.364 \text{ mA}$$

$$\text{or } I_D = 0.248 \text{ mA}$$

$$V_{GS} = -0.92 \text{ V}$$


$$V_{GS} = 2.56 \text{ V}$$

(not valid)

$$V_{DS} = 20 - I_D (30k + 30k)$$

$$V_{DS} = 5.12 \text{ V}$$

2b.

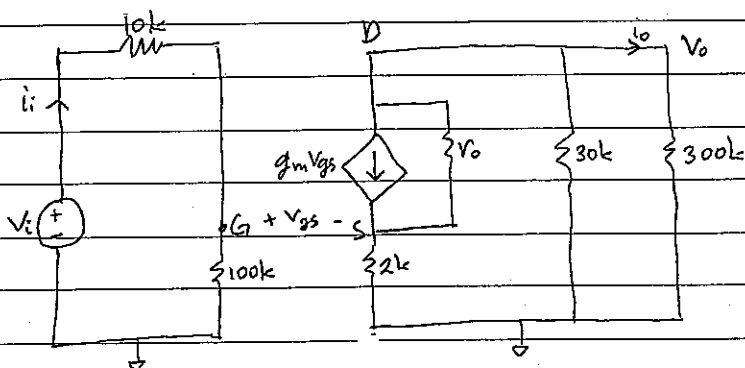

$$g_m = \sqrt{2K_n I_D}$$

$$= \sqrt{2(200\mu)(0.248\text{m})}$$

$$= 3.15 \times 10^{-4}$$

$$r_o = \frac{1}{\lambda I_D} = \frac{1}{(0.01)(0.248\text{m})} = 403.226 \text{ k}\Omega$$

→ can be ignored since r_o is large.

$$V_o = -(30k // 300k) g_m V_{gs}$$

$$V_o = 8.59 (-V_g + V_s) \dots (1)$$

$$V_s = (2k)(g_m V_{gs})$$

$$V_s = 0.63 (V_g - V_s)$$

$$1.63 V_s = 0.63 V_g \dots (2)$$

$$V_g = \frac{100k}{100k + 10k} V_i = \frac{10}{11} V_i \dots (3)$$

Substitute (2) and (3) into (1), we get

$$V_o = 8.59 \left(-1 + \frac{0.63}{1.63} \right) \left(\frac{10}{11} \right) V_i$$



Date

No.

$$A_v = \frac{V_o}{V_i} = -4.79$$

$V_o = i_o (300k)$ and $V_i = i_i (110k)$, hence

$$\frac{300k}{110k} \cdot \frac{i_o}{i_i} = -4.79$$

$$A_i = \frac{i_o}{i_i} = -1.76$$

2c. For small-signal operation, $|V_{gs}| \leq 0.2 (V_{GS} - V_{TH})$

$$|V_{gs}| \leq 0.312 \text{ V}$$


$$|V_g - V_s| \leq 0.312$$

$$|V_g (1 - \frac{0.63}{1.63})| \leq 0.312$$

$$\frac{10}{11} (1 - \frac{0.63}{1.63}) |V_i| \leq 0.312$$

$$|V_i| \leq 0.559 \text{ V}$$

3a.

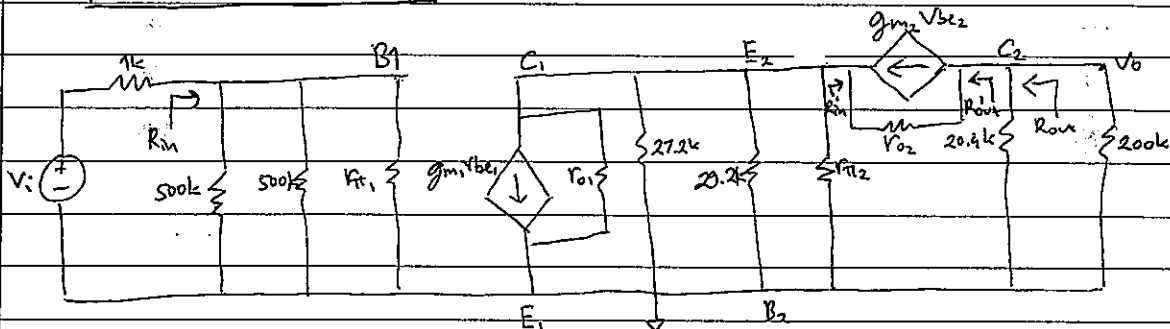

$$g_{m1} = 40 I_{C1} = 6.8 \times 10^{-3}$$

$$r_{\pi 1} = \frac{\beta}{g_{m1}} = \frac{100}{6.8 \times 10^{-3}} = 14.706 \text{ k}\Omega$$

$$r_{o1} = \frac{V_A + |V_{CE1}|}{I_{C1}} = \frac{75 + 4}{170 \mu} = 464.706 \text{ k}\Omega$$

$$g_{m2} = 3.6 \times 10^{-3}$$

$$r_{\pi 2} = 10.417 \text{ k}\Omega$$

$$r_{o2} = \frac{75 + 3}{240 \mu} = 325 \text{ k}\Omega$$

Ignoring current through r_{o2} ,

$$V_o = -g_{m2} V_{be2} (20.4k // 200k)$$

$$\frac{V_o}{V_{be2}} = g_{m2} (20.4k // 200k) \dots (1)$$

$$R'_{in} = \frac{V_{be2}}{g_{m2} V_{be2}} = \frac{1}{g_{m2}}$$

$$V_{e2} = - \left(R_{a1} // 27.2k // 29.2k // R_{E2} // \frac{1}{g_{m2}} \right) g_{m1} V_{be1}$$

$$\frac{V_{e2}}{V_{b1}} = - (R_{o1} // 27.2k // 25.2k // R_{i2} // \frac{1}{g_{m2}}) g_{m1} \dots (2)$$

$$\frac{V_{b1}}{V_{in}} = \frac{500k // 500k // R_{T1}}{(500k // 500k // R_{T1}) + 1k} \dots (3)$$

Multiply (1), (2), and (3)

$$\frac{V_o}{V_i} = \frac{V_o}{V_{e2}} \cdot \frac{V_{e2}}{V_{b1}} \cdot \frac{V_{b1}}{V_{in}}$$

$$A_v = 115.38$$

$$3b. \quad R_{in} = 500k // 500k // r_{\pi 1} = 13.89k\Omega$$

Finding Root,

$$v_x = i_x (r_{o1} \parallel 27.2k \parallel 29.2k \parallel r_{\pi 2}) + (i_x - g_{m2} v_{be2}) r_{o2}$$

$$V_{be2} = -V_{e2} = -i_x (r_{o1} \parallel 27.2k \parallel 29.2k \parallel r_{\pi2})$$

$$R_{o1} = \frac{v_x}{i_x} = r_{o1} \parallel 27.2k \parallel 29.2k \parallel r_{\pi 2} + (1 + g_{m2} (r_{o1} \parallel 27.2k \parallel 29.2k \parallel r_{\pi 2})) r_{o2}$$

$$R_{out}' = 18.77 \text{ M}\Omega$$

$$R_{out} = R_{out'} // 20.4k$$

$$R_{out} = 20.38 \text{ k}\Omega$$

3c. For small-signal operation of Q_2 ,

$$|V_{be2}| \leq 0.005 \text{ V}$$


$$\frac{V_{be2}}{V_{in}} = -\frac{V_{e2}}{V_{b1}} \cdot \frac{V_{b1}}{V_{in}} \quad (\text{refer to (2) and (3)})$$

$$V_{be2} = -0.649 \text{ V}_{in}$$

Substitute back to the range, we get

$$|V_{th}| \leq 7.7 \text{ mV}$$

4a.

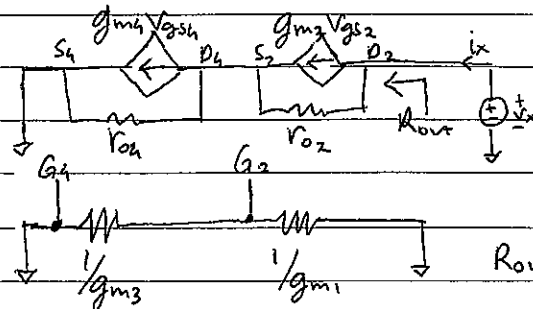

$$V_{gs4} = 0$$

$$V_x = i_x (r_{o4}) + (i_x - g_{m2} V_{gs2}) r_{o2} \dots (1)$$

$$V_{gs2} = -V_{s2} = -i_x R_{o4} \dots (2)$$

Substitute (2) into (1),

$$R_{out} = \frac{V_x}{i_x} = r_{o4} + (1 + g_{m2} r_{o4}) r_{o2}$$

$$R_{out} = r_{o4} + r_{o2} + g_{m2} r_{o2} r_{o4}$$



Date

No.

4b. $r_{o2} = r_{o4} = \frac{1}{\lambda I_D} = \frac{1}{(0.01)(200\mu)} = 0.5 \text{ M}\Omega$

$g_{m2} = \sqrt{2k_p I_D} = \sqrt{2(100\mu)(200\mu)} = 2 \times 10^{-4}$

$R_{out} = 51 \text{ M}\Omega$

4c. For M_2 to be in saturation,

$V_{GS2} < V_{TP}$

$|V_{DS2}| \geq |V_{GS2}| - |V_{TP}|$

At G_4 and G_2

$V_{G4} = 10 - V_{SG}$

$V_{G2} = 10 - 2V_{SG}$

V_{SG} can be obtained from this equation:

$I_D = \frac{K_p}{2} (V_{SG} - |V_{TP}|)^2$

$V_{SG} = 2.5 \text{ V}$

Then $V_{G2} = 5 \text{ V}$

$V_{SD2} \geq V_{SG2} - |V_{TP}|$

$-V_{D2} \geq -V_{G2} - |V_{TP}|$


$V_{D2} \leq 5.5 \text{ V}$

$V_{D2 \text{ max}} = 5.5 \text{ V}$

5a. $A_o = \frac{V_{o1}}{V_{in}} = - \frac{R_2 // \frac{1}{sC_2}}{R_1 + \frac{1}{sC_1}} = \frac{R_2}{1 + sR_2C_2} \cdot \frac{sC_1}{1 + sC_1R_1} = \frac{sR_2C_1}{(1 + sR_2C_2)(1 + sC_1R_1)}$; $s = j\omega$

5b. $\omega_1 = \frac{1}{R_2C_2} = 10^4$, $\omega_2 = \frac{1}{R_1C_1} = 100$ } $\omega_2 < \omega_1$, hence $\omega_L = \omega_2$, $\omega_H = \omega_1$

When $\omega = 1000 \text{ rad/sec}$, $\left| \frac{V_{o1}}{V_{in}} \right| = 9.9 = 19.9 \text{ dB}$

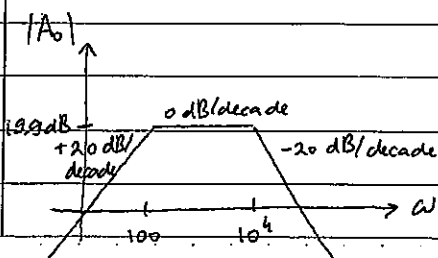

5c.

Since the second stage is the exact copy of the first stage,

$$\frac{V_{o2}}{V_{o1}} = \frac{V_{o1}}{V_{in}}$$

$$\frac{V_{o2}}{V_{in}} = \frac{V_{o2}}{V_{o1}} \cdot \frac{V_{o1}}{V_{in}} = \left(\frac{V_{o1}}{V_{in}} \right)^2$$

Previously, it is known that $\omega_H = \frac{1}{\sum \tau_{oc}} = \frac{1}{\tau_{oc}} = 10^4$ and $\omega_L = \sum \frac{1}{\tau_{sc}} = \frac{1}{\tau_{sc}} = 100$

Since τ_{oc} from stage 1 and stage 2 are the same (and so do τ_{sc}),

$$\omega_H' = \frac{1}{\tau_{oc} + \tau_{oc}} = \frac{1}{\frac{1}{10^4} + \frac{1}{10^4}} = \boxed{5000}$$

$$\omega_L' = \frac{1}{\tau_{sc}} + \frac{1}{\tau_{sc}} = 100 + 100 = \boxed{200}$$

All the best! :)