

NANYANG TECHNOLOGICAL UNIVERSITY**SEMESTER 2 EXAMINATION 2020-2021****EE2002 – ANALOG ELECTRONICS**

April / May 2021

Time Allowed: 2½ hours

INSTRUCTIONS

1. This paper contains 4 questions and comprises 10 pages.
 2. Answer all 4 questions.
 3. All questions carry equal marks.
 4. This is a closed book examination.
 5. Unless specifically stated, all symbols have their usual meanings.
 6. A list of formulae is provided in Appendix A on pages 7-10.
-


1. (a) A non-ideal Op-Amp configured with resistors is shown in Figure 1(a) on page 2. The Op-Amp is powered by $\pm V_{CC}$ power supplies. It has 2 AC input sources, v_1 and v_2 , and 3 non-ideal DC sources, I_+ , I_- and V_{IO} .

Derive the expression for the output voltage v_{OUT} , in terms of all or some of the followings: v_1 , v_2 , R_1 , R_2 , R_3 , R_4 , R_5 , R_6 , R_7 , R_8 , R_9 , R_{10} , R_{11} , I_+ , I_- and V_{IO} .

Note: Parallel resistance of R_x and R_y can be written as $R_x//R_y$ without expanding it.

(12 Marks)

Note: Question No. 1 continues on page 2.

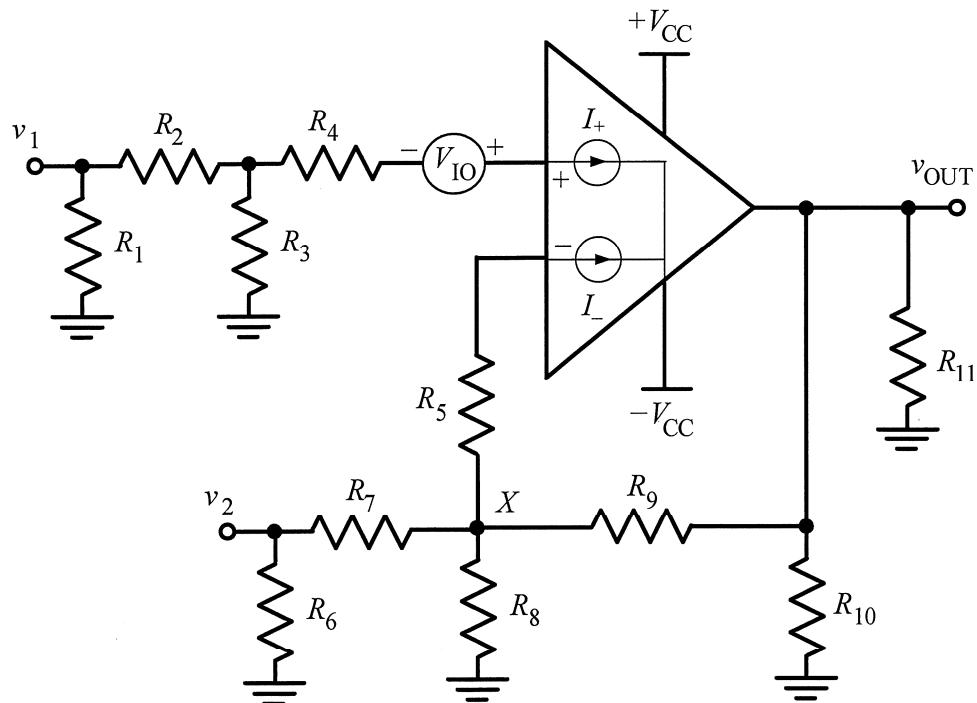**Figure 1(a)**

- (b) In Figure 1(b) on page 3, the empirical junction diode equation is:

$$V_D = nV_T \ln[I_D/I_S]$$

for the identical diodes D_1, D_2, D_3 and D_4 , given that 2 points on the diode $I-V$ characteristic curve are:

$V_{Dx} = 0.680 \text{ V}$ at $I_{Dx} = 600 \mu\text{A}$ and
 $V_{Dy} = 0.800 \text{ V}$ at $I_{Dy} = 6 \text{ mA}$.

- i) Find nV_T and I_S to 3 decimal places in V and nA, respectively.

Also given is $V_{SQ} = 10 \text{ V}_{pp}$ square wave source operating at a very low frequency and $R_L = 10 \text{ k}\Omega$.

- ii) Find the DC operating point or quiescent (Q) - point (I_D, V_D) for the diodes D_1, D_2, D_3 and D_4 (to 3 decimal places in mA and V, respectively).

Note: Question No. 1 continues on page 3.

iii) Hence find the voltage, V_{AB} and current in R_L .

Note: D_1, D_2, D_3 and D_4 have the same nV_T and I_S . Also note that the low frequency square wave can be treated as toggling of $\pm 5V$ DC with respect to ground.

(13 Marks)

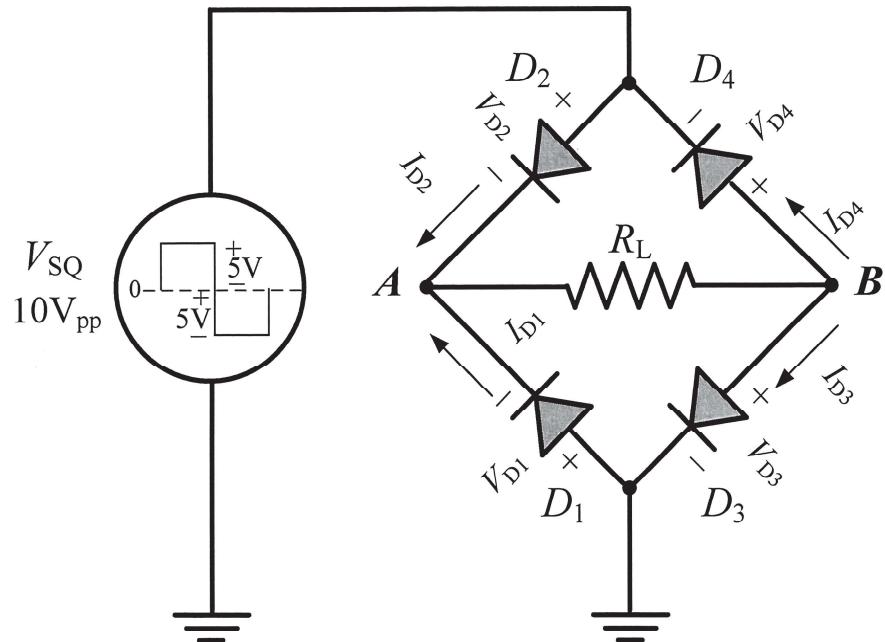
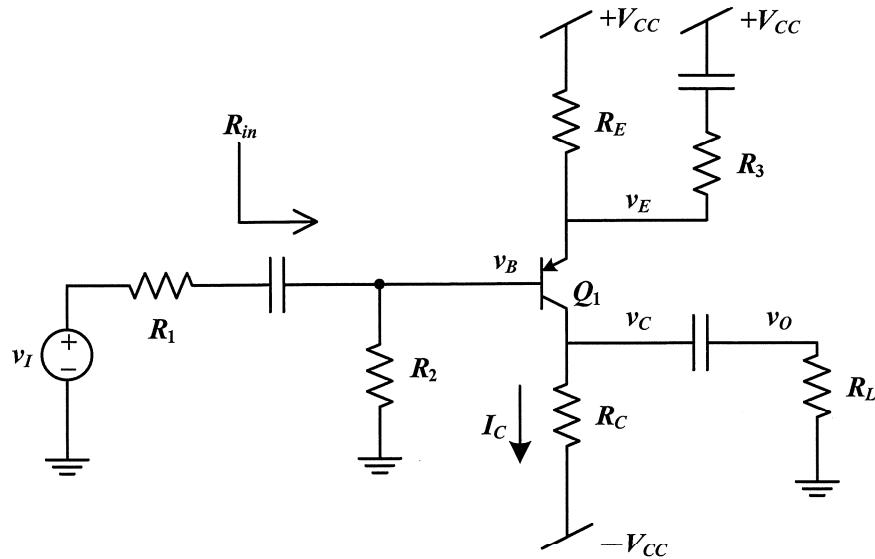


Figure 1(b)

2. A single-stage amplifier biased using dual supplies with $V_{CC} = 3V$ is shown in Figure 2 on page 4. Assume that the transistor Q_1 has $\beta = 100$ and $V_A = 60$ V. The resistor values are as follows: $R_1 = 1\text{ k}\Omega$, $R_2 = 30\text{ k}\Omega$, $R_E = 2\text{ k}\Omega$, $R_C = 3\text{ k}\Omega$, $R_3 = 270\text{ }\Omega$, $R_L = 30\text{ k}\Omega$. Assume that all capacitors have infinite capacitance value.

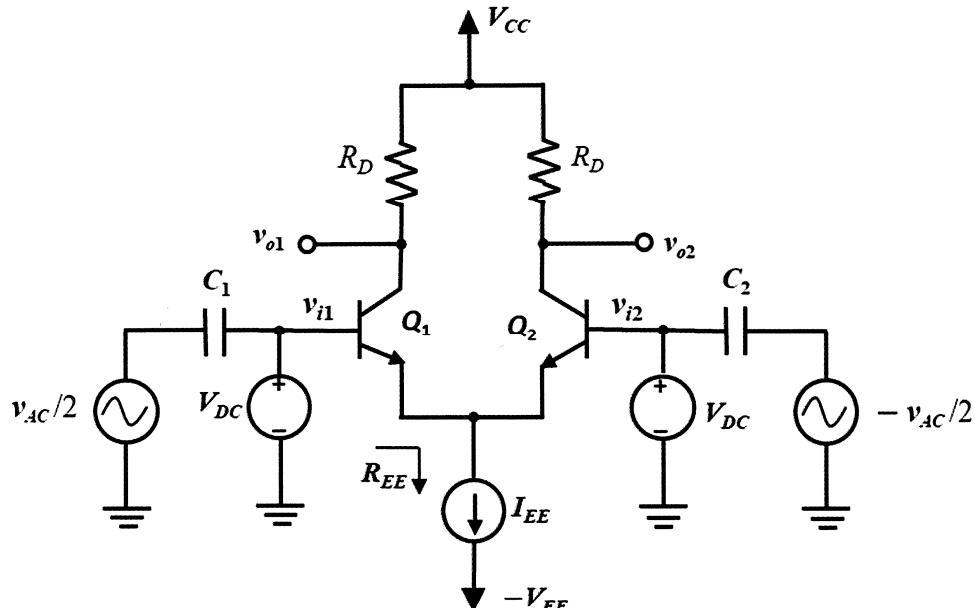
Note: Question No. 2 continues on page 4

**Figure 2**

- (a) Calculate the Q-point of the transistor, and verify its region of operation. (6 Marks)
- (b) Determine the input resistance R_{in} . (6 Marks)
- (c) Determine the voltage gain $A_v = v_O / v_I$. (7 Marks)
- (d) Determine the maximum amplitude v_I for small signal operation. (6 Marks)
3. For the differential circuit in Figure 3 on page 5, assume $V_{CC} = 12$ V, $V_{EE} = 12$ V, $V_{DC} = 1$ V, $I_{EE} = 500 \mu\text{A}$, $R_D = 30 \text{ k}\Omega$, $\beta = 100$, $V_A = \infty$. Here $v_{i1} = V_{DC} + v_{AC}/2$ and $v_{i2} = V_{DC} - v_{AC}/2$ represent the differential inputs (v_{AC} is the small AC signal inputs), and v_{o1} and v_{o2} represent the differential outputs. Assume all the capacitors have infinite values.
- (a) Determine the Q-points for the transistors and R_{EE} . (5 Marks)
- (b) Determine the differential-mode gains, common-mode gains for the cases of single-ended and differential outputs, respectively. (10 Marks)

Note: Question No. 3 continues on page 5.

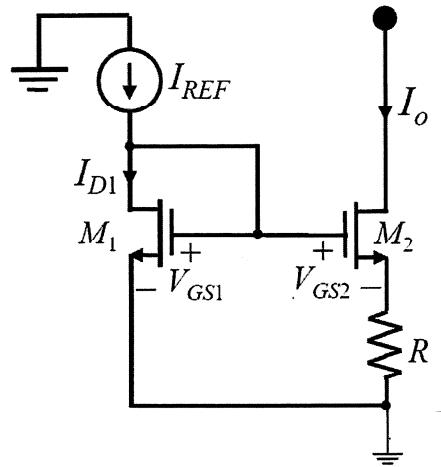
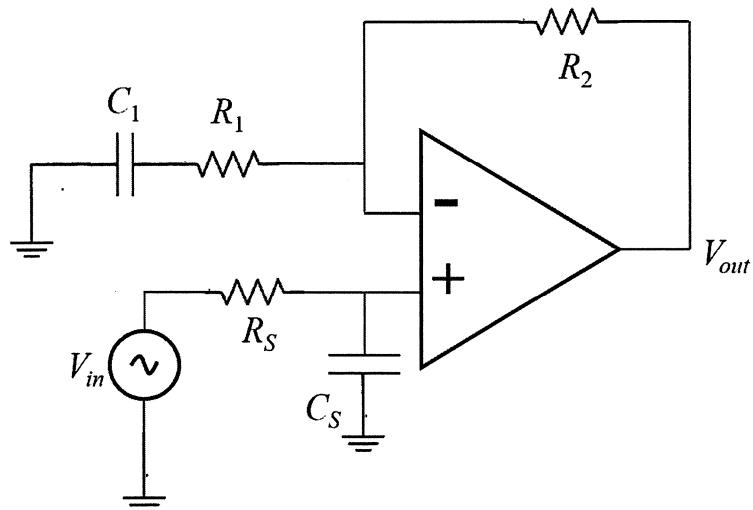
- (c) Determine the common-mode rejection ratios (CMRRs) for the cases of single-ended and differential outputs, respectively. In addition, discuss the effect of variation of R_{EE} to the CMRRs. (6 Marks)
- (d) Determine the input resistances and output resistances for the cases of single-ended and differential outputs. (4 Marks)

**Figure 3**

4. (a) Figure 4(a) on page 6 depicts a MOS Widlar current mirror comprising transistors M_1 , M_2 and resistor R . Given the transconductance parameter $K_n' = 100 \mu\text{A}/\text{V}^2$, $(W/L)_1 = 5$, $(W/L)_2 = 20$, $I_{REF} = 20 \mu\text{A}$ and $I_O = 10 \mu\text{A}$, find the value of the resistor R . You may ignore Early effect and assume both transistors to have the same threshold voltage V_{TN} . (10 Marks)
- (b) Figure 4(b) on page 6 depicts an Opamp based filter circuit. You may assume the Opamp to be ideal.
- (i) For both capacitors C_S and C_1 , determine if they contribute to lower cut-off (ω_L) or higher cut-off (ω_H) frequency. (3 Marks)

Note: Question No. 4 continues on page 6.

- (ii) Using OCTC methods, determine the higher cut-off (ω_H) frequency.
 (4 Marks)
- (iii) Using SCTC methods, determine the lower cut-off (ω_L) frequency.
 (4 Marks)
- (iv) Now derive the transfer function V_{out}/V_{in} for this circuit and match the poles/zeros with the cut-off frequencies derived in the earlier parts.
 (4 marks)

**Figure 4(a)****Figure 4(b)**

Appendix A**List of Formulae (with the usual notations)****Op-Amps:**

Closed-Loop Negative Feedback Inverting Gain, $A_{VCL} = \frac{v_o}{v_i} = -\frac{R_f}{R_i}$ Figure (a)

Closed-Loop Negative Feedback Non-Inverting Gain, $A_{VCL} = \frac{v_o}{v_i} = \left(1 + \frac{R_f}{R_i}\right)$ Figure (b)

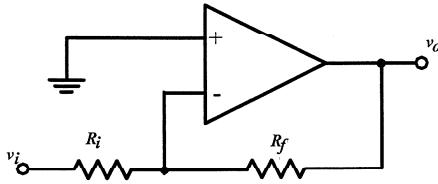


Figure (a)

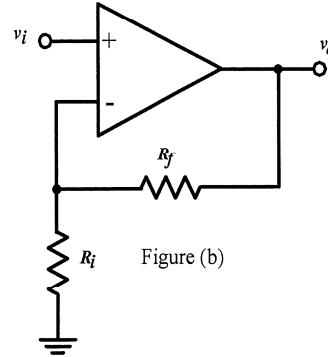


Figure (b)

$$\text{Op-Amp's Slew Rate, } SR \geq \left| \frac{dv_o}{dt} \right|_{\max} = A_{VCL} \omega a_m = A_{VCL} a_m 2\pi f,$$


where $v_i = a_m \sin(\omega t)$, $v_o = A_{VCL} v_i$, $v_o = A_{VCL} a_m \sin(\omega t)$ and $\left| \frac{dv_o}{dt} \right| = A_{VCL} \omega a_m \cos(\omega t)$

$$\text{Op-Amp's frequency response: } A_{VOL}(jf) = \frac{A_o}{\left(1 + \frac{jf}{f_p}\right)}$$

$$\text{Gain-Bandwidth Product: } A_o f_p = f_o = \frac{1}{\beta} (BW)_{CL}$$

$$\text{where } \frac{1}{\beta} = \frac{R_f + R_i}{R_i}$$

$$t_r = \frac{0.35}{(BW)_{CL}}$$

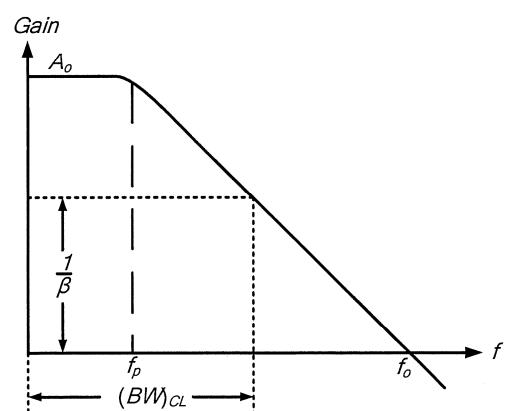

Appendix A (continued)**Diodes:**

$$v_D \approx nV_T \ln\left(\frac{i_D}{I_s}\right) \text{ or } i_D \approx I_s e^{\left(\frac{v_D}{nV_T}\right)}$$

where $e^x = 1 + x + \frac{x^2}{2!} + \frac{x^3}{3!} + \frac{x^4}{4!} + \dots$

$$\text{Diode conductance: } g_D = \frac{1}{r_D} = \frac{I_D}{nV_T}$$

BJT in Forward Active Region:

$$\text{Ignore early effect: } i_C = I_s \exp\left(\frac{|v_{BE}|}{V_T}\right)$$

$$\text{With early effect: } i_C = I_s \exp\left(\frac{|v_{BE}|}{V_T}\right) \left(1 + \frac{|v_{CE}|}{V_A}\right)$$

where I_s : Saturation current,

V_T : Thermal voltage, assume 25 mV at room temperature,

V_A : Early voltage.

For npn transistor, $|v_{BE}| = v_{BE}$ and $|v_{CE}| = v_{CE}$;

For pnp transistor, $|v_{BE}| = v_{EB}$ and $|v_{CE}| = v_{EC}$.

Small-signal model parameters of BJT:

$$g_m = \frac{I_C}{V_T}, \quad r_\pi = \frac{\beta}{g_m} \text{ and } r_o = \frac{V_A + |V_{CE}|}{I_C} \approx \frac{V_A}{I_C}$$

where I_C : DC collector current at Q-point

V_{CE} : DC collector-emitter voltage at Q-point

Criterion for small-signal operation of BJT: $|v_{be}| \leq 0.2V_T$

MOSFET in Saturation Region:

Criterion: $V_{DS} \geq V_{GS} - V_{TN}$ for NMOS;
 $|V_{DS}| \geq |V_{GS}| - |V_{TP}|$ for PMOS

where V_{TN} , V_{TP} : Threshold voltage,

V_{DS} : DC drain-source voltage,

V_{GS} : DC gate-source voltage.

Ignore channel-length modulation effect: $i_D = \frac{K_n}{2} (v_{GS} - V_{TN})^2$ for NMOS,
 $i_D = \frac{K_p}{2} (|v_{GS}| - |V_{TP}|)^2$ for PMOS.

Appendix A (continued)

With channel-length modulation effect:

$$i_D = \frac{K_n}{2} (v_{GS} - V_{TN})^2 (1 + \lambda v_{DS}) \text{ for NMOS,}$$

$$i_D = \frac{K_p}{2} (|v_{GS}| - |V_{TP}|)^2 (1 + \lambda |v_{DS}|) \text{ for PMOS.}$$

where λ : channel length modulation parameter,

For NMOS $K_n = K'_n \left(\frac{W}{L} \right)$ and $K'_n = \mu_n C_{ox}$; For PMOS $K_p = K'_p \left(\frac{W}{L} \right)$ and $K'_p = \mu_p C_{ox}$.

MOSFET in Triode Region:

Criterion: $V_{DS} < V_{GS} - V_{TN}$ for NMOS;
 $|V_{DS}| < |V_{GS}| - |V_{TP}|$ for PMOS

Ignore channel-length modulation effect:

$$i_D = K_n \left(v_{GS} - V_{TN} - \frac{v_{DS}}{2} \right) v_{DS} \text{ for NMOS,}$$

$$i_D = K_p \left(|v_{GS}| - |V_{TP}| - \frac{|v_{DS}|}{2} \right) |v_{DS}| \text{ for PMOS.}$$

With channel-length modulation effect:

$$i_D = K_n \left(v_{GS} - V_{TN} - \frac{v_{DS}}{2} \right) v_{DS} (1 + \lambda v_{DS}) \text{ for NMOS,}$$

$$i_D = K_p \left(|v_{GS}| - |V_{TP}| - \frac{|v_{DS}|}{2} \right) |v_{DS}| (1 + \lambda |v_{DS}|) \text{ for PMOS.}$$
Small-signal model parameters of MOSFET

For NMOS: $g_m = \sqrt{2K_n I_D (1 + \lambda V_{DS})} \approx \sqrt{2K_n I_D}$ and $r_o = \frac{\frac{1}{\lambda} + V_{DS}}{I_D} \approx \frac{1}{\lambda I_D}$

For PMOS: $g_m = \sqrt{2K_p I_D (1 + \lambda |V_{DS}|)} \approx \sqrt{2K_p I_D}$ and $r_o = \frac{\frac{1}{\lambda} + |V_{DS}|}{I_D} \approx \frac{1}{\lambda I_D}$

where I_D : DC drain current at Q-point


V_{DS} : DC drain-source voltage at Q-point

Criterion for small-signal operation:

For NMOS: $|v_{gs}| \leq 0.2(V_{GS} - V_{TN})$

For PMOS: $|v_{gs}| \leq 0.2(|V_{GS}| - |V_{TP}|)$

where V_{GS} : DC gate-source voltage at Q-point.

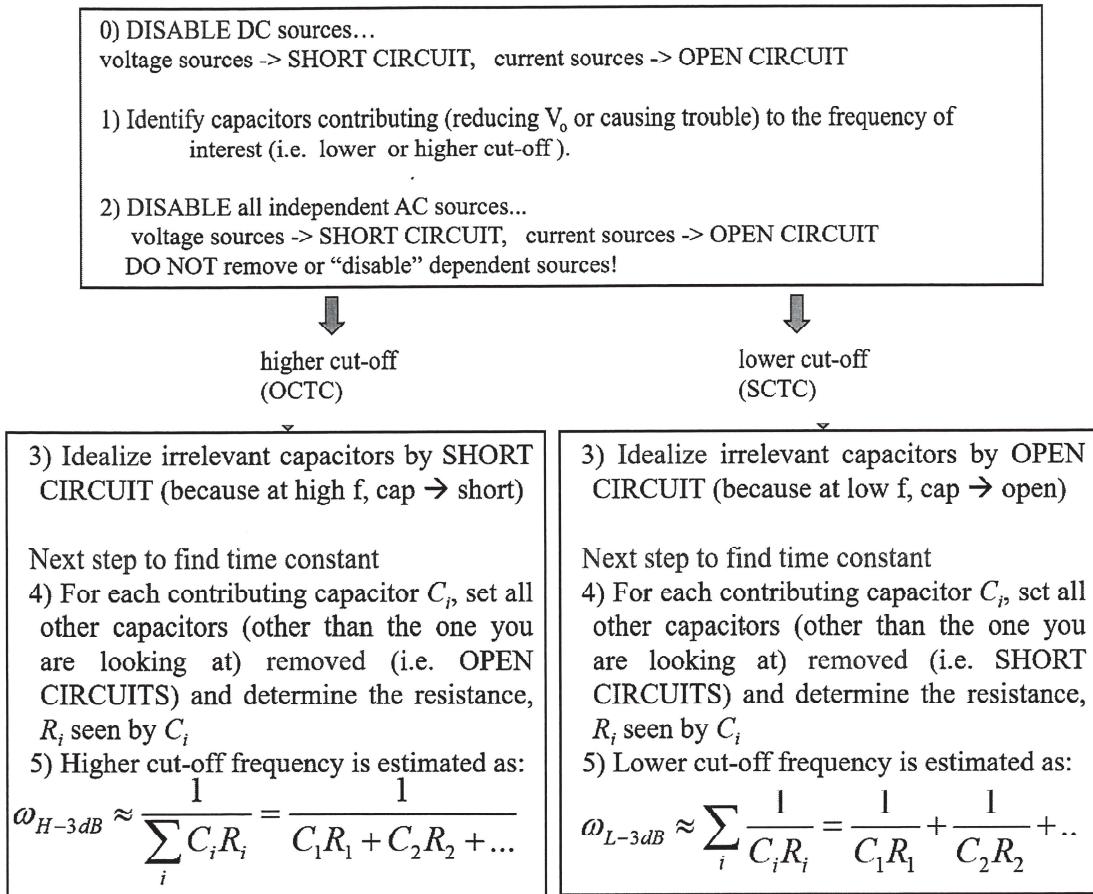Appendix A (continued)Frequency Response: OCTC and SCTC

END OF PAPER

1. (a).

$$V_{V_1} = V_1 \times \frac{R_3}{R_2 + R_3} \times \left(\frac{R_7 // R_8 + R_9}{R_7 // R_8} \right)$$

$$V_{V_{IO}} = V_{FO} \times \left(\frac{R_7 // R_8 + R_9}{R_7 // R_8} \right)$$

$$V_{I_f} = -I_f \times [R_2 // R_3 + R_4] \times \left(\frac{R_7 // R_8 + R_9}{R_7 // R_8} \right)$$

$$V_{V_2} = -V_2 \times \frac{R_9}{R_7}$$

$$V_{I_-} = I_- \times R_5 \times \frac{R_5 // R_7 // R_8 + R_9}{R_5 // R_7 // R_8}$$

$$V_{out} = V_{V_1} + V_{V_{IO}} + V_{I_f} + V_{V_2} + V_{I_-} \quad \cancel{\text{X}}$$

$$1. (b). (i) 0.68 = nV_T \ln \left(\frac{6 \times 10^{-4}}{I_S} \right) \dots (1)$$

$$0.8 = nV_T \ln \left(\frac{6 \times 10^{-3}}{I_S} \right) \dots (2)$$

$$0.8 - 0.68 = nV_T \ln \left(\frac{6 \times 10^{-3}}{6 \times 10^{-4}} \right)$$

$$0.12 = nV_T \ln (10)$$

$$nV_T = 0.052 \text{ V} \quad \cancel{\text{X}}$$

$$I_S = 1.256 \text{ nA} \quad \cancel{\text{X}}$$

(ii) When $V_{SD} = 5 \text{ V}$

$$5 = V_{D2} + R_L \cdot I_D + V_{D3}$$

$$5 = 2V_D + 10k \cdot I_D \dots (1)$$

$$V_D = 0.052 \ln \left(\frac{I_D}{1.256 \times 10^{-9}} \right) \dots (2)$$

use eq (2) Take $V_D = 0.7 \text{ for iteration}$

$V_D (\text{V})$	0.7	0.653	0.655	0.655
$I_D (\text{mA})$	0.36	0.369	0.369	

use eq (1)

$$V_D = 0.655 \text{ V}$$

$$I_D = 0.369 \text{ mA} \quad \cancel{\text{X}}$$

(iii) $I_{R_L} = I_D = 0.369 \text{ mA}$

$$V_{AB} = R_L \times I_{R_L} = 3.69 \text{ V} \quad \cancel{\text{X}}$$

2. Assume forward active

(a) $30k \text{ } I_B + V_{BE} + 2k \text{ } I_E = 3$

$$30k \text{ } I_B + 0.7 + 2k (101) \text{ } I_B = 3$$

$$232k \text{ } I_B = 2.3$$

$$I_B = 9.9 \text{ mA}$$

$$I_C = 100 \cdot I_B = 0.99 \text{ mA} \times \cancel{\text{X}} = 0.297$$

$$V_C = -3 + 0.99 \times 3 = -0.03$$

$$V_E = 3 - 2 \times 0.9999 = 1.0002$$

$$V_B = 30 \times 9.9 \times 10^{-3} = 0.297$$

$$30k \text{ } I_B = V_{CB} + 3k \text{ } I_C + (-3)$$

$$V_{CB} = 0.327$$

$$V_{CE} = V_{CB} + V_{BE}$$

$$= 0.327 + 0.7$$


$$= 1.027 \text{ V}$$

$$\approx 1.03 \text{ V} \cancel{\text{X}}$$

$$V_E > V_B > V_C$$

Forward Active ~~X~~

(b)

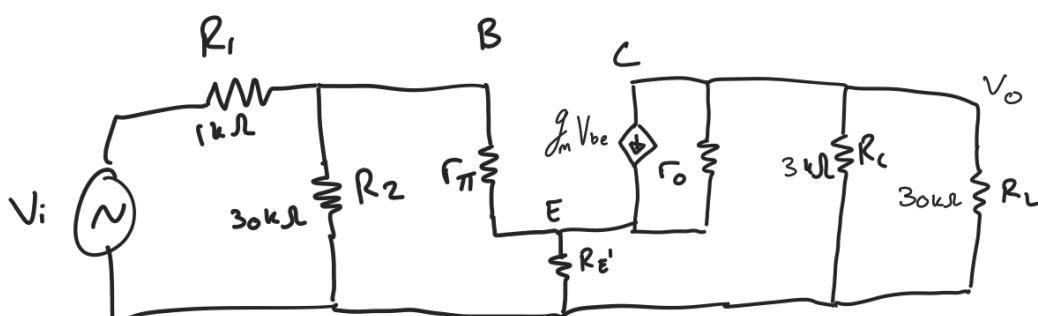

$$g_m = \frac{I_c}{V_T} = \frac{0.99}{25} = 39.6 \text{ mS}$$

$$r_\pi = \frac{\beta}{g_m} = 2525 \cdot 25 \Omega$$

$$r_o = \frac{V_A}{I_c} = \frac{60}{9.9 \times 10^{-4}} = 60606 \Omega$$

$$R_E' = R_E // R_3 = 237.88 \Omega$$

$$R_{in} = R_2 // [r_\pi + (\beta + 1)R_E']$$

$$= 14.085 \text{ k}\Omega$$

(c) $V_o = V_C = -i_C \cdot (R_C // R_L)$
 $= 100 i_b (2.727)$
 $= -272.7 \text{ V}$

$$V_B = r_\pi i_b + R_E' i_E$$

$$= i_b (r_\pi + 101 R_E')$$

$$= 26551.13 \text{ V}$$

$$V_i = \frac{R_{in}}{R_{in} + R_1} \times V_B = 24.7 \text{ V}$$

$$A_V = \frac{V_o}{V_i} = \frac{-272.7 \text{ V}}{24.7 \text{ V}} = -11 \cancel{\text{X}}$$

$$(d) V_{be} = r_\pi \cdot i_b$$

$$V_{be} = 2.525 \mu A \cdot i_b$$

$$V_i = 25.666 \mu A \cdot i_b$$

$$V_i = \frac{25.666 \mu A}{2.525 \mu A} V_{be}$$

$$V_i = 10.165 V_{be}$$

$$V_i \leq 50.825 mV \times$$

$$V_{be} \leq 0.2 V_T$$

$$V_{be} \leq 5 mV$$

3(a).

$$V_B = 1 V$$

$$V_E = 0.3 V \rightarrow \text{Assume forward active}$$

$$I_{EE/2} = \frac{0.3 - (-12)}{R_{EE}}$$

$$2R_{EE} = \frac{12.3 V}{250 \text{ mA}}$$

$$R_{EE} = 24.6 k\Omega \times$$

$$\frac{12 - V_C}{30 k\Omega} = \frac{I_{EE}}{2} \times \frac{\beta}{\beta + 1}$$

$$12 - V_C = 7.43$$

$$V_C = 4.57$$

$$V_{CE} = 4.27 V \times$$

$$I_C = \frac{I_{EE}}{2} \times \frac{\beta}{\beta + 1} = 247.5 \text{ mA} \times$$


$$(b). g_m = \frac{I_C}{V_T} = 9.9 \text{ mS}$$

$$r_\pi = \frac{\beta}{g_m} = 10.1 \mu \Omega$$

$$r_o = \frac{V_A}{I_C} = \infty \rightarrow \text{Open}$$

diff-mode

Common mode

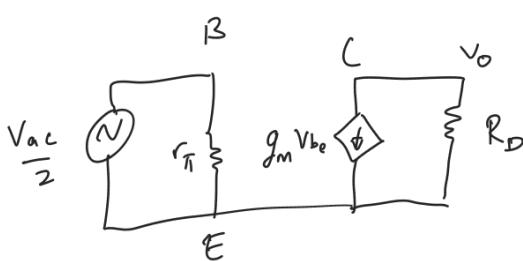


$$V_c = -g_m V_{be} \cdot R_D = -g_m \frac{V_{ac}}{2} \cdot R_D$$

$$A_{dm-se_1} = \frac{-g_m \frac{V_{ac}}{2} \cdot R_D}{V_{ac}} = 148.5 \times$$

$$A_{dm-se_2} = \frac{g_m \frac{V_{ac}}{2} \cdot R_D}{V_{ac}} = -148.5 \times$$
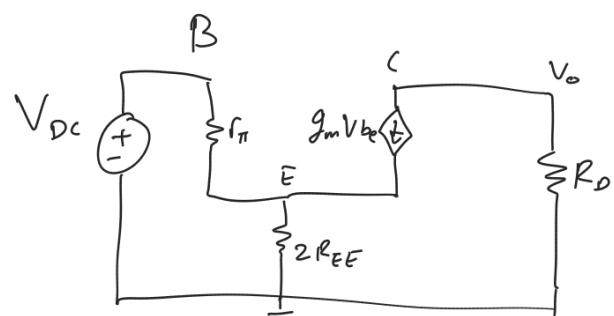
$$A_{dm-diff} = A_{dm-se_1} - A_{dm-se_2} = -297 \times$$



$$V_{be} = r_\pi \cdot i_b = 10.1 \mu A \cdot i_b$$

$$V_{DC} = r_\pi \cdot i_b + 2R_{EE} \cdot 10.1 \mu A = 4.975 \text{ mV} \cdot i_b$$

$$V_{DC} = 493 \text{ mV}$$

$$V_O = g_m V_{be} \cdot R_D = -99.99 \text{ V} \cdot R_D$$

$$A_{cm-se_1} = \frac{V_O}{V_{DC}} = \frac{-99.99 V_{be}}{493 \text{ mV}} = -0.2028 \times$$

$$A_{cm-se_2} = A_{cm-se_1} = -0.2028 \times$$

$$A_{cm-diff} = 0 \times$$

$$(c). \text{ CMRR}_{\text{se}} = \frac{A_{\text{dm-se}_1}}{A_{\text{cm-se}_1}} = 732.25$$

$$\text{CMRR diff} = \frac{A_{\text{dm-diff}}}{A_{\text{cm-diff}}} = \infty$$

$$A_{\text{cm-se}_1} = \frac{V_o}{V_{DC}} = \frac{-g_m V_{be} R_D}{r_T \times i_b + 2R_E \times 10i_b}$$

\hookrightarrow Increase in R_E will reduce $A_{\text{cm-se}_1}$, and increase CMRR_{se} .


$$(d) R_{\text{in-cmse}} = \frac{V_{DC}}{i_b} = r_T + (\beta+1) 2 \cdot R_E = 4.979 \text{ M}\Omega \cancel{\text{X}}$$

$$R_{\text{in-cm diff}} = R_{\text{in-cmse}_1} // R_{\text{in-cmse}_2} = 2.4895 \text{ M}\Omega \cancel{\text{X}}$$

$$R_{\text{out-dm se}} = R_D // r_o = R_D = 30 \text{ k}\Omega \cancel{\text{X}}$$

$$R_{\text{out-dm diff}} = 2 R_{\text{out-dm se}} = 60 \text{ k}\Omega \cancel{\text{X}}$$

4(a)

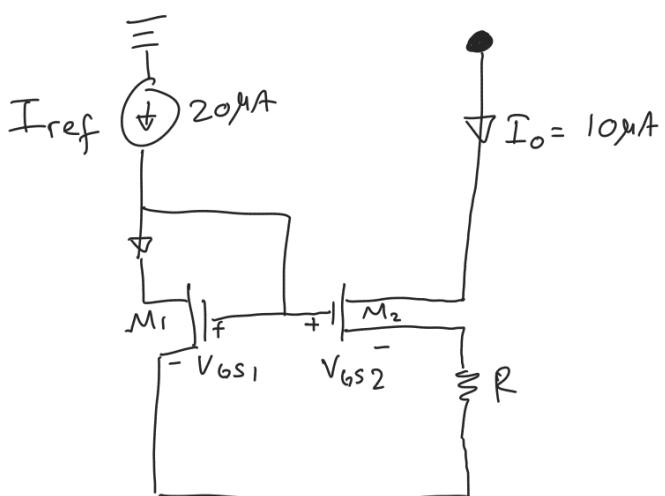

$$I_{\text{ref}} = \frac{V_n}{2} \left(\frac{w}{l} \right)_1 (V_{GS_1} - V_{TN})^2$$

$$20 \text{ mA} = 50 \text{ mA} \cdot 5 (V_{GS_1} - V_{TN})^2 \\ 0.08 = (V_{GS_1} - V_{TN})^2 \dots \textcircled{1}$$

$$I_o = \frac{V_n}{2} \left(\frac{w}{l} \right)_2 (V_{GS_2} - V_{TN})^2$$

$$10 \text{ mA} = 50 \text{ mA} \cdot 20 (V_{GS_2} - V_{TN})^2 \\ 0.01 = (V_{GS_2} - V_{TN})^2 \dots \textcircled{2}$$

$$V_{GS_1} = V_{GS_2} + I_o R \\ 0.2 \sqrt{2} + V_{TN} = 0.1 + V_{TN} + I_o \cdot R$$

$$I_o R = 0.183$$

$$R = 18.3 \text{ k}\Omega \cancel{\text{X}}$$

(b).


- (i) Short $C_s \rightarrow V_f = 0$ } Troublemaker for high freq.
 Open $C_s \rightarrow V_f = V_{in}$

$$\text{Short } C_1 \rightarrow V_{out} = \left(1 + \frac{R_2}{R_1} \right) V_f \quad \text{Troublemaker for low freq.}$$

$$\text{Open } C_1 \rightarrow V_{out} = V_f$$

$$(ii) \omega_{H-3dB} = \frac{1}{C_s R_s}$$
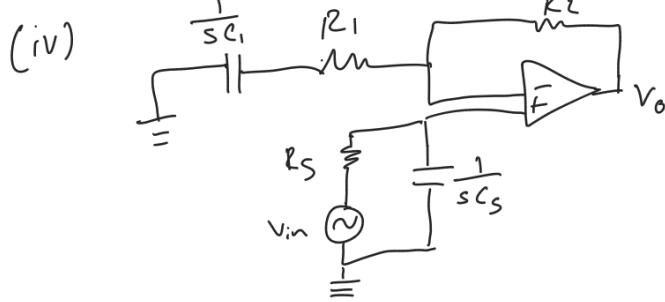
$$(iii) \omega_{S-3dB} = \frac{1}{C_1 R_1}$$



$$V_o = \frac{V_{in}}{R_s + \frac{1}{sC_s}} \times \frac{1}{sC_s} \times \frac{R_1 + \frac{1}{sC_1} + R_2}{R_1 + \frac{1}{sC_1}}$$

$$\frac{V_o}{V_{in}} = \frac{1}{1 + sR_s C_s} \times \frac{1 + sC_1 R_1 + sC_1 R_2}{1 + sC_1 R_1}$$

Zero: $\left(\frac{1}{C_1 R_1 + C_1 R_2} \right)$

Poles: $\left(\frac{1}{C_1 R_1} \right), \left(\frac{1}{C_s R_s} \right)$

Low freq. \downarrow
Cut-off

High freq.
Cut-off

