



# INTEGRATED ELECTRONICS

**Y. P. Zhang, PhD, FIEEE**

**Office: S2-B2c-90**

**[eypzhang@ntu.edu.sg](mailto:eypzhang@ntu.edu.sg)**


**Tel: 6790-4945**

**Joseph Chang**

**Office: S1-B1b-60**


**[ejschang@ntu.edu.sg](mailto:ejschang@ntu.edu.sg)**

**Tel: 6790-4424**

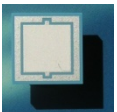


# Topics

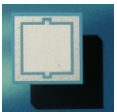- 1. Power Supplies**
- 2. Bias Circuits**
- 3. Operational Amplifiers**
- 4. Applications of Operational Amplifiers**




# Reference Textbooks

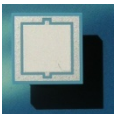1. Sedra and Smith, *Microelectronic Circuits*, 5th Edition, Oxford University Press, 2004.
2. Gray, Hurst, Lewis and Meyer, *Analysis and Design of Analogue Integrated Circuits*, 4th Edition, John Wiley & Sons, 2001.
3. Franco S, *Design with Operational Amplifiers and Analog Integrated Circuits*, 3rd Edition, McGraw-Hill, 2002.



# Bias Circuits

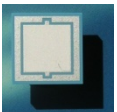1. Introduction
2. Current Mirrors
3. Bias circuits based on  $V_{BE}$  or  $V_{GS}$  of a transistor,  
Thermal voltage  $V_T$ , Breakdown voltage of a reverse-biased pn junction
4. Voltage Level Shifters



# Introduction


**Bias Circuits should provide a *constant* bias current and/or voltage so that the circuit parameters do not change over varying supply voltages, temperature and other variations.**

**The Figure-of-Merit to qualify how well a desired parameter remains unchanged to the variation of a given parameter is Sensitivity.**

**The Sensitivity of a desired parameter (e.g. output current) to the variation of a given parameter (e.g. supply voltage) is:**

$$S_{V_{cc}}^{I_o} = \frac{\Delta I_o / I_o}{\Delta V_{cc} / V_{cc}} = \frac{V_{cc}}{I_o} \frac{\partial I_o}{\partial V_{cc}}$$

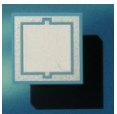**In general, the sensitivity of currents or voltages in a bias circuit to the variation of other parameters should be kept small.**



# Introduction



**Example 1: Determine the sensitivity of  $V_{REF}$  to  $V_{CC}$  for the circuit shown in right. Assume  $V_{CC} \gg V_{REF}$ ,  $V_{CC} = 5V$ ,  $R = 43k\Omega$  and  $I_S = 0.4fA$ .**

**Solution: Since  $I_C = I_S \exp(V_{BE} / V_T)$ ,**

$$V_{REF} = V_{BE} = V_T \ln(I_C / I_S) = V_T \ln\left(\frac{V_{CC} - V_{REF}}{RI_S}\right) \approx V_T \ln\left(\frac{V_{CC}}{RI_S}\right).$$

**Hence** 
$$S_{V_{CC}}^{V_{REF}} = \frac{V_{CC}}{V_{REF}} \frac{\partial V_{REF}}{\partial V_{CC}} \cong \frac{1}{\ln(V_{CC} / RI_S)} \cong 0.0379.$$

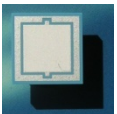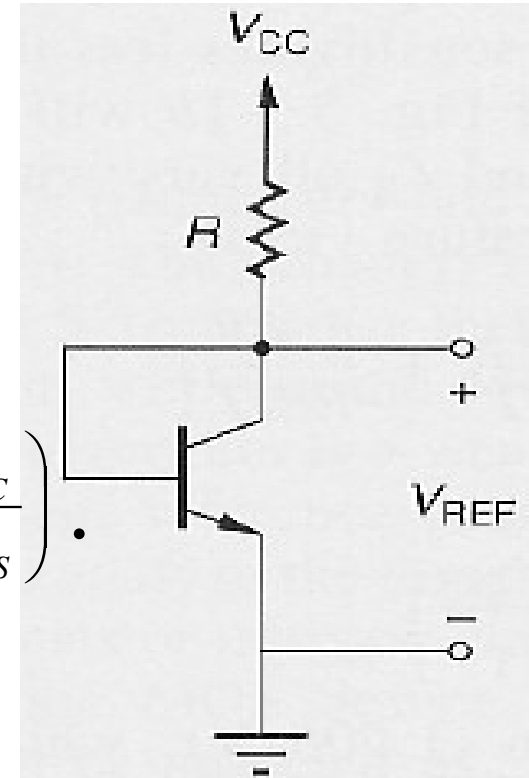**If  $V_{CC}$  changes by 10%,  $V_{REF}$  will change by 0.379%, which is large for a voltage bias circuit.**




# Introduction

**The Fractional Temperature Coefficient of a desired parameter (e.g. output current) is the fractional variation of the desired parameter to the variation of temperature. Denoted as  $TC_F$ , it is defined as:**

$$TC_F = \frac{1}{I_o} \frac{\partial I_o}{\partial T}$$

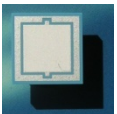**Here the  $TC_F$  of an output current is used, other parameters can similarly be qualified.**



# Introduction



**Example 2:** Determine the  $TC_F(V_{REF})$  for  $V_{CC}$  for the circuit shown. Assume  $V_{CC} \gg V_{BE}$ ,  $I_S = KT^3 \exp(-V_{GO}/V_T)$  where  $V_{GO} = 1.205V$  is the bandgap of silicon and is independent of temperature,  $TC_F(R) = 1500 \text{ ppm}/^\circ\text{C}$ ,  $V_{REF} = 0.7V$ , and  $T = 300^\circ\text{K}$ .

**Solution:**

$$V_{REF} \approx V_T \ln \left( \frac{V_{CC}}{RI_S} \right)$$

where

$$V_T = \frac{kT}{q}$$

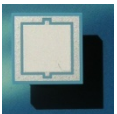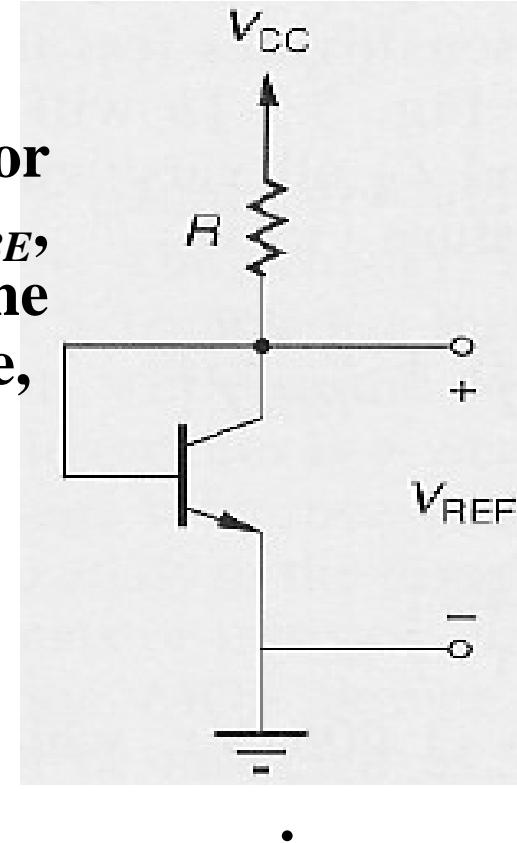





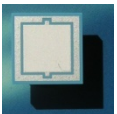
# Introduction


$$\begin{aligned}\frac{\partial V_{REF}}{\partial T} &= \frac{\partial V_T}{\partial T} \ln \frac{V_{CC}}{RI_s} + V_T \frac{\partial}{\partial T} \left( \ln \frac{V_{CC}}{RI_s} \right) = \frac{k}{q} \ln \frac{V_{CC}}{RI_s} + V_T \frac{\partial}{\partial T} \left( \ln \frac{V_{CC}}{RI_s} \right) \\ &= \frac{kT}{qT} \ln \frac{V_{CC}}{RI_s} + V_T \frac{\partial}{\partial T} \left( \ln \frac{V_{CC}}{RI_s} \right) = \frac{V_{REF}}{T} + V_T \frac{\partial}{\partial T} \left( \ln \frac{V_{CC}}{RI_s} \right) \\ &= \frac{V_{REF}}{T} + V_T \frac{RI_s}{V_{CC}} \frac{\partial}{\partial T} \left( \frac{V_{CC}}{RI_s} \right) = \frac{V_{REF}}{T} + V_T \frac{RI_s}{V_{CC}} \left[ \frac{RI_s \cdot 0 - V_{CC} \cdot \frac{\partial}{\partial T} (RI_s)}{(RI_s)^2} \right] \\ &= \frac{V_{REF}}{T} - \frac{V_T}{RI_s} \frac{\partial}{\partial T} (RI_s) = \frac{V_{REF}}{T} - \frac{V_T}{RI_s} \left[ I_s \frac{\partial R}{\partial T} + R \frac{\partial I_s}{\partial T} \right] \\ &= \frac{V_{REF}}{T} - V_T \left( \frac{1}{R} \frac{\partial R}{\partial T} + \frac{1}{I_s} \frac{\partial I_s}{\partial T} \right).\end{aligned}$$


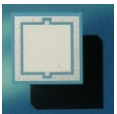
# Introduction

Since  $I_s = kT^3 \exp(-V_{GO}/V_T)$ , we can get

$$\begin{aligned}\frac{\partial I_s}{\partial T} &= 3kT^2 \exp(-\frac{V_{GO}}{V_T}) + kT^3 \frac{\partial}{\partial T} [\exp(-\frac{V_{GO}}{V_T})] \\ &= \frac{3I_s}{T} + kT^3 \exp(-\frac{V_{GO}}{V_T}) \frac{\partial}{\partial T} (-\frac{V_{GO}}{V_T}) = \frac{3I_s}{T} - I_s \frac{\partial}{\partial T} (\frac{V_{GO}}{V_T}) \\ &= \frac{3I_s}{T} - I_s (\frac{V_T \cdot 0 - V_{GO} \frac{\partial V_T}{\partial T}}{V_T^2}) = \frac{3I_s}{T} + I_s (\frac{V_{GO} \frac{k}{q}}{V_T^2}) = \frac{3I_s}{T} + \frac{I_s}{T} \frac{V_{GO}}{V_T} \cdot\end{aligned}$$





# Introduction

$$\begin{aligned}\frac{\partial V_{REF}}{\partial T} &= \frac{V_{REF}}{T} - V_T \left( \frac{1}{I_S} \frac{\partial I_S}{\partial T} + \frac{1}{R} \frac{\partial R}{\partial T} \right) = \frac{V_{REF}}{T} - V_T \left( \frac{1}{I_S} \left( \frac{3I_S}{T} + \frac{I_S}{T} \frac{V_{GO}}{V_T} \right) + \frac{1}{R} \frac{\partial R}{\partial T} \right) \\ &= \frac{V_{REF}}{T} - V_T \left( \frac{3}{T} + \frac{V_{GO}}{TV_T} + \frac{1}{R} \frac{\partial R}{\partial T} \right) = \frac{V_{REF}}{T} - \left( \frac{3V_T}{T} + \frac{V_{GO}}{T} + \frac{V_T}{R} \frac{\partial R}{\partial T} \right) .\end{aligned}$$

$$\begin{aligned}TC_F(V_{REF}) &= \frac{1}{V_{REF}} \frac{\partial V_{REF}}{\partial T} \\ &= \frac{V_{REF} - 3V_T - V_{GO}}{V_{REF}T} - \frac{V_T}{V_{REF}} \frac{1}{R} \frac{\partial R}{\partial T} \\ &= \frac{700 - 78 - 1205}{700 \cdot 300} - \frac{26}{700} 1500 \approx -2832 \text{ ppm}/^\circ\text{C} .\end{aligned}$$

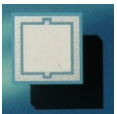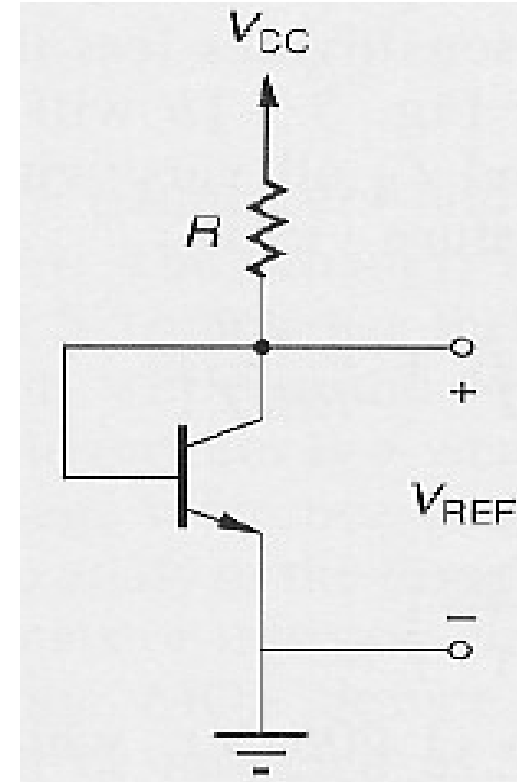**This voltage bias circuit has a large temperature coefficient.**




# Current Mirrors

**For BJT in active mode,**


$$I_{C1} = I_{S1} \exp\left(\frac{V_{BE1}}{V_T}\right) \Rightarrow V_{BE1} = V_T \ln\left(\frac{I_{C1}}{I_{S1}}\right) .$$

**Since  $V_{BE1}=V_{BE2}$ , So**  $\frac{I_{C1}}{I_{C2}} = \frac{I_{S1}}{I_{S2}} .$

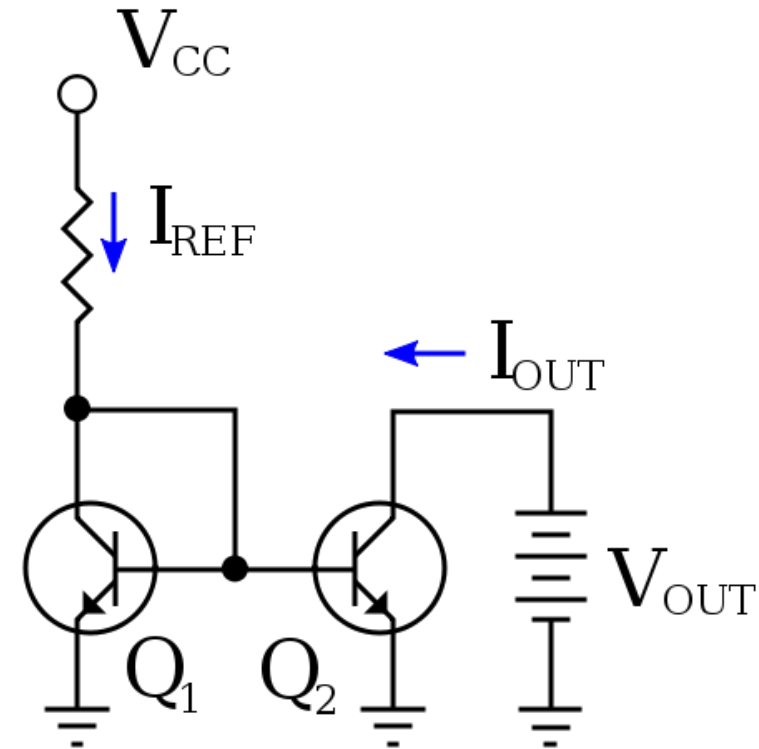**As  $I_S \propto$  emitter area, the ratio of the emitter areas to a first order determines the current ratio of the collectors.**



**Basic BJT current mirror**

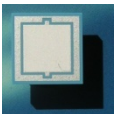

# Current Mirrors


For CMOS in saturation mode,

$$I_D = \frac{\mu C_{ox}}{2} \frac{W}{L} (V_{GS} - V_t)^2 .$$


Since  $V_{GS1} = V_{GS2}$ ,

$$\frac{I_{D1}}{I_{D2}} = \frac{(W/L)_1}{(W/L)_2} .$$

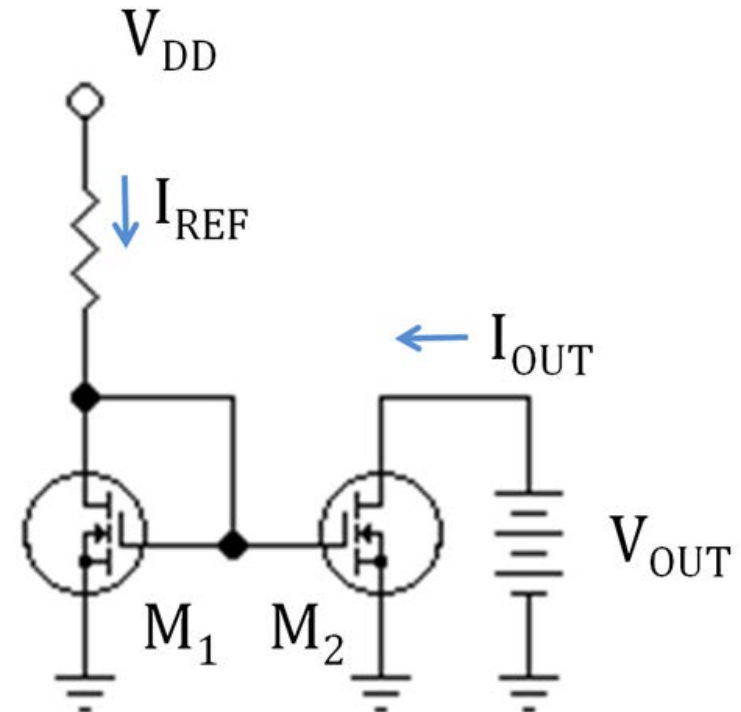The ratio of the (W/L) or aspect ratio of the CMOS transistors to a first order determines the drain current ratio.




Basic MOS current mirror

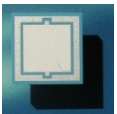


# Current Mirrors

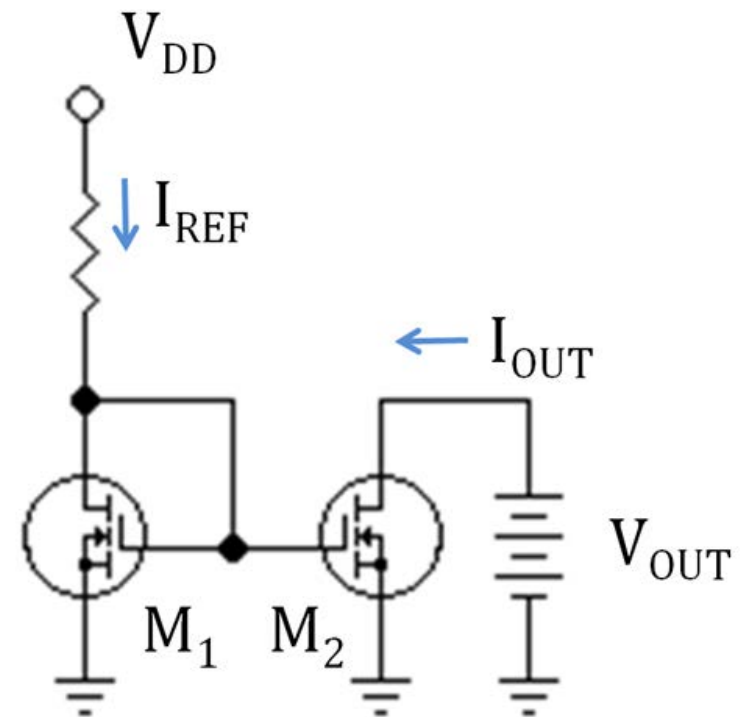**Example 3:** Given two MOSFETs of channel lengths of  $10\ \mu\text{m}$ , channel widths of  $100\ \mu\text{m}$ , threshold voltage of  $1\ \text{V}$ , early voltage of  $100\ \text{V}$  and  $\mu_n C_{\text{ox}} = 20\text{mA/V}^2$ , it is required to design the circuit for a basic MOSFET constant current source to obtain an output of  $100\ \mu\text{A}$  with a power supply  $V_{\text{DD}} = 5\ \text{V}$ . What is the lowest possible value of output voltage? Find the change in output current resulting from a 3-V change in output voltage.



Basic MOS current mirror

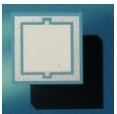

# Current Mirrors


**Solution:** 
$$I_D = \frac{\mu C_{ox}}{2} \frac{W}{L} (V_{GS} - V_t)^2 \left(1 + \frac{V_{DS}}{V_A}\right) .$$

$$100 \times 10^{-6} = \frac{20 \times 10^{-3}}{2} \frac{100}{10} (V_{GS} - 1)^2 \left(1 + \frac{V_{GS}}{100}\right)$$


$$\approx \frac{20 \times 10^{-3}}{2} \frac{100}{10} (V_{GS} - 1)^2 .$$

$$V_{GS} \approx 1.03 \text{ V} .$$
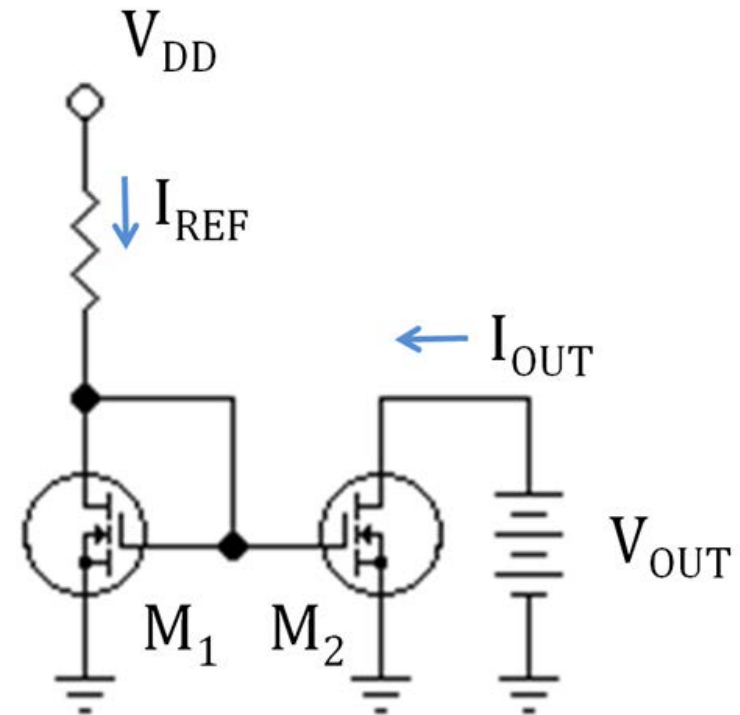
$$R = \frac{V_{DD} - V_{GS}}{I_o} \approx \frac{5 - 1.03}{0.0001} = 39.7 \text{ k}\Omega .$$



**Basic MOS current mirror**

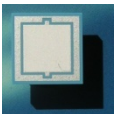


# Current Mirrors

**Solution:**  $V_o = V_{DS2} \geq V_{GS2} - V_t$  .


$$V_{o\min} = V_{DS2} = V_{GS2} - V_t = V_{GS1} - V_t \approx 1.03 - 1 = 0.03 \text{ V} .$$

$$r_o = \frac{V_A}{I_o} = \frac{100}{0.0001} = 1 \text{ M}\Omega \text{ .}$$
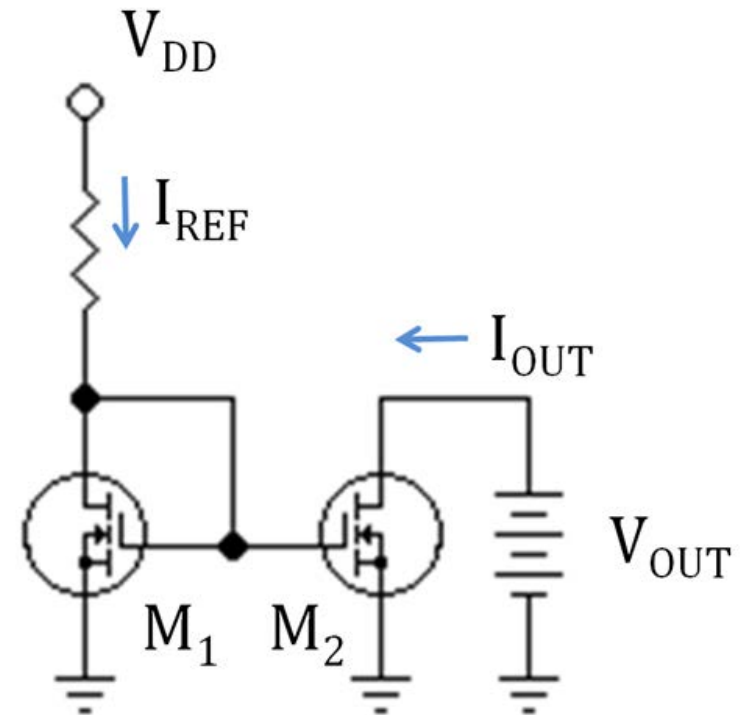
$$\Delta I_o = \frac{\Delta V_o}{r_o} = 3 \text{ }\mu\text{A} \text{ .}$$



Basic MOS current mirror


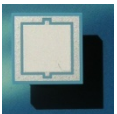



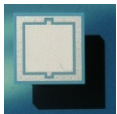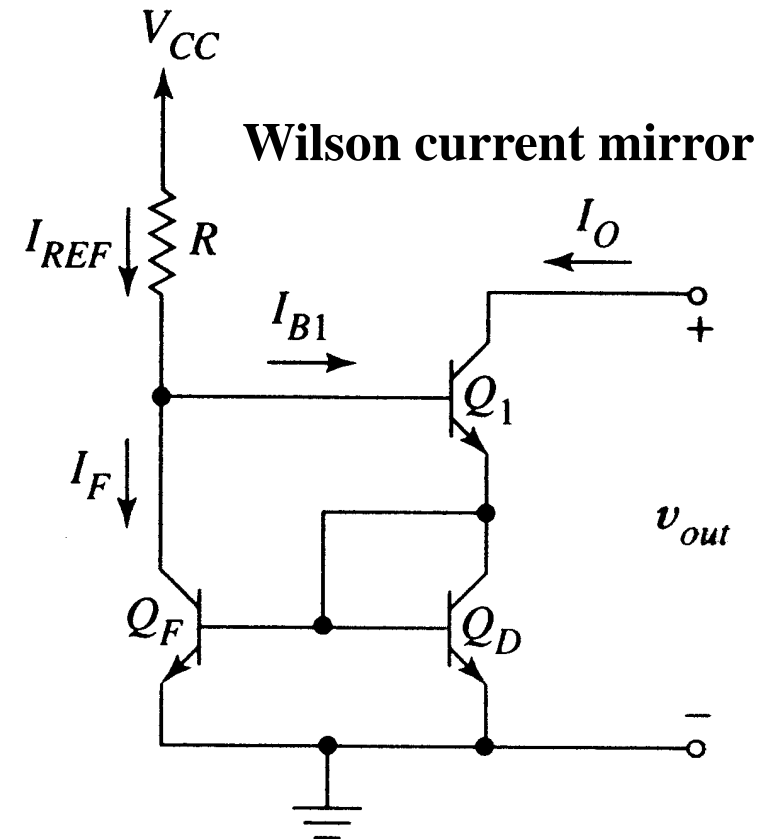
# Current Mirrors



The Wilson current mirror has the advantage of virtually eliminating the base current mis-match of the basic current mirror thereby ensuring that the output current  $I_O$  is almost equal to the reference or input current  $I_{REF}$ . It also has a very high output impedance.

$$\frac{I_o}{I_{REF}} = \frac{\beta^2 + 2\beta}{\beta^2 + 2\beta + 2} \cdot$$



# Current Mirrors

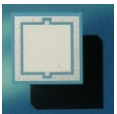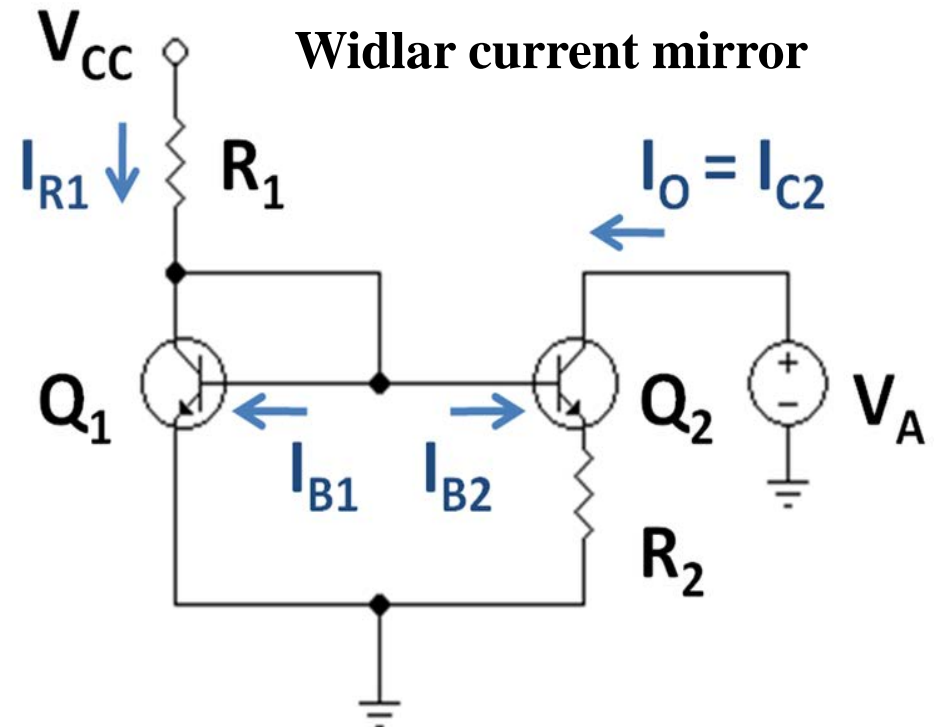**Widlar current mirror uses bipolar transistors, where the emitter resistor  $R_2$  is connected to the output transistor  $Q_2$ , and has the effect of reducing the current in  $Q_2$  relative to  $Q_1$ . The key to this circuit is that the voltage drop across the resistor  $R_2$  subtracts from the base-emitter voltage of transistor  $Q_2$ , thereby turning this transistor off compared to transistor  $Q_1$ .**



# Current Mirrors

**Example 4: Design a Widlar current mirror.**

Select the desired output current  $I_O$ .

Select the reference current  $I_{R1}$ .



Find the collector current of  $Q_1$

$$I_{C1} = \frac{\beta_1}{\beta_1 + 1} (I_{R1} - I_{C2}/\beta_2) .$$

Find the base voltage of  $Q_1$

$$V_{BE1} = V_T \ln \left( \frac{I_{C1}}{I_S} \right) = V_A .$$

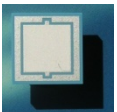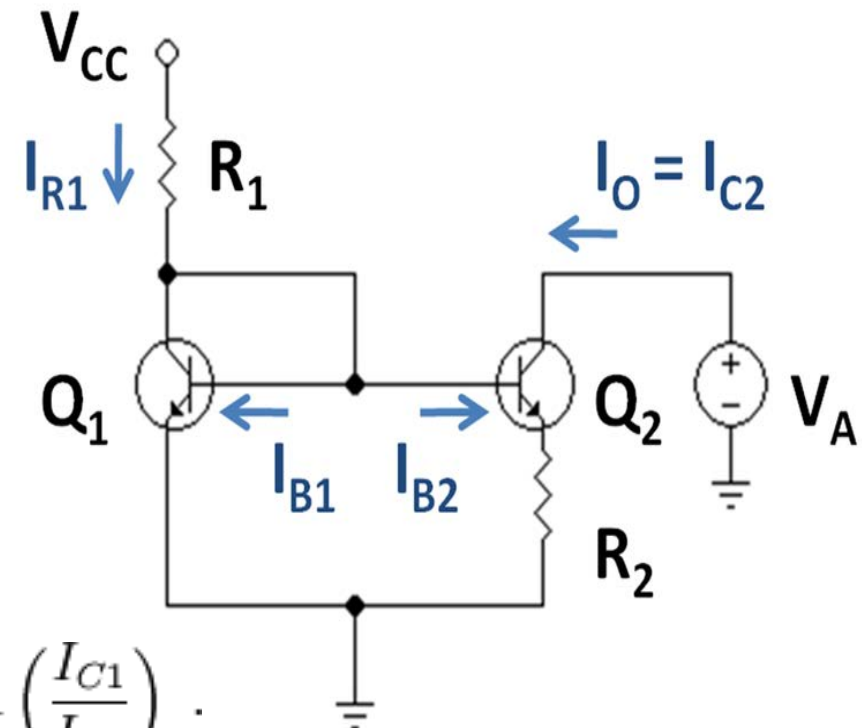Find  $R_1 = \frac{V_{CC} - V_A}{I_{R1}}$  and  $R_2 = \frac{V_T}{(1 + 1/\beta_2) I_{C2}} \ln \left( \frac{I_{C1}}{I_{C2}} \right) .$





# Current Mirrors

**Example 5:** For the Widlar current source given, assuming that the two transistors are identical, the early voltage is infinite, and the base currents are negligible, determine the output current and the sensitivity of the output current to the power-supply voltage.

**Solution:** Based on the given assumptions, we have

$$V_{BE1} - V_{BE2} - I_o R_2 = 0 \quad .$$
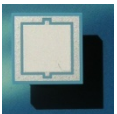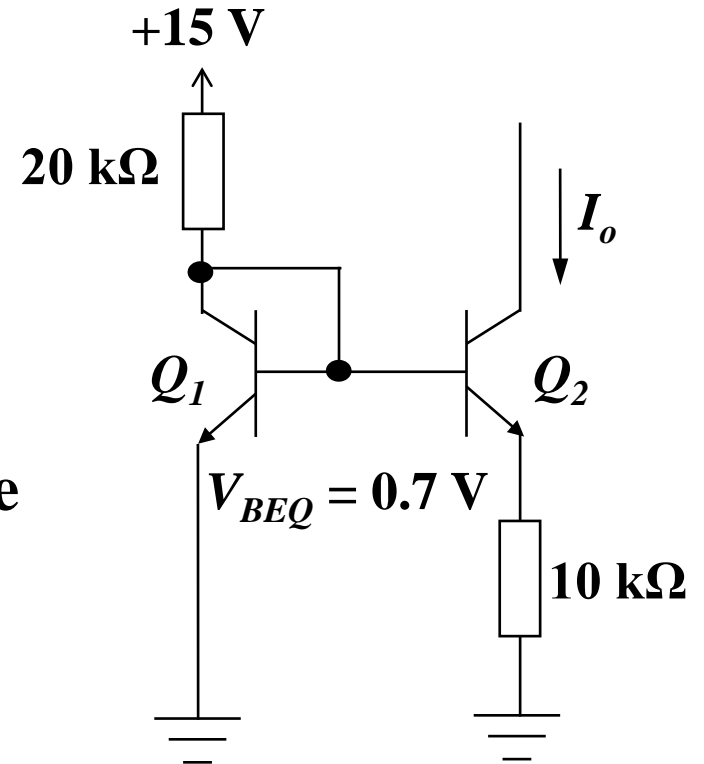
$$V_T \ln \frac{I_{C1}}{I_{S1}} - V_T \ln \frac{I_{C2}}{I_{S2}} - I_o R_2 = 0 \quad .$$







# Current Mirrors

$$I_o R_2 = V_T \ln \frac{I_{C1}}{I_{C2}} = V_T \ln \frac{I_{C1}}{I_o} .$$

$$I_{C1} = \frac{V_{CC} - V_{BEQ}}{R_1} = \frac{15 - 0.7}{20} = 0.715 \text{ mA} .$$

$$I_o \times 10000 = 0.026 \ln \frac{0.000715}{I_o} .$$

$$I_o \approx 11 \mu\text{A} .$$

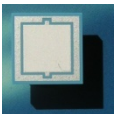
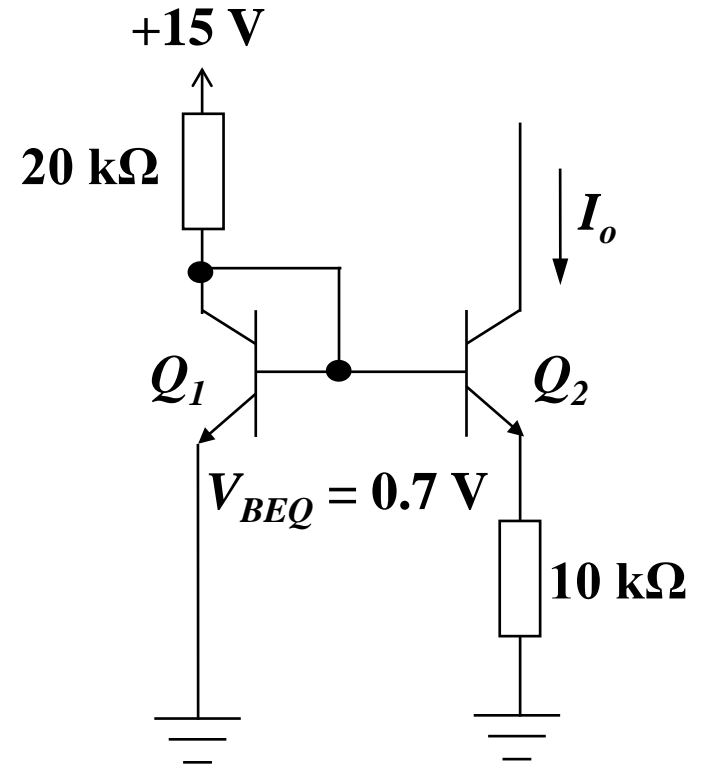


# Current Mirrors

$$I_o R_2 = V_T \ln \frac{I_{C1}}{I_o} .$$

Differentiating the above equation, we have:
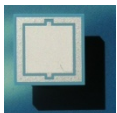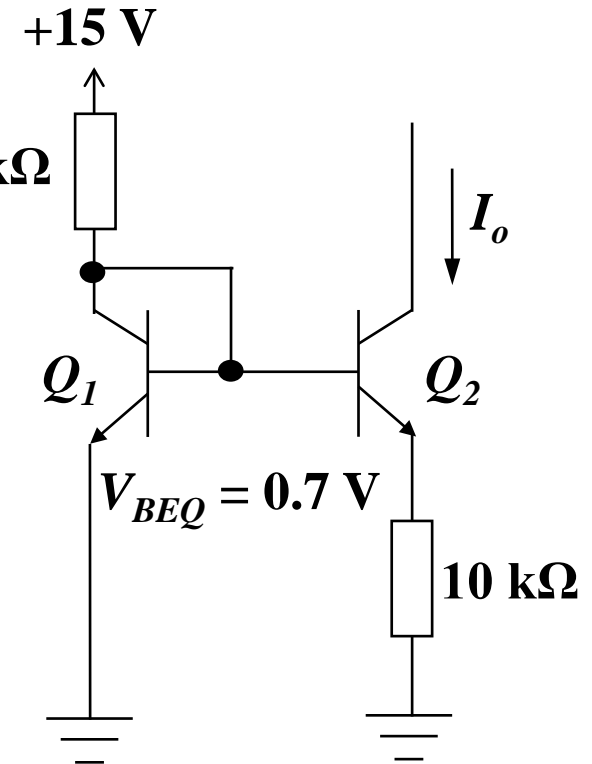
$$\begin{aligned} R_2 \frac{\partial I_o}{\partial V_{CC}} &= V_T \frac{\partial}{\partial V_{CC}} \left( \ln \frac{I_{C1}}{I_o} \right) \\ &= V_T \frac{I_o}{I_{C1}} \left[ - \frac{I_o \frac{\partial I_{C1}}{\partial V_{CC}} - I_{C1} \frac{\partial I_o}{\partial V_{CC}}}{I_o^2} \right] . \end{aligned}$$





# Current Mirrors

$$\frac{\partial I_o}{\partial V_{CC}} = \frac{I_o}{I_{C1}} \left( \frac{\frac{\partial I_{C1}}{\partial V_{CC}}}{1 + \frac{I_o R_2}{V_T}} \right) \cdot$$

$$S_{V_{CC}}^{I_o} = \frac{V_{CC}}{I_o} \frac{\partial I_o}{\partial V_{CC}} = \frac{V_{CC}}{I_{C1}} \left( \frac{\frac{\partial I_{C1}}{\partial V_{CC}}}{1 + \frac{I_o R_2}{V_T}} \right) = \frac{S_{V_{CC}}^{I_{C1}}}{1 + \frac{I_o R_2}{V_T}} \cdot$$
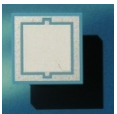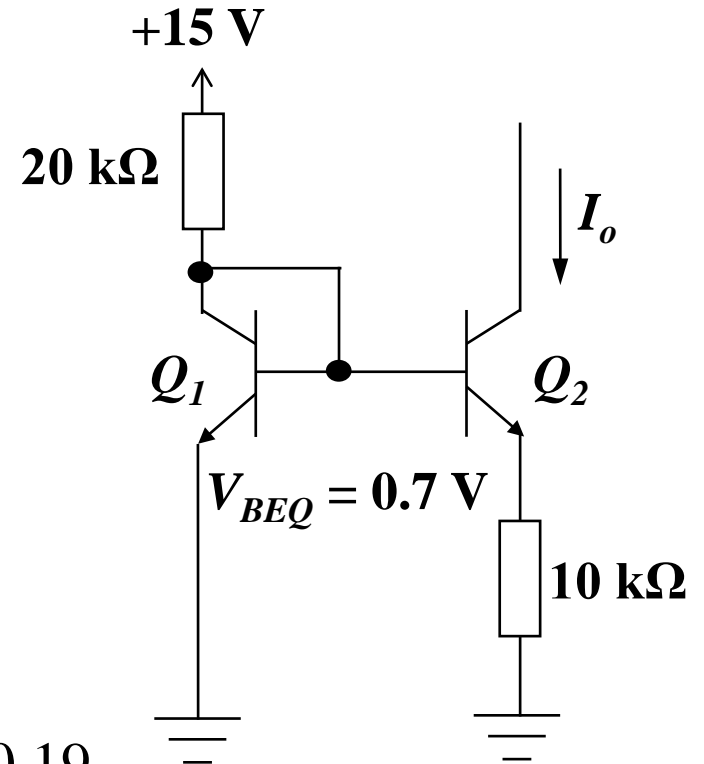
$$I_{C1} \approx \frac{V_{CC}}{R_1}, \quad S_{V_{CC}}^{I_{C1}} \approx 1, \quad S_{V_{CC}}^{I_o} = \frac{1}{1 + \frac{I_o R_2}{V_T}} = \frac{1}{1 + \frac{110}{26}} \approx 0.19 \cdot$$



# $V_{BE}$ -Based Bias Circuit



$I_{ref}$  is forced through  $Q_1$ , so  $Q_2$  must supply enough current into  $R_2$  so that  $V_{BEQ1} = V_{R2}$ .

Neglecting base currents we have  $I_{out} = I_{EQ2} = I_{R2}$ .

Hence we have

$$I_{out} = \frac{V_{BE1}}{R_2} = \frac{V_T}{R_2} \ln \left( \frac{I_{ref}}{I_{S1}} \right).$$

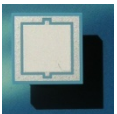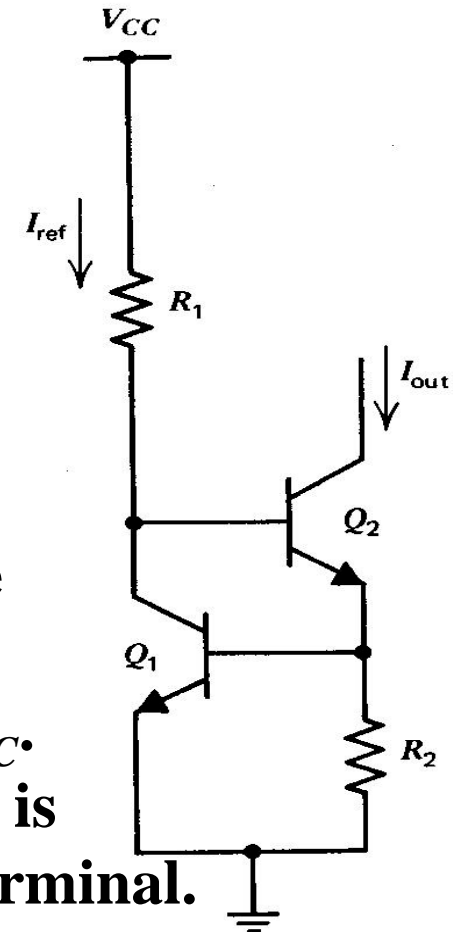This bias circuit is **NOT** supply independent since  $V_{BEQ1}$  will change slightly with the supply voltage because  $I_{CQ1}$  is approximately proportional to  $V_{CC}$ . This is often a problem for bias circuits whose  $I_{out}$  is derived from a resistor connected to the supply terminal.







# $V_{BE}$ -Based Bias Circuit with Bootstrap

The idea is instead of developing the reference current through a resistor, the reference circuit is made to depend on the current source itself.

Assuming  $V_A = \infty$  and neglecting base currents:  $Q_1$ ,  $Q_2$  and  $R$  are same as before.

$Q_3$  is the current mirror of  $Q_1$ .

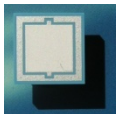
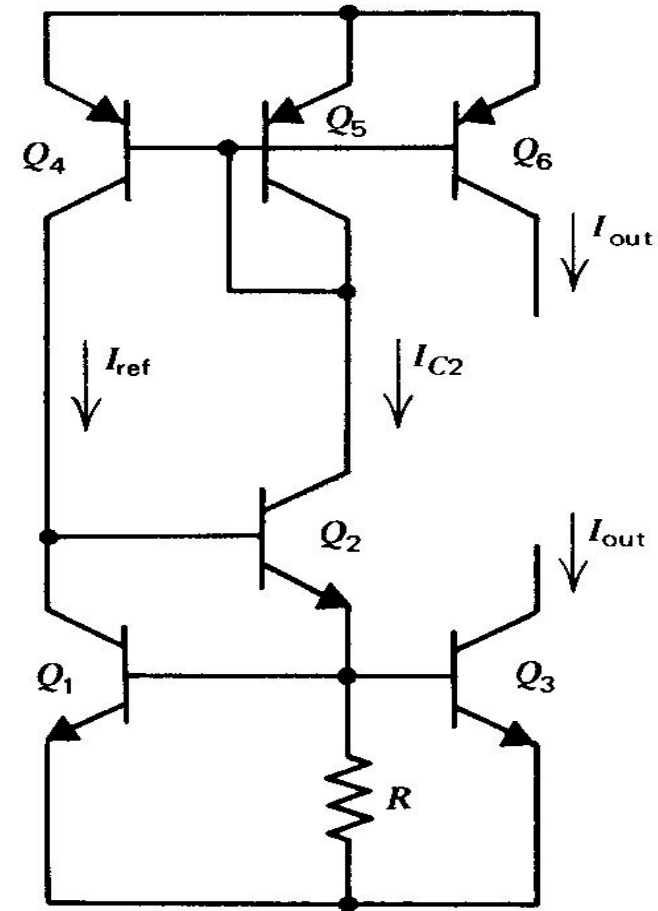
$Q_4$ ,  $Q_5$  and  $Q_6$  are part of a simple current mirror, hence  $I_{ref} = I_{C2}$ .


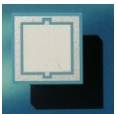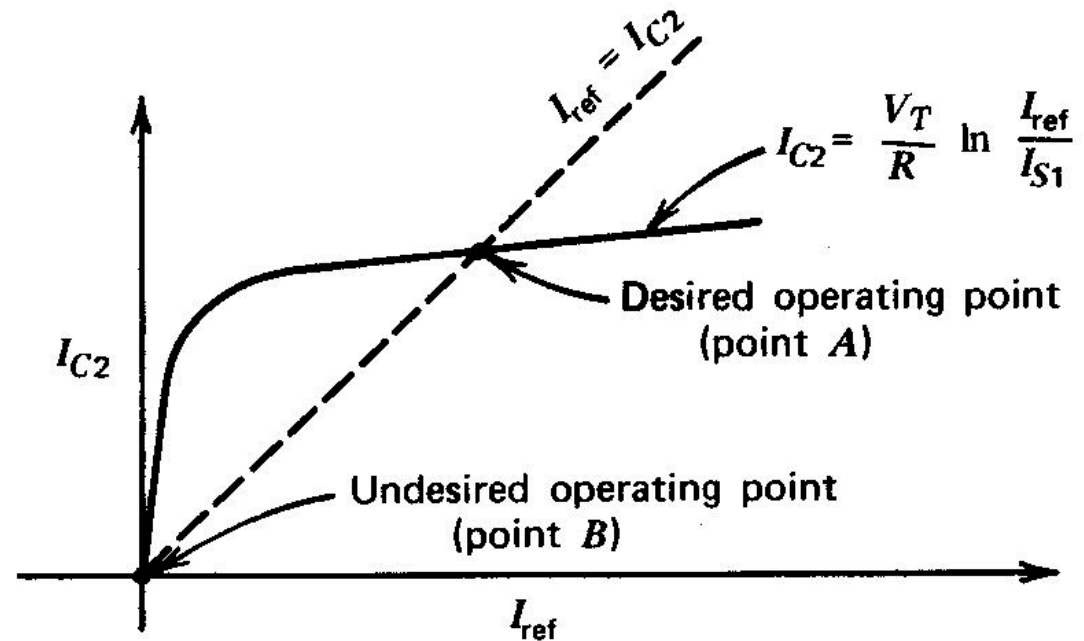
# $V_{BE}$ -Based Bias Circuit with Bootstrap

The operating point must satisfy both the upper current mirror and lower bias reference circuit.

The desired operating point is point A as shown in the figure. Need a start-up circuit to push the circuit out of the other possible operating point B. Here  $I_{out}$  is independent of the supply voltage.



# $V_{BE}$ -Based Bias Circuit with Bootstrap


However, the  $TC_F$  of this circuit is an issue.

Since  $I_{out} = \frac{V_{BE1}}{R}$ ,

$$\frac{\partial I_{out}}{\partial T} = \frac{1}{R} \frac{\partial V_{BE1}}{\partial T} - \frac{V_{BE1}}{R^2} \frac{\partial R}{\partial T} = I_{out} \left( \frac{1}{V_{BE1}} \frac{\partial V_{BE1}}{\partial T} - \frac{1}{R} \frac{\partial R}{\partial T} \right).$$

Hence  $TC_F = \frac{1}{V_{BE1}} \frac{\partial V_{BE1}}{\partial T} - \frac{1}{R} \frac{\partial R}{\partial T}$ .

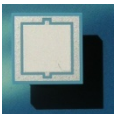As  $TC_F(V_{BE1})$  is -ve and  $TC_F(R)$  is +ve, the net  $TC_F$  is large => sensitive to temperature with a negative gradient, i.e. as  $T \uparrow$ ,  $I_{out} \downarrow$ .





# $V_T$ -Based Bias Circuit

The difference in the junction potential between two junctions operated at different current densities can be shown to be  $\propto V_T$ . From the Widlar current source shown on the right,

$$V_X = I_{C2} R_2 = V_T \ln \left( \frac{I_{C1} I_{S2}}{I_{C2} I_{S1}} \right) .$$

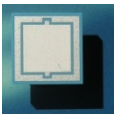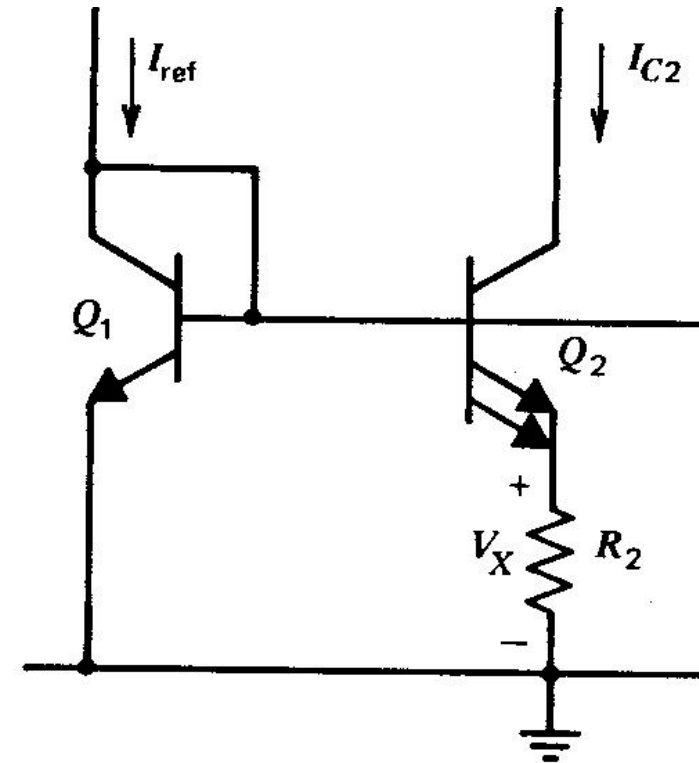If the ratio of the collector currents is constant, then  $V_X \propto V_T$ . If the emitter area of  $Q_2 = 2 \times$  that of  $Q_1$ , then  $I_{S2} = 2 \times I_{S1}$ .



# $V_T$ -Based Bias Circuit with Bootstrap



The reference circuit is again made to depend on the current source itself.

Due to the current mirror formed by  $Q_3$  and  $Q_4$ ,  $I_{C1} = I_{C2}$ . For Widlar current source:  $V_X = V_T \ln 2$ .

Satisfying both the current mirror and current source equations requires that

$$I_{C2} = \frac{V_T}{R_2} \ln 2 .$$

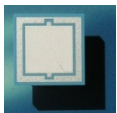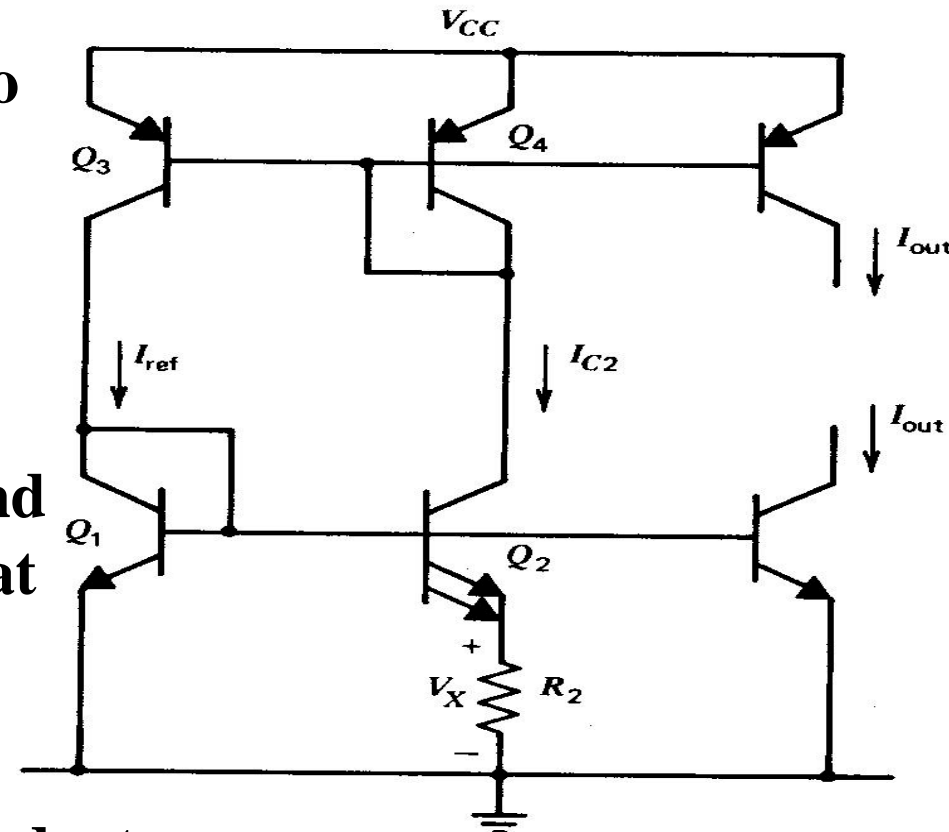The output current is supply independent.






# $V_T$ -Based Bias Circuit with Bootstrap

Since  $TC_F = \frac{1}{I_{C2}} \frac{\partial I_{C2}}{\partial T} = \frac{1}{I_{C2}} \frac{\partial}{\partial T} \left( \frac{V_T}{R_2} \ln 2 \right) = \frac{1}{I_{C2}} \left( \frac{1}{V_T} \frac{\partial V_T}{\partial T} - \frac{1}{R_2} \frac{\partial R_2}{\partial T} \right) \left( \frac{V_T}{R_2} \ln 2 \right)$

$$= \frac{1}{V_T} \frac{\partial V_T}{\partial T} - \frac{1}{R_2} \frac{\partial R_2}{\partial T} .$$


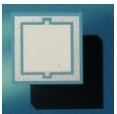
As  $TC_F(V_T)$  is +ve and  $TC_F(R)$  is +ve, they tend to cancel out!  
The net  $TC_F$  is therefore small  $\Rightarrow$  only slightly sensitive to temperature with a positive gradient, i.e. as  $T \uparrow$ ,  $I_{out} \uparrow$ .


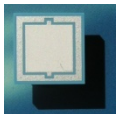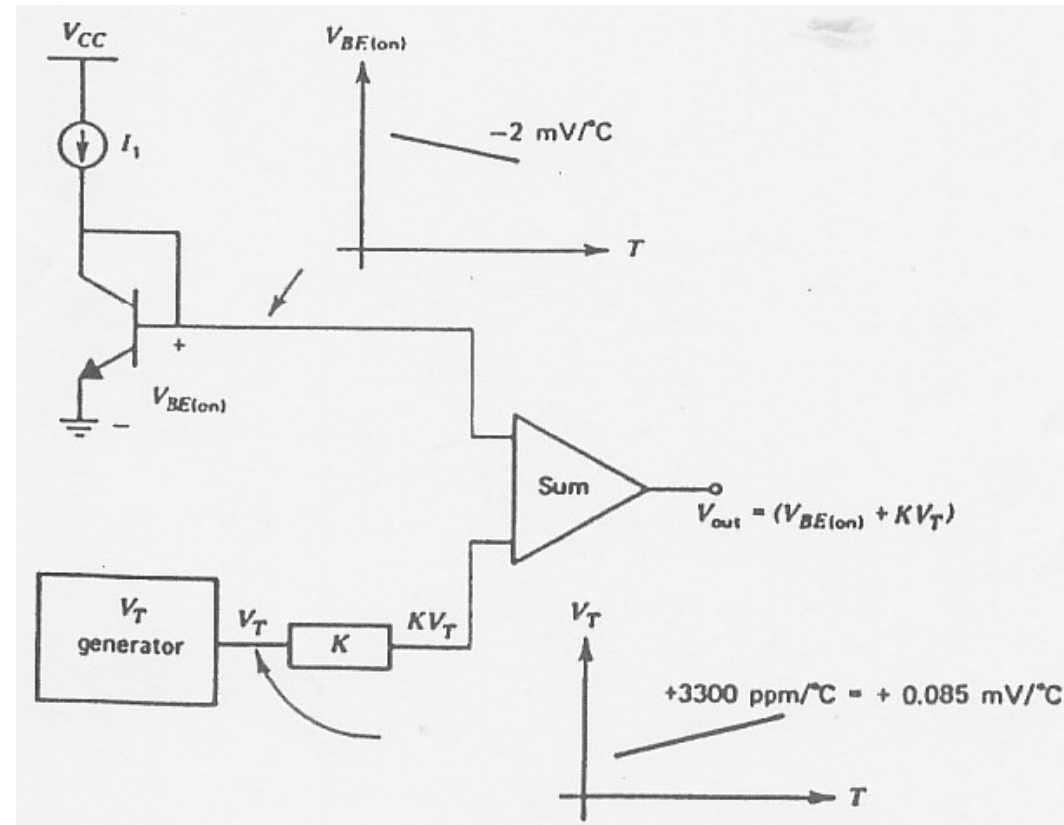
# Bandgap Bias Circuit

Notice that the  $V_{BE}$ -based and  $V_T$ -based reference circuits have opposite  $TC_F$ s, we can obtain a reference current that is a weighted sum of  $V_{BE}$ -based and  $V_T$ -based reference currents. The idea is that by proper weighting of the currents, we can achieve a reference source with  $TC_F=0$ .

$$V_{out} = V_{BE} + KV_T \quad (K = \text{constant})$$



# Bandgap Bias Circuit



In an op amp circuit with negative feedback,  $V_+ = V_-$ .

Hence  $V_{R1} = V_{R2}$  and  $\frac{I_1}{I_2} = \frac{R_2}{R_1}$ .

Assuming negligible base currents, the difference between  $V_{BE1}$  and  $V_{BE2}$  is the voltage across  $R_3$ .

$$\Delta V_{BE} = V_{BE1} - V_{BE2} = V_T \ln \left( \frac{I_1}{I_2} \frac{I_{S2}}{I_{S1}} \right)$$
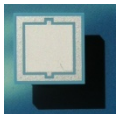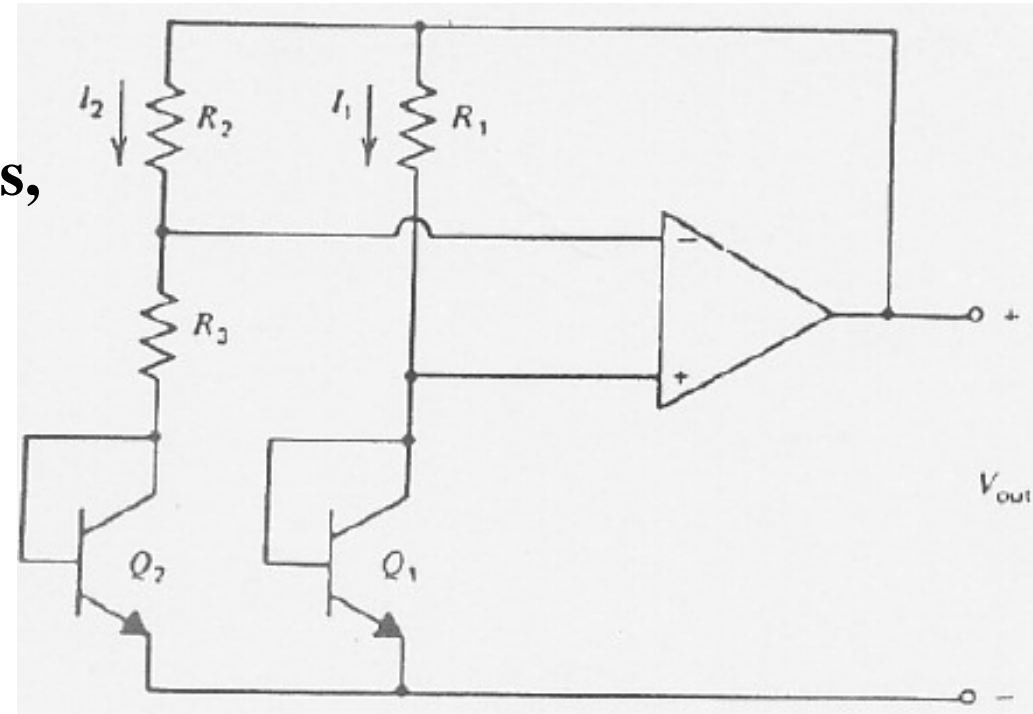
$$= V_T \ln \left( \frac{R_2}{R_1} \frac{I_{S2}}{I_{S1}} \right).$$






# Bandgap Bias Circuit

The voltage across  $R_2$  is  $V_{R2} = \frac{R_2}{R_3} \Delta V_{BE} = \frac{R_2}{R_3} V_T \ln \left( \frac{R_2 I_{S2}}{R_1 I_{S1}} \right)$ .

This means that both  $I_1$  and  $I_2$  are proportional to temperature if the resistors have zero  $TC_F$ . The output voltage is the sum of voltages across  $R_1$  and  $Q_1$ :

$$V_{out} = V_{BE1} + \frac{R_2}{R_3} V_T \ln \left( \frac{R_2 I_{S2}}{R_1 I_{S1}} \right) = V_{BE1} + K V_T \quad \text{where} \quad K = \frac{R_2}{R_3} \ln \left( \frac{R_2 I_{S2}}{R_1 I_{S1}} \right).$$

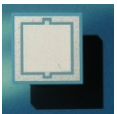By proper choice of  $K$ ,  $V_{out}$  can be made virtually independent of temperature and supply voltage.





# Voltage Level Shifters

**Functions of a voltage level shifter:** Adjust to specific levels the quiescent voltages at various points of a dc coupled circuit and adjust the output voltage to appropriate quiescent level for optimum swing. The quiescent dc levels in each subcircuit have to be managed as all subcircuits are dc coupled.

**By inspection:**  $V_o = V_i - V_{BEQ} \approx V_i - 0.7V$  .

**Two problems:** Voltage gain is slightly less than 1. The voltage level shift is limited to only 0.7V.

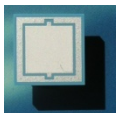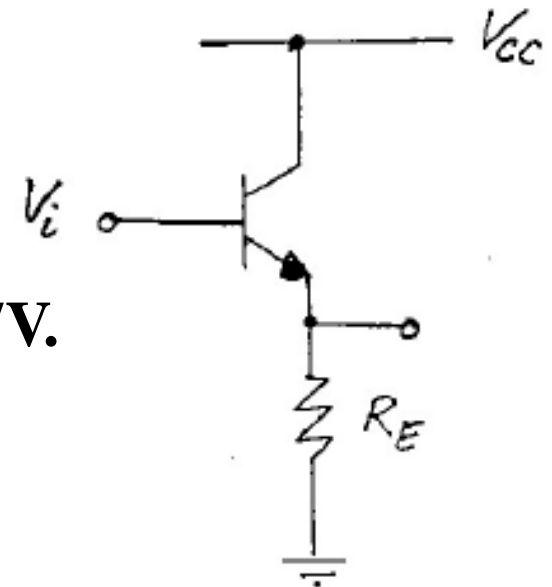**May use a voltage divider to increase the voltage shift.**





# Voltage Level Shifters

By inspection:

$$V_{o2} = \frac{R_2}{R_1 + R_2} (V_i - V_{BEQ}) .$$

The voltage level shift has increased (by how much?). However, the input signal is attenuated => unacceptable!

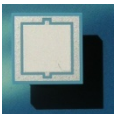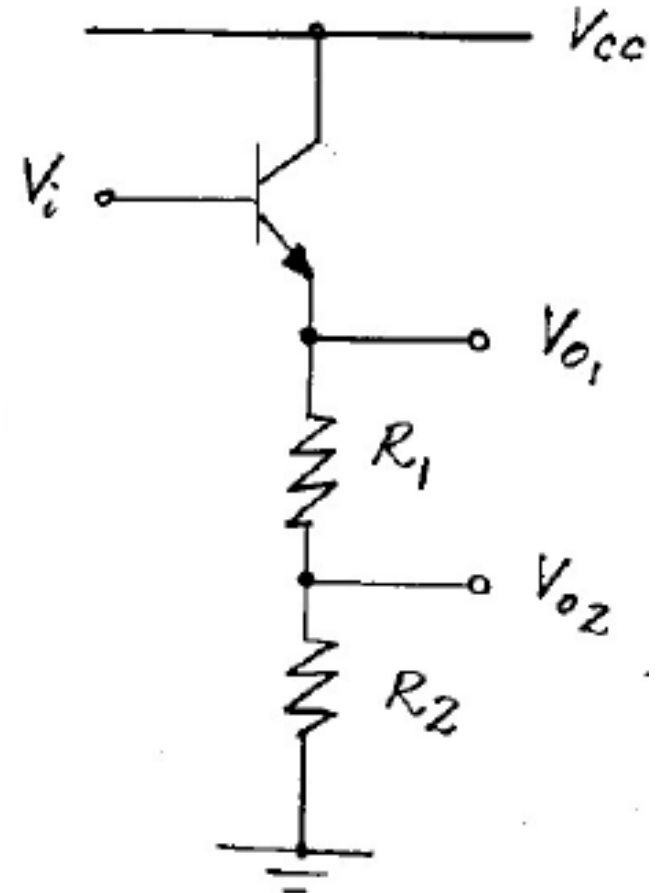Solution: replace  $R_2$  with a current source.



# Voltage Level Shifters

**By inspection:**

$$V_o = V_i - V_{BEQ} - I \times R_1 .$$

The voltage level shift increases by  $I \times R_1$  where  $I$  is the biasing current of the current source.

$R_1$  can be varied to achieve different dc voltage shift.

The ideal impedance of a current source is  $\infty$ , hence for any input signal,  $R_2$  is  $\infty \Rightarrow$  no signal attenuation.

