

EE2002

**NANYANG TECHNOLOGICAL UNIVERSITY**

**SEMESTER 2 EXAMINATION 2017-2018**

**EE2002 – ANALOG ELECTRONICS**

April / May 2018

Time Allowed: 2½ hours

**INSTRUCTIONS**

1. This paper contains 5 questions and comprises 10 pages.
  2. Answer ALL questions.
  3. All questions carry equal marks.
  4. This is a closed book examination.
  5. Unless specifically stated, all symbols have their usual meanings.
  6. A list of Formulae is provided in Appendix A on pages 8 to 10.
- 


1. (a) For the non-ideal Op-Amp in negative feedback shown in Figure 1(a) on page 2, derive the expression for the output voltage  $v_{OUT}$  in terms of all or some of the following variables  $v_1$ ,  $v_2$ ,  $V_{IO}$ ,  $I_+$ ,  $I_-$ ,  $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_4$ ,  $R_5$ ,  $R_6$  and  $R_7$  assuming that the output is in the linear range of operation.

**Note:** Parallel resistance of  $R_a$  and  $R_b$  can be written as  $R_a // R_b$  without expanding it.

(10 Marks)

Note: Question No. 1 continues on page 2

EE2002

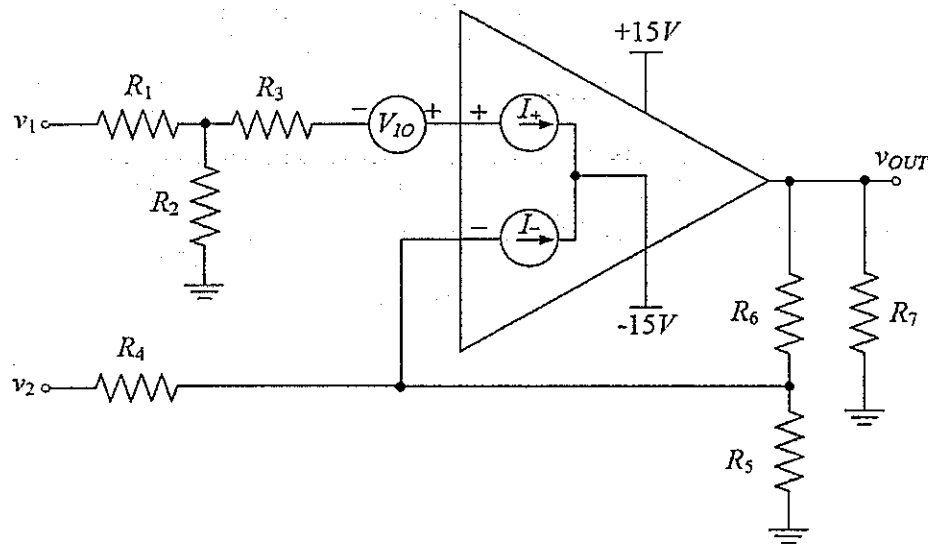**Figure 1(a)**

(b) In Figure 1(b) on page 3, the empirical junction diode equation is:

$$V_D = nV_T \ln [I_D / I_S]$$


for diodes  $D_1, D_2, D_3$  and  $D_4$  where  $n = 1$ ,  $V_T = 26$  mV at room temperature,  $I_S = 5 \times 10^{-17}$  A, the resistors  $R_1 = R_2 = R_4 = 30$  k $\Omega$ ,  $R_3 = R_5 = 15$  k $\Omega$  and the DC voltage source  $V_S = 8$  V. Find the DC quiescent operating point or Q-point ( $I_D$ ;  $V_D$ ) of the diodes  $D_1, D_2, D_3$  and  $D_4$  (to 3 decimal places in  $\mu$ A and V, respectively).

**Note:** The diodes are all identical where  $V_{D1} = V_{D2} = V_{D3} = V_{D4}$  and  $I_{D1} = I_{D2} = I_{D3} = I_{D4}$ .

(10 Marks)

Note: Question No. 1 continues on page 3


EE2002

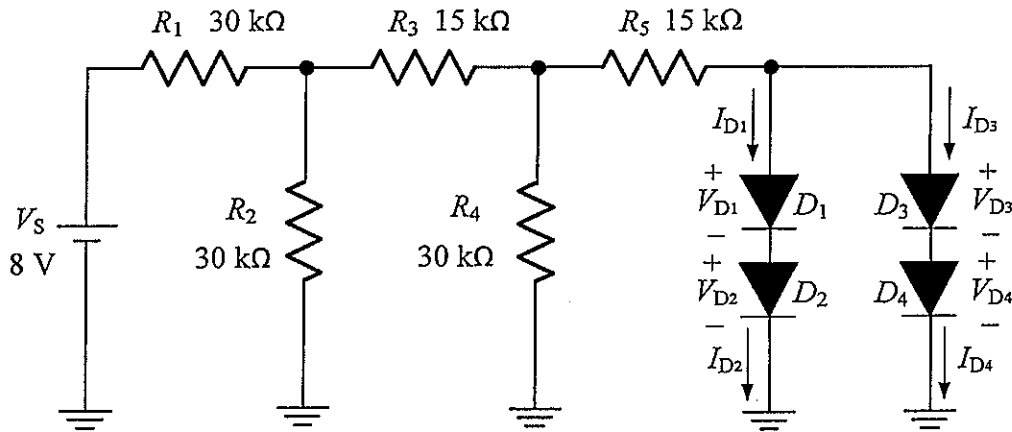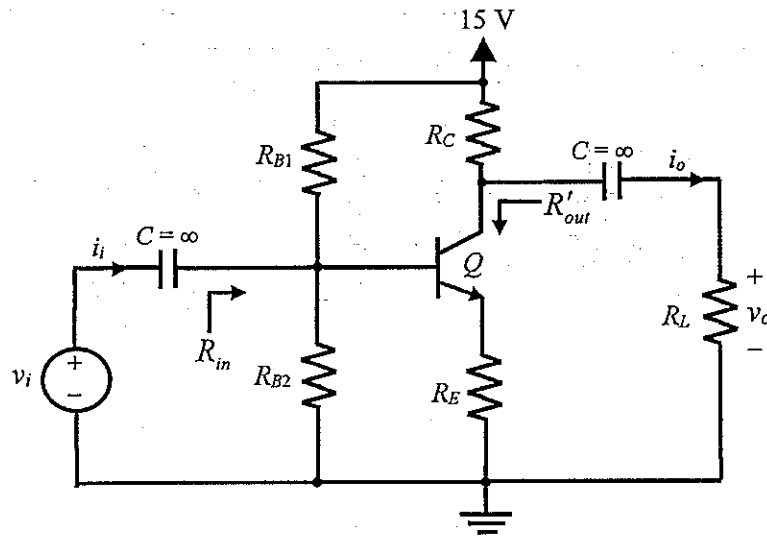**Figure 1(b)**

2. In Figure 2 on page 4,  $R_{B1} = 10 \text{ k}\Omega$ ,  $R_{B2} = 1.2 \text{ k}\Omega$ ,  $R_E = 1.2 \text{ k}\Omega$ ,  $R_C = 10 \text{ k}\Omega$  and  $R_L = 10 \text{ k}\Omega$ . The transistor  $Q$  has  $\beta = 100$  and  $V_A = 80 \text{ V}$ .  $v_i$  and  $v_o$  are the input and output signal voltages, respectively. Assume that all the capacitors are ideal and have infinite capacitance.
- Calculate the Q-point of transistor  $Q$ .  
(7 Marks)
  - Determine the voltage gain  $A_v = \frac{v_o}{v_i}$ , input resistance  $R_{in}$  and the resistance  $R'_{out}$  looking directly into the collector terminal of the amplifier, excluding  $R_C$  and  $R_L$ .  
(10 Marks)
  - What is the current gain  $A_i = \frac{i_o}{i_i}$  of the amplifier?  
(3 Marks)

Note: Question No. 2 continues on page 4

EE2002


**Figure 2**

3. In Figure 3 on page 5, the DC operating point for the PNP transistor  $Q_1$  is  $I_C = 0.33$  mA and  $V_{EC} = 2.4$  V, and the DC operating point for the NMOS transistor  $M_1$  is  $I_D = 2.81$  mA and  $V_{DS} = 2.92$  V.  $Q_1$  has  $\beta = 100$ ,  $V_A = 85$  V at room temperature and  $M_1$  has  $K_n = 1$  mA/V<sup>2</sup>,  $V_{TN} = 1$  V and  $\lambda = 0.02$  V<sup>-1</sup>. Assume that the capacitors have infinite values, and the resistors have the values as indicated in Figure 3.

- Determine the voltage gain  $A_v = \frac{v_o}{v_i}$ .  
(9 Marks)
- Determine the input resistance  $R_{in}$  and output resistance  $R_{out}$  of the amplifier.  
(6 Marks)
- Determine the small signal input range of  $v_i$  for this amplifier.  
(5 Marks)


Note: Question No. 3 continues on page 5

EE2002

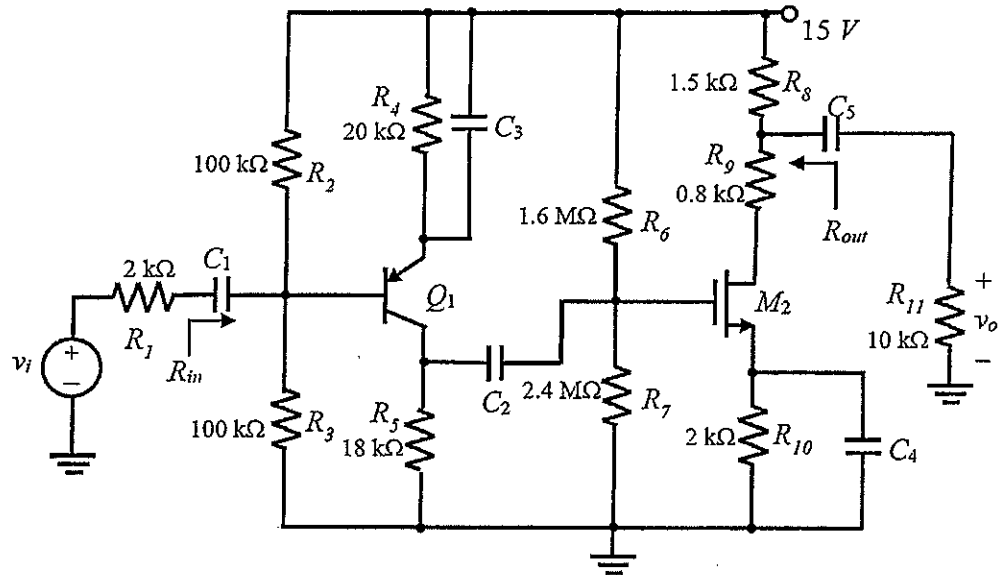

**Figure 3**

4. (a) Consider the circuit in Figure 4(a). Assume all transistors are biased in the Forward Active region and have the same current gain  $\beta$  and Early Voltage  $V_A$ .

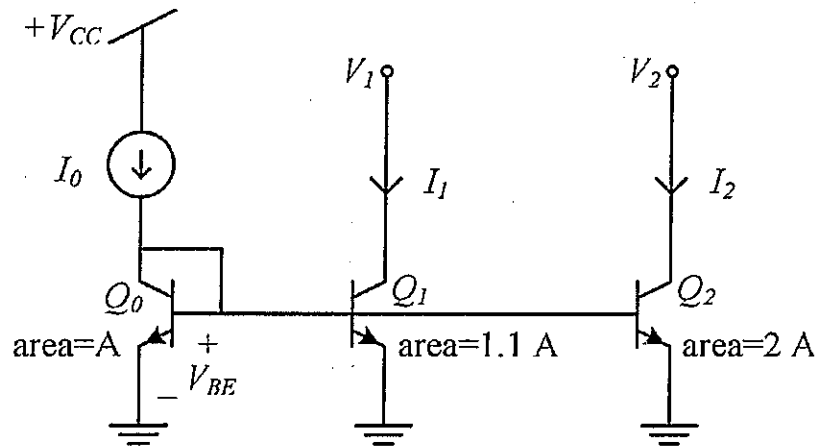

**Figure 4(a)**

Note: Question No. 4 continues on page 6

EE2002

- (i) Find the algebraic expressions for the current mirror ratios  $I_1/I_0$  and  $I_2/I_0$  including the Early Effect (HINT: include the terms  $\beta$ ,  $V_A$  and  $V_{BE}$  in your answer).  
(5 Marks)
- (ii) Using your answer to part (a), choose EITHER transistor  $Q_1$  or  $Q_2$  and calculate its output resistance, i.e.  $r_{o1}$  OR  $r_{o2}$ , respectively (you need not do both). Use the following values:  $\beta = 100$ ,  $V_A = 50$  V,  $V_{BE} = 0.7$  V,  $I_0 = 10$   $\mu$ A,  $V_{CC} = 5$  V,  $V_1 = 4$  V,  $V_2 = 3$  V.  
(5 Marks)
- (b) Consider the current mirror in Figure 4(b). Both transistors are biased in the Saturation region and have the same values for  $K'_n$ ,  $V_{TN}$  and  $\lambda$ . Find the algebraic expression for the current mirror ratio  $I_1/I_0$  including the Early Effect (HINT: include  $\lambda$ ,  $V_1$  and  $V_G$  in your answer).  
(4 Marks)

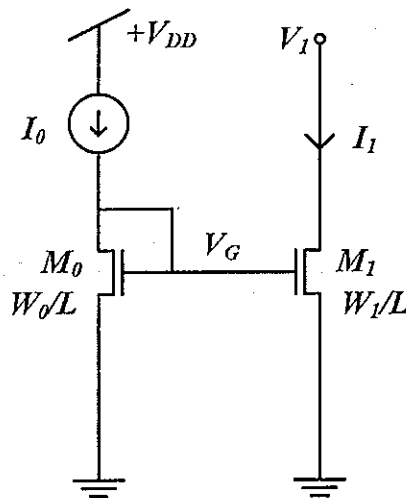


Figure 4(b)


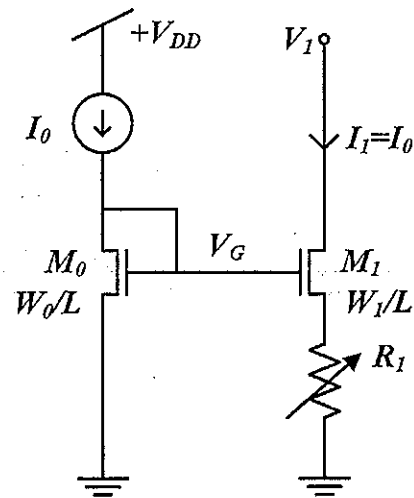


Figure 4(c)

- (c) In Figure 4(c), a potentiometer  $R_1$  is added into the source of  $M_1$  to make  $I_1 = I_0$ . Find the value of  $R_1$  given the following:  $W_0 = 10$   $\mu$ m,  $W_1 = 11$   $\mu$ m,  $L = 1$   $\mu$ m,  $I_0 = 10$   $\mu$ A,  $V_{DD} = 5$  V,  $V_1 = 4$  V,  $K'_n = 50$   $\mu$ A/V<sup>2</sup>,  $V_{TN} = 0.75$  V,  $\lambda = 0.01$  V<sup>-1</sup> (HINT: start by calculating the value of  $V_G$ ).  
(6 Marks)

EE2002

5. Consider the circuit shown in Figure 5 and assume that the Op-amp is ideal.
- Derive the transfer function  $V_{o1}/V_s$ . How many poles and zeros are there in this transfer function?  
(5 Marks)
  - Derive the transfer function  $V_{out}/V_s$ . How many poles and zeros are there in this transfer function?  
(5 Marks)
  - Find the algebraic expressions of the poles and zeros in the transfer function found in part (b) of this question.  
(3 Marks)
  - Given that  $R_f = 5 \text{ k}\Omega$ ,  $R_L = 0.2 \text{ k}\Omega$ ,  $C_s = C_f = 2 \text{ }\mu\text{F}$  and  $C_L = 5 \text{ }\mu\text{F}$ , draw the Bode plot for the transfer function derived in part (b) of this question. Clearly mark the slopes for all the regions in the plot and indicate the gain at frequency  $\omega = 100 \text{ rad/sec}$ .  
(7 Marks)

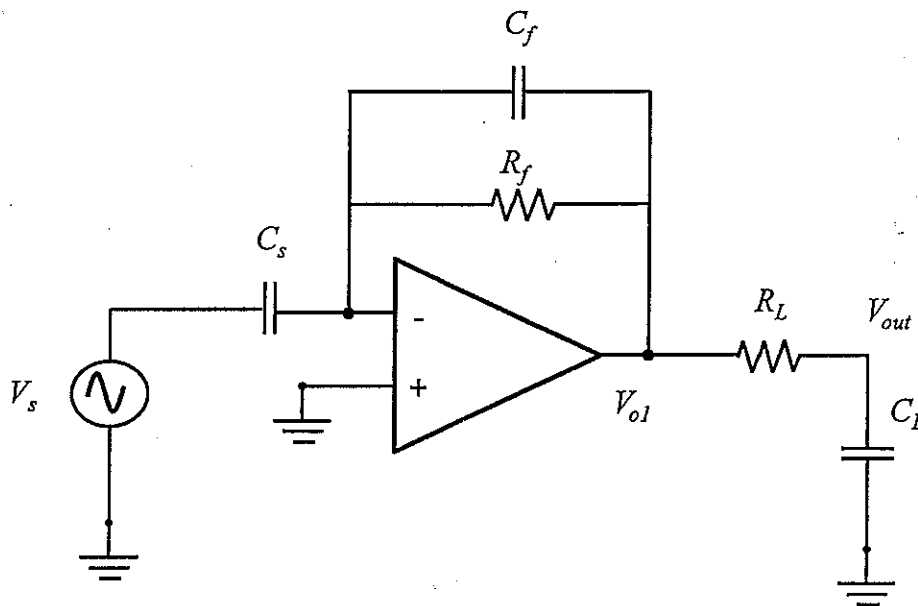

**Figure 5**

**Appendix A****List of Selected Formulae (with the usual notations)****Op-Amps:**

Closed-Loop Negative Feedback Inverting Gain,  $A_{vCL} = \frac{v_o}{v_i} = -\frac{R_f}{R_i}$

Figure (a)

Closed-Loop Negative Feedback Non-Inverting Gain,  $A_{vCL} = \frac{v_o}{v_i} = \left(1 + \frac{R_f}{R_i}\right)$

Figure (b)

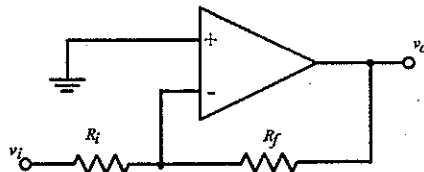


Figure (a)

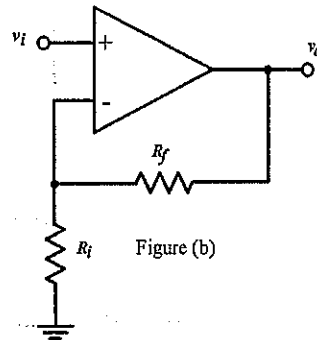


Figure (b)

Op-Amp's Slew Rate,  $SR \geq \left| \frac{dv_o}{dt} \right|_{\max} = A_{vCL} \omega a_m = A_{vCL} a_m 2\pi f$ ,


where  $v_i = a_m \sin(\omega t)$ ,  $v_o = A_{vCL} v_i$ ,  $v_o = A_{vCL} a_m \sin(\omega t)$  and  $\left| \frac{dv_o}{dt} \right| = A_{vCL} \omega a_m \cos(\omega t)$

Op-Amp's frequency response:  $A_{vOL}(jf) = \frac{A_o}{\left(1 + \frac{jf}{f_p}\right)}$

Gain-Bandwidth Product:  $A_o f_p = f_o = \frac{1}{\beta} (BW)_{CL}$

where  $\frac{1}{\beta} = \frac{R_f + R_i}{R_i}$

$t_r = \frac{0.35}{(BW)_{CL}}$

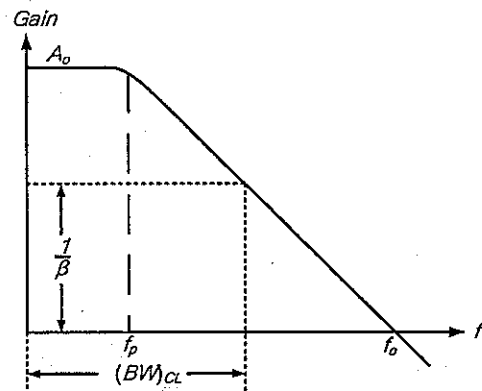**Diodes:**

$v_D \approx nV_T \ln\left(\frac{i_D}{I_S}\right)$  or  $i_D \approx I_S e^{\left(\frac{v_D}{nV_T}\right)}$

where  $e^x = 1 + x + \frac{x^2}{2!} + \frac{x^3}{3!} + \frac{x^4}{4!} + \dots$

Diode conductance:  $g_D = \frac{1}{r_D} = \frac{I_D}{nV_T}$



EE2002

### BJT in Forward Active Region:

Ignore early effect:  $i_C = I_S \exp\left(\frac{|v_{BE}|}{V_T}\right)$

With early effect:  $i_C = I_S \exp\left(\frac{|v_{BE}|}{V_T}\right) \left(1 + \frac{|v_{CE}|}{V_A}\right)$

where  $I_S$ : Saturation current,

$V_T$ : Thermal voltage, assume 25 mV at room temperature,

$V_A$ : Early voltage.

For npn transistor,  $|v_{BE}| = v_{BE}$  and  $|v_{CE}| = v_{CE}$ ;

For pnp transistor,  $|v_{BE}| = v_{EB}$  and  $|v_{CE}| = v_{EC}$ .

### Small-signal model parameters of BJT:

$$g_m = \frac{I_C}{V_T}, r_\pi = \frac{\beta}{g_m} \text{ and } r_o = \frac{V_A + |V_{CE}|}{I_C} \approx \frac{V_A}{I_C}$$

where  $I_C$ : DC collector current at Q-point

$V_{CE}$ : DC collector-emitter voltage at Q-point

Criterion for small-signal operation of BJT:  $|v_{be}| \leq 0.2V_T$

### MOSFET in Saturation Region:

Criterion:  $V_{DS} \geq V_{GS} - V_{TN}$  for NMOS;

$|V_{DS}| \geq |V_{GS}| - |V_{TP}|$  for PMOS

where  $V_{TN}, V_{TP}$ : Threshold voltage,

$V_{DS}$ : DC drain-source voltage,

$V_{GS}$ : DC gate-source voltage.

Ignore channel-length modulation effect:

$$i_D = \frac{K_n}{2} (v_{GS} - V_{TN})^2 \text{ for NMOS,}$$

$$i_D = \frac{K_p}{2} (|v_{GS}| - |V_{TP}|)^2 \text{ for PMOS.}$$

With channel-length modulation effect:  $i_D = \frac{K_n}{2} (v_{GS} - V_{TN})^2 (1 + \lambda v_{DS})$  for NMOS,

$$i_D = \frac{K_p}{2} (|v_{GS}| - |V_{TP}|)^2 (1 + \lambda |v_{DS}|) \text{ for PMOS.}$$

where  $\lambda$ : channel length modulation parameter,

For NMOS  $K_n = K'_n \left(\frac{W}{L}\right)$  and  $K'_n = \mu_n C_{ox}$ ; For PMOS  $K_p = K'_p \left(\frac{W}{L}\right)$  and  $K'_p = \mu_p C_{ox}$ .

### MOSFET in Triode Region:

Criterion:  $V_{DS} < V_{GS} - V_{TN}$  for NMOS;

$|V_{DS}| < |V_{GS}| - |V_{TP}|$  for PMOS

Ignore channel-length modulation effect:

$$i_D = K_n \left( v_{GS} - V_{TN} - \frac{v_{DS}}{2} \right) v_{DS} \text{ for NMOS,}$$

$$i_D = K_p \left( |v_{GS}| - |V_{TP}| - \frac{|v_{DS}|}{2} \right) |v_{DS}| \text{ for PMOS.}$$

EE2002

With channel-length modulation effect:  $i_D = K_n \left( v_{GS} - V_{TN} - \frac{v_{DS}}{2} \right) v_{DS} (1 + \lambda v_{DS})$  for NMOS,

$$i_D = K_p \left( |v_{GS}| - |V_{TP}| - \frac{|v_{DS}|}{2} \right) |v_{DS}| (1 + \lambda |v_{DS}|) \text{ for PMOS.}$$

### Small-signal model parameters of MOSFET

For NMOS:  $g_m = \sqrt{2K_n I_D (1 + \lambda V_{DS})} \approx \sqrt{2K_n I_D}$  and  $r_o = \frac{\frac{1}{\lambda} + V_{DS}}{I_D} \approx \frac{1}{\lambda I_D}$

For PMOS:  $g_m = \sqrt{2K_p I_D (1 + \lambda |V_{DS}|)} \approx \sqrt{2K_p I_D}$  and  $r_o = \frac{\frac{1}{\lambda} + |V_{DS}|}{I_D} \approx \frac{1}{\lambda I_D}$

where  $I_D$ : DC drain current at Q-point

$V_{DS}$ : DC drain-source voltage at Q-point

Criterion for small-signal operation:

For NMOS:  $|v_{gs}| \leq 0.2(V_{GS} - V_{TN})$

For PMOS:  $|v_{gs}| \leq 0.2(|V_{GS}| - |V_{TP}|)$

where  $V_{GS}$ : DC gate-source voltage at Q-point.

### Miller Effect

The equivalent shunt input capacitance:  $C_X = C \times (1 + A_v)$

The equivalent shunt output capacitance:  $C_Y = C \times (1 + \frac{1}{A_v})$

where  $-A_v$ : the gain of the voltage amplifier

$C$ : the original capacitance between the input and output terminals of the voltage amplifier

### Frequency Response

By using OCTC and SCTC method, the upper cut-off frequency is estimated by  $\omega_{H, \text{OCTC}} \approx \frac{1}{\sum_i C_i R_i}$

and the lower cut-off frequency is estimated by  $\omega_{L, \text{OCTC}} \approx \sum_i \frac{1}{C_i R_i}$

where  $C_i$ : the contributing capacitor for the cut-off frequency

$R_i$ : the equivalent resistance seen by the capacitor  $C_i$

END OF PAPER

April/May 2018

EE2002

$$1.(a) V_1: V_{t1} = V_1 \cdot \frac{R_L}{R_1 + R_L} = V_{-1}$$

$$V_{out1} = V_{-1} \cdot \frac{R_4/R_5 + R_6}{R_4/R_5} = V_1 \cdot \frac{R_L}{R_1 + R_L} \cdot \frac{R_4/R_5 + R_6}{R_4/R_5}$$

$$V_2: V_{t2} = V_{t2} = 0$$

$$V_{out2} = -V_2 \cdot \frac{R_6}{R_4/R_5}$$

$$I_+ : V_{t3} = V_{-3} = -I_+ \cdot (R_1/R_2 + R_3)$$

$$V_{out3} = -I_+ (R_1/R_2 + R_3) \cdot \frac{R_4/R_5 + R_6}{R_4/R_5}$$

$$I_- : V_{t4} = V_{-4} = 0$$


$$V_{out4} = I_- \cdot R_6$$

$$V_{IO} : V_{t5} = V_{-5} = V_{IO}$$

$$V_{out5} = V_{IO} \cdot \frac{R_4/R_5 + R_6}{R_4/R_5}$$

$$\Rightarrow V_{out} = \sum_{i=1}^5 V_{out_i} = \left( V_1 \cdot \frac{R_L}{R_1 + R_L} - I_+ (R_1/R_2 + R_3) + V_{IO} \right) \cdot \frac{R_4/R_5 + R_6}{R_4/R_5} - V_2 \cdot \frac{R_6}{R_4/R_5} + I_- \cdot R_6$$


(b)

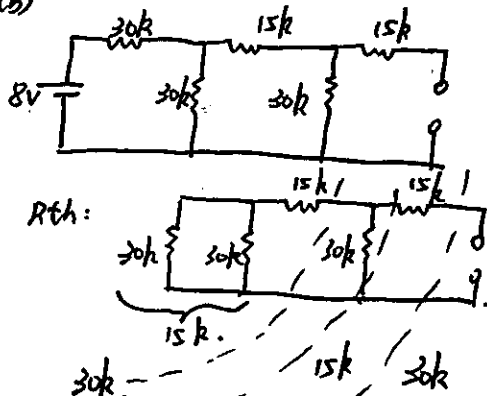

$$\Rightarrow R_{th} = 30k\Omega$$



$$\Rightarrow V_{th} = 2V$$

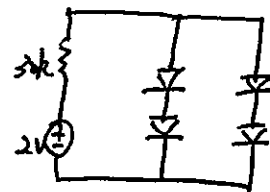

$$I_S = 5 \times 10^{-17} A = 5 \times 10^{-14} mA, n=1, V_T = 26mV, V_D = nV_T \ln(I_D/I_S)$$

$$① V_D = 0.7V \quad 2I_D = 0.02mA \quad I_D = 0.01mA \quad V_{D1} = 0.67656V$$


$$② V_{D1} = 0.67656V \quad 2I_D = 0.02156mA \quad I_D = 0.01078mA \quad V_{D2} = 0.67851V$$

$$③ V_{D2} = 0.67851V \quad 2I_D = 0.02143mA \quad I_D = 0.01072mA \quad V_{D3} = 0.67837V$$


$$④ V_{D3} = 0.67837V \quad 2I_D = 0.02144mA \quad I_D = 0.01072mA \quad V_{D4} = 0.67837V$$

$I_D = 10.7\mu A, 0.678V$   
for  $D_1$  to  $D_4$

2.

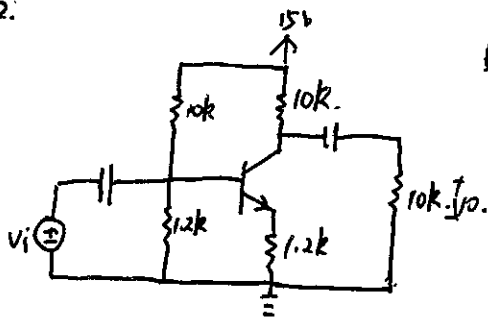

$$\beta = 100 \quad V_A = 80V$$

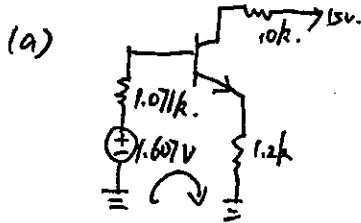

$$1.607 - 1.071 I_E - 1.2 \times 10 I_E + 0.7 = 0$$

$$I_E = 7.418 \times 10^{-3} \text{ mA}$$

$$I_C = 0.7418 \text{ mA}$$


$$V_C = 7.582 \text{ V}$$

$$V_E = 0.899 \text{ V}$$

$$V_{CE} = 6.683 \text{ V}$$

$$\Rightarrow Q(0.7418 \text{ mA}, 6.683 \text{ V})$$

(b)

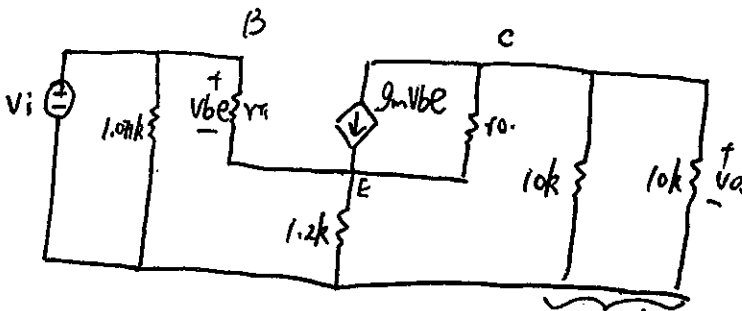

$$g_m = \frac{I_C}{V_T} = 303.28 \text{ ms}$$

$$r_{\pi} = \frac{\beta}{g_m} = 0.333 \text{ k}\Omega$$

$$r_o = \frac{V_A + V_{CE1}}{I_C} = 116.855 \text{ k}\Omega$$

$$A_{vt} = \frac{-g_m R_L'}{1 + g_m R_E} = \frac{-303.28 \times 5}{1 + 303.28 \times 1.2} = -4.155$$

$$\Rightarrow A_V = -4.155$$



$$R_{in} = [r_{\pi} + (\beta + 1) R_E] \parallel R_B = (0.333 + 101 \times 1.2) \parallel 1.071 = 121.533 \parallel 1.071 = 1.0616 \text{ k}\Omega$$

$$R_{out} = \left( 1 + g_m \left( \frac{r_{\pi}}{r_{\pi} + R_{in}} \right) \right) \{ (r_{\pi} + R_{in}) \parallel R_E \} \parallel r_o, \quad R_{th} = 1.071 \text{ k}\Omega$$

$$= \left( 1 + 303.28 \times \frac{0.333}{0.333 + 1.071} \right) \times ((0.333 + 1.071) \parallel 1.2) \parallel 116.855$$

$$= (1 + 71.932 \times 0.647) \parallel 116.855 = 555.29 \text{ k}\Omega$$
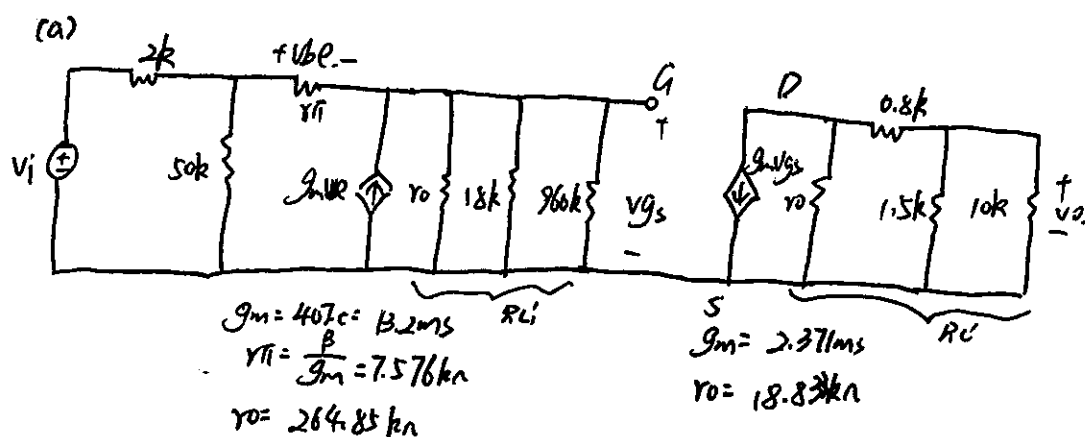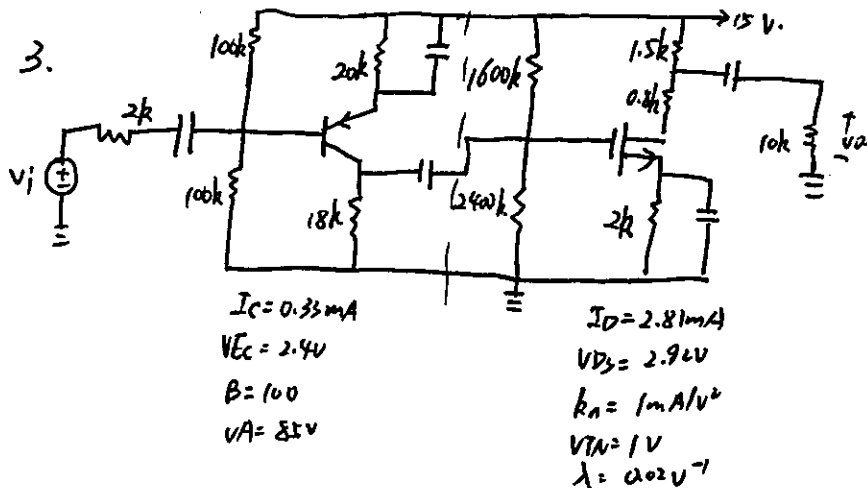
$$(c) A_i = A_V \times \frac{R_L \parallel R_{in}}{R_L} = -4.155 \times \frac{0 + 1.0616}{10} = -0.441$$



$$A_{v1} = -g_m R_{L1}' = -2.371 \times (18.83 \parallel (0.8 + 1.5 \parallel 10)) = -2.371 \times (18.83 \parallel 2.104) = -4.487$$


$$A_{v2} = \frac{g_m R_{L2}'}{1 + g_m R_{L1}'} = \frac{13.2 \times (264.85 \parallel 18 \parallel 960)}{1 + 13.2 \times (264.85 \parallel 18 \parallel 960)} = \frac{218.641}{219.641} = 0.9954$$

$$R_{in} = (r_{\pi} + (\beta + 1) R_{L1}') \parallel 100 \text{ k}\Omega = (7.576 + 101 \times 16.564) \parallel 100 = 1680.54 \parallel 100 = 48.56 \text{ k}\Omega$$

$$\Rightarrow A_v = -4.2897$$

(b)  $R_{in} = 48.56 \text{ k}\Omega$        $R_{out} = 1.5 \parallel (0.8 + 18.83) = 1.394 \text{ k}\Omega$

(c)  $|V_{GS}| \leq 0.2 (V_{GS} - V_{TN})$

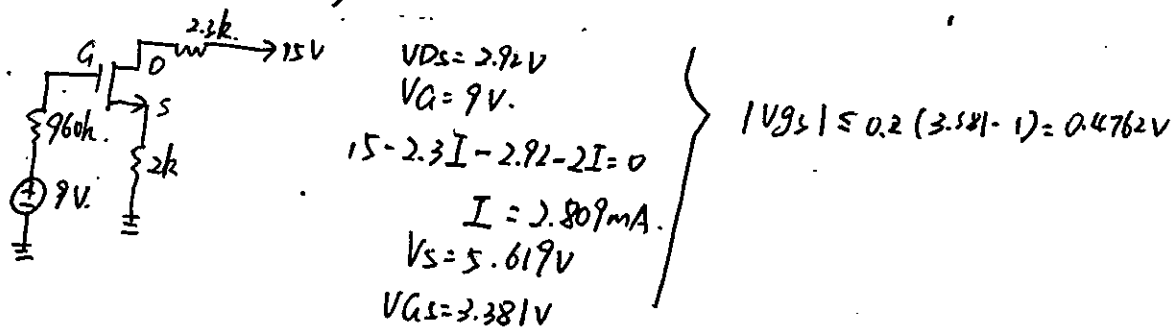

$$|V_{GS}| = |v_i| \times \frac{48.56}{2 + 48.56} \times 0.9954 \Rightarrow |v_i| \leq 0.4981 \text{ V}$$

4.(a)

$$(i) \frac{I_1}{I_0} = \frac{\gamma(1 + V_{CE2}/V_A)}{1 + \frac{V_{BE}}{V_A} + \frac{\beta+1}{\beta}} = \frac{(1 + V_1/V_A)1.1}{1 + \frac{V_{BE}}{V_A} + \frac{\beta+1}{\beta}}$$

$$\frac{I_2}{I_0} = \frac{2(1 + \frac{V_2}{V_A})}{1 + \frac{V_{BE}}{V_A} + \frac{\beta+1}{\beta}}$$

(ii) choose  $Q_1 \Rightarrow r_{O1}$

$$r_{O1} = \frac{V_A + |V_{CE1}|}{I_{C1}} = \frac{50 + 0.7}{I_1}$$

$$I_1 = I_0 \cdot \frac{1.1(1 + 4/50)}{1 + \frac{0.7}{50} + \frac{21}{100}} = 11.478 \mu A$$


$$r_{O1} = 4.417 M\Omega$$

$$(b) \frac{I_1/I_0}{(I_2/I_0)} = \frac{(1 + \lambda V_1)}{(1 + \lambda V_A)}$$

$$(c) R_1 = \frac{1}{I_0} \sqrt{\frac{2I_{REF}}{K_{n1}}} \left( 1 - \sqrt{\frac{I_0(W/L)_0}{I_{REF}(W/L)_1}} \right)$$

$$= \frac{1}{10 \mu A} \sqrt{\frac{2 \times 10 \mu A}{50 \mu A}} \left( 1 - \sqrt{\frac{10}{11}} \right)$$

$$= 2.943 k\Omega$$

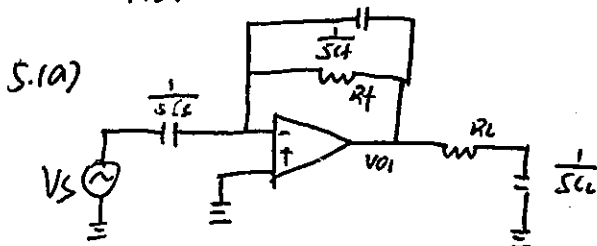

$$\frac{V_{01}}{V_S} = \frac{\frac{1}{SC_S} + \frac{1}{SC_F} || R_f}{\frac{1}{SC_S}} = \frac{\frac{1}{SC_S} + \frac{R_f}{SC_F}}{\frac{1}{SC_S}} = \frac{\frac{1}{C_F} + (R_f + \frac{R_f C_S}{C_F})s}{\frac{1}{C_F} + R_f s} \Rightarrow 1 \text{ pole, 1 zero}$$

$$(b) \frac{V_{out}}{V_{01}} = \frac{\frac{1}{SC_L}}{\frac{1}{SC_L} + R_L} = \frac{\frac{1}{C_L}}{\frac{1}{C_L} + R_L s} \Rightarrow 1 \text{ pole} \Rightarrow \frac{V_{out}}{V_S} = \frac{\frac{1}{C_L} (\frac{1}{C_F} + (R_f + \frac{R_f C_S}{C_F})s)}{(\frac{1}{C_L} + R_L s) (\frac{1}{C_F} + R_f s)}$$

$$(c) \text{poles: } -\frac{1}{R_L C_L} \quad -\frac{1}{R_f C_F}$$

$$\text{zero: } -\frac{1}{R_f + \frac{R_f C_S}{C_F}}$$

$$(d) \text{poles: } -10^3 \quad -10^2$$

