

Lecture 7: Transformers

EE3010: Electrical Devices and Machines

School of Electrical and Electronic Engineering

Associate Professor So Ping Lam

Tel: +65 6790 5026 | Email: episo@ntu.edu.sg

The preceding/ following videos contain slides with materials that were originally used for delivery in lecture halls and/ or classrooms in Nanyang Technological University. They might contain adapted materials. While every effort has been made to undertake due diligence to identify the original source, this was not always possible for all materials. The videos are used solely for educational purposes to support the Technology-Enhanced Learning (TEL) aspects of the course. TEL is hosted and deployed in NTULearn and i-NTULearn, a learning management system accessed by students at NTU assigned with a user ID and password. This disclaimer states that no copyright infringement was intended. Should any disagreement or dispute arise, including any claims to rightful ownership, kindly contact CITS, NTU, at +65 6790 5231.

By the end of this lecture, you should be able to:

- ❖ Describe the operating principles and basic construction of a single-phase transformer.
- ❖ Explain the basic assumptions of an ideal transformer and apply the concepts learnt to derive equations related to the turns ratio.
- ❖ Identify the concepts of referred values and dot convention of a single-phase transformer.

(Chapter 4 - Bhag S. Guru, Electric Machinery and Transformers)

1. Introduction: Construction
2. Basic Principles: Ideal Transformer
3. Practical Transformer: Equivalent Circuit
4. Performance Analysis:
 - i. Regulation
 - ii. Losses and Efficiency

5. Testing: Determination of Parameters
6. Autotransformers
7. Three-phase Transformers:
 - i. Three-phase Transformer Banks
 - ii. Three-phase Transformers

Notations	Description
$V, I, \text{ or } \tilde{V}, \tilde{I}$	Normal letters or letters with the tilde signs above them indicate phasor quantities. The phase angles of these quantities may change with respect to the reference quantity.
$S, Z, \text{ or } \hat{S}, \hat{Z}$	Normal letters or letters with the hat signs above them indicate complex (vector) quantities. The phase angles of these quantities are independent of the reference quantity.
V, I, S, Z	Italic letters indicate the magnitudes of the corresponding phasors or vectors.

- ❖ Revision of concepts on '**Electric Circuits**', '**Three-phase Systems**' and '**Magnetic Circuits**' would be very helpful for this topic.
- ❖ Please refer to the notes on those topics to recall important quantities, their symbols and their units.

❖ A simplest transformer shown in Fig. 1 consists of two coils wound on a common magnetic core:

- Primary winding
- Secondary winding

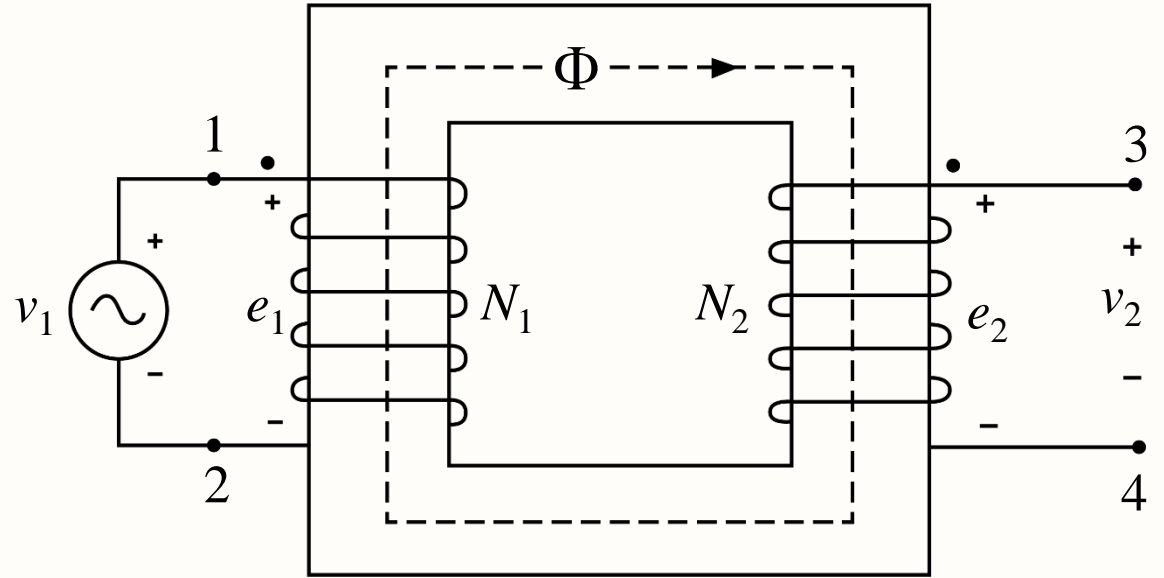


Fig. 1. The simplest transformer.

- ❖ A time varying current produced by a time varying voltage connected to one winding establishes a time varying flux in the coil. The flux links the secondary winding inducing a voltage in the secondary winding.
 - Step-up transformer, e.g., 110 Vac \Rightarrow 220 Vac
 - Step-down transformer, e.g., 220 Vac \Rightarrow 110 Vac
- ❖ Either winding can be connected to the source or the load.
- ❖ Power transfer from one winding to the secondary winding occurs through the magnetic field or magnetic flux in the core.
- ❖ The frequency in the secondary winding is the same as in the primary winding, i.e., $f_1 = f_2$

- ❖ The core is made of thin 'electrical steel' laminations in order to reduce the core (eddy current and hysteresis) losses. The core is of two types (see Figs. 2 and 3):
 - Shell type
 - Core type

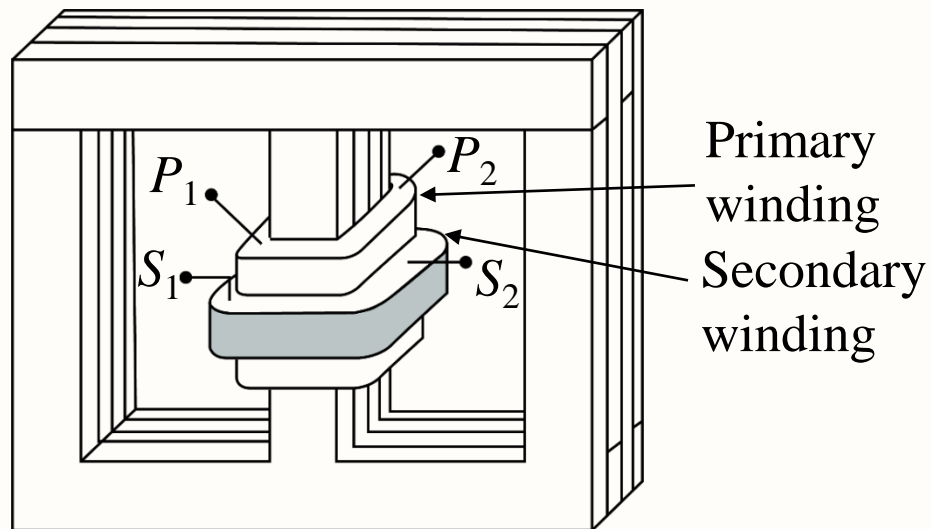


Fig. 2. Shell type transformer.

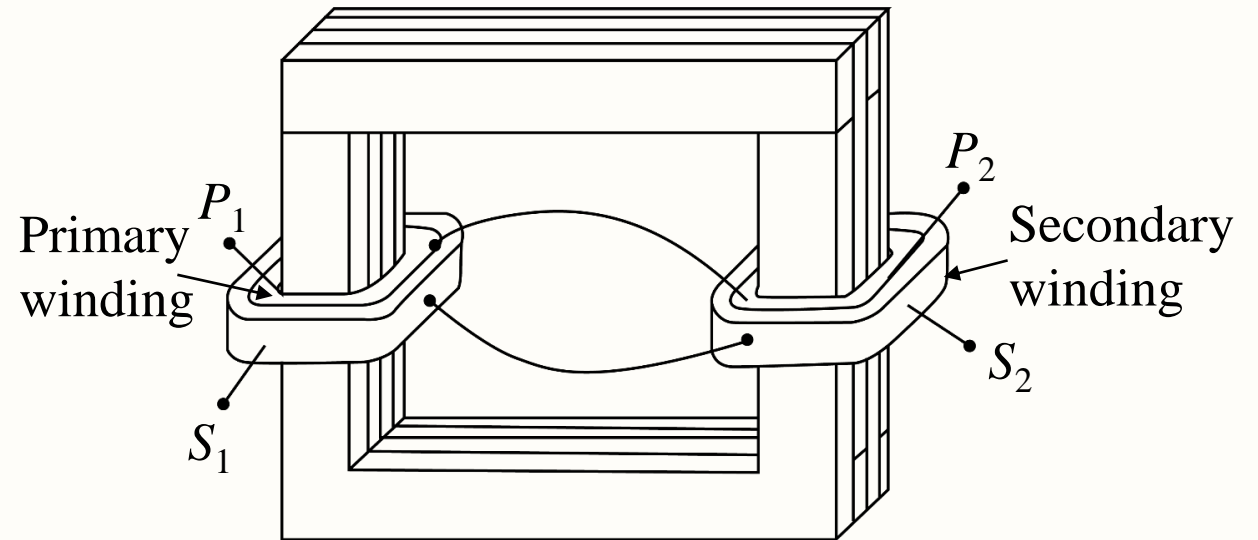


Fig. 3. Core type transformer.

- ❖ The windings may be directly wound on the core in small transformers. However, for high-power transformers, the windings are usually form-wound and then assembled over the core.
- ❖ A cooling system is an integral part of the transformer. Usually, a transformer may be cooled by natural air or forced air circulation. When natural air or forced air circulation is not enough, the whole transformer is immersed in a transformer oil tank.

Primary
windings

Oil tank



Secondary
windings

Cooling
tower

❖ The ideal condition assumptions are:

- The windings have negligible resistance \Rightarrow no copper losses in the windings, no voltage drops.
- All the flux is confined to the core and therefore the same flux links both the windings.
- The permeability of the core is infinitely high, which implies that a vanishingly small mmf (current) is required to set up the flux φ .

$$\text{As } \mu_c \rightarrow \infty, R_c = \left(\frac{l}{\mu_c A} \right) \rightarrow 0, \quad Ni \downarrow = \varphi R_c \downarrow$$

- The core does not incur any hysteresis or eddy current loss \Rightarrow no core losses.

Ideal Transformer

- ❖ If the number of turns in the two windings are N_1 and N_2 as shown in Fig. 4, Faraday's Law gives

$$v_1 = e_1 = N_1 \frac{d\phi}{dt}$$

$$v_2 = e_2 = N_2 \frac{d\phi}{dt}$$

$$\frac{v_1}{v_2} = \frac{e_1}{e_2} = \frac{N_1}{N_2} = a$$

where ' a ' is called the turns ratio.

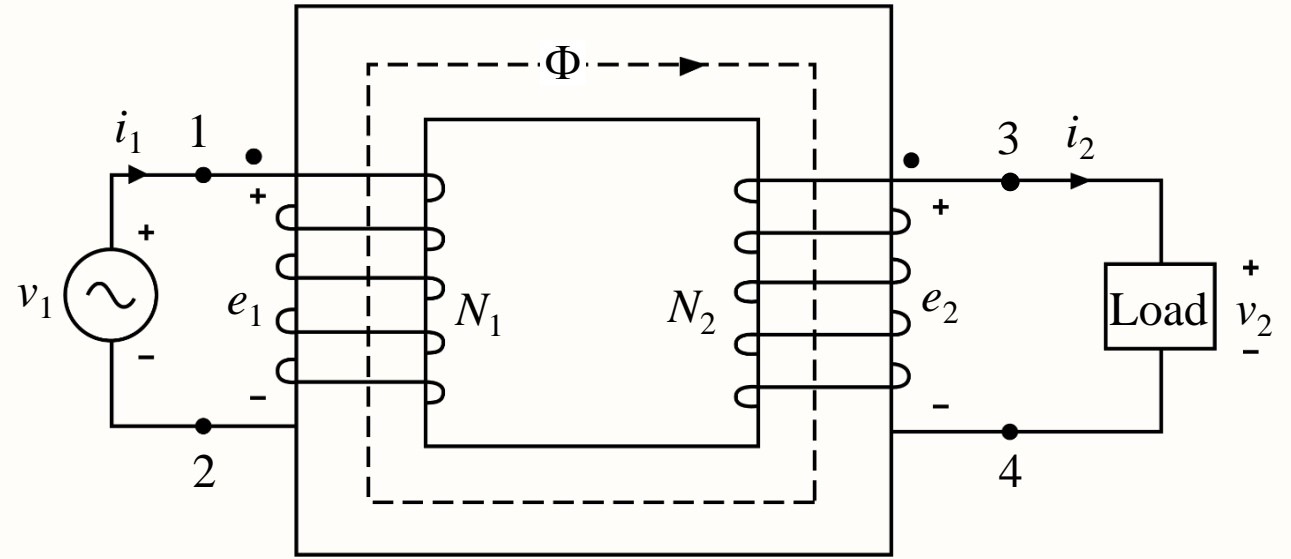


Fig. 4. An ideal transformer under load.

- ❖ As the core material is ideal, the total mmf required to create the flux would be vanishingly small, so that

$$N_1 i_1 - N_2 i_2 = 0 \Rightarrow N_1 i_1 = N_2 i_2 \Rightarrow \frac{i_2}{i_1} = \frac{N_1}{N_2} = a$$

- ❖ From the above two equations,

$$\frac{v_1}{v_2} = a = \frac{i_2}{i_1} \Rightarrow v_1 i_1 = v_2 i_2$$

- ❖ Expressing these equations in effective or rms quantities,

$$\frac{V_1}{V_2} = a, \quad \frac{I_2}{I_1} = a, \quad \text{and, } V_1 I_1^* = V_2 I_2^* \quad (\text{also } V_1 I_1 = V_2 I_2)$$

Ideal Transformer

- ❖ An ideal transformer connected to a source on one side and a load on the other side can be schematically represented as shown in Fig. 5, where

$$\frac{V_1}{V_2} = \frac{E_1}{E_2} = a, \text{ and } \frac{I_2}{I_1} = a \Rightarrow \frac{I_2}{a} = I_1$$

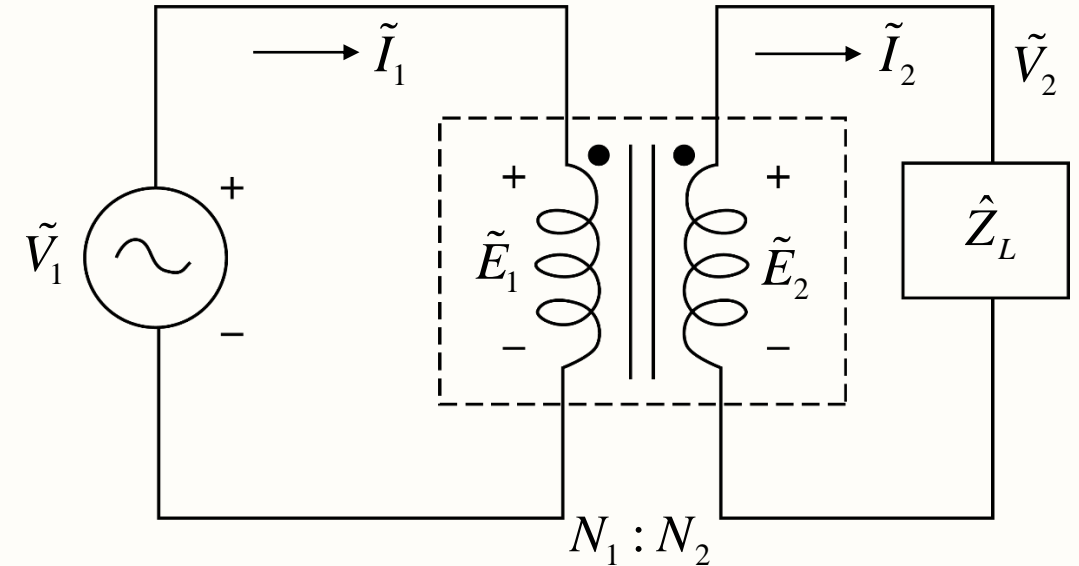


Fig. 5. An ideal transformer connected to a source and a load.

Referred Values

- ❖ As shown in Fig. 6, for a voltage V_2 in the secondary side of the transformer, the primary voltage will be: $V_1 = aV_2 = V_2'$
- ❖ For a current I_2 in the secondary side, the current in the primary will be:

$$I_1 = \frac{I_2}{a} = I_2'$$

- ❖ V_2' and I_2' are called the referred values of V_2 and I_2 referred to the primary side respectively.

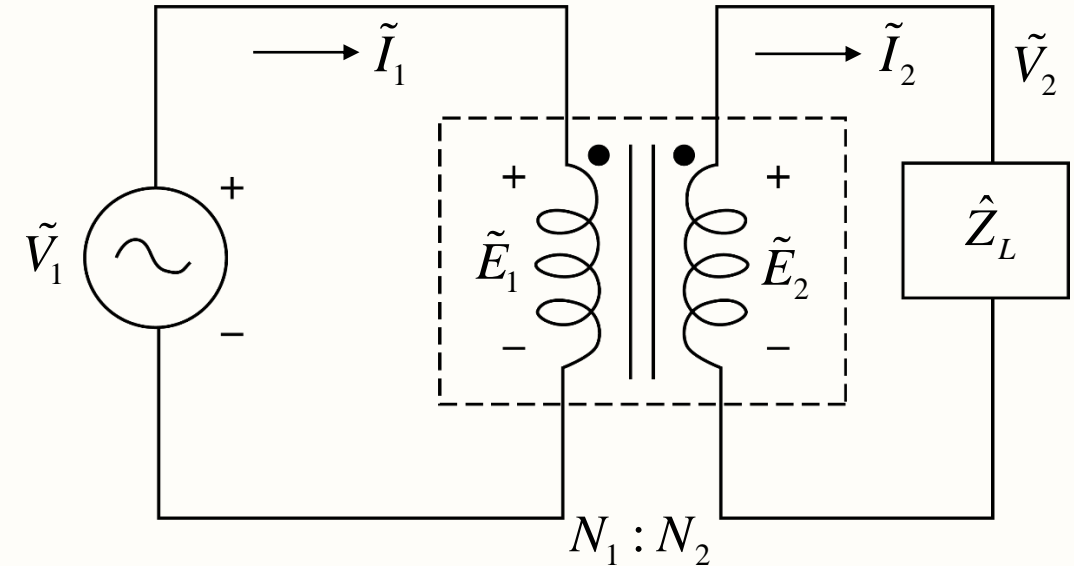


Fig. 6. An ideal transformer.

- ❖ If Z_2 is the load impedance on the secondary side, then

$$Z_2 = \frac{V_2}{I_2}$$

- ❖ On the primary side the impedance will appear to be

$$Z_1 = \frac{V_1}{I_1} = \frac{aV_2}{I_2 / a} = a^2 \frac{V_2}{I_2} = a^2 Z_2 = Z_2'$$

Z_2' is the referred value of Z_2 referred to the primary side.

- ❖ Similarly, V_1 , I_1 , and Z_1 when referred to the secondary side become

$$V_1' = \frac{V_1}{a}, \quad I_1' = aI_1, \quad \text{and} \quad Z_1' = \frac{Z_1}{a^2}$$

Transformer Polarity – Dot Convention

- ❖ It is very important to know the polarity (i.e., the relative direction of induced voltages) of transformer windings to make proper circuit connections.
- ❖ For the connections shown in Fig. 7:
 - e_1 has to oppose v_1 , and so terminal **1** is positive with respect to terminal **2** on side 1.

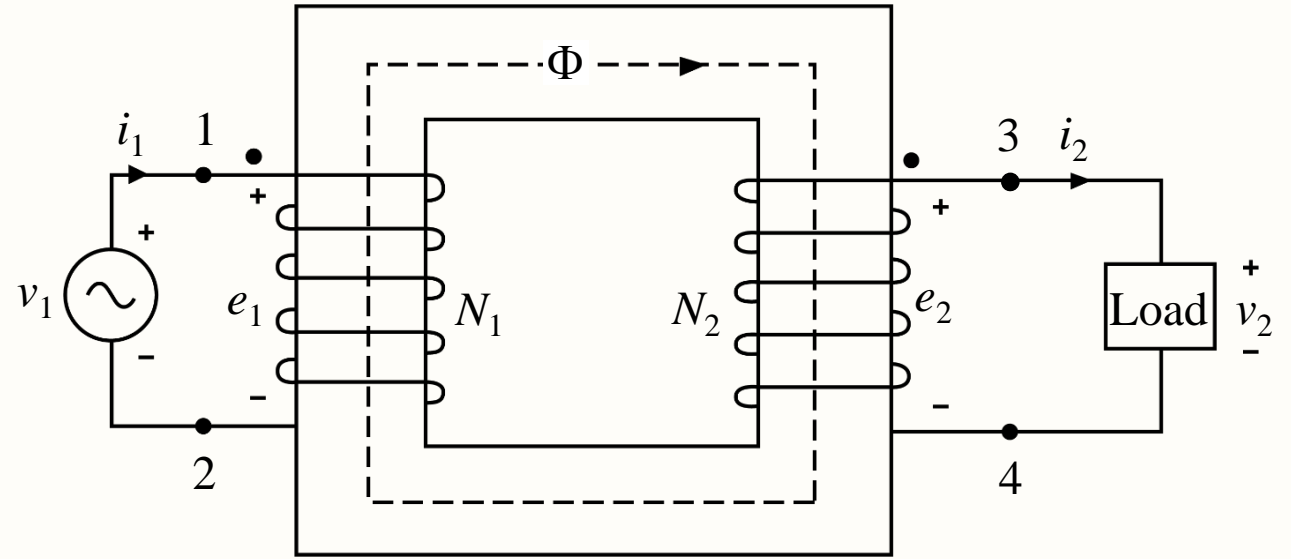


Fig. 7. An ideal transformer under load.

Transformer Polarity – Dot Convention

- The current i_2 on side 2 has to oppose the flux ϕ created by i_1 , so that i_2 will flow in the direction as shown in Fig. 7, for the direction of the winding shown in Fig. 6. Therefore, terminal **3** is positive with respect to terminal **4** on side 2.
 - Thus, terminals **1** and **3** are of like polarity (positive in this case), and so are terminals **2** and **4** (negative).
- ❖ Therefore, terminals **1** and **3** are marked by similar ‘dots’ as shown.

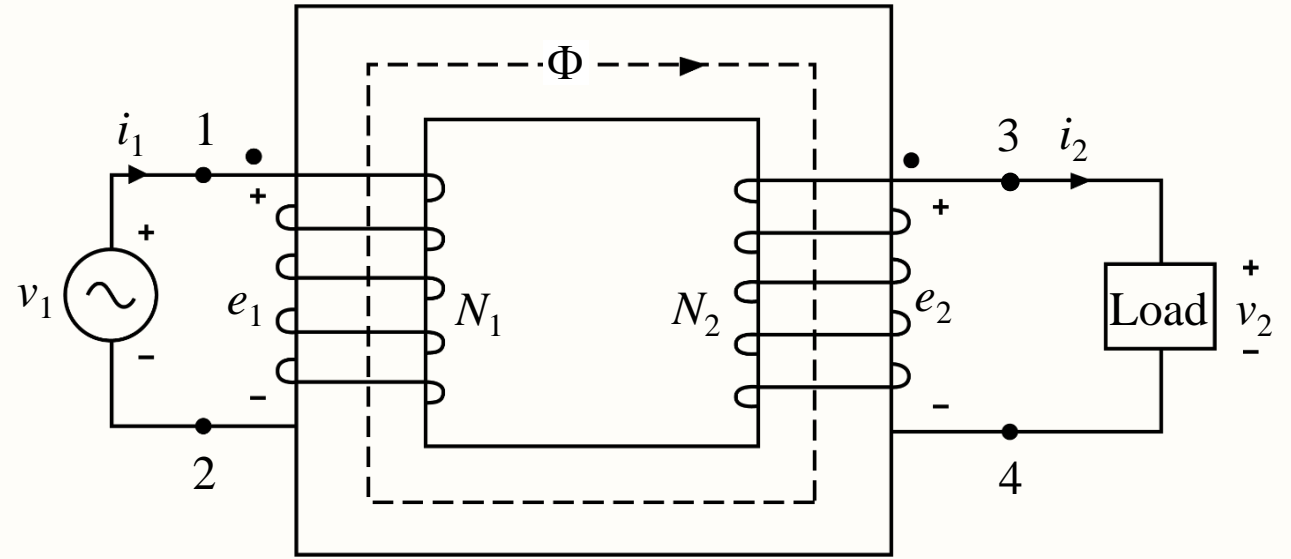


Fig. 7. An ideal transformer under load.

Transformer Polarity – Dot Convention

- ❖ It should be noted that the terminal polarity depends on actual directions of the windings on the core. If the direction of the secondary winding is changed as shown in Fig. 8, the direction of the secondary current and therefore the polarity of the secondary terminals will change as shown.

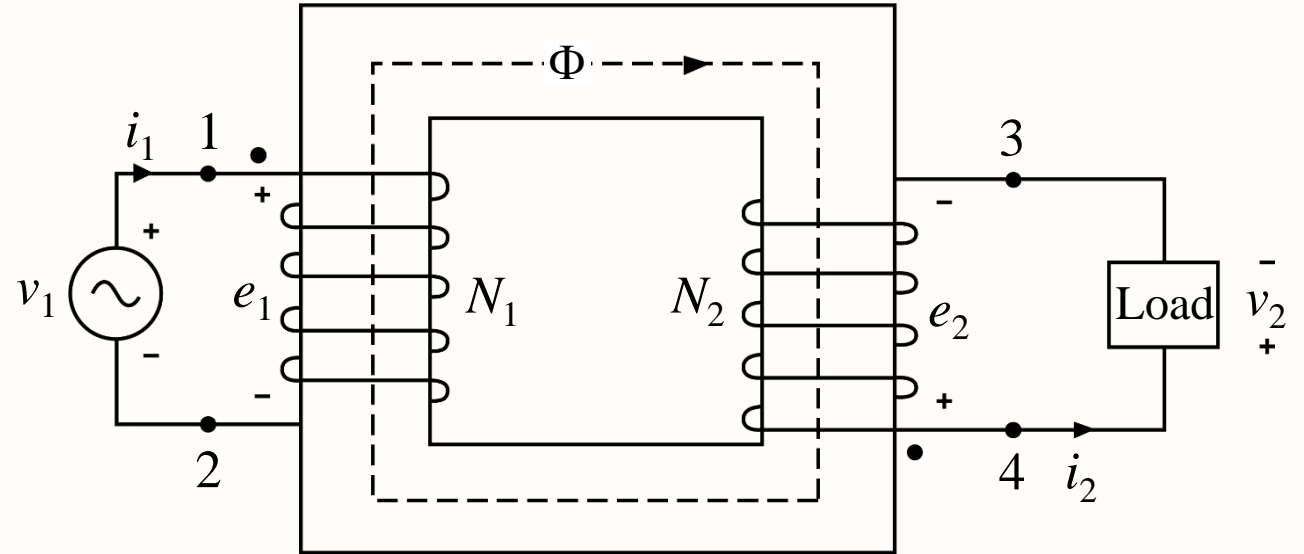


Fig. 8. An ideal transformer under load.




Transformer Polarity – Dot Convention



- ❖ But the windings are hidden inside the tank and the winding directions will not be visible in practice. Therefore, terminals with like polarities are indicated by similar 'dots' as shown, outside the transformer tank itself. This practice is known as '**Dot-convention**', which basically means that the terminals with similar 'dots' will have the same polarity.
- ❖ It should also be noted that, while the current enters the positive terminal of transformer winding on the source side, the current comes out of the positive terminal on the load side.

In this lecture, you have learnt:

- ❖ The operating principles and basic construction of a single-phase transformer.
- ❖ The basic assumptions of an ideal transformer and the concepts learnt to derive equations related to the turns ratio.
- ❖ The concepts of referred values and dot convention of a single-phase transformer.

References

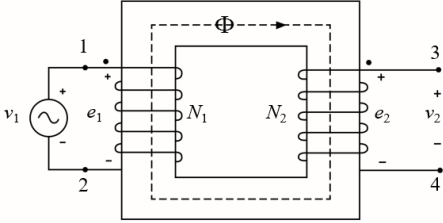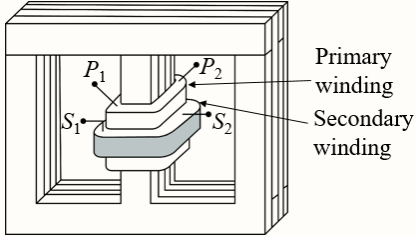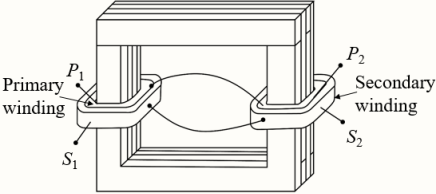No.	Slide No.	Image	Reference
1	8		Reprinted from <i>Electric Machinery and Transformers, 3rd ed.</i> , (p. 205), by B. S. Guru, & H. R. Hiziroglu, 2001, New York, NY: Oxford University Press. Copyright 2001 by Oxford University Press.
2	10		Reprinted from <i>Electric Machinery and Transformers, 3rd ed.</i> , (p. 204), by B. S. Guru, & H. R. Hiziroglu, 2001, New York, NY: Oxford University Press. Copyright 2001 by Oxford University Press.
3	10		Reprinted from <i>Electric Machinery and Transformers, 3rd ed.</i> , (p. 205), by B. S. Guru, & H. R. Hiziroglu, 2001, New York, NY: Oxford University Press. Copyright 2001 by Oxford University Press.

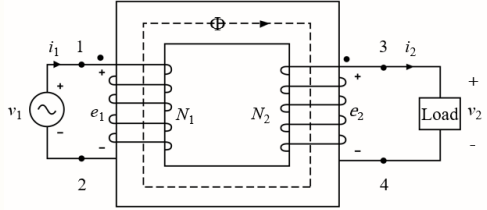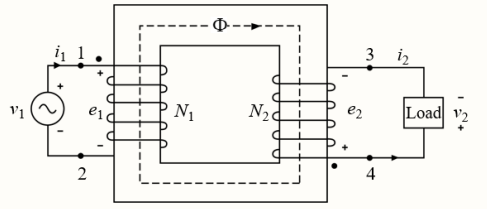No.	Slide No.	Image	Reference
4	14, 19 and 20		Reprinted from <i>Electric Machinery and Transformers, 3rd ed.</i> , (p. 207), by B. S. Guru, & H. R. Hiziroglu, 2001, New York, NY: Oxford University Press. Copyright 2001 by Oxford University Press. Reprinted with permission.
5	21		Reprinted from <i>Electric Machinery and Transformers, 3rd ed.</i> , (p. 207), by B. S. Guru, & H. R. Hiziroglu, 2001, New York, NY: Oxford University Press. Copyright 2001 by Oxford University Press. Reprinted with permission.