
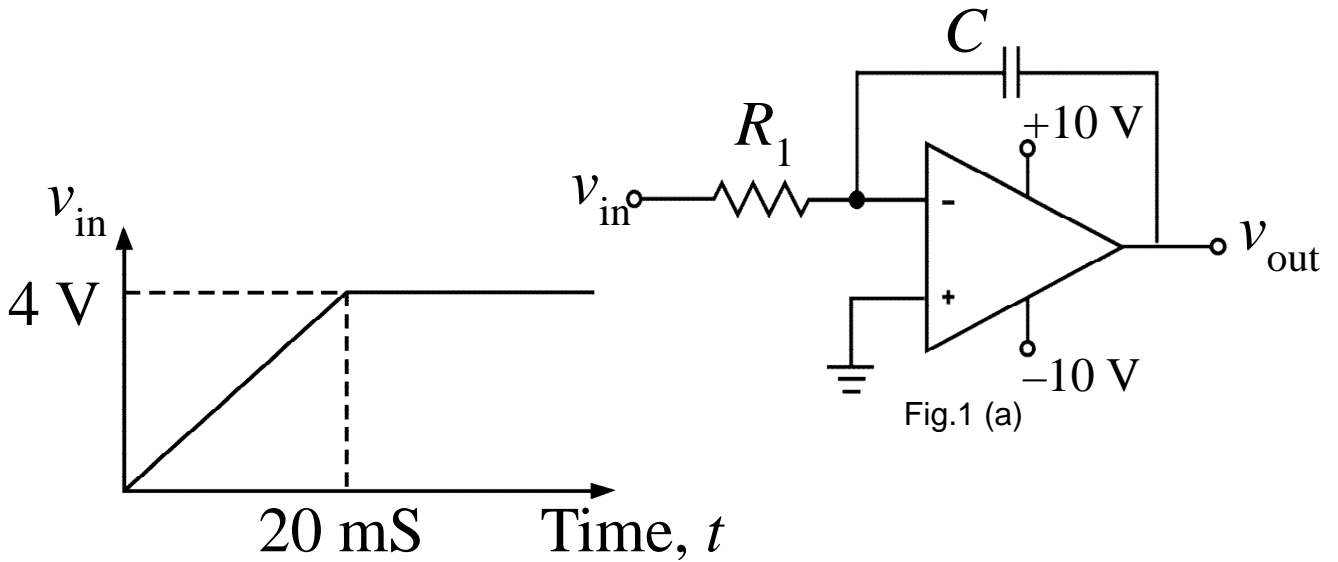


EE2002 Tutorial 4

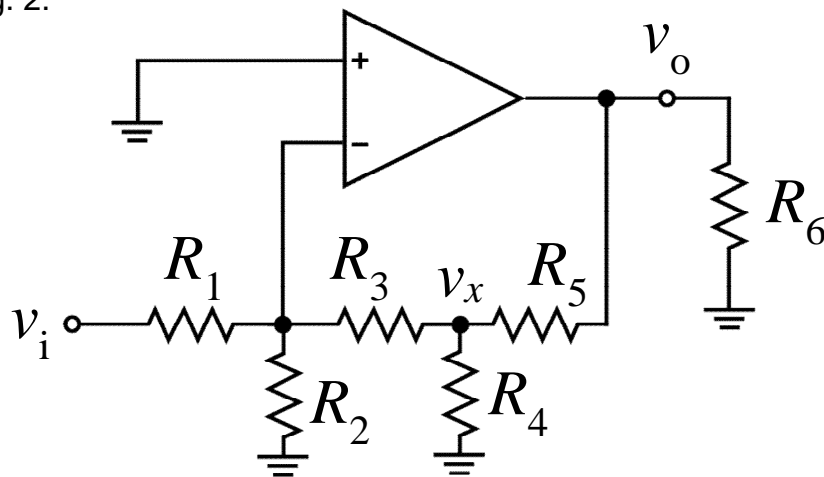- Plot the output, v_{out} , of the inverting integrator in Fig. 1(a) using an ideal op-amp if v_{in} is a ramp that levels off at the value $v_{in} = 4$ V after 20 mS as in Fig 1(b). For the inverting integrator, $R_1 = 5$ k Ω and $C = 1$ μ F. Assume the initial output is zero and the power supply voltages for the op-amp are ± 10 V.



- Find the closed loop Gain of the negative feedback opamp circuit, $A_{VCL} = v_o/v_i$ in Fig. 2.



3. For the circuit in Fig. 3 commonly known as an absolute value circuit, given that R_1 , R_2 and R_3 are of the same value R , and R_4 and R_5 are of value $2R$. Determine the peak magnitude of v_{out} and also sketch the expected waveform of v_{out} , given that the sinewave input voltage, v_{in} is $2V_{pk-pk}$ at an arbitrary frequency. The OpAmps are ideal and the diodes are treated in simple diode model with $V_D = 0.7V$.


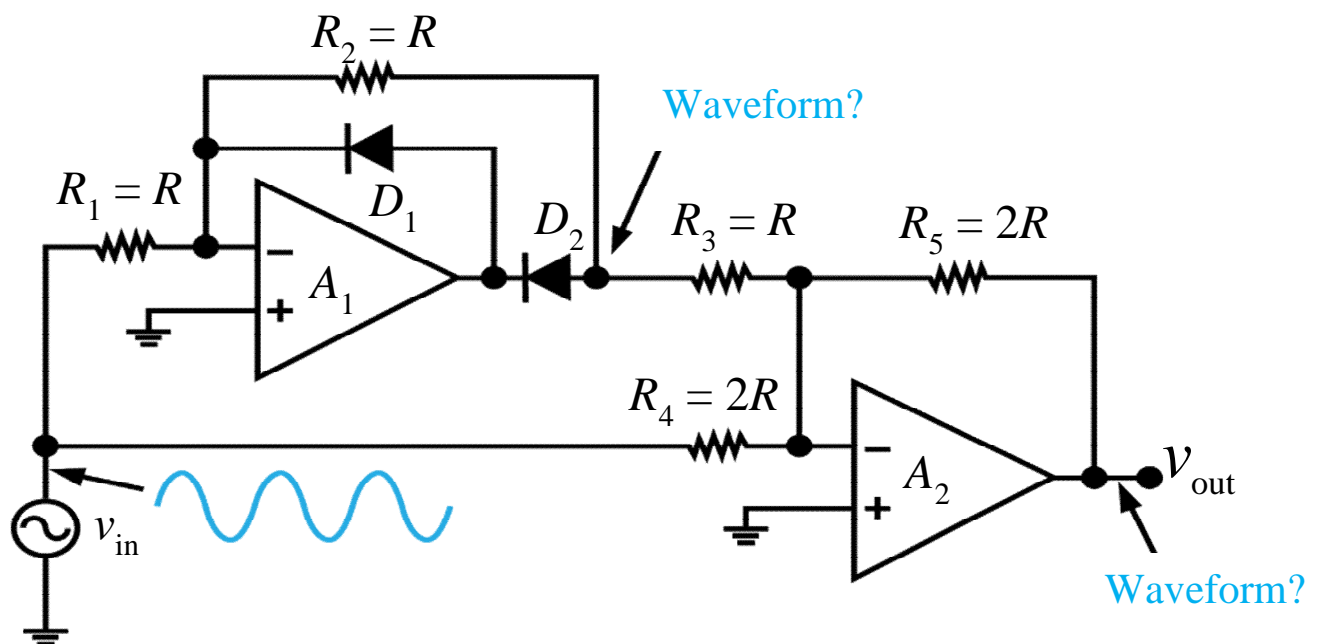


Fig. 3

Answers to Tutorial 4

1.

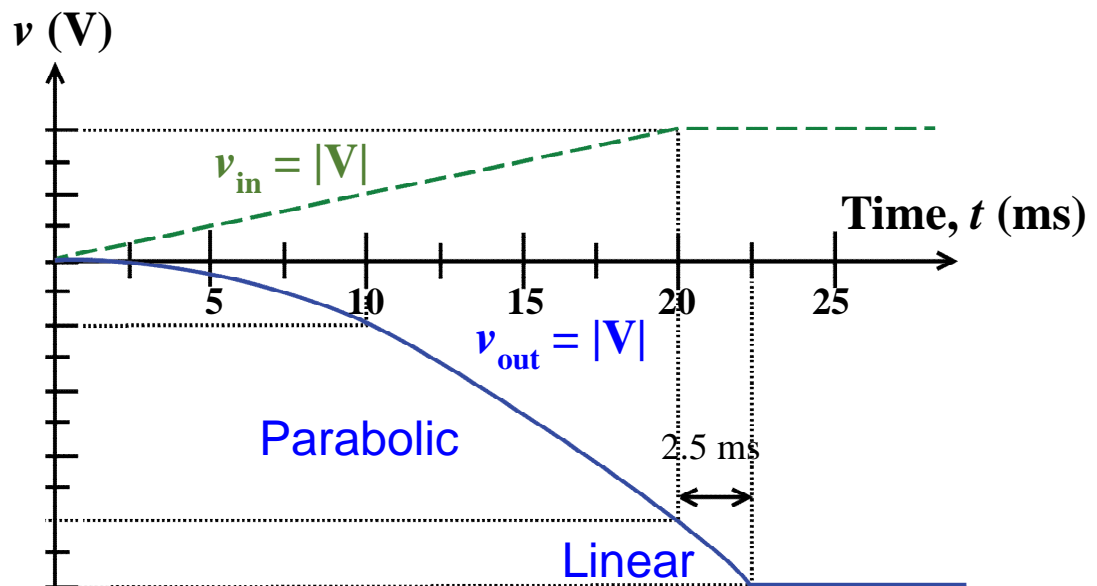

2.

$$\frac{V_o}{V_i} = -\frac{R_3}{R_1} \times \frac{R_5 + R_3 // R_4}{R_3 // R_4}$$

3.

$V_{out} = |V_{in}|$ = rippled DC output voltage with 1 V peak

