



# INTEGRATED ELECTRONICS

**Y. P. Zhang, PhD, FIEEE**

**Office: S2-B2c-90**

**[eypzhang@ntu.edu.sg](mailto:eypzhang@ntu.edu.sg)**


**Tel: 6790-4945**

**Joseph Chang**

**Office: S1-B1b-60**


**[ejschang@ntu.edu.sg](mailto:ejschang@ntu.edu.sg)**

**Tel: 6790-4424**

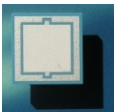


# Topics

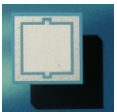- 1. Power Supplies**
- 2. Bias Circuits**
- 3. Operational Amplifiers**
- 4. Applications of Operational Amplifiers**



# Reference Textbooks

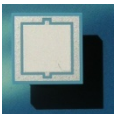
1. Sedra and Smith, *Microelectronic Circuits*, 5th Edition, Oxford University Press, 2004.
2. Gray, Hurst, Lewis and Meyer, *Analysis and Design of Analogue Integrated Circuits*, 4th Edition, John Wiley & Sons, 2001.
3. Franco S, *Design with Operational Amplifiers and Analog Integrated Circuits*, 3rd Edition, McGraw-Hill, 2002.







# Applications of Operational Amplifiers

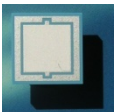1. Introduction
2. Amplifier
3. Summer and Subtractor
4. Integrator and Differentiator
5. Active filter
6. Switched capacitor filter
7. Precision rectifier
8. Comparator
9. Schmitt Trigger
10. Oscillator
11. Sample-and-Hold




# Introduction

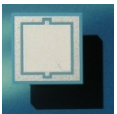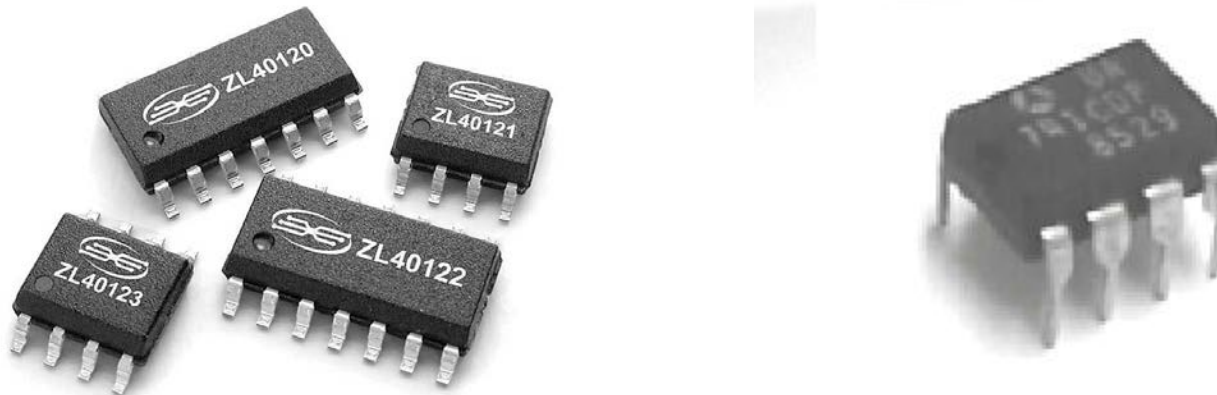**As we know that the term operational amplifier is presently applied to a general class of high-gain, direct coupled, monolithic integrated circuit amplifiers. These Op Amps can be easily used in many applications such as inverting, non-inverting, and differential amplifiers, summer, integrator, differentiator, filter, comparator, and etc.**






# Amplifier

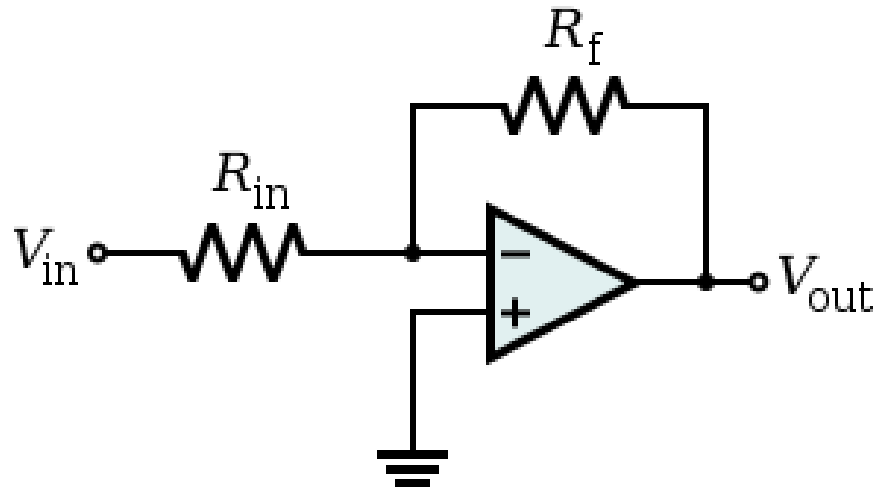


$$V_{\text{out}} = -V_{\text{in}}(R_f/R_{\text{in}})$$

**Inverting configuration**

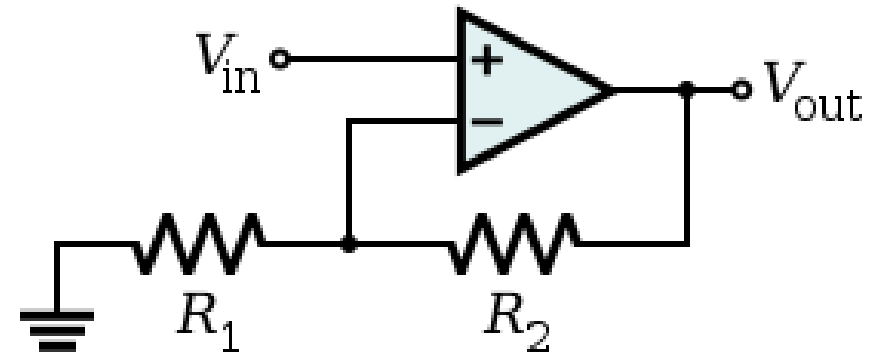


$$V_{\text{out}} = V_{\text{in}} \left( 1 + \frac{R_2}{R_1} \right)$$

**Non-inverting configuration**

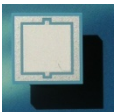

# Summer and Subtractor

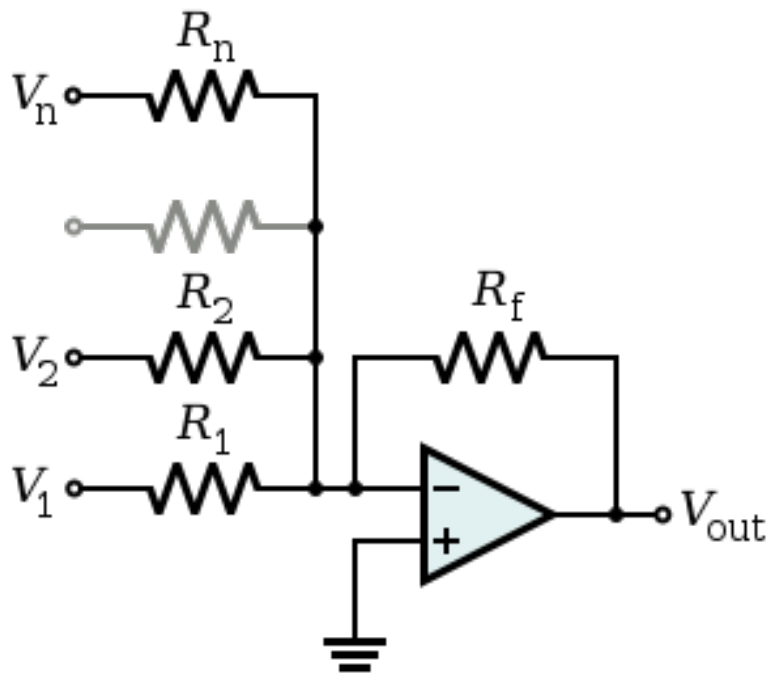

Summer


$$V_{out} = -R_f \left( \frac{V_1}{R_1} + \frac{V_2}{R_2} + \cdots + \frac{V_n}{R_n} \right)$$

When  $R_1 = R_2 = \dots = R_n$ , and  $R_f$  independent


$$V_{out} = -\frac{R_f}{R_1} (V_1 + V_2 + \cdots + V_n)$$

When  $R_1 = R_2 = \dots = R_n = R_f$
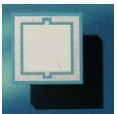
$$V_{out} = -(V_1 + V_2 + \cdots + V_n)$$



# Summer and Subtractor

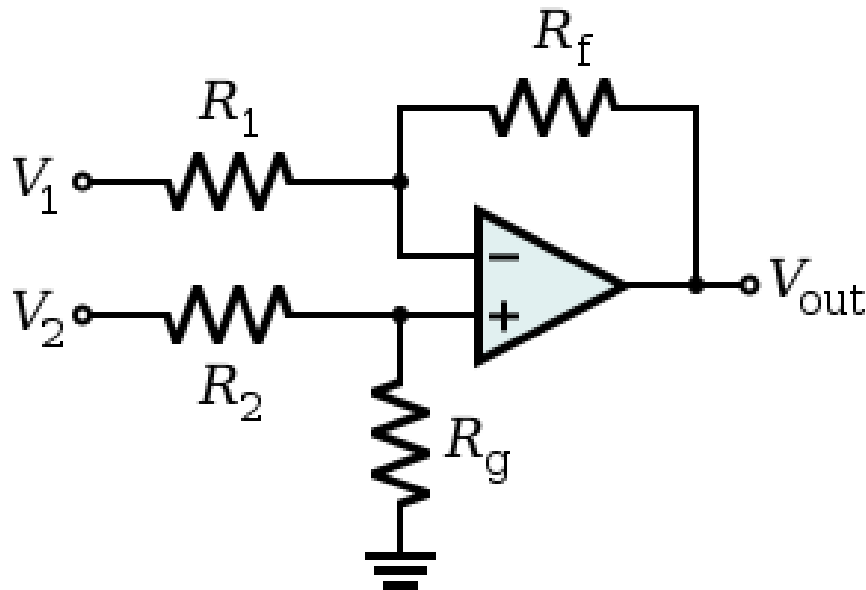

**Subtractor**


$$V_{out} = V_2 \left( \frac{(R_f + R_1) R_g}{(R_g + R_2) R_1} \right) - V_1 \left( \frac{R_f}{R_1} \right)$$

When  $R_1 = R_2$  and  $R_g = R_f$

$$V_{out} = \frac{R_f}{R_1} (V_2 - V_1)$$

When  $R_1 = R_f$  and  $R_2 = R_g$


$$V_{out} = (V_2 - V_1)$$

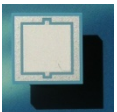






# Integrator and Differentiator

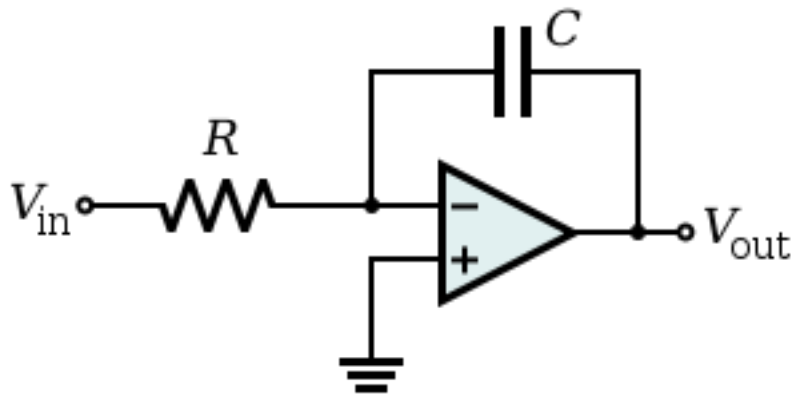


$$V_{out} = - \int_0^t \frac{V_{in}}{RC} dt + V_{initial}$$

Integrator

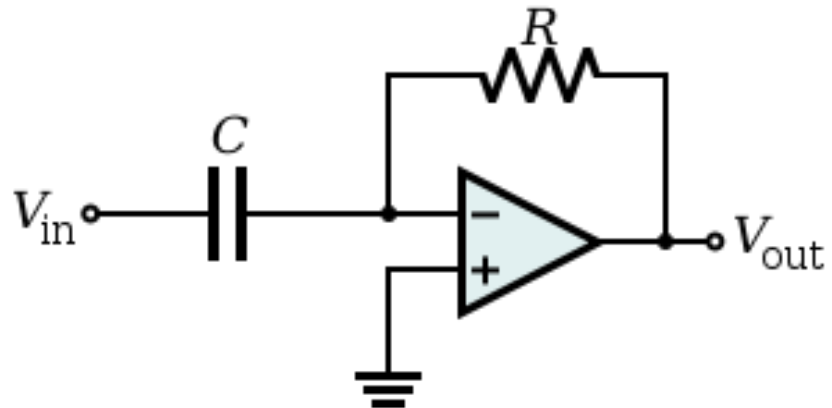


$$V_{out} = -RC \frac{dV_{in}}{dt}$$

Differentiator

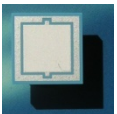


# Active Filter

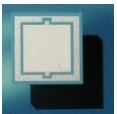**A filter separates signal from additive noise or competing signals by selectively passing the desired frequencies while attenuating undesired frequencies. The active-RC filters and switched-capacitor (SC) filters make use of op amp. Most integrated monolithic filters are based on switched-capacitor technique.**




# Active Filter

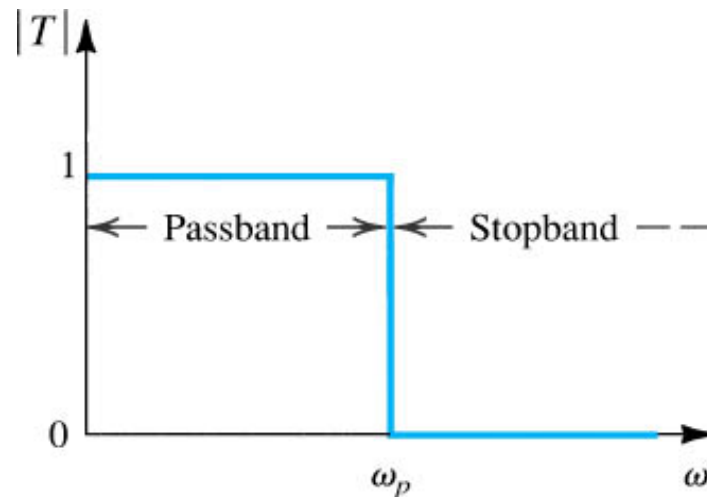
**Frequency selection function: Passband (unity transmission); Stopband (zero transmission). Low-pass (LP), high-pass (HP), bandpass (BP) and bandstop (BS).**



(a) Low-pass (LP)

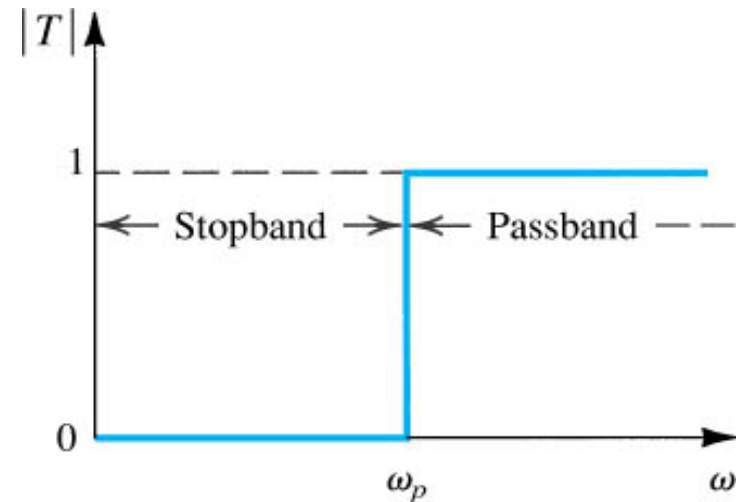


(b) High-pass (HP)

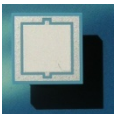


# Active Filter

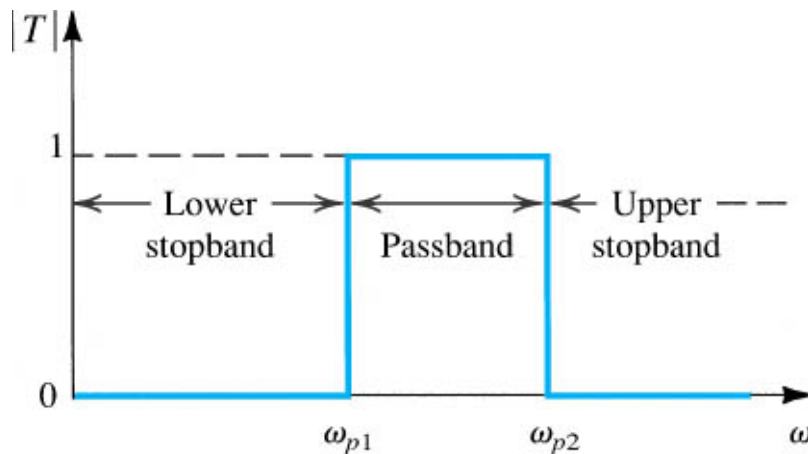
**These idealized features as demonstrated in the vertical edges are known as brick-wall responses. Can never be realized with physical circuits.**



(c) Bandpass (BP)

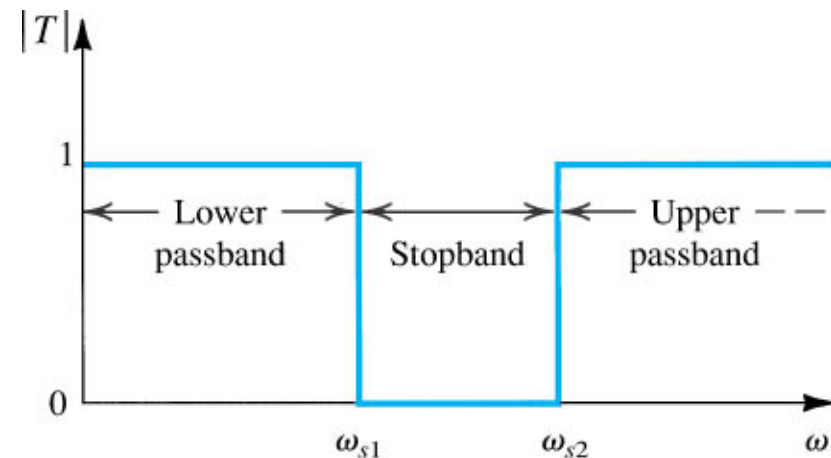

(d) Bandstop (BS)

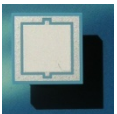

# Active Filter



**The 4 main parameters:**

**Passband edge:  $\omega_p$**

**Max. passband ripple:  $A_{max}$**



**Stopband edge:  $\omega_s$**

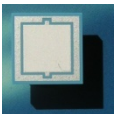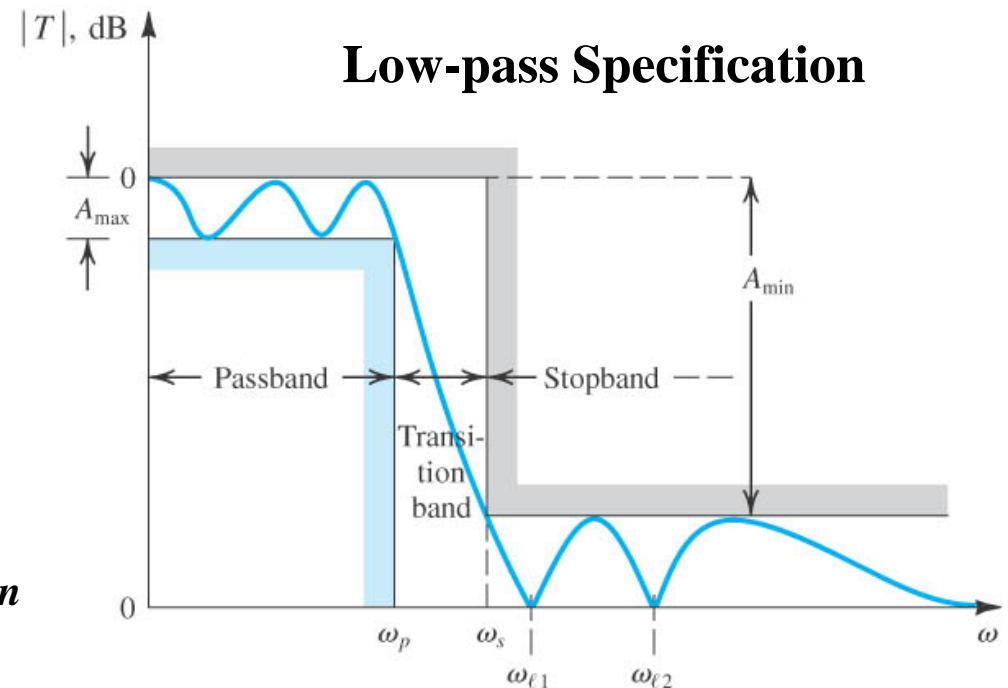**Min. stopband attenuation:  $A_{min}$**





# Active Filter

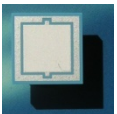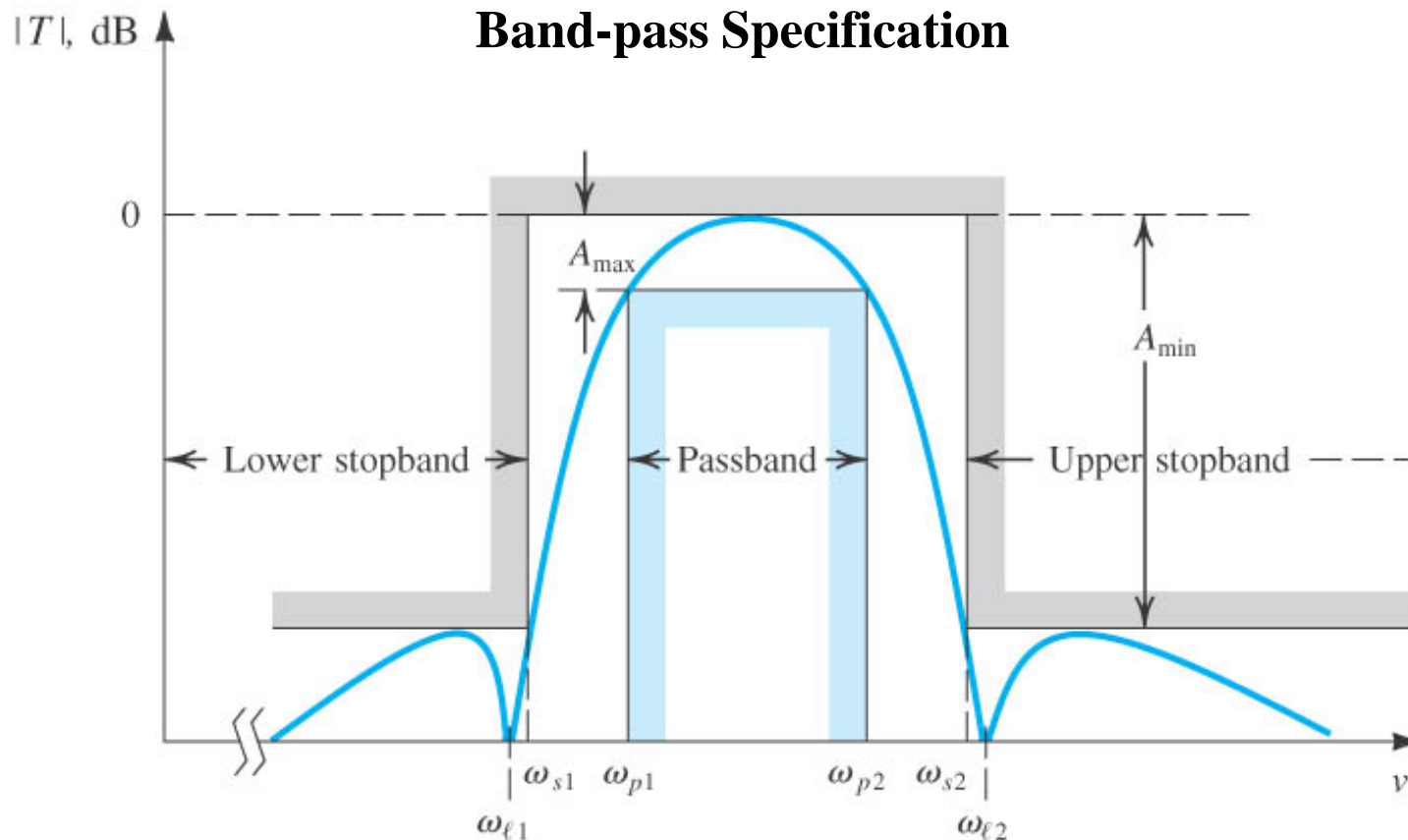


# Active Filter

The filter transfer function  $T(s)$  can be written as a ratio of two polynomials:

$$T(s) = \frac{a_M s^M + a_{M-1} s^{M-1} + \cdots + a_0}{s^N + b_{N-1} s^{N-1} + \cdots + b_0}$$

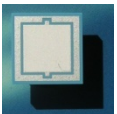The degree of denominator,  $N$ , is the filter order. For filter to be stable,  $M \leq N$ . The coefficients  $a_0, a_1, \dots, a_M$  and  $b_0, b_1, \dots, b_{N-1}$  are real numbers.




# Active Filter

The polynomials can be factored and  $T(s)$  can also be expressed as:

$$T(s) = \frac{a_M (s - z_1)(s - z_2) \cdots (s - z_M)}{(s - p_1)(s - p_2) \cdots (s - p_N)}$$

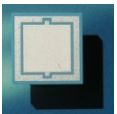The numerator roots,  $z_1, z_2, \dots, z_M$ , are the transfer function zeros or transmission zeros. The denominator roots,  $p_1, p_2, \dots, p_M$ , are the transfer function poles or natural modes. For filter to be stable, all poles must lie in the left half of the  $s$  plane.






# Active Filter

**Example 1:** A fourth-order filter has zeros  $\pm j2$ . The poles are  $-0.6 \pm j0.8$  and  $-0.9 \pm j1.2$ . The dc gain is 8. Find  $T(s)$ .

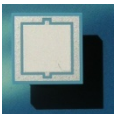**From the given information,**

$$\begin{aligned} T(s) &= \frac{a_2(s + j2)(s - j2)}{(s + 0.6 - j0.8)(s + 0.6 + j0.8)(s + 0.9 - j1.2)(s + 0.9 + j1.2)} \\ &= \frac{a_2(s^2 + 4)}{(s^2 + 1.2s + 1)(s^2 + 1.8s + 1.5)} \end{aligned}$$




# Active Filter

**At dc,  $\omega=0$  and solving for dc gain=8 we have:**

$$T(s=0) = \frac{a_2(0+4)}{(0+0+1)(0+0+1.5)} = 8 \Rightarrow a_2 = 3$$

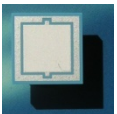**Hence the overall transfer function  $T(s)$  is:**

$$T(s) = \frac{3(s^2 + 4)}{(s^2 + 1.2s + 1)(s^2 + 1.8s + 1.5)}$$



# Active Filter


**The general first-order filter transfer function is given by:**

$$T(s) = \frac{a_1 s + a_0}{s + \omega_0}$$

**Pole at  $s = -\omega_0$  and transmission zero at  $s = -a_0/a_1$ . The high frequency gain approaches  $a_1$ . The numerator coefficients  $a_1$  and  $a_0$  determine whether the filter is low pass or high pass.**

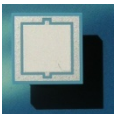**The general second-order filter transfer function is given by:**

$$T(s) = \frac{a_2 s^2 + a_1 s + a_0}{s^2 + (\omega_0 / Q)s + \omega_0^2}$$



# Active Filter


The numerator coefficients  $a_2$ ,  $a_1$  and  $a_0$  determine the filter types.

If  $a_2=a_1=0$  and  $a_0\neq 0 \rightarrow$  low-pass filter.

If  $a_1=a_0=0$  and  $a_2\neq 0 \rightarrow$  high-pass filter.


If  $a_2=a_0=0$  and  $a_1\neq 0 \rightarrow$  band-pass filter.

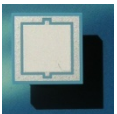We can cascade a number of first-order and/or second-order filters to realize high-order ( $N\geq 3$ ) filters. For example, to realize a 5<sup>th</sup>-order filter, we can cascade a first-order and two second-order filters.




# Active Filter
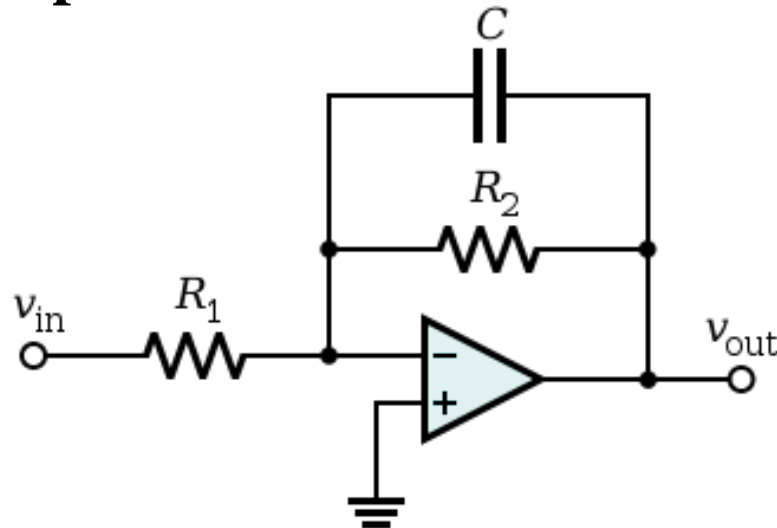
## Implementation of the first-order active filter




$$T(s) = \frac{V_{out}(s)}{V_{in}(s)} = -\frac{R_2 // \frac{1}{sC}}{R_1} = -\frac{R_2}{R_1} \frac{\omega_c}{s + \omega_c}$$

$$\omega_c = \frac{1}{R_2 C}$$

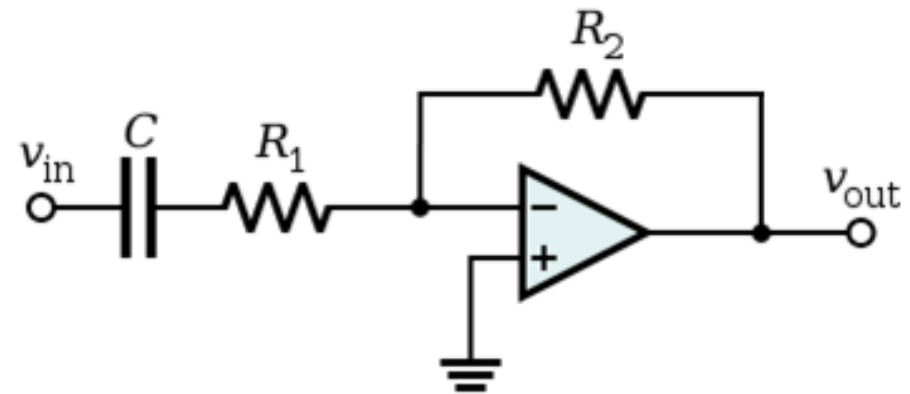


$$T(s) = \frac{V_{out}(s)}{V_{in}(s)} = -\frac{R_2}{R_1 + \frac{1}{sC}} = -\frac{R_2}{R_1} \frac{s}{s + \omega_c}$$

$$\omega_c = \frac{1}{R_1 C}$$

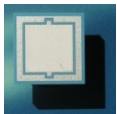

# Active Filter
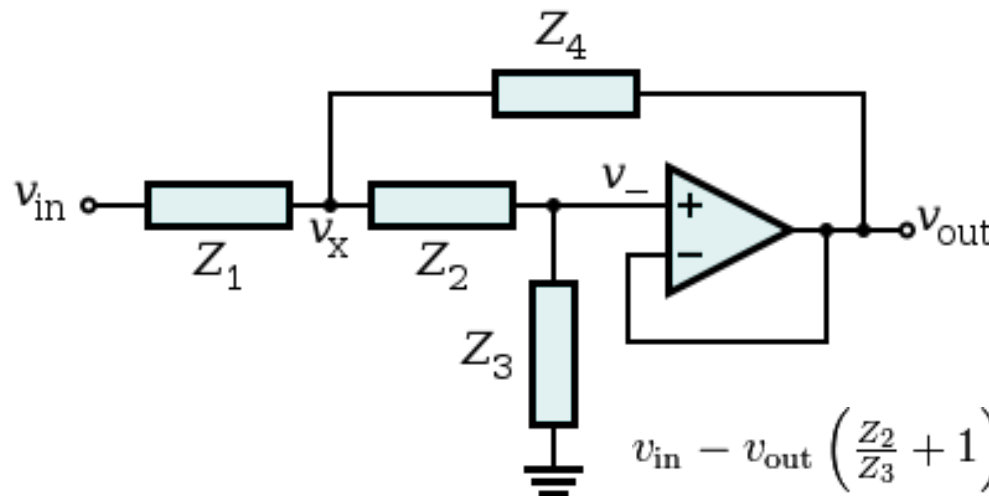
## Implementation of the second-order active filter




$$\frac{v_{in} - v_x}{Z_1} = \frac{v_x - v_{out}}{Z_4} + \frac{v_x - v_{out}}{Z_2}$$

$$\frac{v_x - v_{out}}{Z_2} = \frac{v_{out}}{Z_3}, \quad v_x = v_{out} \left( \frac{Z_2}{Z_3} + 1 \right).$$

$$\frac{v_{in} - v_{out} \left( \frac{Z_2}{Z_3} + 1 \right)}{Z_1} = \frac{v_{out} \left( \frac{Z_2}{Z_3} + 1 \right) - v_{out}}{Z_4} + \frac{v_{out} \left( \frac{Z_2}{Z_3} + 1 \right) - v_{out}}{Z_2}.$$

$$v_+ = v_- = v_{out}.$$
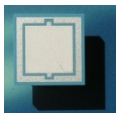
$$\frac{v_{in} - v_x}{Z_1} = \frac{v_x - v_{out}}{Z_4} + \frac{v_x - v_-}{Z_2}, \quad \frac{v_{out}}{v_{in}} = \frac{Z_3 Z_4}{Z_1 Z_2 + Z_4 (Z_1 + Z_2) + Z_3 Z_4},$$



# Active Filter


## Implementation of the second-order active filter

Let  $Z_1 = R_1$

$$Z_2 = R_2$$


$$Z_3 = \frac{1}{sC_2}$$

$$Z_4 = \frac{1}{sC_1}$$

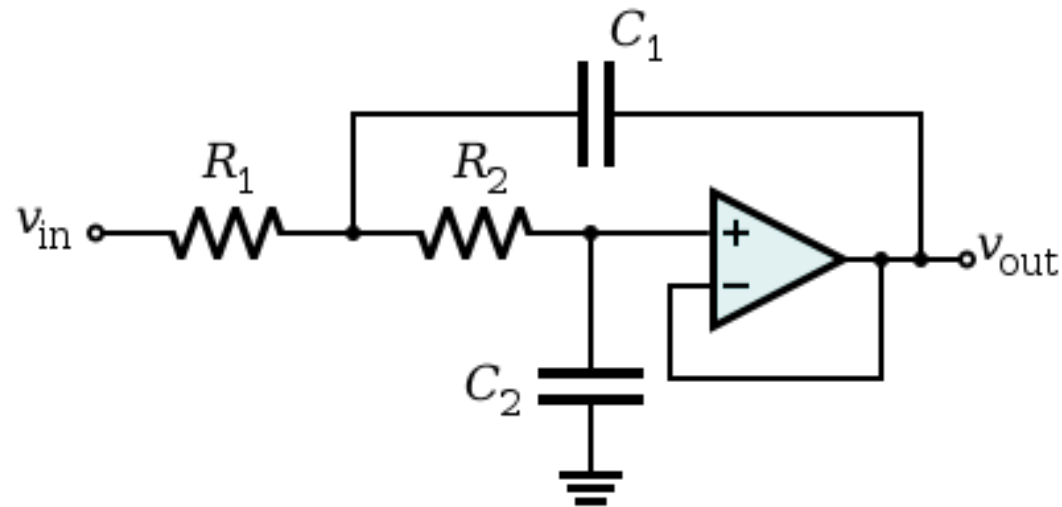

$$T(s) = \frac{V_{out}}{V_{in}} = \frac{\omega_0^2}{s^2 + (\omega_0 / Q)s + \omega_0^2} \quad Q = \frac{\sqrt{R_1 R_2 C_1 C_2}}{C_2 (R_1 + R_2)} \quad \omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

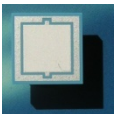**It is the second-order Sallen-Key low-pass filter.**



# Active Filter


## Implementation of the second-order active filter

Let  $Z_1 = \frac{1}{sC_1}$      $Z_2 = \frac{1}{sC_2}$      $Z_3 = R_2$      $Z_4 = R_1$

We have  $T(s) = \frac{V_{out}}{V_{in}} = \frac{s^2}{s^2 + (\omega_0 / Q)s + \omega_0^2}$

$$Q = \frac{\sqrt{R_1 R_2 C_1 C_2}}{R_1 (C_1 + C_2)} \quad \omega_0 = \frac{1}{\sqrt{R_1 R_2 C_1 C_2}}$$

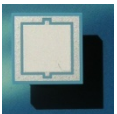Swap  $R_1$  and  $C_1$  positions as well as  $R_2$  and  $C_2$  positions, the filter changes from low-pass to high-pass.





# Switched-Capacitor Filter


**Disadvantages of active-RC filter circuits:**

**Need for large value capacitors**

**Requirement of accurate RC time constants**



**Active-RC filter is impractical for monolithic IC implementation.**

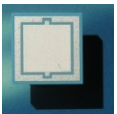**Switched-capacitor circuits could overcome these disadvantages.**





# Switched-Capacitor Filter

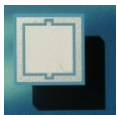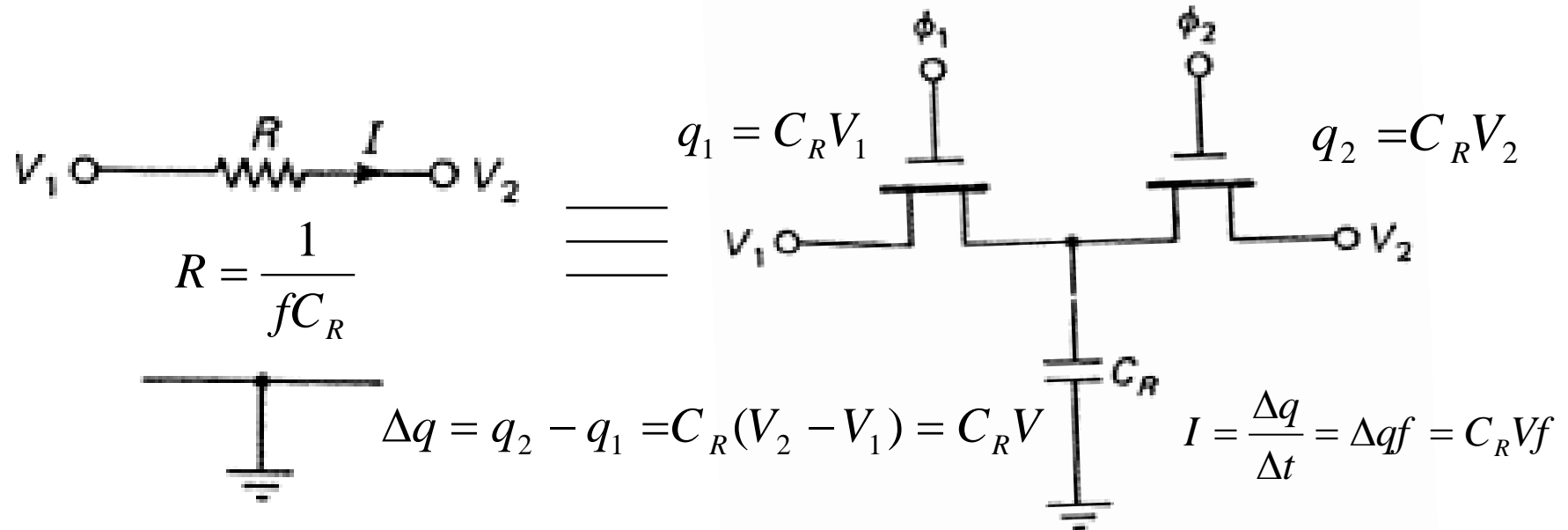**The idea: a capacitor switched between two circuit nodes at a sufficiently high rate is equivalent to a resistor connecting these two nodes.**


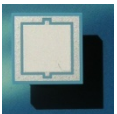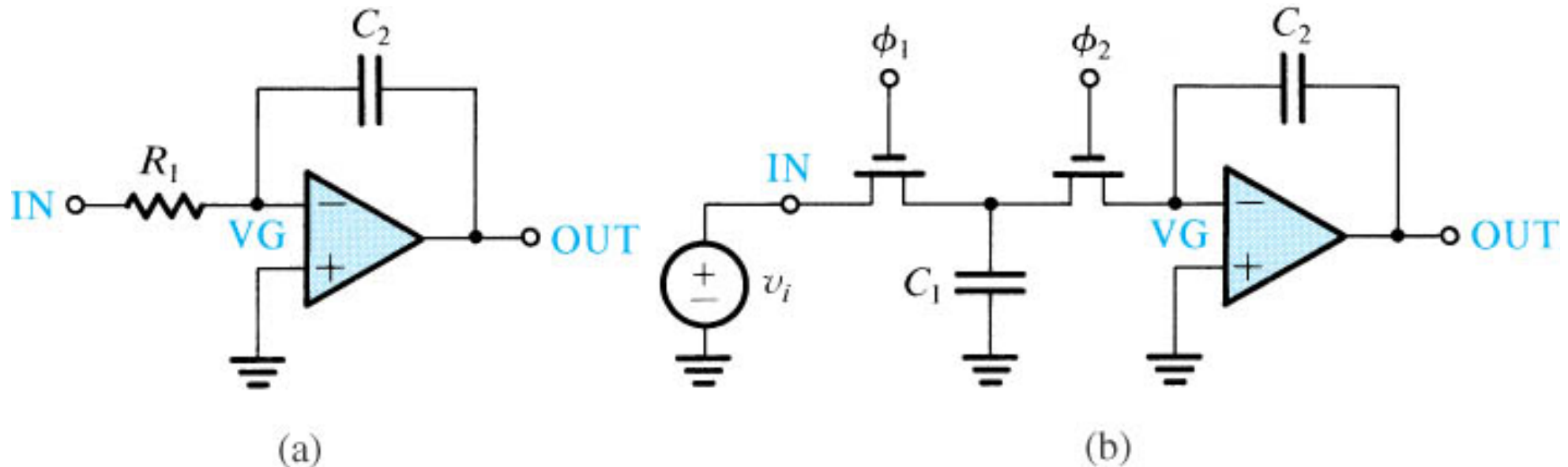
# Switched-Capacitor Filter

Consider an active-RC integrator:  $R_1$  is replaced by  $C_1$  together with two MOS transistors acting as switches.





# Switched-Capacitor Filter

The two MOS switches are driven by a *non-overlapping* two-phase clock.



The clock frequency  $f_c$  ( $f_c = 1/T_c$ ) is much higher than the signal bandwidth.

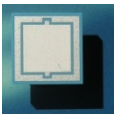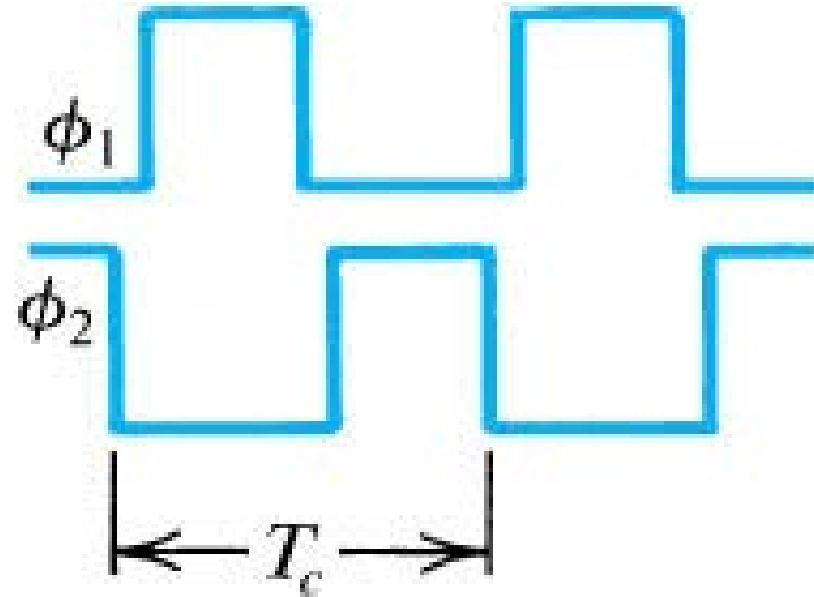When the clock signal applied to the gate terminal of MOS is high, the MOS switch is “ON”, else it is “OFF”.


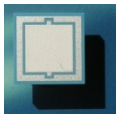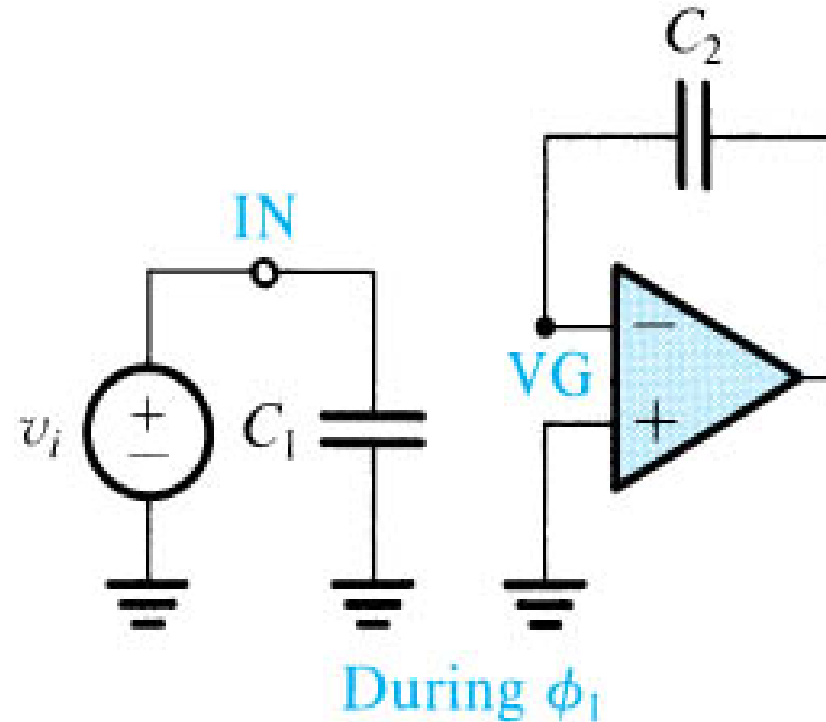
# Switched-Capacitor Filter



During clock phase  $\phi_1$ , the variations in  $v_i$  connected across  $C_1$  is negligibly small.  $C_1$  is charged to the voltage  $v_i$ :  $q_{C1} = C_1 v_i$


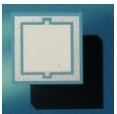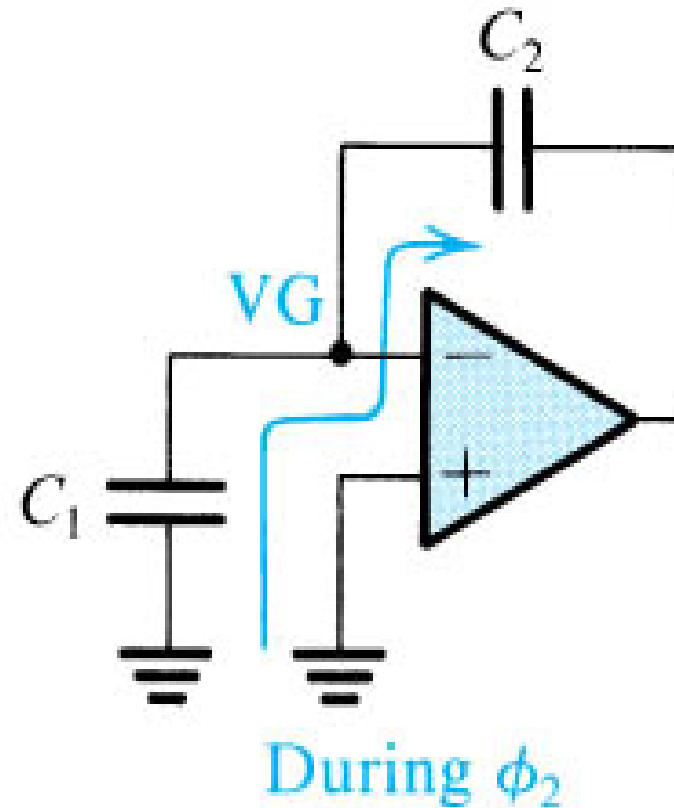
# Switched-Capacitor Filter

During clock phase  $\phi_2$ ,  $C_1$  is connected to the virtual ground input of op amp.



$C_1$  is thus discharged and its previous stored charge  $q_{C1}$  is transferred to  $C_2$ , in the direction indicated.


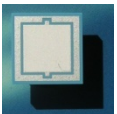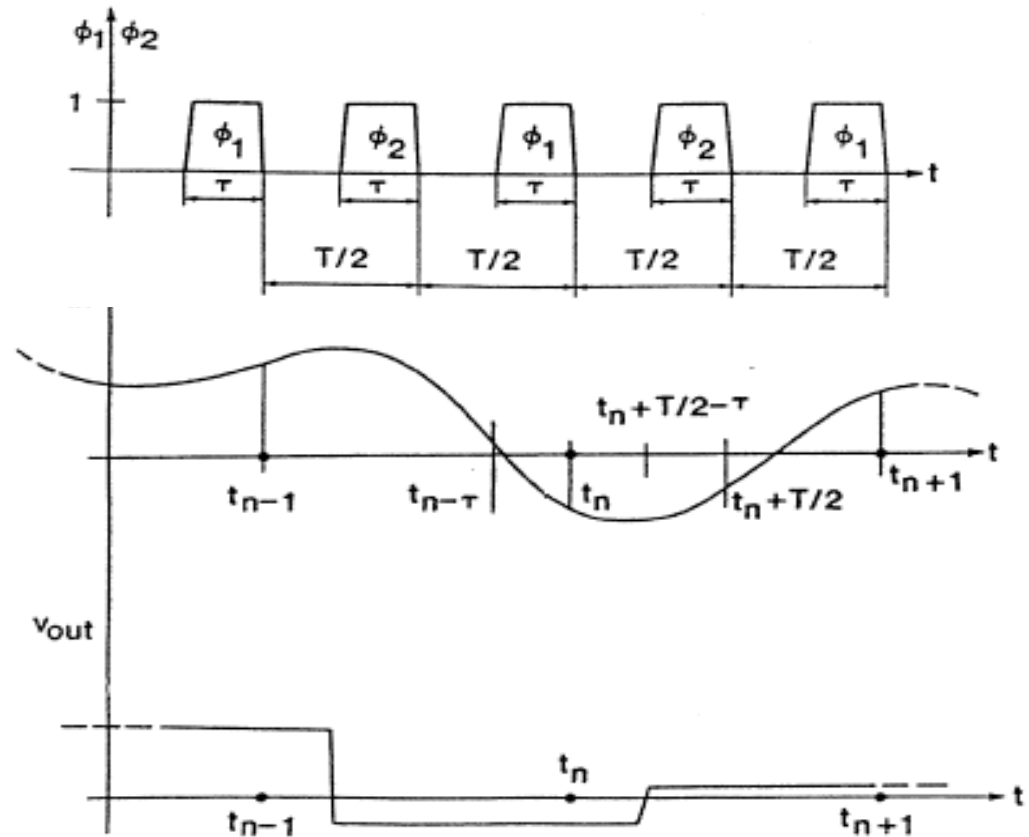
# Switched-Capacitor Filter

The input could be a continuous time signal.

The output is a sampled-data signal which only changes at the beginning of  $\phi_2$  when charge transfer takes place.




# Switched-Capacitor Filter

During each clock period  $T_C$  an amount of charge  $q_{C1} = C_1 v_i$  is transferred from the input source to the integrator capacitor  $C_2$ .

Hence the average current flowing between the input node (IN) and the virtual ground node (VG) is:  $i_{av} = C_1 v_i / T_c$ .

If  $T_C$  is sufficiently short, the charge transfer is almost continuous and we can define an equivalent resistance  $R_{eq}$  that is in effect present between nodes IN and VG as:  $R_{eq} = T_c / C_1$ .

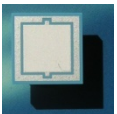The equivalent time constant for the integrator:  $R_{eq} C_2$ .






# Switched-Capacitor Filter

Thus the time constant that determines the frequency response of a filter is governed by the clock period  $T_C$  and the capacitor ratio  $C_2/C_1$ .


Both these parameters can be well controlled in an IC process.

The accuracy of capacitor ratios in MOS technology can be controlled to within 0.1%.

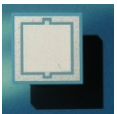
Another advantage is that large time constant can be realized with small capacitor.




# Switched-Capacitor Filter

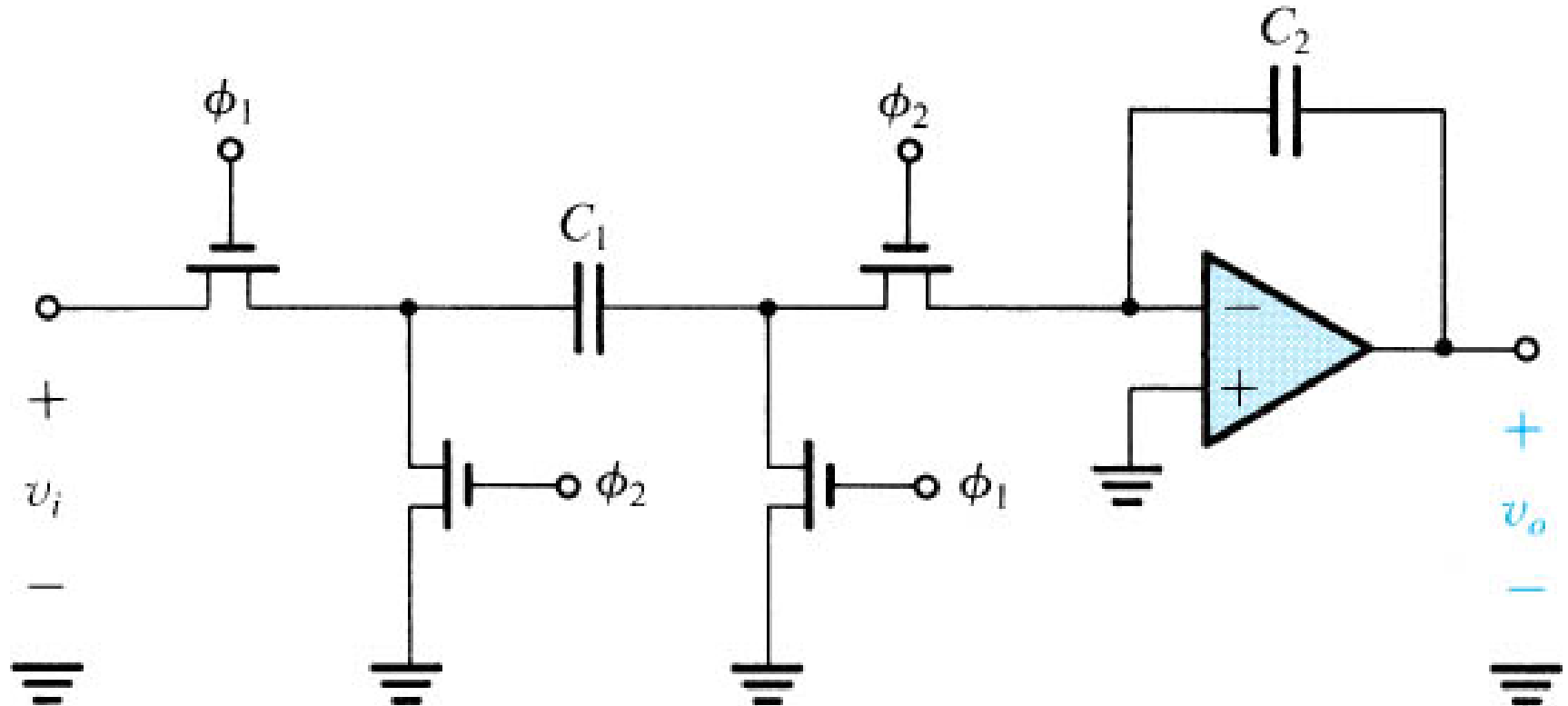

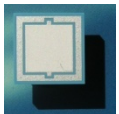
Non-inverting switched-capacitor integrator



# Switched-Capacitor Filter

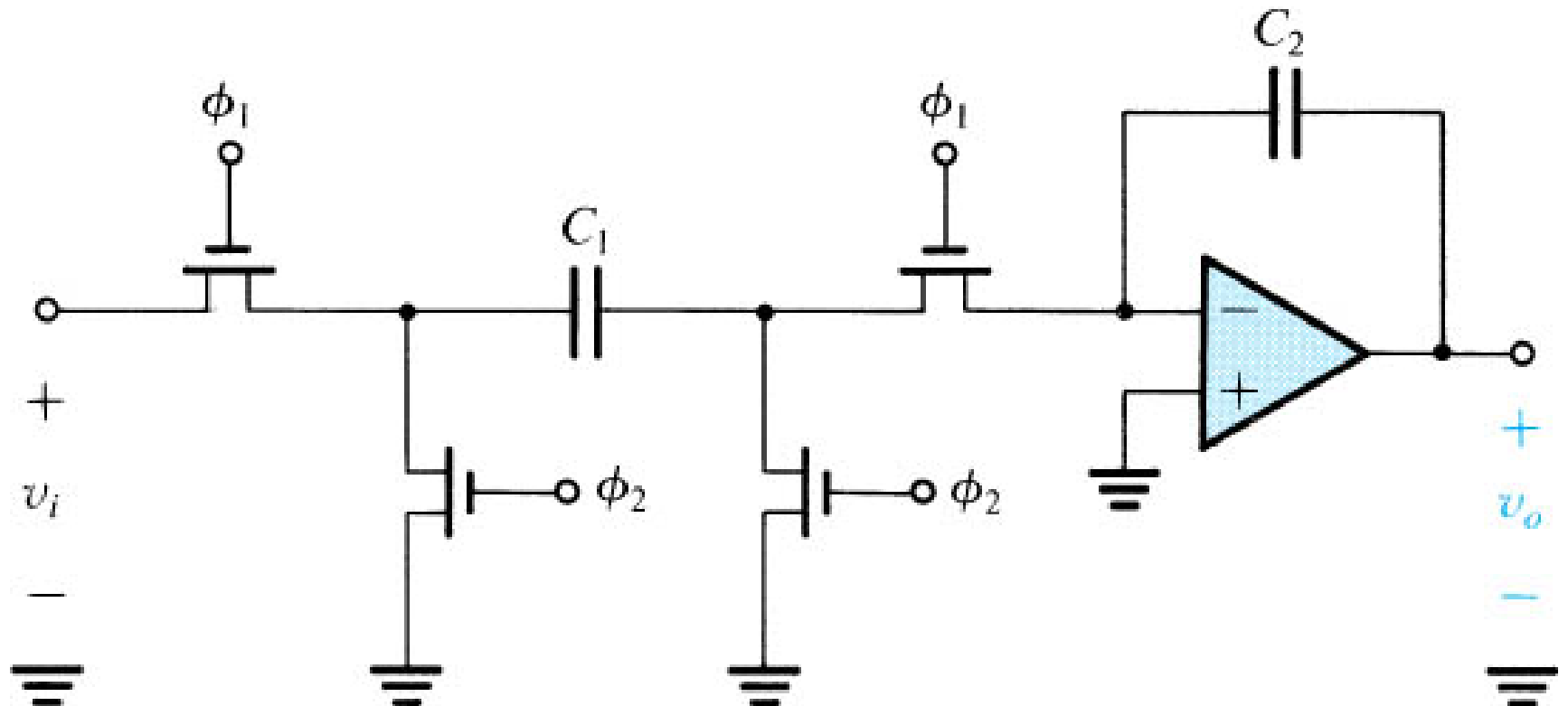


Inverting switched-capacitor integrator

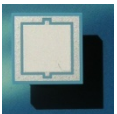


# Precision Rectifier


## Precision Half-Wave Rectifier

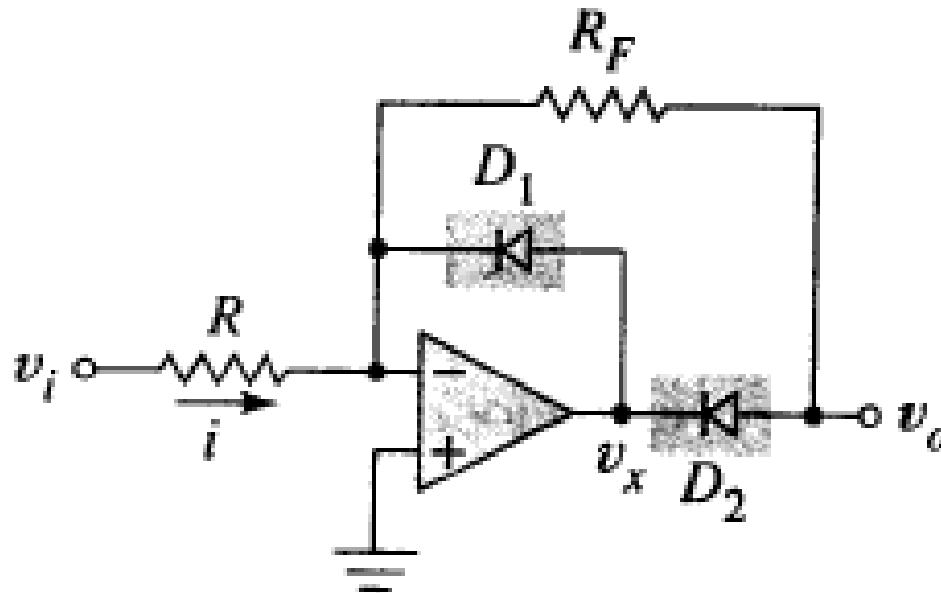

Circuit

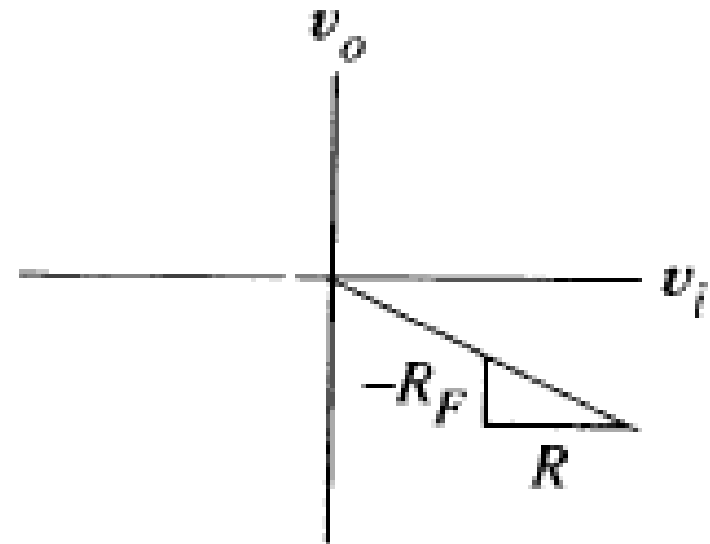

Transfer Characteristic

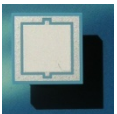

# Precision Rectifier

For  $v_i > 0$ , current  $i$  can only flow through  $R_F$  and  $D_2$  but not  $D_1$ .




We have

$$i = \frac{v_i - 0}{R} = \frac{0 - v_o}{R_F}$$

$$\Rightarrow v_o = -\frac{R_F}{R} v_i \quad \text{for } v_i \geq 0$$

For  $v_i < 0$ ,  $D_2$  turns OFF and  $D_1$  turns ON.

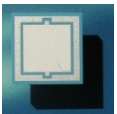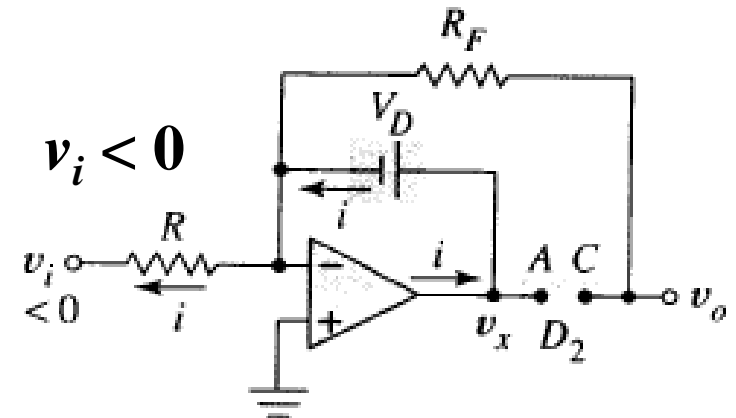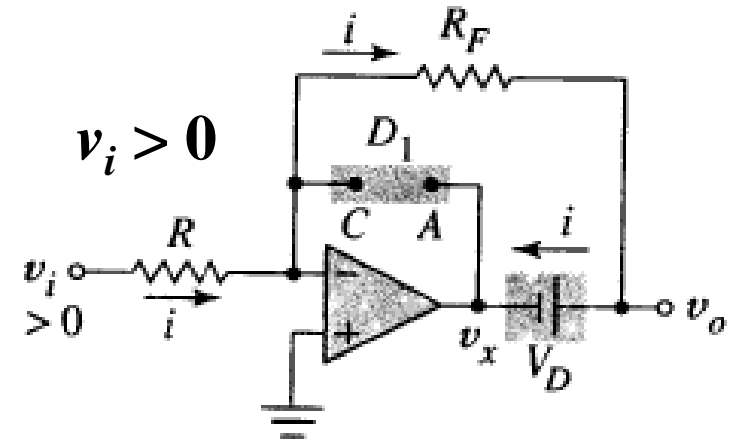The virtual ground requires that  $v_o = 0$  for  $v_i < 0$ .




# Precision Rectifier

The precision full-wave rectifier is formed by a precision half-wave rectifier and a summing amplifier.


$$\Rightarrow v_o = -(v_i + 2v_R)$$

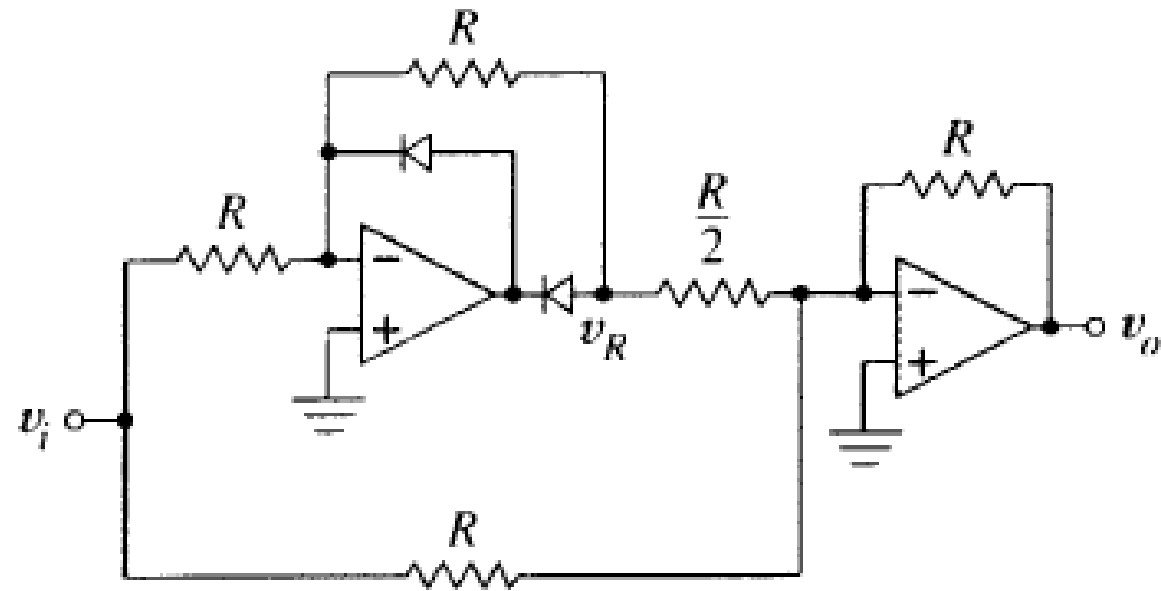where  $v_R$  is the output of the precision half-wave rectifier





When  $v_i > 0$ ,  $v_R = -v_i \Rightarrow v_o = -(v_i + 2v_R) = v_i$

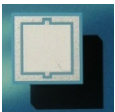When  $v_i < 0$ ,  $v_R = 0 \Rightarrow v_o = -(v_i + 2v_R) = -v_i$



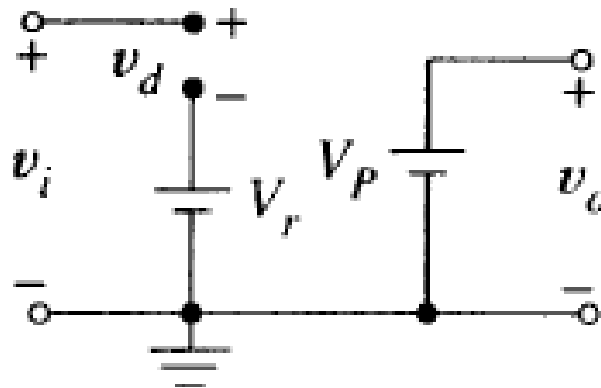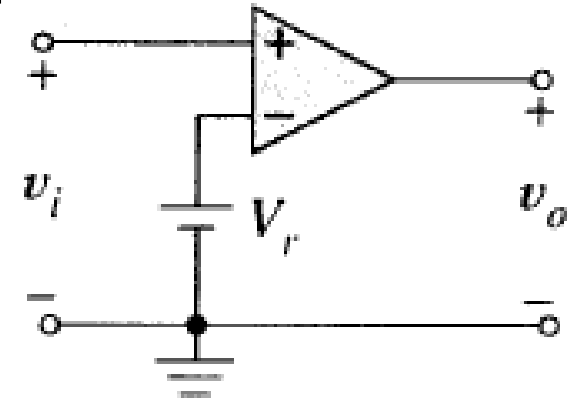
# Comparator


The comparator circuit compares signal  $v_i(t)$  with reference voltage  $V_r$ . It produces a binary output, one value for  $v_i(t) > V_r$  and another for  $v_i(t) < V_r$ .  $v_d = v_i - V_r$



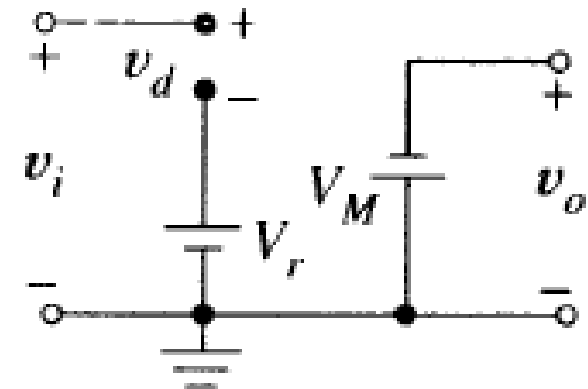When  $v_i > V_r$ ,  $v_d > 0$  the output is  $V_P$ , the positive saturation of op amp.



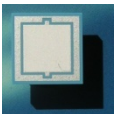When  $v_i < V_r$ ,  $v_d < 0$  the output is  $-V_M$ , the negative saturation of op amp.





# Comparator

The comparator extracts binary information from its analog input. One possible application is the temperature warning system shown in this figure.

In comparator circuit op amp is used in open-loop mode => non-linear.

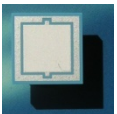
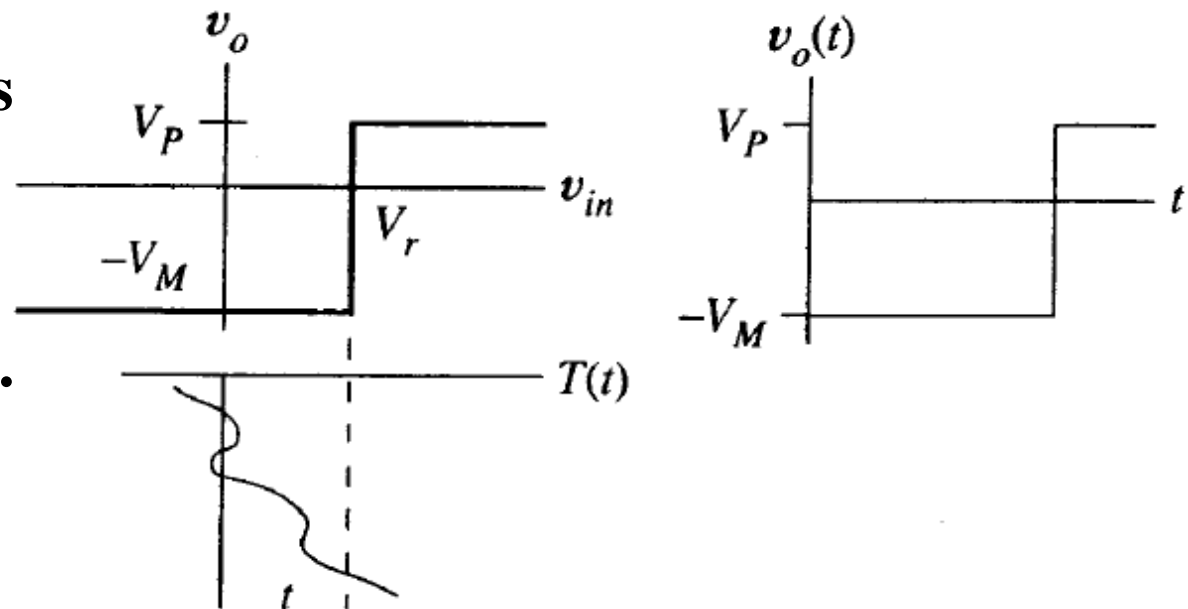
In some applications high slew rate is important to ensure rapid transitions.





# Schmitt Trigger

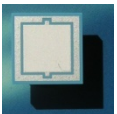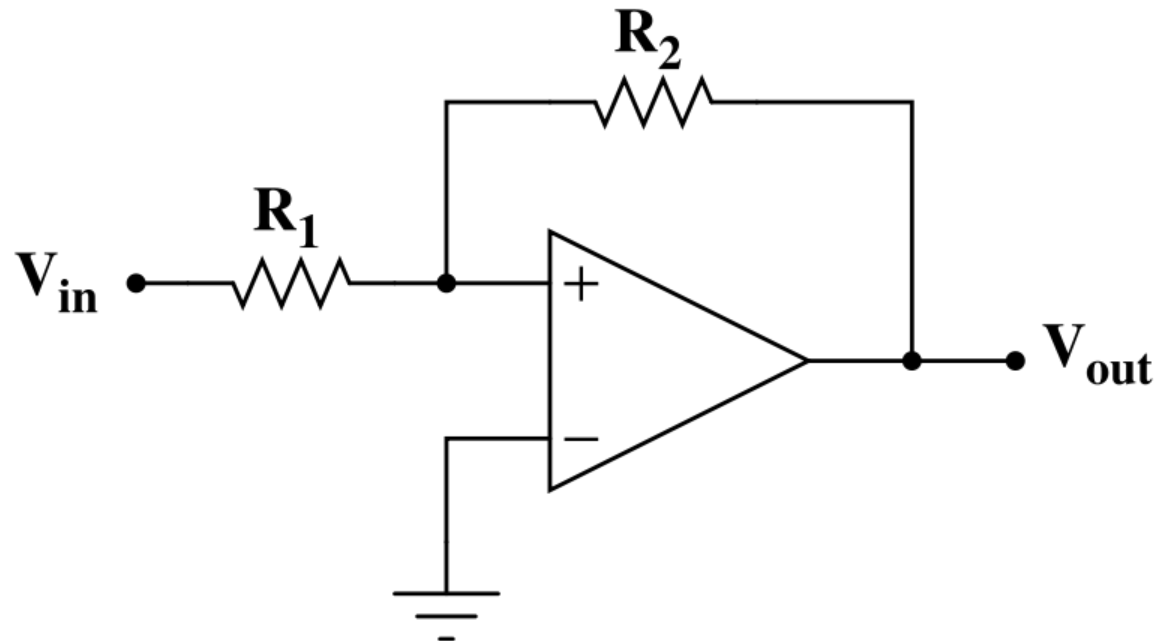**Invented by Otto Schmitt, a biomedical engineer. The circuit employs positive feedback.**





# Schmitt Trigger

Assuming  $v_i$  is very negative, then  $v_d < 0$  and output saturates at  $-V_M$ . By superposition,

$$v_d = \frac{R_2}{R_1 + R_2} v_i + \frac{R_1}{R_1 + R_2} (-V_M)$$

This implies that  $v_i$  must attain some +ve value before  $v_d$  goes positive. By setting  $v_d = 0$ , we obtain the critical value as

$$v_i = \frac{R_1}{R_2} V_M = v^+$$

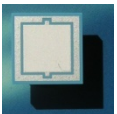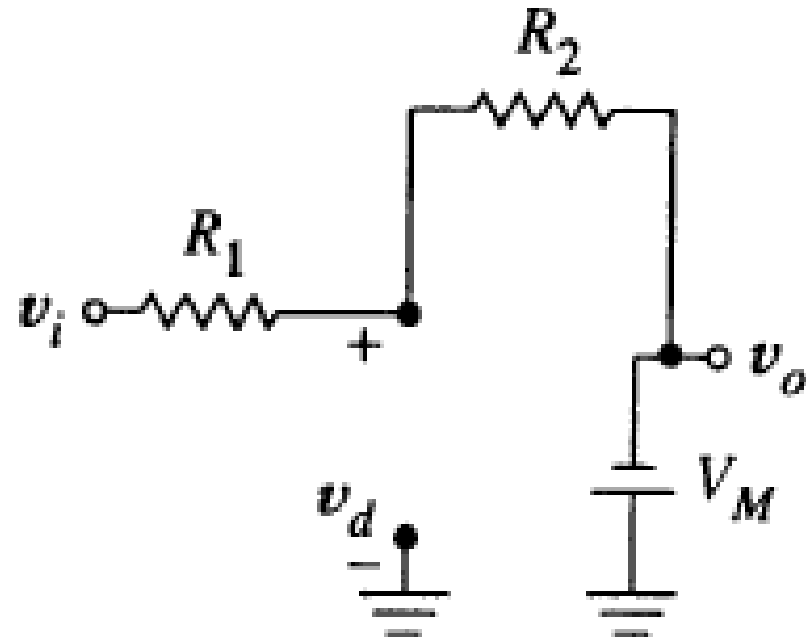



# Schmitt Trigger

Once  $v_i > v^+$ ,  $v_o = -V_M \rightarrow V_P$ , i.e. op amp changes state to that as shown on the right. Now  $v_d$  is given by:

$$v_d = \frac{R_2}{R_1 + R_2} v_i + \frac{R_1}{R_1 + R_2} (V_P)$$

This implies that  $v_i$  must attain some -ve value before  $v_d$  goes -ve. By setting  $v_d = 0$ , we obtain the critical value as



$$v_i = -\frac{R_1}{R_2} V_P = v^-$$

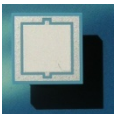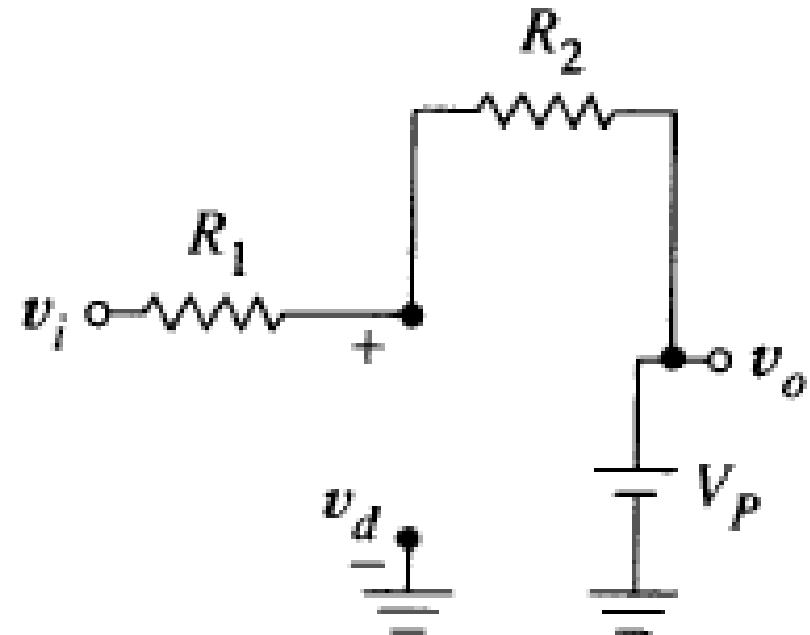
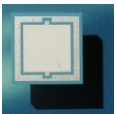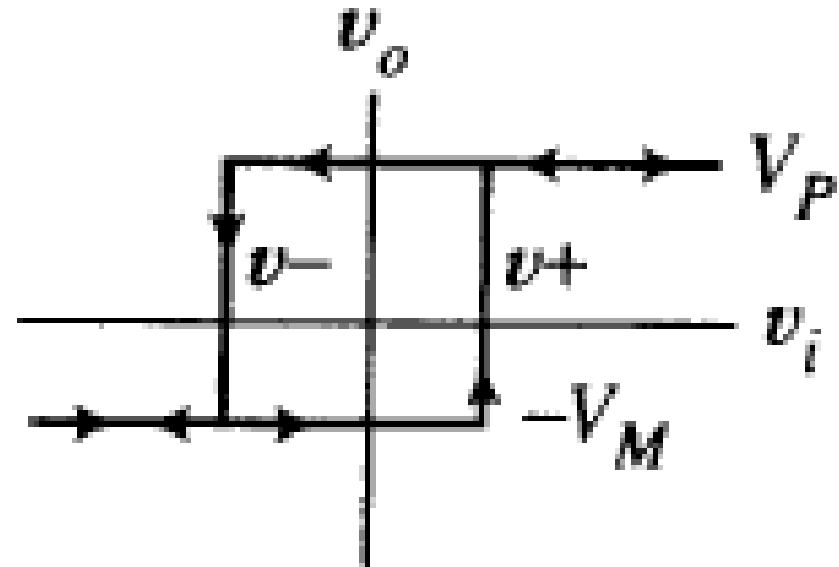
# Schmitt Trigger

The transfer characteristic of the circuit is as shown. In effect, the circuit has memory. The Schmitt circuit is a comparator with hysteresis. The width of hysteresis region is

$$W = v^+ - v^- = \frac{R_1}{R_2} (V_P + V_M)$$




# Schmitt Trigger

The width of the hysteresis region can be determined by the ratio of  $R_1$  and  $R_2$ . By adding a positive reference  $V_R$  between the inverting node and the ground, the transfer characteristic can be shifted to the right by

$$\left( \frac{R_1 + R_2}{R_2} \right) V_R$$

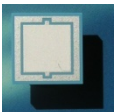while the hysteresis  $W$  remains the same. Adding a negative reference  $V_R$  shift the transfer characteristic can be shifted to the left.




# Oscillator


A square-wave oscillator can be built using an integrator plus a comparator with controlled hysteresis. The period of the oscillator output is given as:

$$T = 2RC \ln \left( \frac{1+B}{1-B} \right)$$

where  $B = \frac{R_1}{R_1 + R_2}$

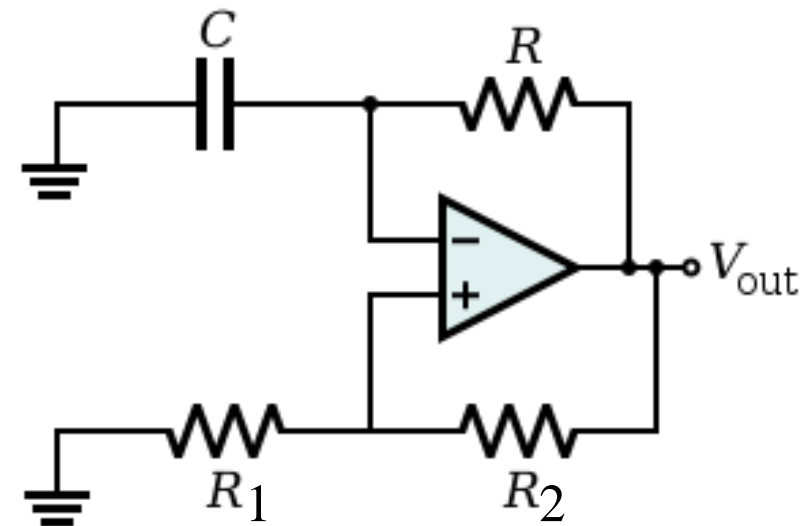



Oscillator

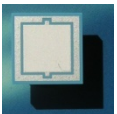
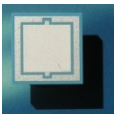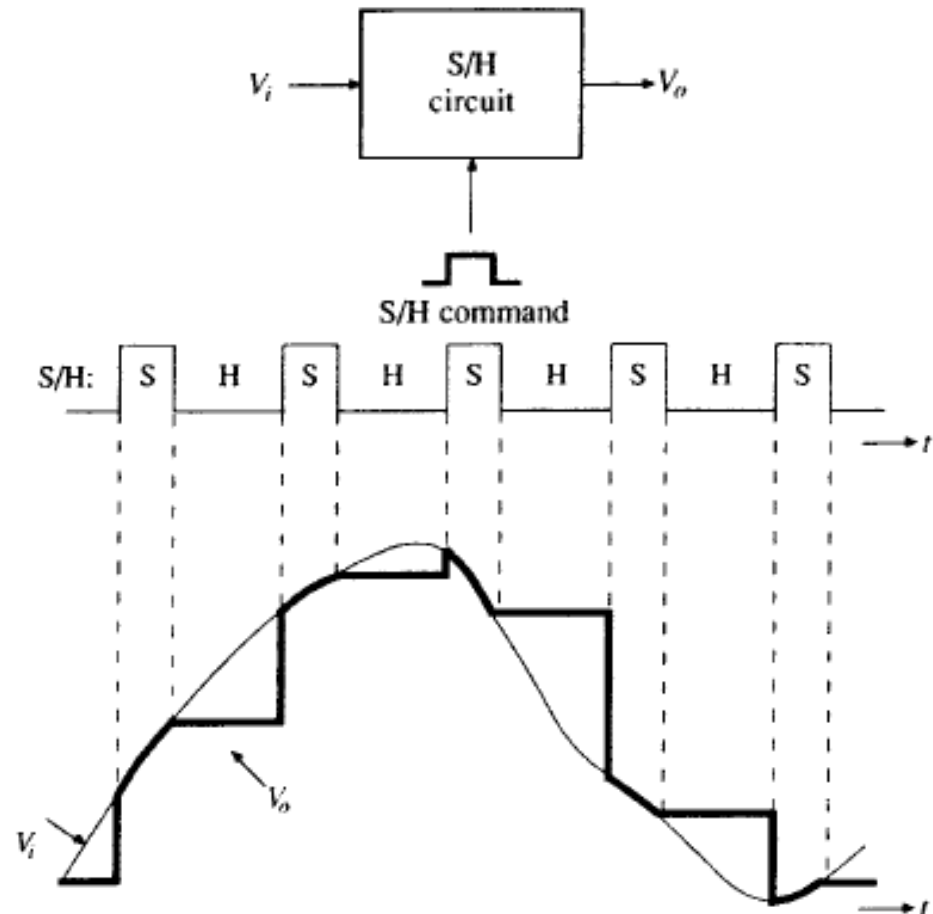
# Sample-and-Hold

The function of a S/H circuit is to capture the value of the input signal in response to a sampling command and hold it at the output until the arrival of the next command.



The figures depict the block diagram and the idealized response.


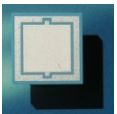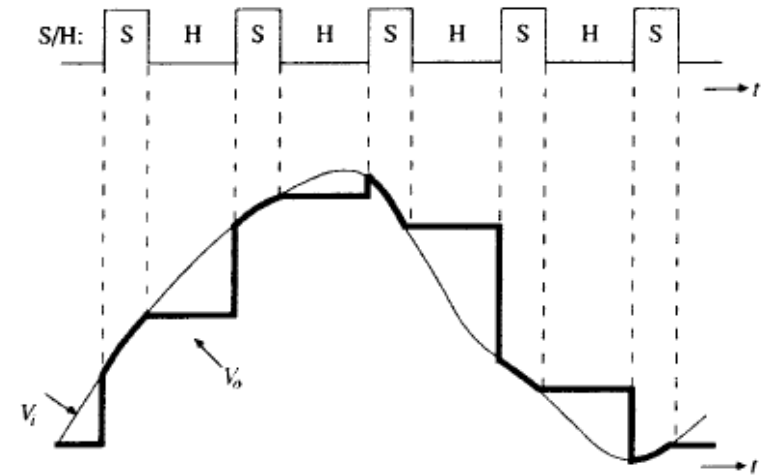
# Sample-and-Hold

**Track mode:** Once S/H command is received, the circuit swings  $V_o$  towards  $V_i$  and then forces  $V_o$  to track or follow  $V_i$  for the remainder of the pulse.

**Hold mode:** After the S/H pulse is removed, the circuit holds  $V_o$  at the value  $V_i$  had at the instant of pulse deactivation.





# Sample-and-Hold

The most popular S/H configuration.

During the sampling interval, the driver closes the switch, and

$$V_o = V_i$$

At the end of the sampling interval, the driver opens the switch, and  $V_o = V_{CH} = \text{value of } V_i \text{ at the instant of switch.}$

