

EE2002

**NANYANG TECHNOLOGICAL UNIVERSITY**

**SEMESTER 2 EXAMINATION 2016-2017**

**EE2002 - ANALOG ELECTRONICS**

April / May 2017

Time Allowed: 2½ hours

**INSTRUCTIONS**

1. This paper contains 5 questions and comprises 9 pages.
  2. Answer ALL questions.
  3. All questions carry equal marks.
  4. This is a closed-book examination.
  5. Unless specifically stated, all symbols have their usual meanings.
  6. A List of Formulae is provided in Appendix A on pages 7 to 9.
- 

1. (a) A negative feedback non-ideal op-amp circuit is shown in Figure 1 on page 2.

- (i) Derive the expression for the output voltage  $v_{OUT}$  in terms of  $V_{IO}$ ,  $I_+$ ,  $I_-$ ,  $v_{in}$ ,  $R_1$ ,  $R_2$ ,  $R_3$  and  $R_4$ .

**Note:** Parallel resistance of  $R_a$  and  $R_b$  can be written as  $R_a // R_b$  without expanding it.


(4 Marks)

- (ii) Assume that  $v_{in} = 510 \text{ mV}_{\text{peak}}$  sinusoid,  $V_{IO} = 10 \text{ mV}$ ,  $I_+ = 10 \mu\text{A}$ ,  $I_- = 10 \mu\text{A}$ , and  $R_1 = R_2 = R_3 = 2 \text{ k}\Omega$ . Find the value of  $R_4$  that would give the maximum gain within the output linear range no closer than 1 V to either power supply voltage. (Hint:  $v_{OUT|DC}$  is positive.)

(8 Marks)

Note: Question No. 1 continues on page 2.

EE2002

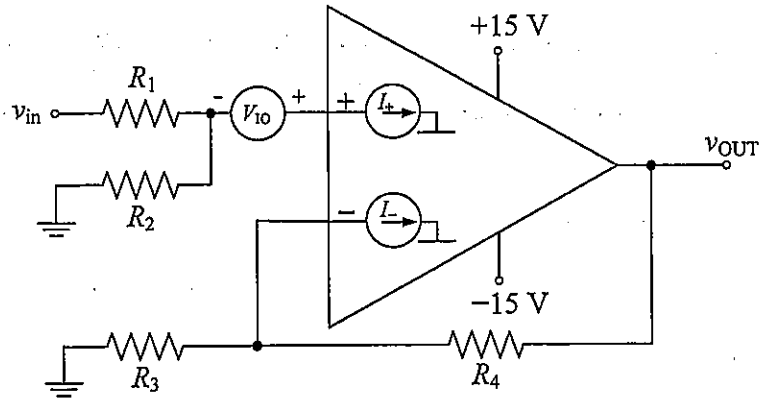

**Figure 1**

- (b) The empirical diode junction equations expressed in voltage and current are as follows:

$$v_D \cong nV_T \ln \frac{i_D}{I_S} \text{ and } i_D \cong I_S e^{\frac{v_D}{nV_T}}.$$

Assume that the total current  $i_D = i_d + I_D$  and total voltage  $v_D = v_d + V_D$  in the diode, where  $i_d$  and  $v_d$  are the ac current and voltage components, respectively, and  $I_D$  and  $V_D$  are the dc current and voltage components, respectively.

- (i) Prove that  $i_d$  and  $v_d$  are linearly related for small values of  $\frac{v_d}{nV_T}$ .
- (ii) Hence, within the linear validity range, calculate the numerical value of  $v_d$  in mV, given that the thermal voltage  $V_T = 26$  mV at  $27^\circ\text{C}$ , and the forward emission coefficient  $n = 1$ .

(Note:  $e^x = 1 + x + \frac{x^2}{2!} + \frac{x^3}{3!} + \dots$  and  $e^x \cong 1 + x$  for small values of  $x$  where  $\frac{x^2}{2!} \ll x$ .)

(8 Marks)

EE2002

2. For the amplifier shown in Figure 2, the MOSFET transistor  $M$  has  $V_{TN} = 1\text{ V}$ ,  $K_n = 0.2\text{ mA/V}^2$  and  $\lambda = 0.01\text{ V}^{-1}$ . Assume that  $R_{G1} = 50\text{ k}\Omega$ ,  $R_{G2} = 100\text{ k}\Omega$ ,  $R_D = R_S = 10\text{ k}\Omega$  and  $R_L = 100\text{ k}\Omega$ . The DC blocking capacitors are assumed to have infinite capacitance.

- (a) Find the Q-point of the amplifier.


(6 Marks)

- (b) Draw the small signal equivalent circuit. Determine the voltage gain  $A_v = \frac{v_o}{v_i}$ , input resistance  $R_{in}$  and output resistance  $R_{out}$  of the amplifier.

(10 Marks)

- (c) Determine the input signal range of  $v_i$  for small-signal linear amplification. If the signal source  $v_i$  is not ideal and has an internal resistance of  $10\text{ k}\Omega$ , what will be the input signal range to maintain the small-signal operation?

(4 Marks)

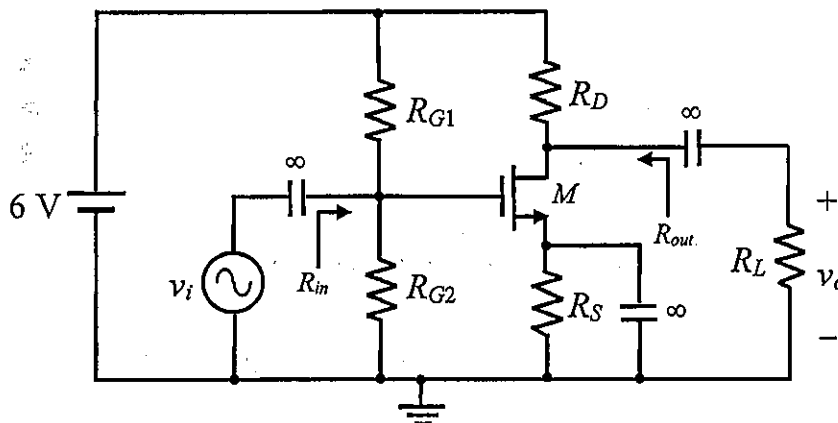


**Figure 2**

3. In Figure 3 on page 4, the DC operating point for MOSFET  $M_1$  is at  $I_D = 83.6\text{ }\mu\text{A}$  and  $V_{DS} = 5.97\text{ V}$ , and the DC operating point for BJT  $Q_2$  is at  $I_C = 1.27\text{ mA}$  and  $V_{CE} = 1.65\text{ V}$ .  $M_1$  has  $K_n = 0.5\text{ mA/V}^2$  and  $\lambda = 0.02\text{ V}^{-1}$ , and  $Q_2$  has  $\beta = 100$ ,  $V_T = 25\text{ mV}$  and  $V_A = 70\text{ V}$  at room temperature. Assume that the capacitors have infinite values, and resistors have the values as indicated in Figure 3 on page 4.

Note: Question No. 3 continues on page 4.

EE2002

- (a) Determine the voltage gain  $A_v = \frac{v_o}{v_i}$ . (9 Marks)
- (b) Determine the input resistance  $R_{in}$  and output resistance  $R_{out}$  of the amplifier. (6 Marks)
- (c) Determine the input small signal range for this amplifier to remain in the linear output range. (5 Marks)

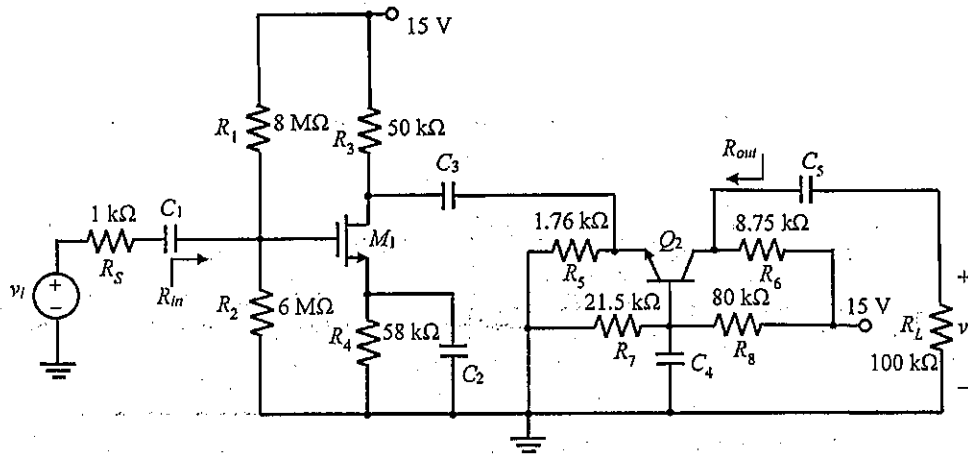


**Figure 3**

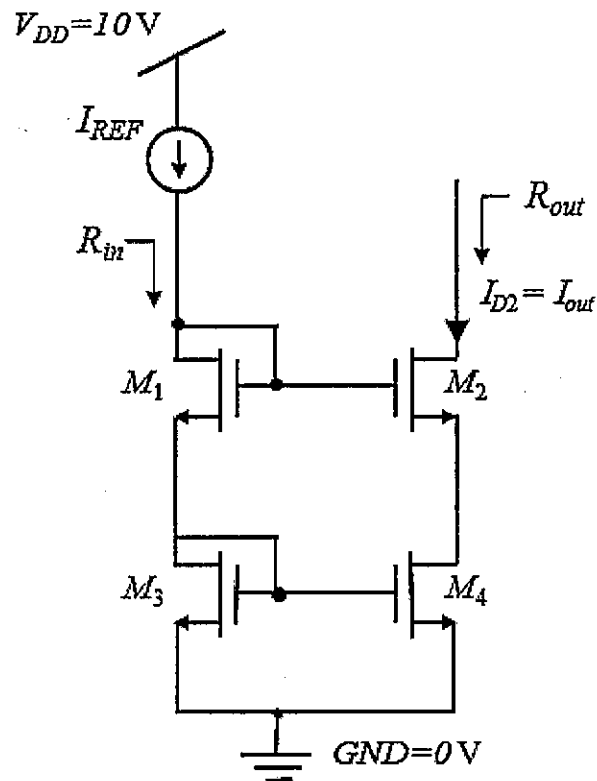4. Consider the cascode current mirror circuit shown in Figure 4 on page 5. Assume all transistors are identical and in saturation. In the following small-signal analysis, indicate clearly the  $g_m$  and  $r_o$  of the  $i$ -th transistor as  $g_{m,i}$  and  $r_{o,i}$ . For example, the  $g_m$  and  $r_o$  for transistor  $M_2$  should be written as  $g_{m,2}$  and  $r_{o,2}$ , respectively.
- (a) Draw the AC small signal model of the circuit and derive the expression for the output resistance  $R_{out}$  in terms of the small signal parameters  $g_m$  and  $r_o$  of the MOSFET. (8 Marks)
- (b) Draw the AC small signal model of the circuit and derive the expression for the input resistance  $R_{in}$  in terms of the small signal parameters  $g_m$  and  $r_o$  of the MOSFET. (7 Marks)

Note: Question No. 4 continues on page 5.

- (5 Marks)



5. (a) A voltage amplifier has the transfer function:

$$A = \frac{200\omega}{(1 + j\frac{\omega}{20^3})(1 + j\frac{\omega}{10^6})(1 + j\frac{\omega}{10^9})}$$

- (4 Marks)

- (2 Marks)


5

EE2002

- (iii) What is the magnitude of gain at the frequency determined in part (ii)? Express it in dB.

(2 Marks)

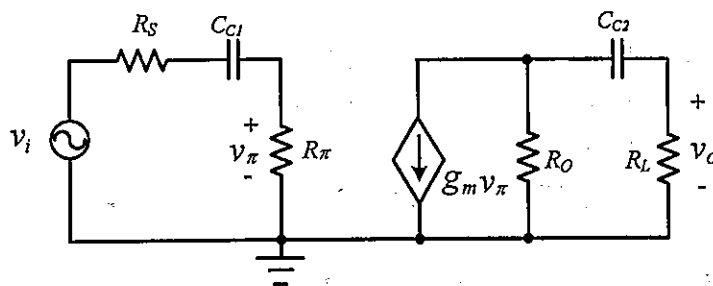- (b) Figure 5 shows the small-signal model of a single stage amplifier. All the design and operation parameters are given as follows.



$$\begin{aligned} R_S &= 100 \, \Omega \\ R_O &= 50 \, \text{k}\Omega \\ R_L &= 20 \, \text{k}\Omega \\ R_\pi &= 5 \, \text{k}\Omega \\ g_m &= 0.04 \, \text{A/V} \\ C_{C1} &= 100 \, \text{pF} \\ C_{C2} &= 100 \, \text{pF} \end{aligned}$$

**Figure 5**

- (i) Derive the transfer function of the amplifier, and determine the number of poles and zeros.

(6 Marks)

- (ii) In order to find out the contribution of capacitor  $C_{C1}$  to the **lower** roll-off frequency, what should you do with the capacitor  $C_{C2}$ ? In other words, should it be short-circuited, or open-circuited? Determine the equivalent resistance seen by the capacitor  $C_{C1}$ .

(6 Marks)

\* The <sup>no.</sup> solution is only for your references.

DATE: .....

$$\text{Iai. } V_1 = I R_4$$

$$V_2 = -I_+(R_1 // R_2) \left(1 + \frac{R_4}{R_3}\right)$$

$$V_3 = \frac{R_2}{R_1 + R_2} V_{in} \left(1 + \frac{R_4}{R_3}\right)$$

$$V_4 = V_{io} \left(1 + \frac{R_4}{R_3}\right)$$

$$V_{out} = V_1 + V_2 + V_3 + V_4$$

$$= I R_4 + \left(-\frac{R_2}{R_1 + R_2} V_{in} + V_{io} - I_+(R_1 // R_2)\right) \left(1 + \frac{R_4}{R_3}\right)$$

$$\text{ii. } 14 = 10 \mu R_4 + \left(\frac{2k}{2k + 2k} \times 510m + 10m - 10m\right) \left(1 + \frac{R_4}{2k}\right)$$

$$= 10 \mu R_4 + 255m \left(1 + \frac{R_4}{2k}\right)$$

$$= 137.5 \mu R_4 + 0.255$$

$$R_4 \approx 100k \Omega$$

\* The solution is only for your references

NO:.....

DATE:.....

b1. Assume  $I_D = I_S e^{\frac{V_D}{nV_T}}$ ,  $V_D = 0.7V$

$$I_D = I_D \frac{V_D}{nV_T}$$

$$\frac{I_D}{I_S} = 4.9266 \times 10^{11}$$

$$I_D = I_S e^{\frac{V_D}{nV_T}} = I_S \left[ 1 + \frac{V_D}{nV_T} \right] = I_D \frac{V_D}{nV_T}$$

$$1 + \frac{V_D}{nV_T} = \frac{I_D}{I_S} = 4.9266 \times 10^{11}$$

$$V_D = 7.81 \times 10^{-11} V$$




\*The solution is only for your references

NO:.....

DATE:.....

2a.

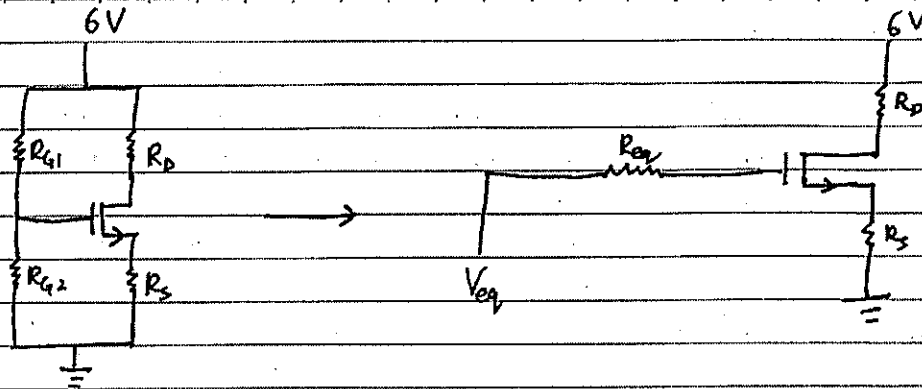

$$V_{eq} = \frac{R_{G2}}{R_{G1} + R_{G2}} \times 6 = \frac{2}{3} \times 6 = 4V$$

$$R_{eq} = R_{G1} \parallel R_{G2} = 33.33k\Omega$$

$$V_{eq} = V_{GS} + I_D R_S \Rightarrow 4 = V_{GS} + \frac{0.2m}{2} (V_{GS} - 1)^2 \times 10k$$

$$4 = V_{GS} + (V_{GS} - 1)^2$$

$$V_{GS} = 3.79V$$

$$I_D = \frac{4 - 3.79}{10k} = 2\mu A$$

$$V_{DS} = 6 - I_D R_D - I_D R_S$$

$$= 6 - 2\mu(10k + 10k)$$

$$= 5.58V$$

$$\therefore V_{DS} > V_{GS} - V_{th}$$

$\therefore M$  is in saturation region


$$Q(2\mu A, 3.79V)$$

\* The solution is only for your references

NO: .....

DATE: .....

b.

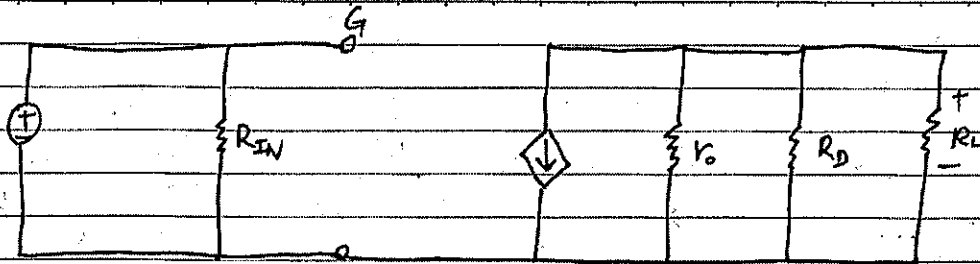


$$A_{v_L} = -g_m R_L'$$

$$= -91.65 \mu (R_D // R_L)$$

$$= -91.65 \mu (10k // 100k)$$

$$A_v = -0.833$$
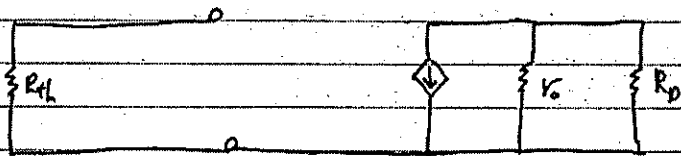
$$R_{in} = R_{G1} // R_{G2} = 33.33k \Omega$$



$$R_{th} = R_{G1} // R_{G2} = 33.33k \Omega$$

$$R_{out} = r_o // R_D$$

$$= 4.762M // 10k$$

$$= 9.98k \Omega$$

$$r_o = \frac{1}{\lambda I_D}$$

$$= \frac{1}{0.01 \times 21 \mu}$$

$$= 4.762M \Omega$$

$$C. |V_i| \leq 0.2 (V_{GS} - V_{TN}) \left( \frac{10k + R_{in}}{R_{in}} \right)$$

$$= 0.2 (3.79 - 1) \left( \frac{10k + 33.33k}{33.33k} \right)$$


$$= 0.725V$$

\* The solution is only for your reference

NO: .....

DATE: .....

3a.

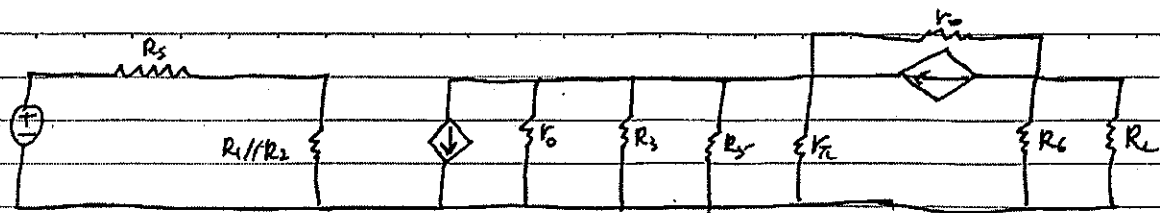

$$A_{v_{e1}} = -g_{m1}(R_3 // R_5)$$

$$= -g_m(50k // 1.76k)$$

$$= -0.4913$$

$$g_{m1} = \sqrt{2K_n I_D}$$

$$= \sqrt{2 \times 0.5m \times 83.6\mu}$$

$$= 0.289mS$$

$$A_{v_{e2}} = g_{m2}(R_6 // R_L)$$

$$= g_{m2}(8.75k // 100k)$$

$$= 410.3$$

$$g_{m2} = \frac{I_C}{V_T}$$

$$= \frac{1.27m}{25m}$$

$$= 0.051mS$$

$$A_{ve} = A_{v_{e1}} \times A_{v_{e2}} = -201.6$$

$$A_v = A_{ve} \times \frac{R_{in}}{R_s + R_{in}}$$

$$= 201.6 \times \frac{3.429m}{1k + 3.429m}$$

$$= 201.6 \times 201.5$$

$$R_{in} = R_1 // R_2$$

$$= 8m // 6m$$

$$= 3.429m\Omega$$

b.  $R_{in} = 3.429m\Omega$

$$R_{out} = [1 + g_{m1}(\frac{r_o // R_3}{R_5})] r_o // R_6$$

$$= [1 + 0.289m(\frac{598k // 50k}{1.76k})] \times 598k // 8.75k$$

$$= 8.625k\Omega$$

$$r_o = \frac{1}{\lambda I_D}$$

$$= \frac{1}{0.02 \times 83.6\mu}$$

$$= 598k\Omega$$

\* The solution is only for your references

NO:.....

DATE:.....

$$C. V_2 = \frac{R_{in}}{R_I + R_{in}} \times A_{v_{mid}} V_i; |V_2| \leq 0.005$$

$$|V_2| \leq \frac{0.005 (R_I + R_{in})}{R_{in} A_{v_{mid}}}$$

$$= \frac{0.005 (1k + 3.429M)}{3.429M \times 0.4913}$$


$$= 0.0102V$$

\*The solution is only for your references

NO: .....

DATE: .....

4a.

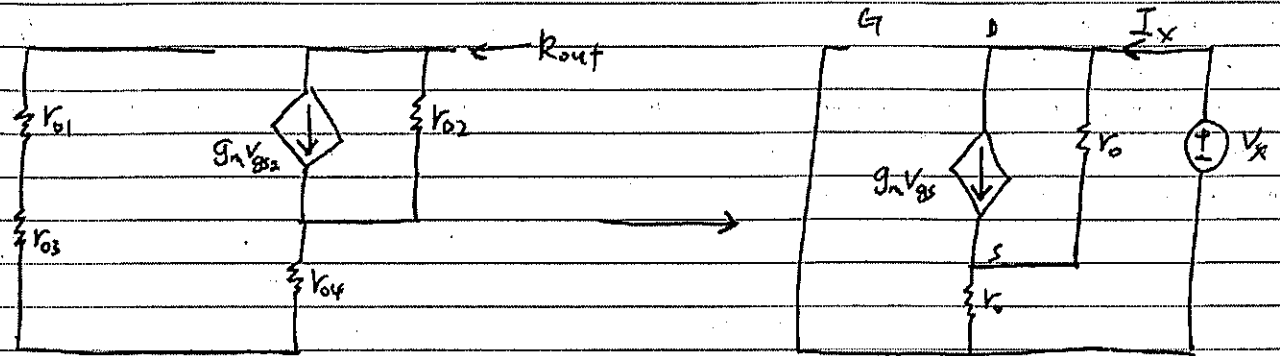



$$I_x = g_m V_{gs} + \frac{V_x - V_{gs}}{r_o}$$

$$V_{gs} = -V_s = -I_x r_o$$

$$I_x = -g_m r_o I_x + \frac{V_x}{r_o} + I_x$$

$$\frac{V_x}{I_x} = g_m r_o^2 = R_{out}$$

b.

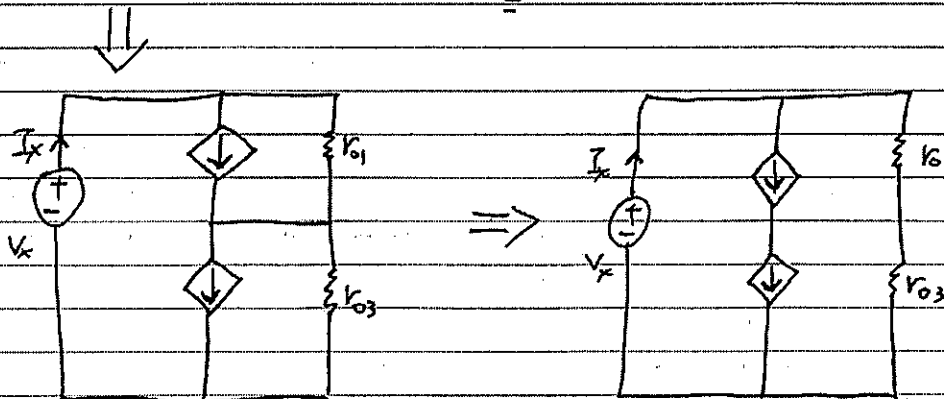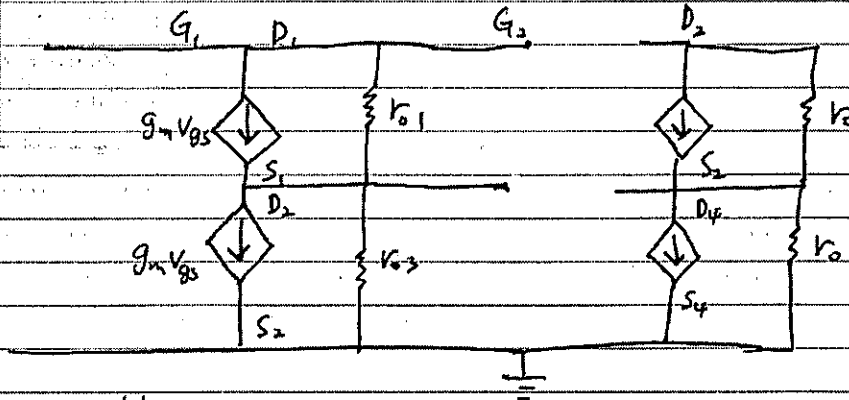

∴ Identical, ∴  $g_m V_{gs1} = g_m V_{gs3}$ ,  $r_{o1} = r_{o3}$ ,  $2V_{gs} = V_x$

$$I_x = g_m V_{gs} + \frac{V_x}{2r_o} \Rightarrow I_x = \frac{g_m V_x}{2} + \frac{V_x}{2r_o}$$

$$\frac{V_x}{I_x} = \frac{2r_o}{g_m r_o + 1} = R_{in}$$

\* The solution is only for your reference


NO: .....

DATE: .....

5a.  $\frac{200 \omega}{(1+j \cdot \frac{\omega}{20^3})(1+j \cdot \frac{\omega}{10^6})(1+\frac{\omega}{10^9})}$

~~$z_1 = 0$~~   $z_1 = 0$

$p_1 = 20^3, p_2 = 10^6, p_3 = 10^9$

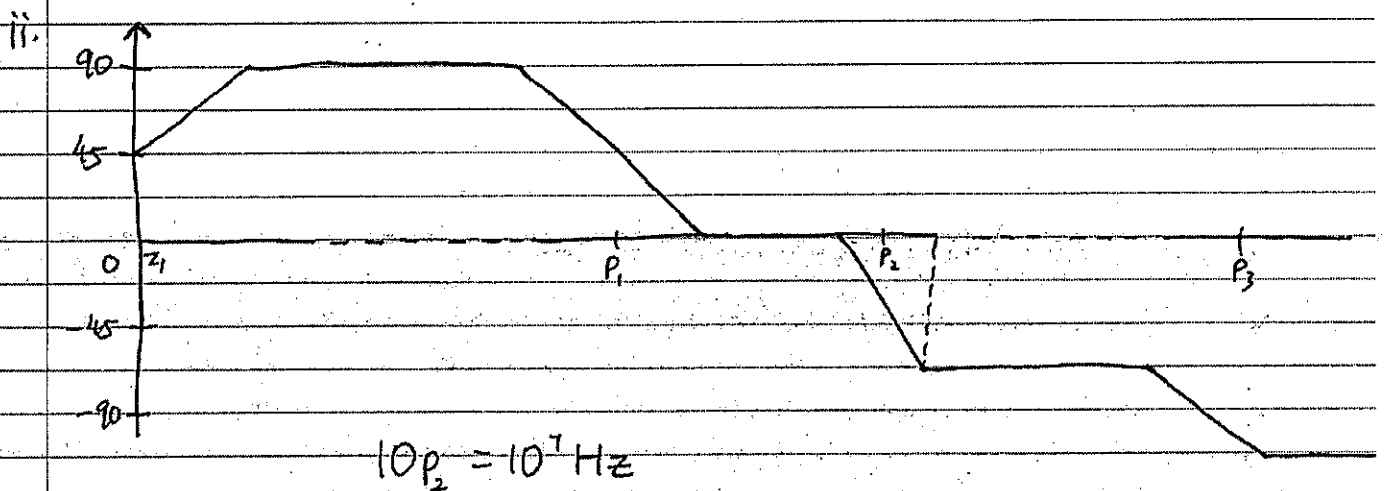

iii.  $\text{gain (dB)} = 20 \left[ \log 200 + \log 10^7 - \log \frac{10^7}{20^3} - \log \frac{10^7}{10^6} \right]$   
 $= 104 \text{ dB}$

\*The solution is only for your references

NO: .....

DATE: .....

~~bi. Answer =  $\left(\frac{R_L}{R_L + R_{cc2}}\right) \left(\frac{R_{\pi}}{R_s + R_{cc1}}\right) (-g_m [R_o // (R_L + R_{cc2})])$~~   
~~4 zeros, 4 poles~~

b ii. Short  $C_{c2}$

$$R_{cc1} = R_s + R_{\pi}$$

$$= 5100 \Omega$$

$$i. V_{\pi} = \frac{R_{\pi}}{R_s + R_{\pi} + \frac{1}{sC_{c1}}} V_i \quad (1)$$

$$V_o = -(g_m V_{\pi} + I_{R_o}) R_L \quad (2)$$

$$\text{Sub (1) into (2), } V_o = -\left[g_m \left(\frac{R_{\pi}}{R_s + R_{\pi} + \frac{1}{sC_{c1}}}\right) V_i + I_{R_o}\right] R_L$$

$$\approx -g_m R_L \left(\frac{R_{\pi}}{R_s + R_{\pi} + \frac{1}{sC_{c1}}}\right) V_i$$

$$\frac{V_o}{V_i} \approx -g_m R_L \left(\frac{R_{\pi}}{R_s + R_{\pi} + \frac{1}{sC_{c1}}}\right)$$

$$= \frac{-g_m R_L R_{\pi} s C_{c1}}{s(C_L R_s + C_L R_{\pi} + \frac{1}{s})}$$

Zero:  $\frac{1}{s}$

Pole:  $\frac{1}{s}$

$$-I(R_L + \frac{1}{sC_{c2}}) = V_x \Rightarrow V_x = \frac{-V_o}{R_L} \left(R_L + \frac{1}{sC_{c2}}\right) \quad (1)$$

$$iR_{\pi} = V_{\pi}$$

$$V_i = i[R_s + sC_{c1} + R_{\pi}] \Rightarrow V_i = \frac{V_{\pi}}{R_{\pi}} [R_s + \frac{1}{sC_{c1}} + R_{\pi}]$$

$$V_{\pi} = \frac{sR_{\pi} V_i C_{c1}}{[R_s C_{c1} + 1 + R_{\pi} s C_{c1}]} \quad (2)$$

$$g_m V_{\pi} = \left(\frac{V_x}{R_o} + \frac{V_x}{\frac{1}{sC_{c2}} + R_L}\right) \quad (3)$$

$$\text{Sub (1) \& (2) into (3), } g_m \cdot \frac{sR_{\pi} V_i C_{c1}}{R_s C_{c1} + 1 + R_{\pi} s C_{c1}} = \frac{V_o}{R_L} \left(R_L + \frac{1}{sC_{c2}}\right) \left(\frac{1}{R_o} + \frac{1}{\frac{1}{sC_{c2}} + R_L}\right)$$

$$\frac{V_o}{V_i} = \frac{g_m s R_{\pi} C_{c1} R_L}{s R_{\pi} C_{c1} + 1 + s R_{\pi} C_{c1}} \cdot \frac{s C_{c2}}{1 + s R_L C_{c2}} \cdot \frac{R_o \cdot (R_L + \frac{1}{sC_{c2}})}{R_o + \frac{1}{sC_{c2}} + R_L}$$

Zeros: 4

Poles: 4

