

EE3019 - Integrated Electronics Tutorial 9

1. For the circuit of Figure 9.1, the BJT (Q_1) has $\beta = 100$ and $V_{BE} = 0.7V$, and the (ideal) Zener diode has a breakdown current $I_{zk} = 10mA$. The unregulated supply voltage V_{UR} is a sawtooth signal that ripples between 19V and 21V.
 - (a) If the circuit is designed to provide a 10V-1A regulated power supply to a load R_L , determine the Zener voltage V_Z required and the maximum value of R_1 allowable.
 - (b) If this maximum value of R_1 is used, find the required minimum power ratings of the Zener diode and the series pass transistor Q_1 .

[(a) 10.7V, 417 Ω ; (b) 264.3mW, 11W]

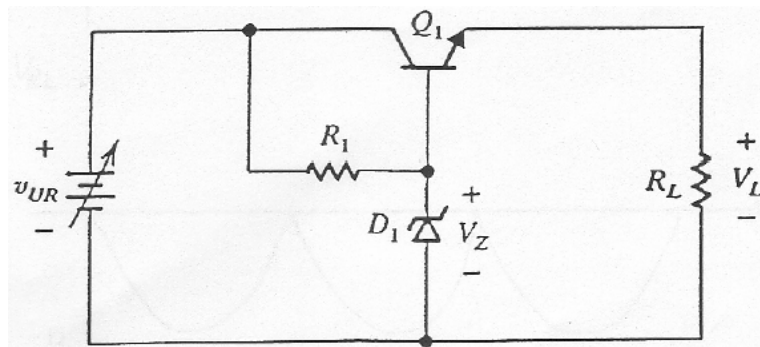


Figure 9.1

2. For the series regulator shown in Figure 9.2, assume that $R_L = 32\Omega$, $V_Z = 10V$, and for the BJTs, $\beta = 100$ and $V_{BE} = 0.7V$.
 - (a) Calculate the power efficiency of the regulator. (*Hint:* Express V_L in terms of V_Z and other components in the circuit. Verify the assumptions made in deriving V_L).
 - (b) The Zener diode voltage thermal coefficient is +3mV/K and the base-emitter voltage thermal coefficient is -2mV/K. Assuming that the Zener diode and base-emitter voltages as well as their thermal voltages have negligible change with their existing operating currents. Calculate the thermal coefficient of the output voltage.

[(a) 52.6%; (b) +1.5mV/K]

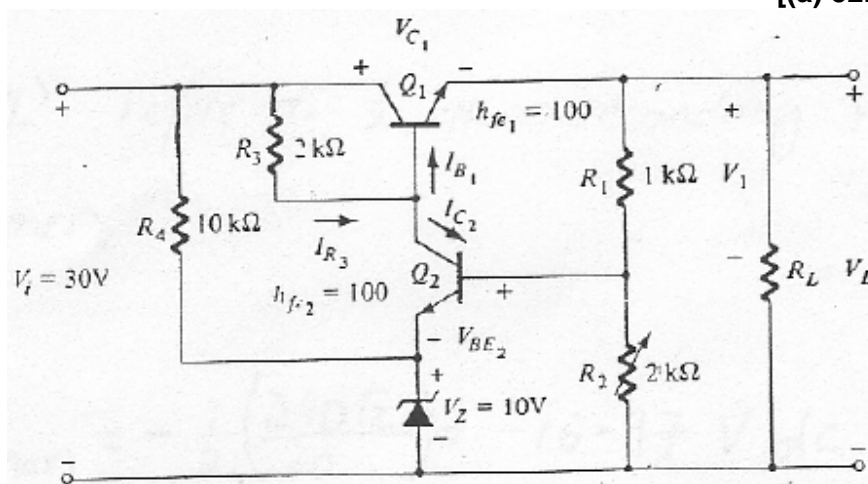


Figure 9.2

3. A simple current bias reference circuit based on the base-emitter junction voltage is depicted in Figure 9.3. Determine the sensitivity S of the output current to supply voltage V_{CC} . It is given that $I_S = 5 \times 10^{-15} \text{ A}$ and assume that $V_T = 26 \text{ mV}$.

(Hint: Assume that $V_{CC} \gg V_{BE(\text{on})}$ and use this to simplify the calculation.)

[0.04]

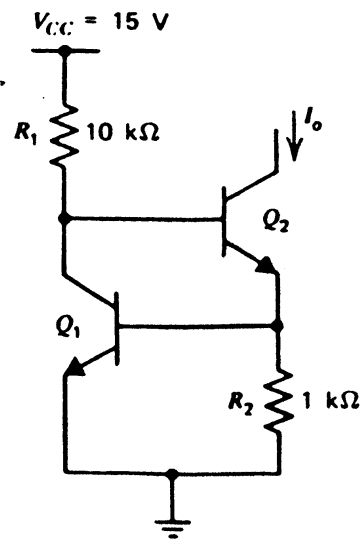


Figure 9.3