



# INTEGRATED ELECTRONICS

**Y. P. Zhang, PhD, FIEEE**

**Office: S2-B2c-90**

**[eypzhang@ntu.edu.sg](mailto:eypzhang@ntu.edu.sg)**


**Tel: 6790-4945**

**Joseph Chang**

**Office: S1-B1b-60**


**[ejschang@ntu.edu.sg](mailto:ejschang@ntu.edu.sg)**

**Tel: 6790-4424**

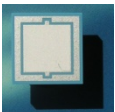


# Topics

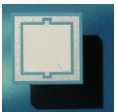- 1. Power Supplies**
- 2. Bias Circuits**
- 3. Operational Amplifiers**
- 4. Applications of Operational Amplifiers**



# Reference Textbooks

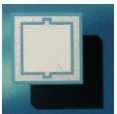1. Sedra and Smith, *Microelectronic Circuits*, 5th Edition, Oxford University Press, 2004.
2. Gray, Hurst, Lewis and Meyer, *Analysis and Design of Analogue Integrated Circuits*, 4th Edition, John Wiley & Sons, 2001.
3. Franco S, *Design with Operational Amplifiers and Analog Integrated Circuits*, 3rd Edition, McGraw-Hill, 2002.



# Power Supplies

## 1. Introduction


## 2. Rectifiers

*Half-wave, full-wave, and full-wave bridge rectifiers*

## 3. Capacitor filters

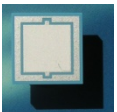
## 4. Voltage regulators

*Zener-diode circuits and series voltage regulators*


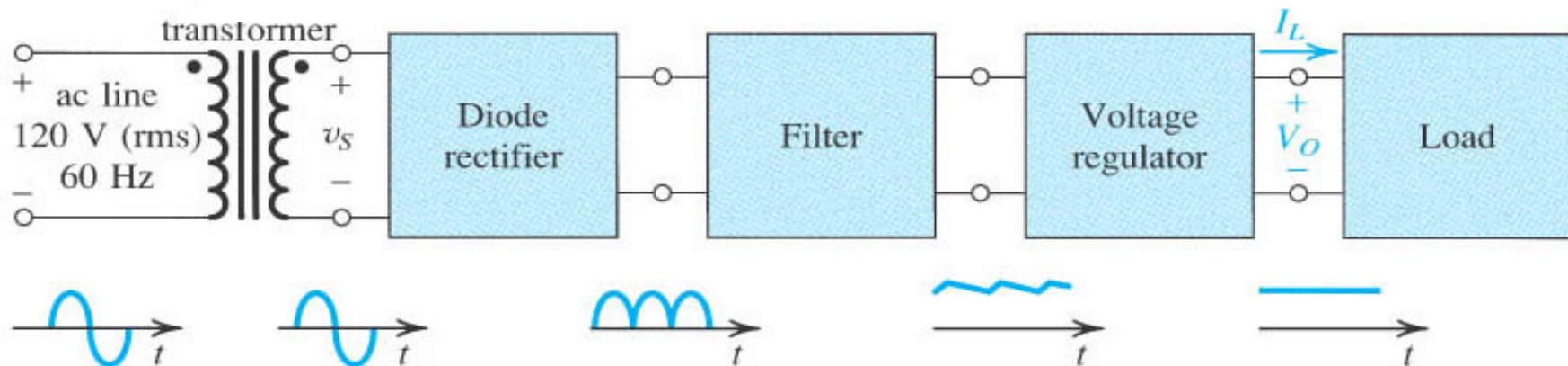
# Introduction


The design of power supply depends on the target application, ranging from providing half-wave rectified output for battery chargers to highly regulated output for precision instruments



**Rectifier converts ac to pulsating dc.**


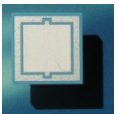
**Filter smoothes pulsating voltage .**

**Regulator maintains constant output voltage,  
under variations in line voltage and current.**


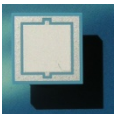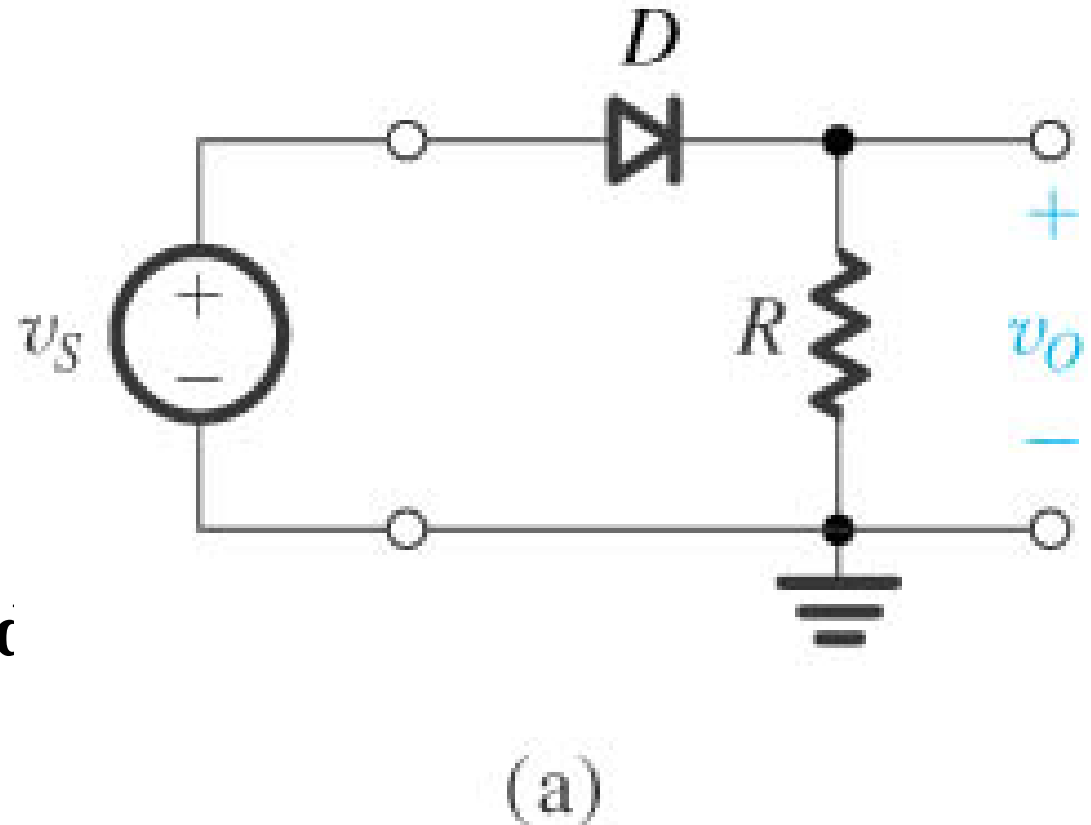
# Half-Wave Rectifier

Let the voltage drop of the conducting diode be  $V_{D0}$  (normally  $\sim 0.7\text{V}$ ). Diode does not conduct until voltage across it is greater than  $V_{D0}$  (in this figure, the  $V_{D0}$  is assumed zero).




# Half-Wave Rectifier


When  $v_S < V_{D0}$ , diode is off and  $v_O = 0$ .

When  $v_S \geq V_{D0}$ , diode conducts and


$$v_O = \frac{R}{R + r_D} v_S - \frac{R}{R + r_D} V_{D0}$$
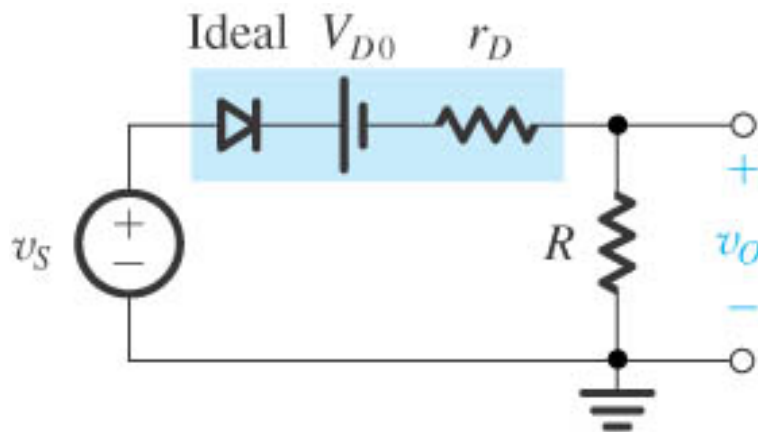
$$\approx v_S - V_{D0} \quad (r_D \ll R)$$


(b)

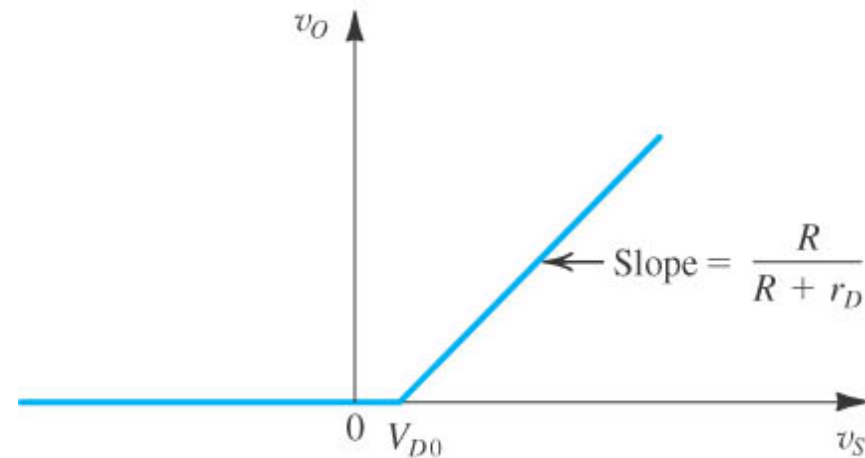



(c)

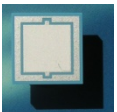
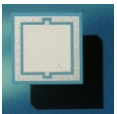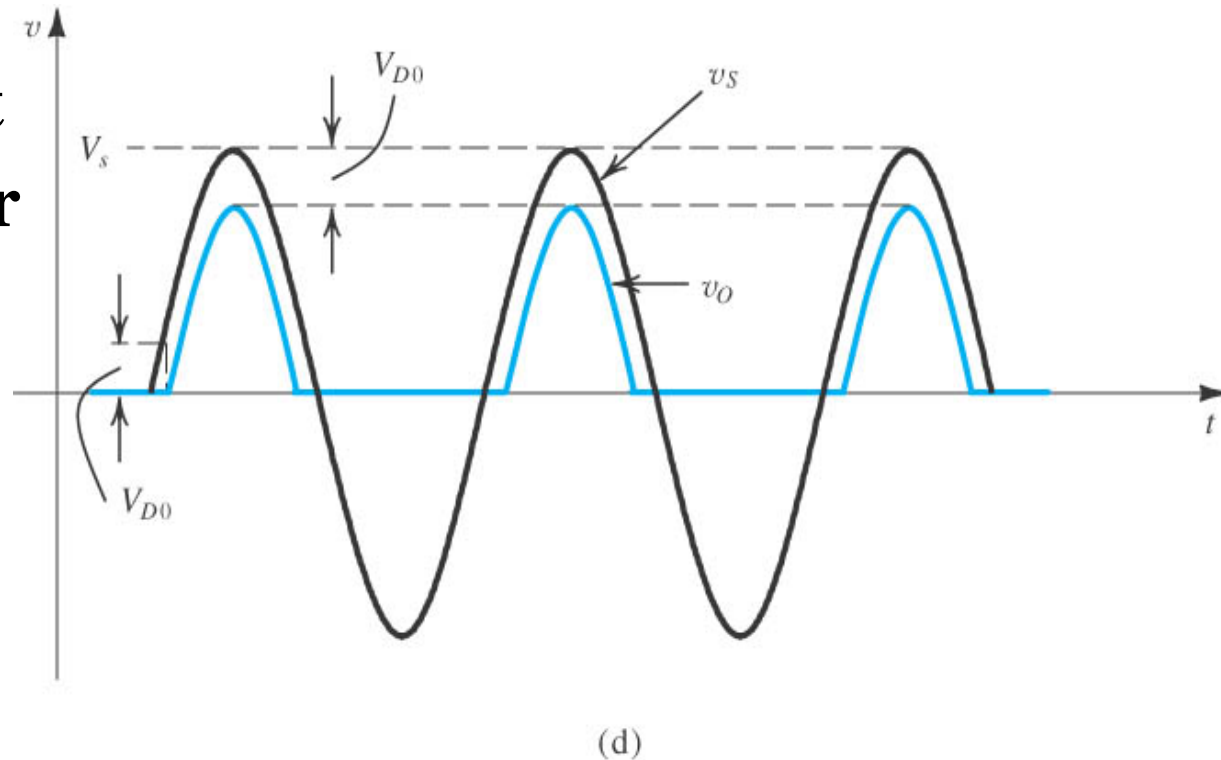
# Half-Wave Rectifier

For  $v_s(t) = V_s \sin \omega t$ ,  
diode starts to conduct  
when  $V_s \sin \omega t = V_{D0}$  or  
in terms of conduction  
angle,

$$\omega t = \sin^{-1} \frac{V_{D0}}{V_s}$$





# Half-Wave Rectifier

**Diode stops conduction when**  $\omega t = \pi - \sin^{-1} \frac{V_{D0}}{V_S}$

**So for the first period, output voltage**  $v_O = V_S \sin \omega t - V_{D0}$


**for**  $\left\{ \sin^{-1} \frac{V_{D0}}{V_S} \leq \omega t \leq \pi - \sin^{-1} \frac{V_{D0}}{V_S} \right\}$

**and**  $v_O = 0$  , **for**  $\left\{ 0 \leq \omega t \leq \sin^{-1} \frac{V_{D0}}{V_S} \text{ and } \pi - \sin^{-1} \frac{V_{D0}}{V_S} \leq \omega t \leq 2\pi \right\}$

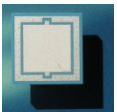**If**  $V_S \gg V_{D0}$  , **then**  $\sin^{-1} \frac{V_{D0}}{V_S} \rightarrow 0$  , **so we have**

$$v_O = (V_S - V_{D0}) \sin \omega t \quad \text{for } 0 \leq \omega t \leq \pi$$


$$v_O = 0 \quad \text{for } \pi \leq \omega t \leq 2\pi$$


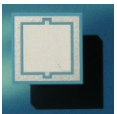
# Half-Wave Rectifier

To find the average load voltage, we have

$$\begin{aligned} v_{O(av)} &= \frac{1}{2\pi} \int_0^{2\pi} v_O(\omega t) d\omega t \\ &= \frac{1}{2\pi} \int_0^{\pi} (V_S - V_{D0}) \sin \omega t d\omega t \\ &= \frac{V_S - V_{D0}}{2\pi} \int_0^{\pi} \sin \omega t d\omega t \quad \left( = [-\cos \omega t]_0^{\pi} = 2 \right) \\ &= \frac{V_S - V_{D0}}{\pi} \approx \frac{V_S}{\pi} \end{aligned}$$




# Half-Wave Rectifier

To determine the rms value of  $v_o$ ,

$$v_{O(rms)} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} v_o^2(\omega t) d\omega t} = \frac{V_S - V_{D0}}{2} \approx \frac{V_S}{2}$$

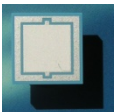**Ripple factor  $\gamma$  is a measure of the ac content of a waveform, it is defined as:**

$$\gamma = \frac{\text{rms value of ac component}}{\text{dc (average) component}} = \frac{v_{O(ac,rms)}}{v_{O(av)}}$$



# Half-Wave Rectifier


It would be ideal if  $\gamma = 0$ , i.e. no ac component.

To find  $v_{o(ac,rms)}$ , note that rms value measures the power dissipation or heating effect of a waveform on a load.

Let  $R$  be the load resistor. Then  $P_R = \frac{v_{o(rms)}^2}{R}$

This has to be the same as the combined heating effects of the ac and dc (av) components:

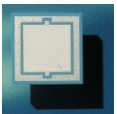
$$P_R = \frac{v_{o(rms)}^2}{R} = \left( \frac{v_{o(ac,rms)}^2}{R} + \frac{v_{o(av)}^2}{R} \right)$$


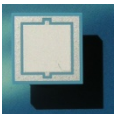
# Half-Wave Rectifier

This gives,  $v_{O(ac,rms)} = \sqrt{v_{O(rms)}^2 - v_{O(av)}^2}$ , and

$$\gamma = \frac{\sqrt{v_{o(rms)}^2 - v_{o(av)}^2}}{v_{o(av)}} = \sqrt{\frac{(V_S / 2)^2}{(V_S / \pi)^2} - 1} = \sqrt{\frac{\pi^2}{4} - 1} = 1.21$$




# Half-Wave Rectifier

**Peak inverse voltage (PIV) rating of a diode determines its maximum permissible reverse biased voltage without breakdown.**

**In the Half-Wave Rectifier circuit, when  $v_s$  is negative, the diode is reverse biased and  $v_o=0$ ,**



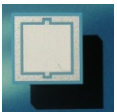
**The maximum reverse biased voltage experienced by the diode is  $V_s$  and we have to choose a diode with a minimum  $PIV = V_s$ .**



# Half-Wave Rectifier

**Example 1:** A half-wave rectifier using diode for which  $V_{D0} = 0.7\text{V}$ , is supplied by an  $8V_{\text{rms}}$  sine wave at 50 Hz.

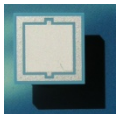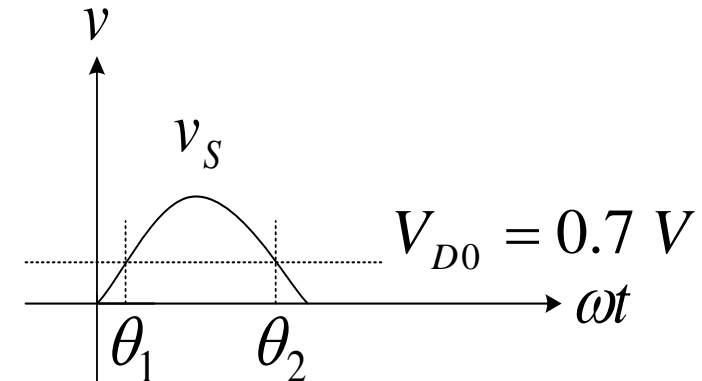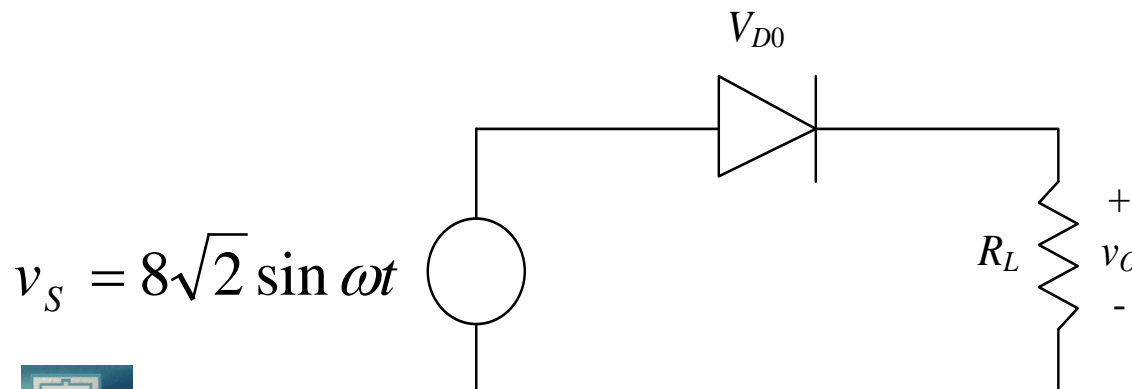- (a) What is the peak value of the output voltage?
- (b) For what fraction of a cycle does the diode conduct?
- (c) What is the average value of the output voltage?



# Half-Wave Rectifier


(a) **Peak output** =  $V_S - V_{D0} = 8\sqrt{2} - 0.7 = 10.6 \text{ V}$

**Diode starts to conduct when voltage across it is equal to 0.7 V, so**  $V_S \sin \omega t = V_{D0}$  **or**  $\theta_1 = \omega t_1 = \sin^{-1} \frac{V_{D0}}{V_S} = \sin^{-1} \frac{0.7}{8\sqrt{2}} = 3.55^\circ$

**Diode stops conducting when**  $\theta_2 = \pi - \sin^{-1} \frac{V_{D0}}{V_S} = 176.45^\circ$

(b) **So diode conducts for**  $\frac{\theta_2 - \theta_1}{360^\circ} = \frac{176.45^\circ - 3.55^\circ}{360^\circ} = 48\%$

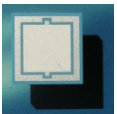(c) **Average output:**  $v_{O(av)} = \frac{V_S - V_{D0}}{\pi} = 3.37 \text{ V}$






# Full-Wave Rectifier


For  $v_S$  sufficiently positive,  $D_1$  conducts and  $D_2$  is reverse biased.

For  $v_S$  sufficiently negative,  $D_2$  conducts and  $D_1$  is reverse biased.


$$PIV = 2V_S - V_{D0} \approx 2V_S$$

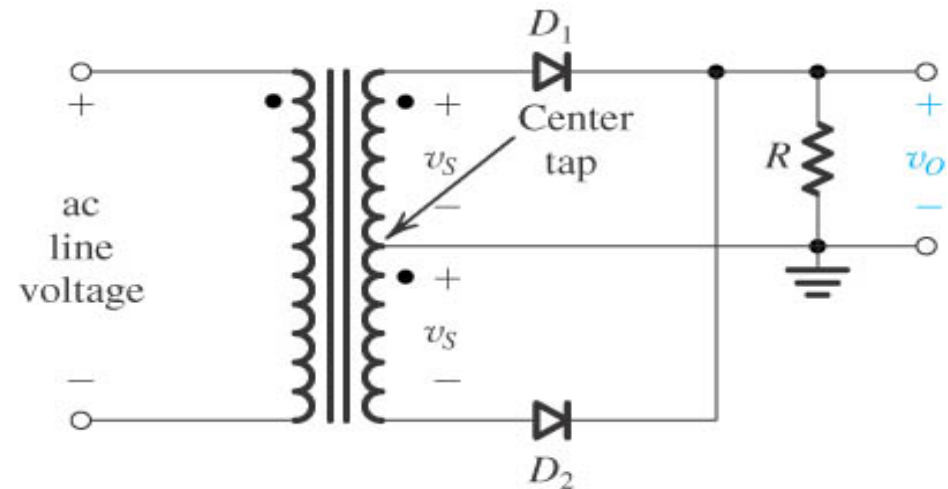

(a)

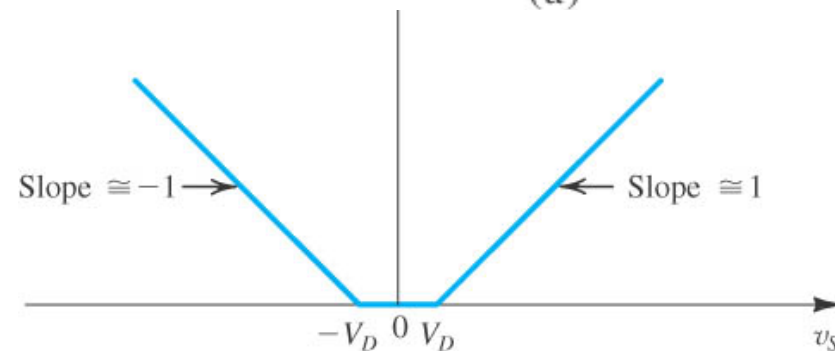

(b)

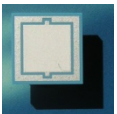


# Full-Wave Rectifier

$$v_o = V_S \sin \omega t - V_{D0}$$


**when**

$$\left\{ \sin^{-1} \frac{V_{D0}}{V_S} \leq \omega t \leq \pi - \sin^{-1} \frac{V_{D0}}{V_S} \right\}$$

$$v_o = 0$$

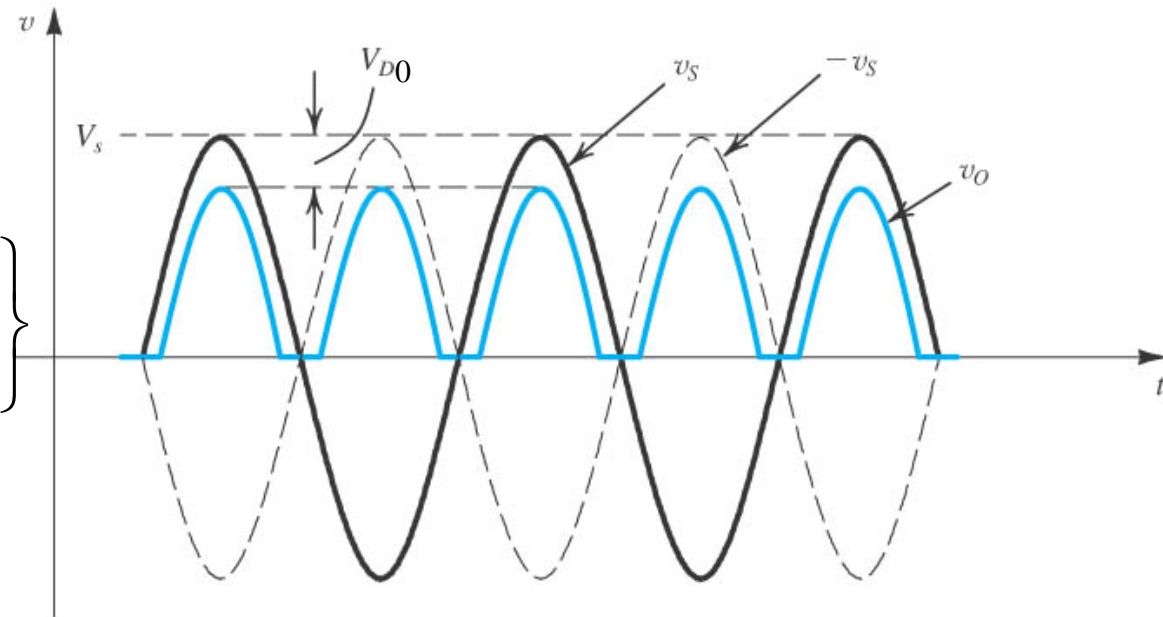

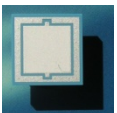for  $\left\{ 0 \leq \omega t \leq \sin^{-1} \frac{V_{D0}}{V_S} \text{ and } \pi - \sin^{-1} \frac{V_{D0}}{V_S} \leq \omega t \leq \pi \right\} \quad (c)$



# Full-Wave Rectifier


If  $V_s \gg V_{D0}$ , then  $v_o = (V_s - V_{D0}) \sin \omega t$  for  $0 \leq \omega t \leq \pi$

The average component can be similarly found as

$$v_{o(av)} = \frac{1}{2\pi} \int_0^{2\pi} v_o(\omega t) d\omega t \approx \frac{2V_s}{\pi}$$

and the rms value as
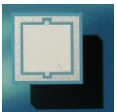
$$v_{o(rms)} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} v_o^2(\omega t) d\omega t} = \frac{V_s - V_D}{\sqrt{2}} \approx \frac{V_s}{\sqrt{2}}$$




# Full-Wave Rectifier

Hence the ripple factor can be calculated:

$$\gamma = \frac{v_{o(ac,rms)}}{v_{o(av)}} = \frac{\sqrt{v_{o(rms)}^2 - v_{o(av)}^2}}{v_{o(av)}} = \sqrt{\frac{\pi^2}{8} - 1} = 0.483$$

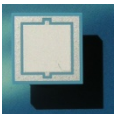As expected, the full-wave rectifier has smaller ripple factor than that of half-wave rectifier.





# Full-Wave Bridge Rectifier

No need for center-tapped transformer.

$V_S \sin \omega t$  positive,  
 $D_1$  and  $D_2$  conduct.


$V_S \sin \omega t$  negative,  
 $D_3$  and  $D_4$  conduct.

$$PIV = V_S - V_{D0}$$

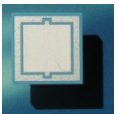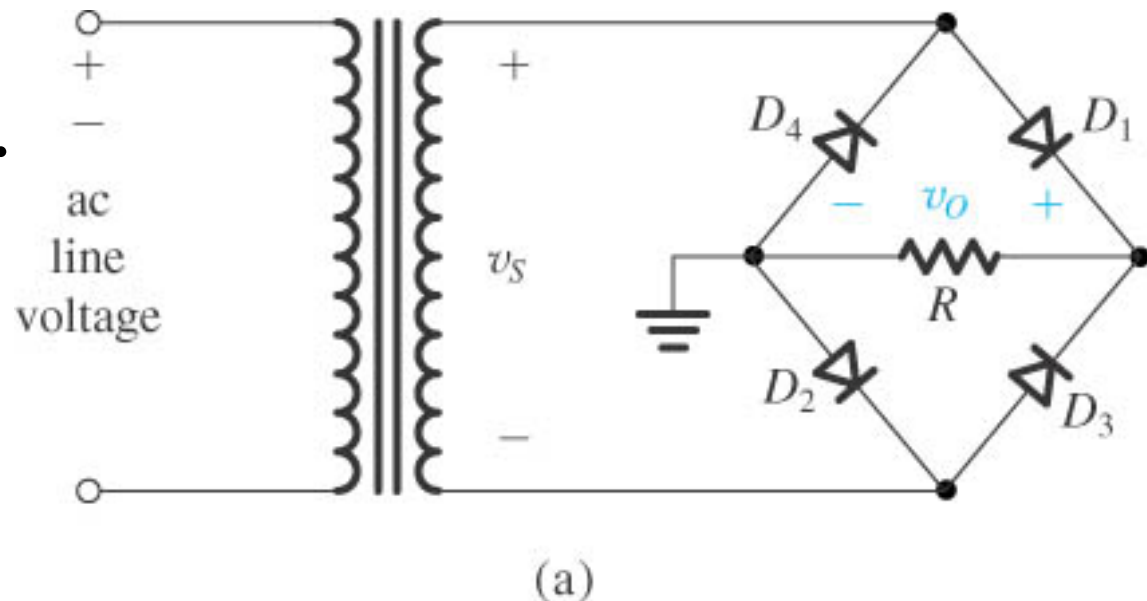

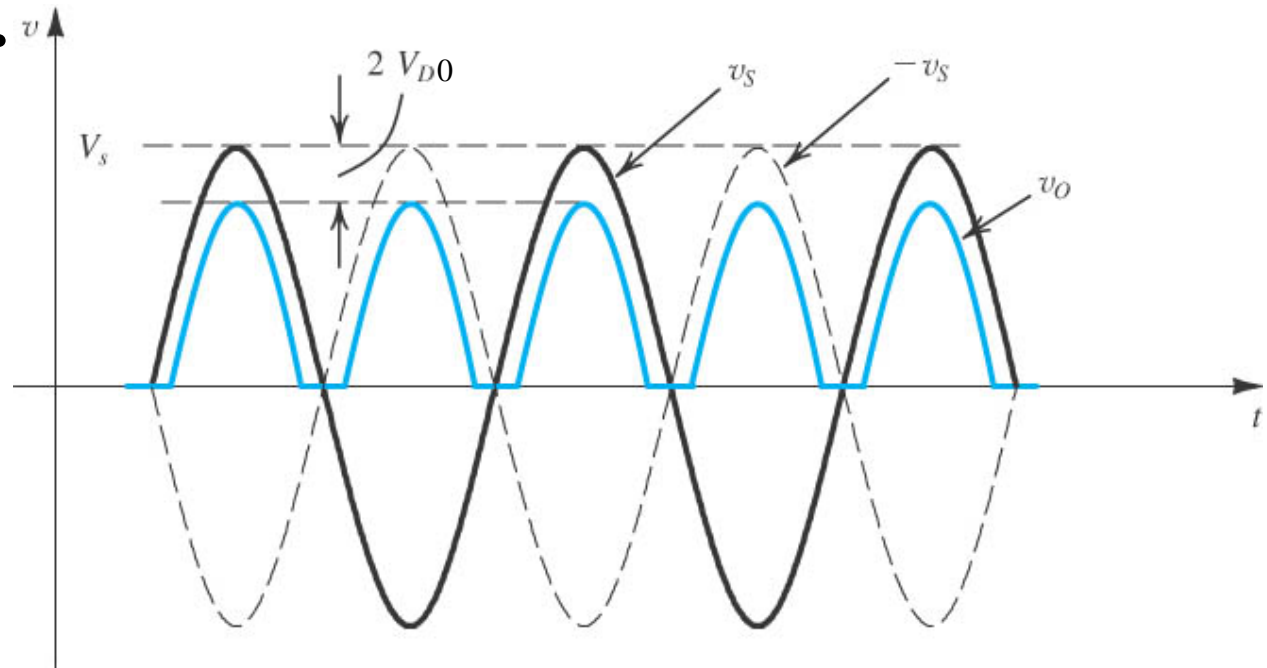
# Full-Wave Bridge Rectifier

Equations for full-wave rectifier are valid in full-wave bridge rectifier, except that the total diode voltage drop is  $2V_{D0}$  instead of  $V_{D0}$ .





(b)

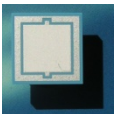

# Full-Wave Bridge Rectifier

**Example 2:** A transformer secondary winding whose output is  $12V_{\text{rms}}$  sinusoid at 50 Hz is used to drive a bridge rectifier, whose diodes' conduction can be modeled by 0.7V drops. The load is a  $1k\Omega$  resistor.

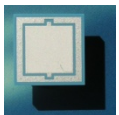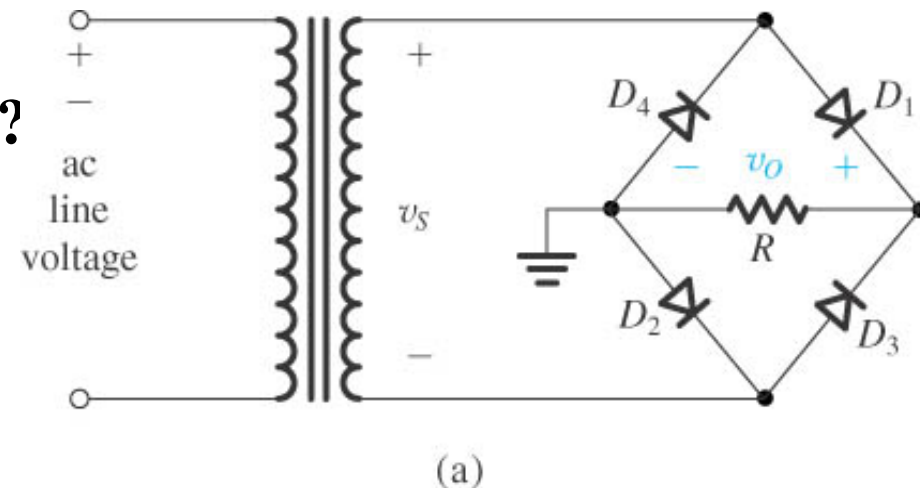- (a) Sketch the load voltage waveform.
- (b) What is the peak value?
- (c) Over what time interval is it zero?
- (d) What is the average value?
- (e) What is the PIV for each diode?



# Full-Wave Bridge Rectifier

(a) The load voltage waveform as shown on page 22.

(b) The transformer peak voltage,  $V_s = 12\sqrt{2} = 16.97 \text{ V}$



Load peak voltage,  $V_o = 16.97 - 2 \times 0.7 = 15.57 \text{ V}$

(c) From the figure below, we have  $V_s \sin \theta_1 = 2V_{D0}$

$$\theta_1 = \sin^{-1} \frac{2V_{D0}}{V_s} = \sin^{-1} \frac{1.4}{16.97} = 4.73^\circ$$

Within one period, there are four such intervals, so the time interval in one period:
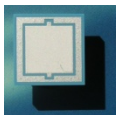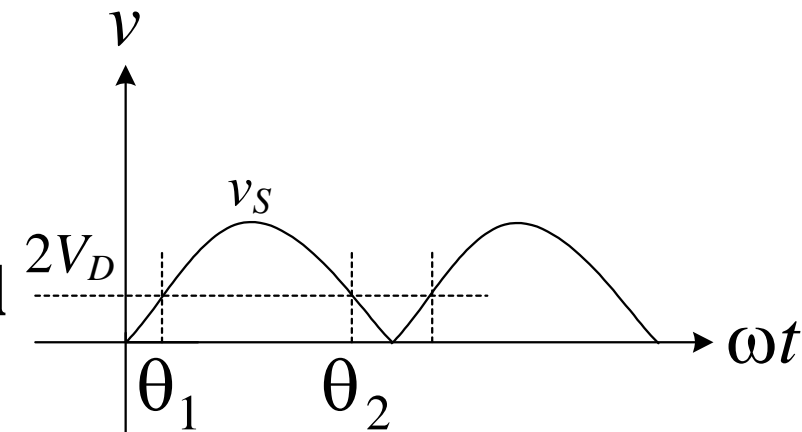
$$\frac{4 \times 4.73^\circ}{360^\circ} \times \frac{1}{50} = 1.05 \text{ ms}$$






# Full-Wave Bridge Rectifier

**(d) The average output**

$$V_{o(av)} = \frac{2(V_S - 2V_{D0})}{\pi} = 9.91 \text{ V}$$

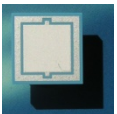**(e) PIV for each diode:**

$$V_{PIV} = V_S - V_{D0} = 16.97 - 0.7 = 16.27 \text{ V}$$




# Filter

**For 50 Hz ac source, rectified output comprises: dc component, ac fundamental component of 50 Hz, and ac harmonic components that are integer multiples of 50Hz.**

**For smooth output voltage, the ac components have to be removed or reduced. A low pass filter needs to be used to filter those ac components.**

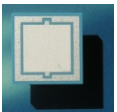**The quality of the filtered voltage is expressed by the ripple factor. A good filter should greatly reduce the ripple factor.**





# Filter

With a load  $R$  connected across the capacitor, the capacitor discharges when the diode is off.

Capacitor will be charged up to  $V_P$  when the diode conducts for  $v_O < v_I$ .

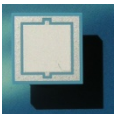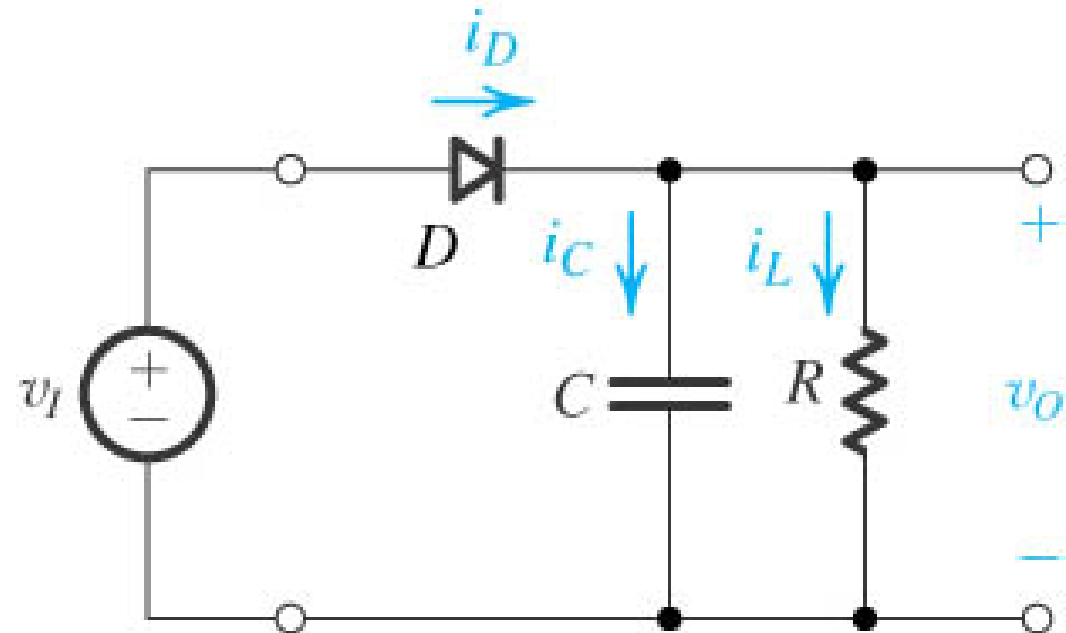$RC \gg T$ , the input period to reduce the output voltage drop.





# Filter

Since  $RC \gg T$ , it can be shown that the peak-to-peak ripple voltage:

$$V_r \approx \frac{V_P}{fRC}$$

where  $f = 1/T$  is the input frequency. The output dc (average) voltage:



$$V_o = V_P - \frac{1}{2}V_r$$

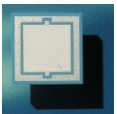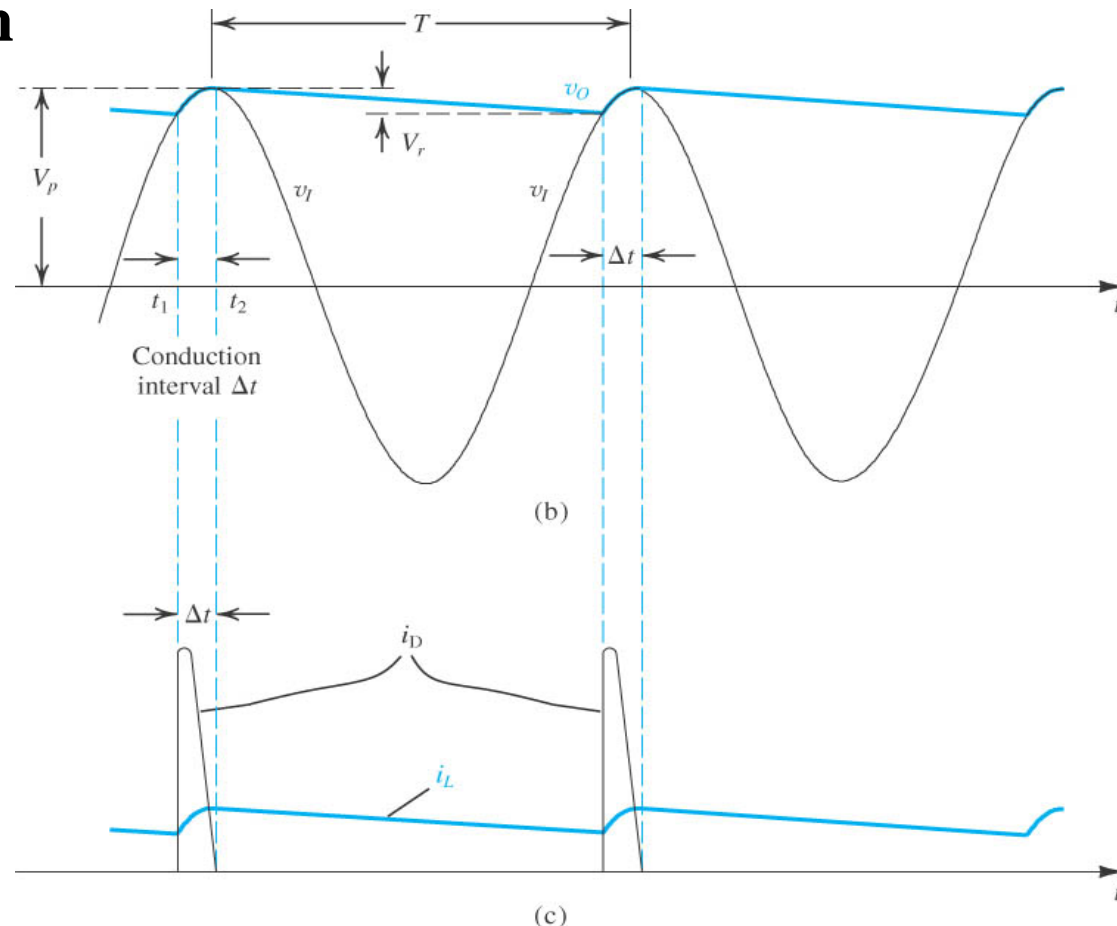

# Filter

**For Full-Wave Rectifier, with  $RC \gg T$ , the peak-to-peak ripple voltage is:**

$$V_r \approx \frac{V_P}{2fRC}$$

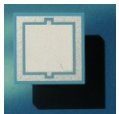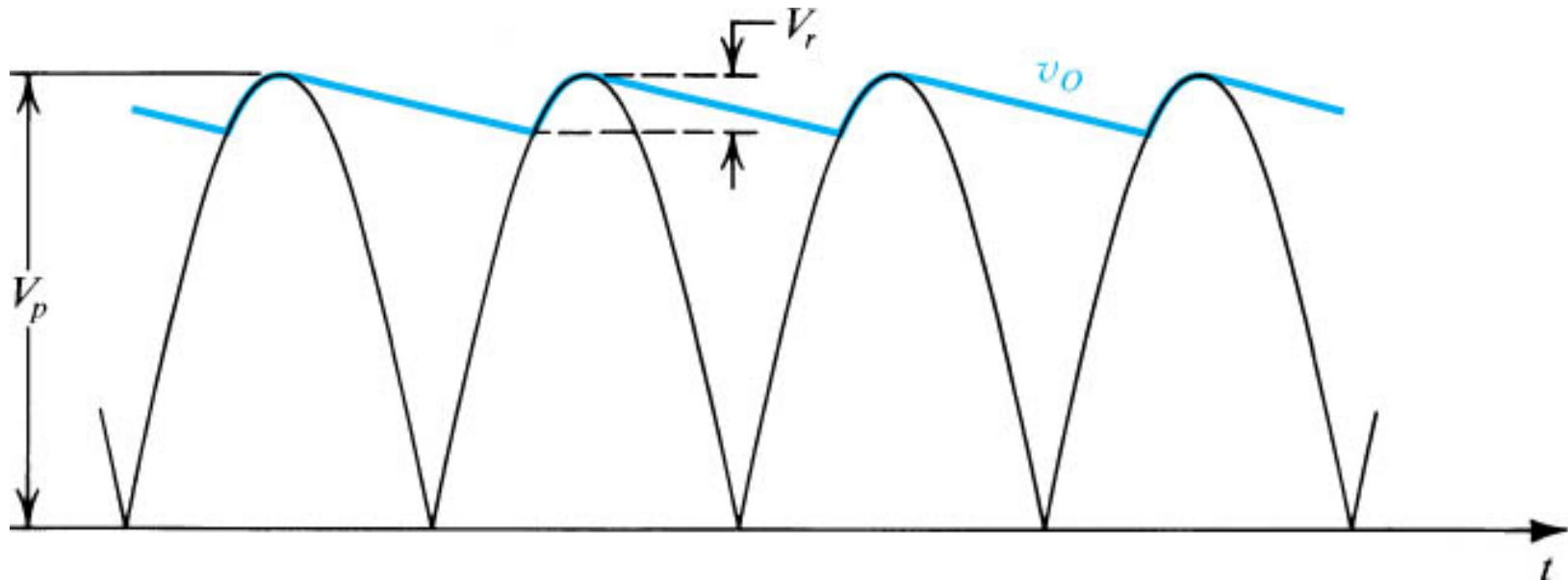

# Filter


**Example 3:** A full-wave bridge rectifier with a capacitor filter is driven by a 50Hz 12V<sub>rms</sub> sinusoid to drive a 100Ω load. The ripple voltage should not exceed 0.4V peak-to-peak. Assume that diodes' conduction can be modeled by 0.7V drops, determine the required capacitance of the filter capacitor and the dc output.

**(a) The filter capacitor peak input voltage is:**

$$V_P = 12 \times \sqrt{2} - 2V_{D0} = 12 \times \sqrt{2} - 2 \times 0.7 = 15.57 \text{ V and } R_L = 100 \Omega$$

**Hence,** 
$$C = \frac{V_P}{2fRV_r} = \frac{15.57}{2 \times 50 \times 100 \times 0.4} = 3892.5 \mu\text{F}$$

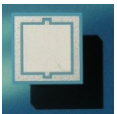**(b) The dc output voltage is:** 
$$V_O = V_P - \frac{1}{2}V_r = 15.57 - \frac{1}{2} \times 0.4 = 15.37 \text{ V}$$




# Voltage Regulator

**An ideal voltage regulator maintains a constant dc output voltage, irrespective of external factors.**

**Output voltage from a practical voltage regulator is affected by a number of factors, such as:**

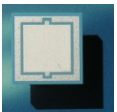- (a) Load variations**
- (b) Line variations**
- (c) Ambient temperature variations**





# Voltage Regulator

**Load regulation is the change in output voltage (or current for current source) for any given load change within the specified limits, with the other factors such as input line voltage and ambient temperature held constant. The specified limit is usually the no-load voltage and the full-load voltage.**

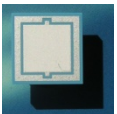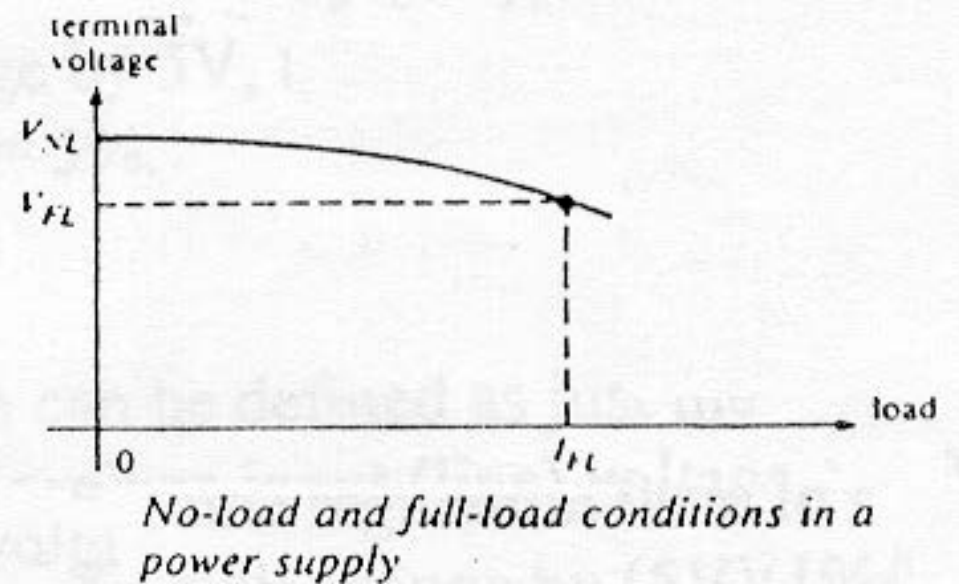**Load regulation is defined as:**

$$VR = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100\%$$







# Voltage Regulator

Model the power supply with Thevenin equivalent circuit, with an output resistance  $R_o$ . Note that the slope of load voltage versus load current gives the output resistance:

$$R_o = \frac{\Delta V_L}{\Delta I_L}$$

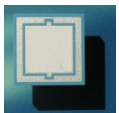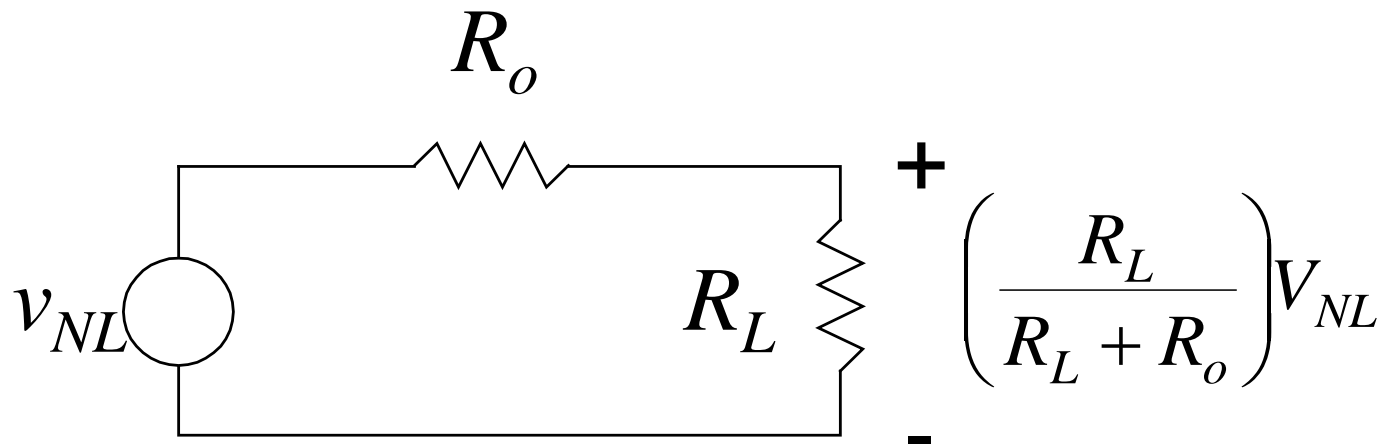

# Voltage Regulator


In general, the terminal voltage changes nonlinearly with load current (e.g. see earlier  $V_L$  vs  $I_L$  plot). The result is that output resistance  $R_o$  depends on the actual load current.

Since we are usually concerned with the performance of a power supply at its rated or full-load output,  $R_o$  is usually specified as full-load. Let the full-load resistance be

$$R_{FL} = \frac{V_{FL}}{I_{FL}}$$

By voltage-divider,
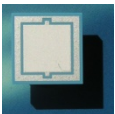
$$V_{FL} = \left( \frac{R_{FL}}{R_{FL} + R_o} \right) V_{NL}$$




# Voltage Regulator

**Load regulation is calculated by:**

$$VR = \frac{V_{NL} - \left( \frac{R_{FL}}{R_{FL} + R_o} \right) \cdot V_{NL}}{\left( \frac{R_{FL}}{R_{FL} + R_o} \right) \cdot V_{NL}} = \frac{R_o}{R_{FL}} = R_o \left( \frac{I_{FL}}{V_{FL}} \right)$$

**Comments:**  $VR \propto R_o$ . If  $R_o = 0$ , then  $VR = 0$  % .

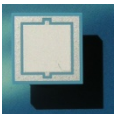**Low  $R_o$  is essential for low load regulation.**




# Voltage Regulator

**Line regulation is the percentage change in the output voltage that occurs per one-volt change in input (line) voltage.**

**Line regulation is defined as:**

$$\frac{\Delta V_o / V_o}{\Delta V_{in}} \times 100\% \quad (\text{unit} = \% / \text{V})$$



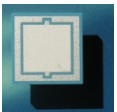
**If the input to power supply having a 1%/V line regulation is to change by 5 V, then the output will change by (5 V)( 1%/V) = 5 %.**



# Voltage Regulator



**Zener diodes are also called breakdown diodes and widely used in realizing voltage regulator.**

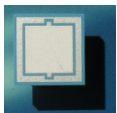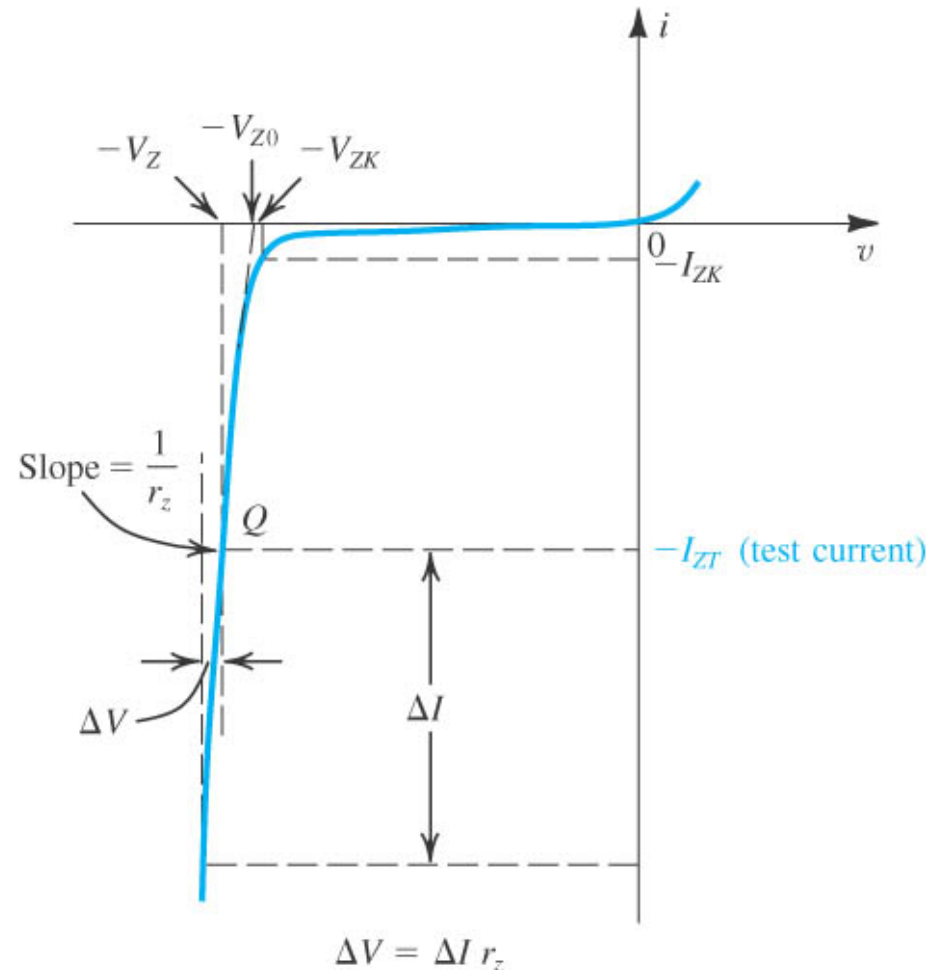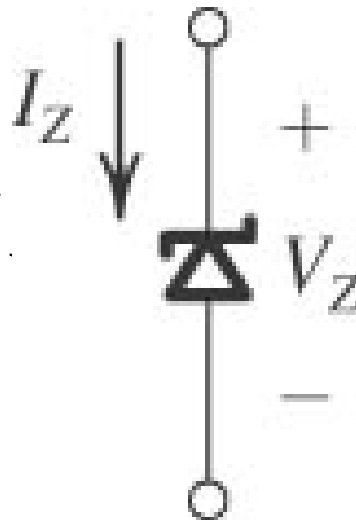**Zener diodes are to be used in the reverse region.**


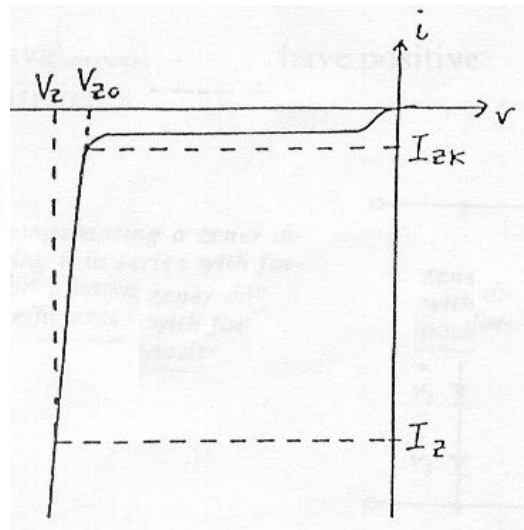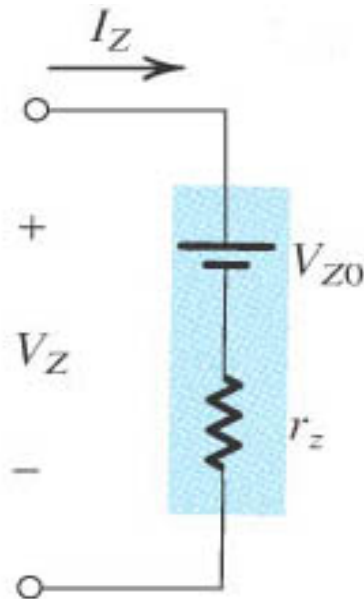
# Voltage Regulator

The breakdown characteristics of an ideal Zener diode is a perfectly vertical line, signifying zero change in voltage, for any change in current.




$$V_Z = V_{Z0} + r_Z (I_Z - I_{ZK})$$

for  $I_Z > I_{ZK}$



and  $V_Z > V_{Z0}$

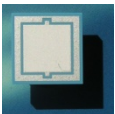where  $r_Z$  is the incremental or dynamic resistance.  $I_{ZK}$  is the knee current, min  $I$  required to drive the Zener diode to obtain reverse breakdown. The corresponding voltage is called knee voltage.



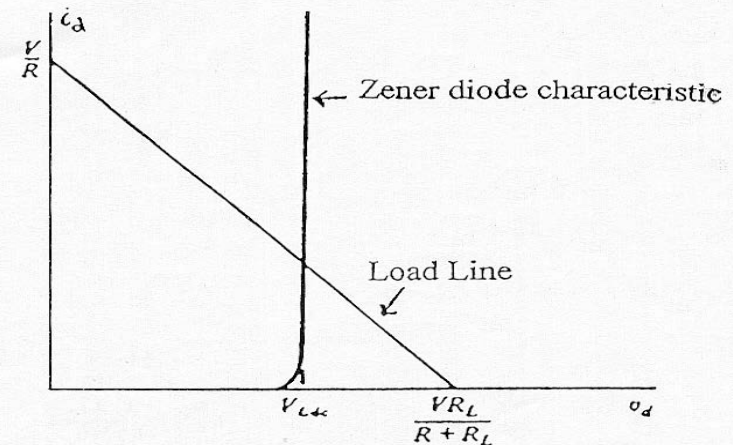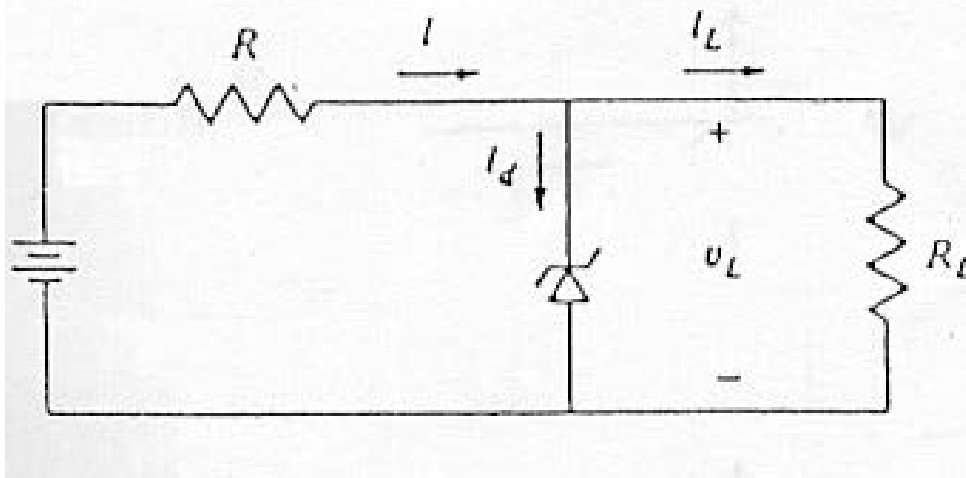
# Voltage Regulator

The Zener diode is connected in parallel with load. As long as unregulated power supply is large enough to cause reverse breakdown,  $V_L$  is almost constant. Suppose the unregulated voltage changes, load line shifts parallel to itself. Suppose  $R_L$  changes, slope of load line changes. However, in both cases,  $V_L$  changes little. Any changes in  $V_L$  depend on the characteristics of the Zener diode.



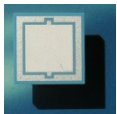The voltage-current characteristics for a Zener diode. Note that the breakdown region (reverse bias) is plotted.



# Voltage Regulator


**Example 5:** A 6.8 V Zener diode specified at 5mA with  $r_Z = 20\Omega$  and  $I_{ZK} = 0.2\text{mA}$ , is operated in a regulator circuit using a  $200\Omega$  resistor. For no-load, what is the lowest supply voltage for which the Zener remains in breakdown operation? For a supply voltage of 9 V, what is the maximum load current for which the Zener remains in breakdown operation?

Since  $V_Z = 6.8 \text{ V}$ ,  $I_Z = 5 \text{ mA}$ ,  $r_Z = 20\Omega$ ,  $I_{ZK} = 0.2 \text{ mA}$ ,

$$V_Z = V_{ZO} + r_Z(I_Z - I_{ZK})$$

$$V_{ZO} = V_Z - r_Z(I_Z - I_{ZK})$$
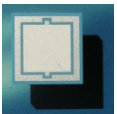
$$= 6.8 - (5 - 0.2) \times (20) \times 10^{-3} = 6.7 \text{ V}$$





# Voltage Regulator

**For no-load breakdown,**

$$V_{S(\text{lowest})} = V_{ZO} + I_{zk} \times 200 = 6.74 \text{ V}$$

**Supply voltage lower than this,**



**no breakdown.  $I_S = I_{ZK} + I_L$**

**From the diagram,**

$$I_S = \frac{9 - 6.7}{200} = 11.5 \text{ mA}$$

**So, the maximum load current for which the Zener remains in**

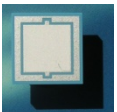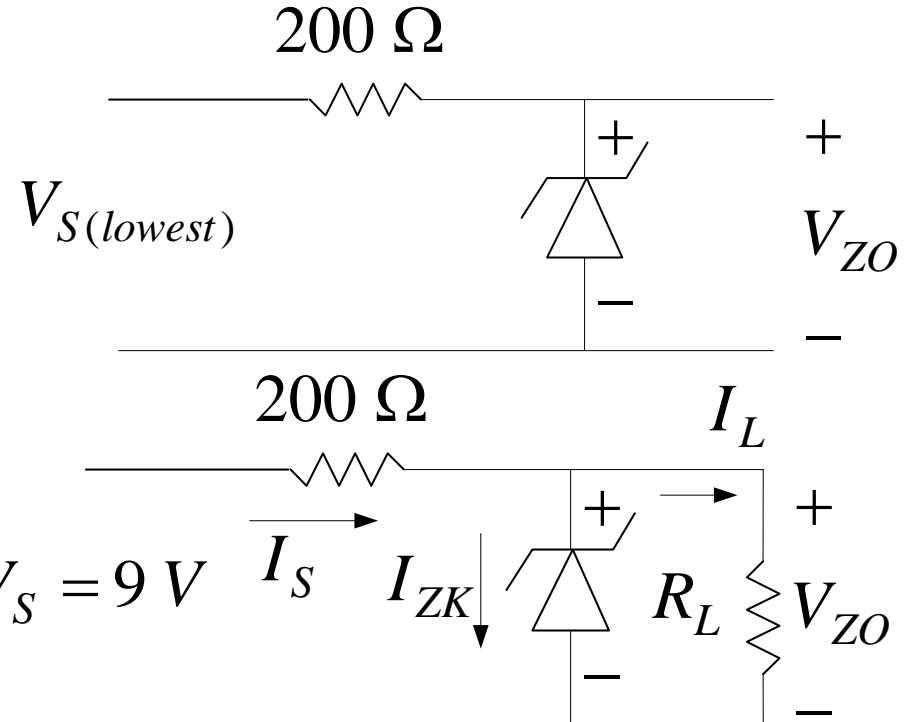**breakdown:  $I_L = I_S - I_{ZK} = 11.5 - 0.2 = 11.3 \text{ mA}$**




# Voltage Regulator

**Zener diodes are available with breakdown voltage ranging from 2.4 V to 200 V. Temperature coefficient of a Zener diode:**

$$T.C. = \frac{\Delta V_Z}{\Delta T} \quad (mV / ^\circ C)$$


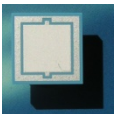
**Low-voltage Zener diodes (<5 V) break down by *Zener mechanism* have *negative* temperature coefficients. Between 5 V and 8 V, both avalanching and Zener mechanisms contribute to breakdown; the coefficients may be positive or negative, depending on current.**


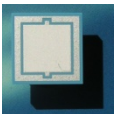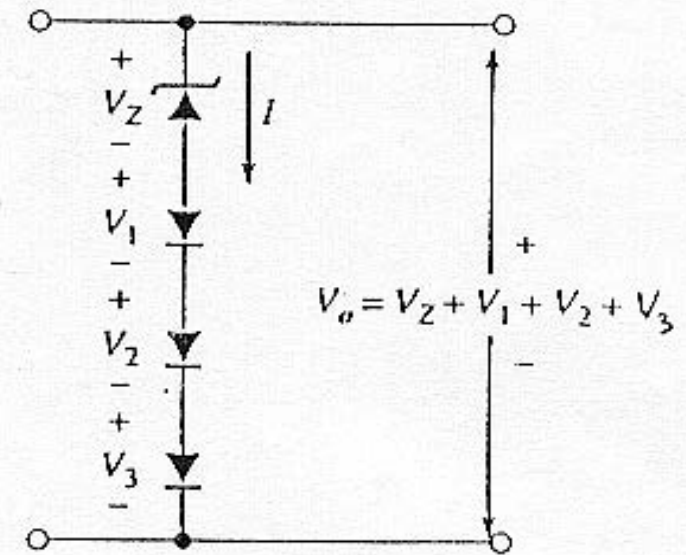
# Voltage Regulator

Higher-voltage avalanche Zener diodes have positive temperature coefficients. Temperature-compensated Zener diodes are available, but must be operated at manufacture's specified value.

Temperature compensating a Zener diode by connecting it in series with forward-biased diodes having opposite temperature coefficients.



# Voltage Regulator

For the simple circuit, Zener current is sensitive to fluctuation in unregulated voltage  $V_S$ . To improve regulation, it is important to keep Zener current insensitive to unregulated voltage  $V_S$  changes.

**Operation:**

$$\begin{aligned} V_{REF} &= V_Z + V_{BEQ_1} = V_{ZO} + I_Z r_Z + V_{BEQ_1} \\ &= V_{ZO} + V_{BEQ_1} \left(1 + \frac{r_Z}{R_{SC}}\right) \end{aligned}$$

So  $V_{REF}$  is not sensitive to  $V_S$  changes.  
To further prevent changes in the Zener current, the reference output is usually fed into a very high impedance op-amp.

