



---

# Input Signal Range of BJT and MOSFET

Assoc Prof Chang Chip Hong

email: [echchang@ntu.edu.sg](mailto:echchang@ntu.edu.sg)

---

**EE2002 Analog Electronics**



# Lesson Objectives

At the end of this lesson, you should be able to:

- Derive the small signal operation criterion for BJT and MOSFET
- Analyse the input signal range of BJT and MOSFET

# Small-Signal Operation of BJT

$$i_C \approx I_S \exp\left(\frac{v_{BE}}{V_T}\right) = I_S \exp\left(\frac{V_{BE} + v_{be}}{V_T}\right)$$

$$\therefore i_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right) \exp\left(\frac{v_{be}}{V_T}\right) = I_C \left[ 1 + \frac{v_{be}}{V_T} + \frac{1}{2!} \left(\frac{v_{be}}{V_T}\right)^2 + \frac{1}{3!} \left(\frac{v_{be}}{V_T}\right)^3 + \dots \right]$$

$$i_c = i_C - I_C = I_C \left[ \frac{v_{be}}{V_T} + \frac{1}{2} \left(\frac{v_{be}}{V_T}\right)^2 + \frac{1}{6} \left(\frac{v_{be}}{V_T}\right)^3 + \dots \right]$$

For linearity,  $i_c$  should be proportional to  $v_{be}$ .

$$\frac{1}{2} \left(\frac{v_{be}}{V_T}\right)^2 \ll \frac{v_{be}}{V_T} \Rightarrow |v_{be}| \ll 2V_T = 0.05 \text{ V} \Rightarrow |v_{be}| \leq 0.005 \text{ V}$$

# C-E Amplifier Input Signal Range

For BJT small-signal operation,  $|v_{be}| \leq 5 \text{ mV}$ .



$$|v_{be}| = i_b r_\pi = \frac{|v_b| r_\pi}{R'_{in}} = \frac{|v_b| r_\pi}{r_\pi + (\beta + 1) R_{E1}}$$

$$|v_{be}| \leq 0.005$$

$$\Rightarrow |v_b| \leq 0.005 \left( \frac{r_\pi + (\beta + 1) R_{E1}}{r_\pi} \right)$$

$$\because \beta + 1 \approx \beta = g_m r_\pi, \quad |v_b| \leq 0.005 (1 + g_m R_{E1})$$

$$\because v_b = \left( \frac{R_{in}}{R_I + R_{in}} \right) v_i \Rightarrow |v_i| \leq 0.005 (1 + g_m R_{E1}) \left( \frac{R_I + R_{in}}{R_{in}} \right)$$

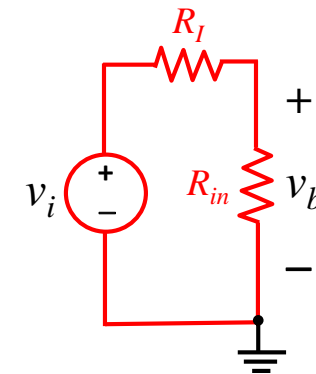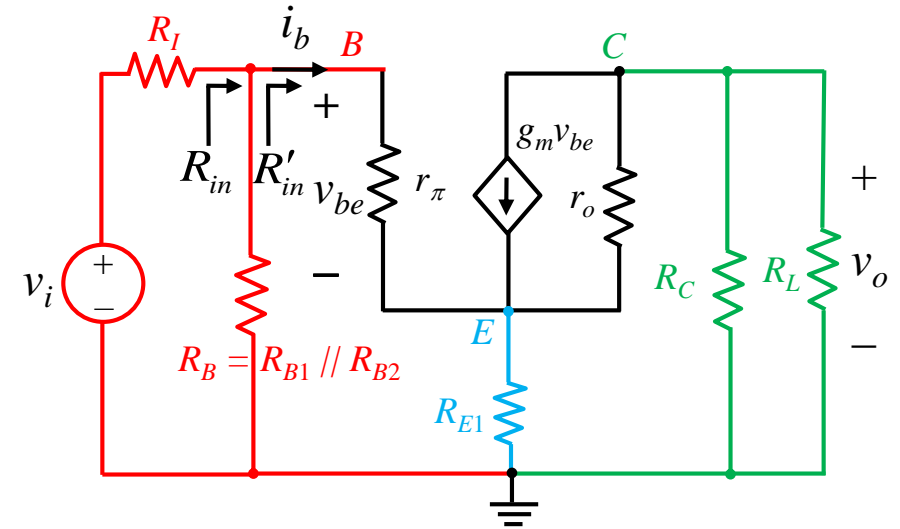



# C-C Amplifier Input Signal Range

For BJT small-signal operation,  $|v_{be}| \leq 5 \text{ mV}$ .

$$|v_{be}| = i_b r_\pi = \frac{|v_b| r_\pi}{R'_{in}} = \frac{|v_b| r_\pi}{r_\pi + (\beta + 1) R'_L}$$

$$\Rightarrow |v_b| \leq 0.005 \left( \frac{r_\pi + (\beta + 1) R'_L}{r_\pi} \right) \approx 0.005 (1 + g_m R'_L)$$

$$\because v_b = \left( \frac{R_{in}}{R_I + R_{in}} \right) v_i \Rightarrow |v_i| \leq 0.005 (1 + g_m R'_L) \left( \frac{R_I + R_{in}}{R_{in}} \right)$$

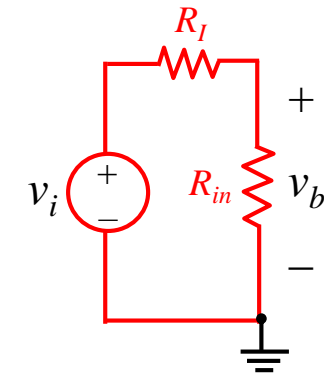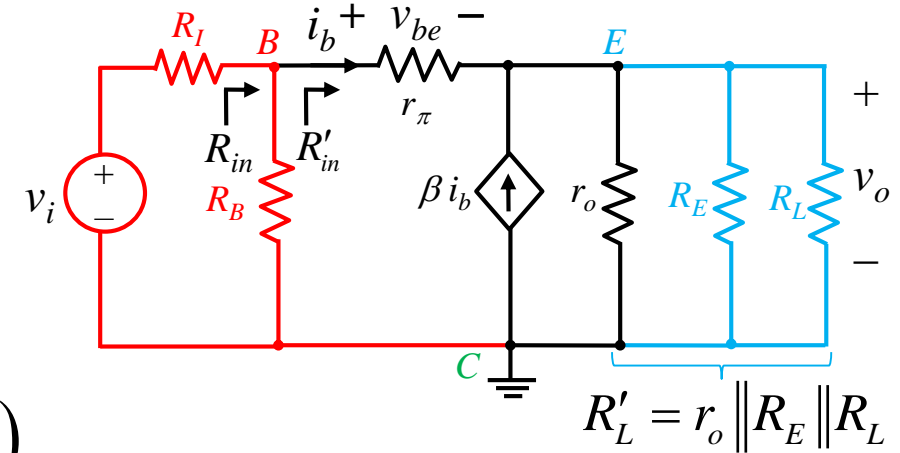



# C-B Amplifier Input Signal Range

For BJT small-signal operation,  $|v_{be}| \leq 5 \text{ mV}$ .

$$v_{be} = -v_e = -\left(\frac{R_{in}}{R_I + R_{in}}\right)v_i$$

$$|v_{be}| \leq 0.005$$

$$\Rightarrow |v_i| \leq 0.005 \left(\frac{R_I + R_{in}}{R_{in}}\right)$$

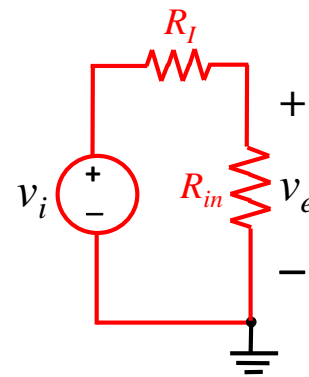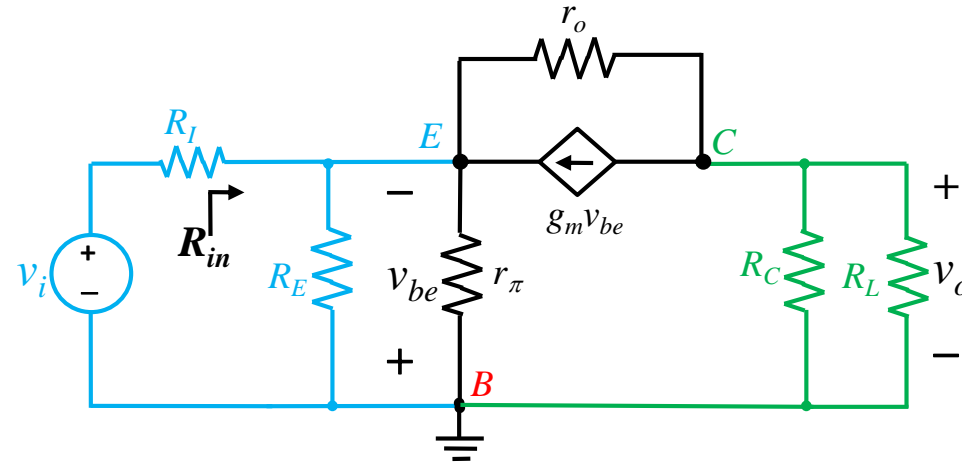

# Small-Signal Operation of MOSFET

$$i_D = \frac{K_n}{2} (v_{GS} - V_{TN})^2 \text{ for } v_{DS} \geq v_{GS} - V_{TN}$$

$$i_D = \frac{K_n}{2} (V_{GS} + v_{gs} - V_{TN})^2 = \frac{K_n}{2} \left[ (V_{GS} - V_{TN})^2 + 2v_{gs} (V_{GS} - V_{TN}) + v_{gs}^2 \right]$$

$$i_d = i_D - I_D = \frac{K_n}{2} \left[ 2v_{gs} (V_{GS} - V_{TN}) + v_{gs}^2 \right]$$

For linearity,  $i_d$  should be proportional to  $v_{gs}$ .

$$|v_{gs}| \ll 2(V_{GS} - V_{TN}) \Rightarrow |v_{gs}| \leq 0.2(V_{GS} - V_{TN})$$

# C-S Amplifier Input Signal Range

For MOSFET small-signal operation,  $|v_{gs}| \leq 0.2(V_{GS} - V_{TN})$ .



$$v_g \approx v_{gs} + g_m v_{gs} R_{S1} = v_{gs} (1 + g_m R_{S1})$$

$$v_{gs} = \frac{v_g}{1 + g_m R_{S1}}$$

$$\frac{|v_g|}{1 + g_m R_{S1}} \leq 0.2(V_{GS} - V_{TN})$$

$$\Rightarrow |v_g| \leq 0.2(V_{GS} - V_{TN})(1 + g_m R_{S1})$$

$$\because v_g = \left( \frac{R_{in}}{R_I + R_{in}} \right) v_i \Rightarrow |v_i| \leq 0.2(V_{GS} - V_{TN})(1 + g_m R_{S1}) \left( \frac{R_I + R_{in}}{R_{in}} \right)$$

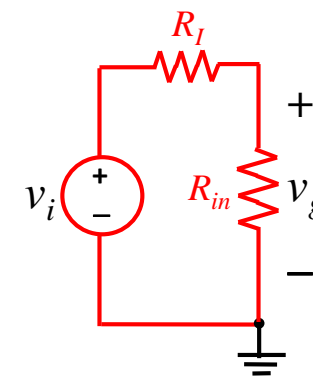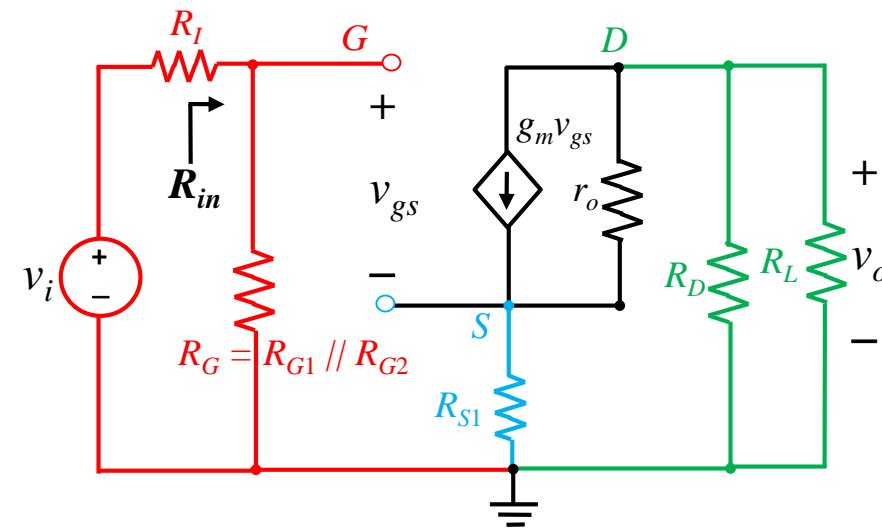



# C-D Amplifier Input Signal Range

For MOSFET small-signal operation,  $|v_{gs}| \leq 0.2(V_{GS} - V_{TN})$ .


$$v_g \approx v_{gs} + g_m v_{gs} R'_L$$

$$v_{gs} = \frac{v_g}{1 + g_m R'_L}$$

$$\frac{|v_g|}{1 + g_m R'_L} \leq 0.2(V_{GS} - V_{TN})$$

$$\Rightarrow |v_g| \leq 0.2(V_{GS} - V_{TN})(1 + g_m R'_L)$$

$$\because v_g = \left( \frac{R_G}{R_I + R_G} \right) v_i \Rightarrow |v_i| \leq 0.2(V_{GS} - V_{TN})(1 + g_m R'_L) \left( \frac{R_I + R_G}{R_G} \right)$$

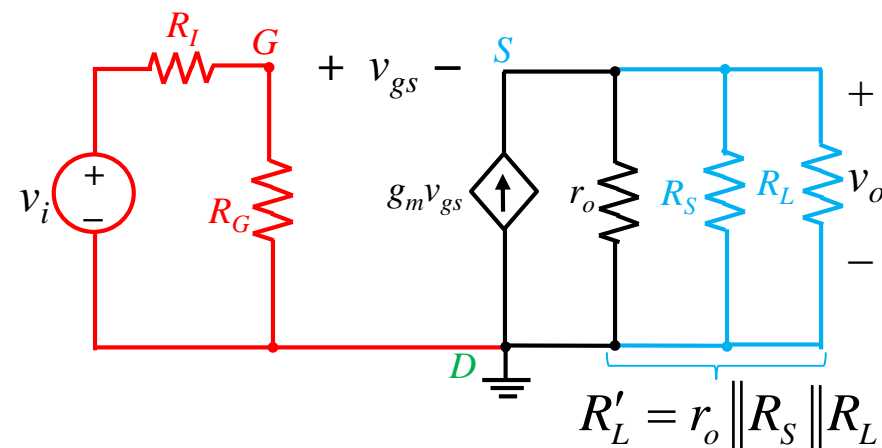

# C-G Amplifier Input Signal Range

For MOSFET small-signal operation,  $|v_{gs}| \leq 0.2(V_{GS} - V_{TN})$ .

$$v_{gs} = -v_s = -\left(\frac{R_{in}}{R_I + R_{in}}\right)v_i$$

$$|v_{gs}| \leq 0.2(V_{GS} - V_{TN})$$

$$\Rightarrow |v_i| \leq 0.2(V_{GS} - V_{TN}) \left(\frac{R_I + R_{in}}{R_{in}}\right)$$

