

Lecture 9: Transformers

EE3010: Electrical Devices and Machines

School of Electrical and Electronic Engineering

Associate Professor So Ping Lam

Tel: +65 6790 5026 | Email: ep Iso@ntu.edu.sg

The preceding/ following videos contain slides with materials that were originally used for delivery in lecture halls and/or classrooms in Nanyang Technological University. They might contain adapted materials. While every effort has been made to undertake due diligence to identify the original source, this was not always possible for all materials. The videos are used solely for educational purposes to support the Technology-Enhanced Learning (TEL) aspects of the course. TEL is hosted and deployed in NTULearn and i-NTULearn, a learning management system accessed by students at NTU assigned with a user ID and password. This disclaimer states that no copyright infringement was intended. Should any disagreement or dispute arise, including any claims to rightful ownership, kindly contact CITS, NTU, at +65 6790 5231.

Learning Objectives

By the end of this lecture, you should be able to:

- ❖ Describe the methods to develop the exact equivalent circuits and approximate equivalent circuits of a practical transformer.
- ❖ Calculate the input voltage and input current using the exact equivalent circuits and approximate equivalent circuits.
- ❖ Compare the results obtained by the approximate method with those obtained by the exact method.

Exact Equivalent Circuits

- ❖ Fig. 17 shows the exact equivalent circuit of a transformer. The calculations involved in transformer problems can be significantly reduced if the transformer circuit is simplified by referring all the circuit parameters to only one side. The circuits thus obtained are called the exact equivalent circuits referred to that side.

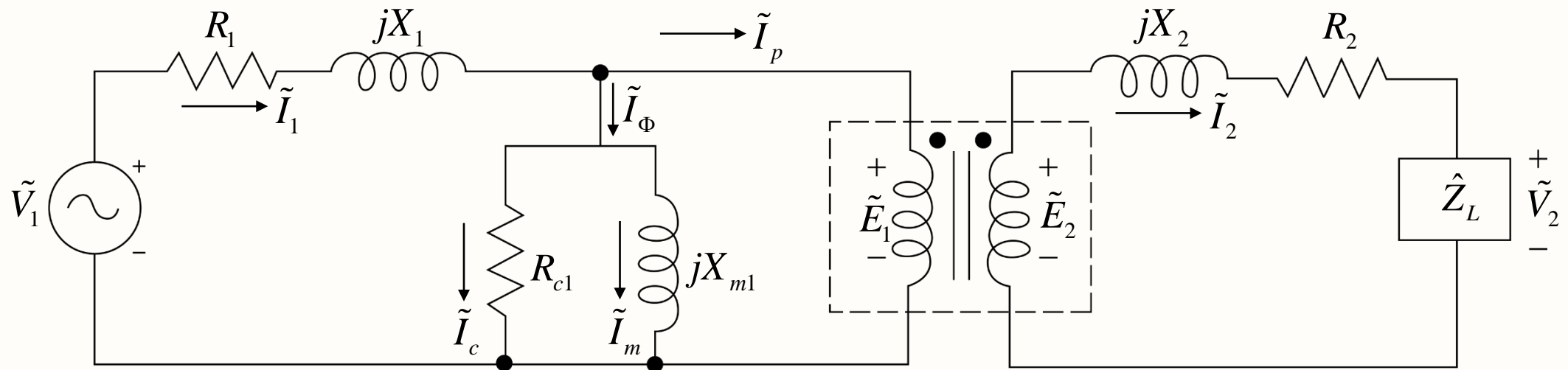


Fig. 17. Exact equivalent circuit of a transformer.

Exact Equivalent Circuits

- ❖ The equivalent circuit can be referred to the primary side (see Fig. 18) by making the following transformations:

$$Z_2 \rightarrow Z_2' = a^2 Z_2 \quad (R_2' = a^2 R_2, X_2' = a^2 X_2, Z_L' = a^2 Z_L)$$

$$V_2 \rightarrow V_2' = aV_2, E_2 \rightarrow E_2' = aE_2 = E_1$$

$$I_2 \rightarrow I_2' = \frac{1}{a} I_2$$

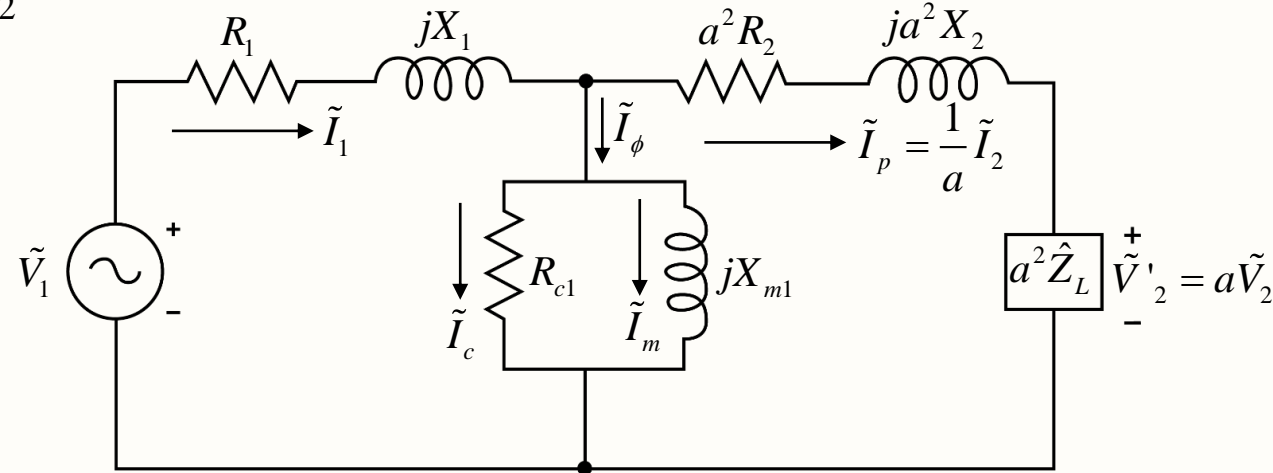


Fig. 18. Exact equivalent circuit referred to the primary.

Exact Equivalent Circuits

- ❖ The equivalent circuit can be referred to the secondary side (see Fig. 19) by making the following transformations:

$$Z_1 \rightarrow Z_1' = \frac{1}{a^2} Z_1$$

$$R_1 \rightarrow R_1' = \frac{R_1}{a^2}, \quad X_1 \rightarrow X_1' = \frac{X_1}{a^2}$$

$$R_{c1} \rightarrow R_{c1}' = \frac{R_{c1}}{a^2}, \quad X_{m1} \rightarrow X_{m1}' = \frac{X_{m1}}{a^2}$$

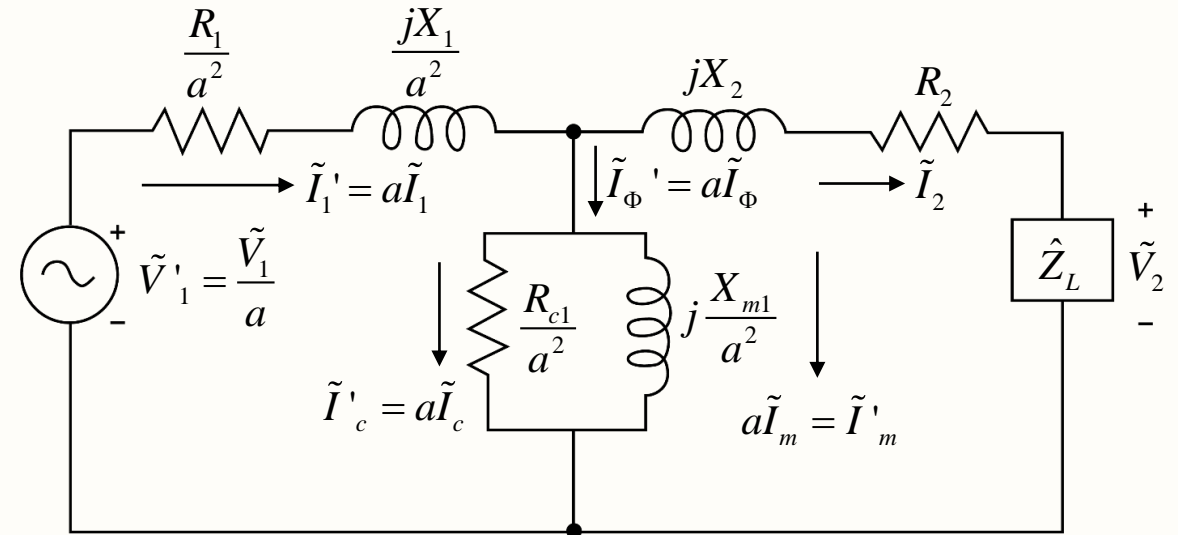


Fig. 19. Exact equivalent circuit referred to the secondary.

Exact Equivalent Circuits

$$I_1 \rightarrow I_1' = aI_1$$

$$I_\Phi \rightarrow I_\Phi' = aI_\Phi$$

$$I_c \rightarrow I_c' = aI_c$$

$$I_m \rightarrow I_m' = aI_m$$

$$V_1 \rightarrow V_1' = \frac{V_1}{a}$$

$$E_1 \rightarrow E_1' = \frac{E_1}{a} = E_2$$

- ❖ These equivalent circuits can be used to analyse transformer circuits to obtain any desired results. The referred values can be converted back to the actual values as required.
- ❖ Solve Example 2 in Lecture 8 using these exact equivalent circuits.

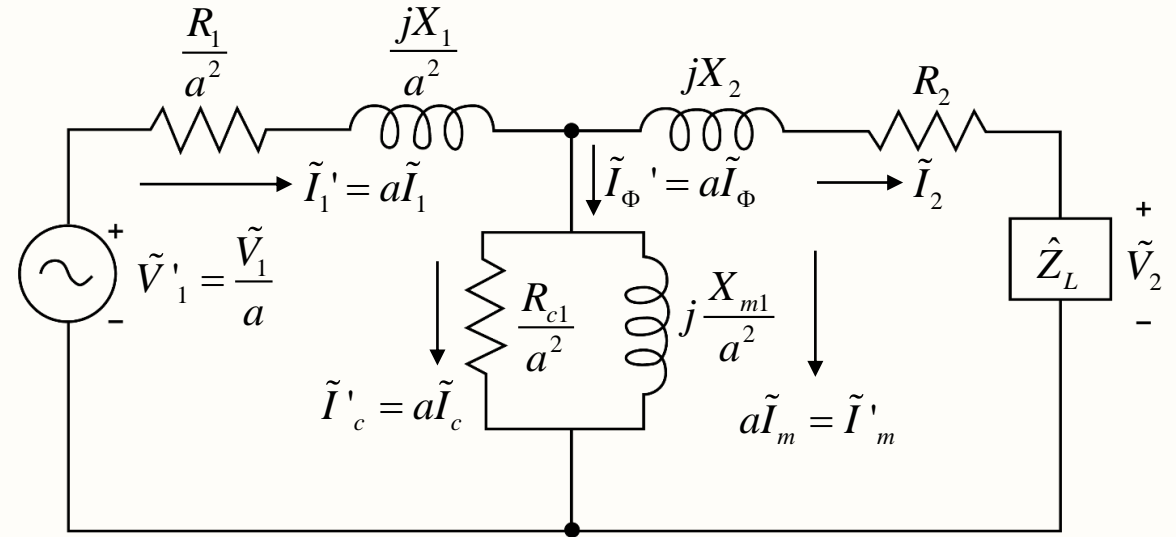


Fig. 19. Exact equivalent circuit referred to the secondary.

Transformer Parameter Values

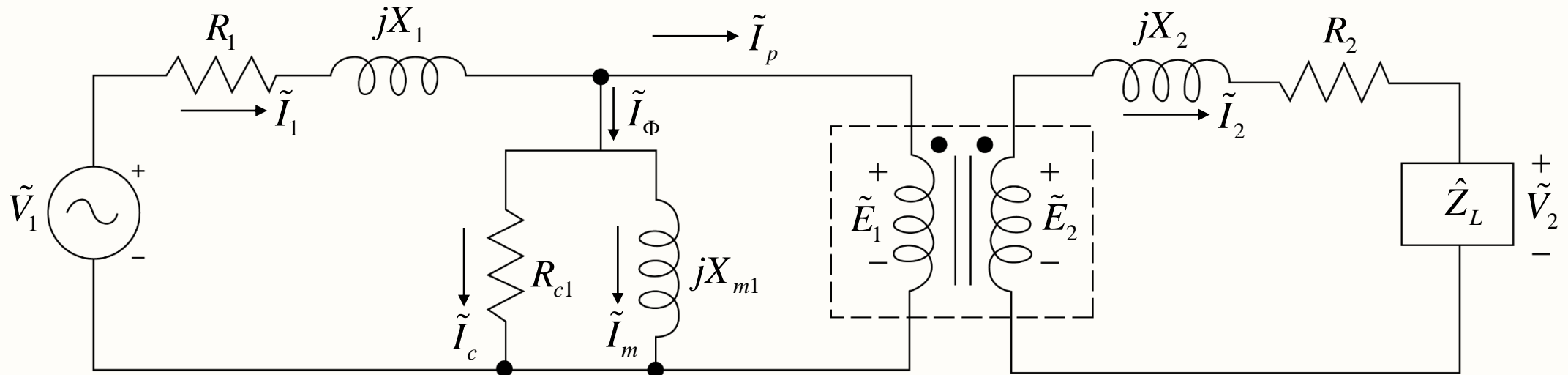


Fig. 20. Exact equivalent circuit of a transformer.

❖ Series Components:

- R_1 and R_2 represent the resistances of the copper coils, and therefore these resistances are usually very small.
- X_1 and X_2 represent the reactances arising from the leakage fluxes, which are very small. Therefore their magnitudes are also very small.
- The losses and the voltage drops in these series parameters are usually very small, and often ignorable.

❖ Shunt Components:

- I_m represents the currents drawn to set up the magnetic flux in the core, and I_c represents the current that accounts for the core loss.
- Since very good magnetic material is used in transformers, both these currents are very small, often ignorable.
- The corresponding shunt impedances R_{c1} and X_{m1} are very large, often taken as infinity and ignored from the circuit.

Approximate Equivalent Circuits

- ❖ More practically, because of the relative values of the series and the shunt components, it introduces very small error if we move the shunt branch from the middle position to the input side, as indicated in Fig. 21.

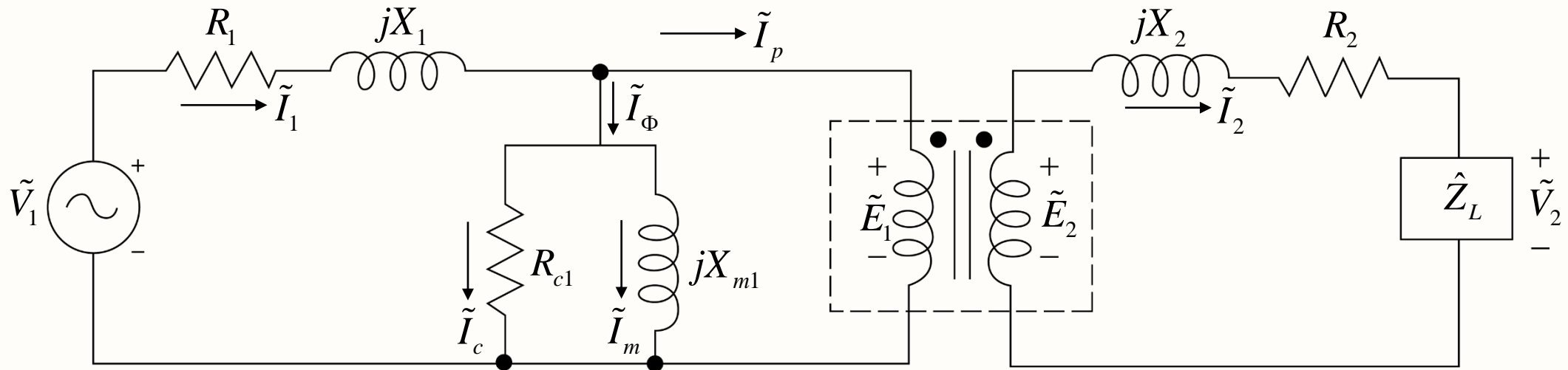


Fig. 21. Exact equivalent circuit of a transformer.

Approximate Equivalent Circuits

- ❖ Such a simplified circuit is called the **approximate equivalent circuit** as shown in Fig. 22, and commonly used to simplify the computations. This, however, will introduce a small amount of error.
- ❖ The circuit may be further simplified by referring all the secondary quantities to the primary side.

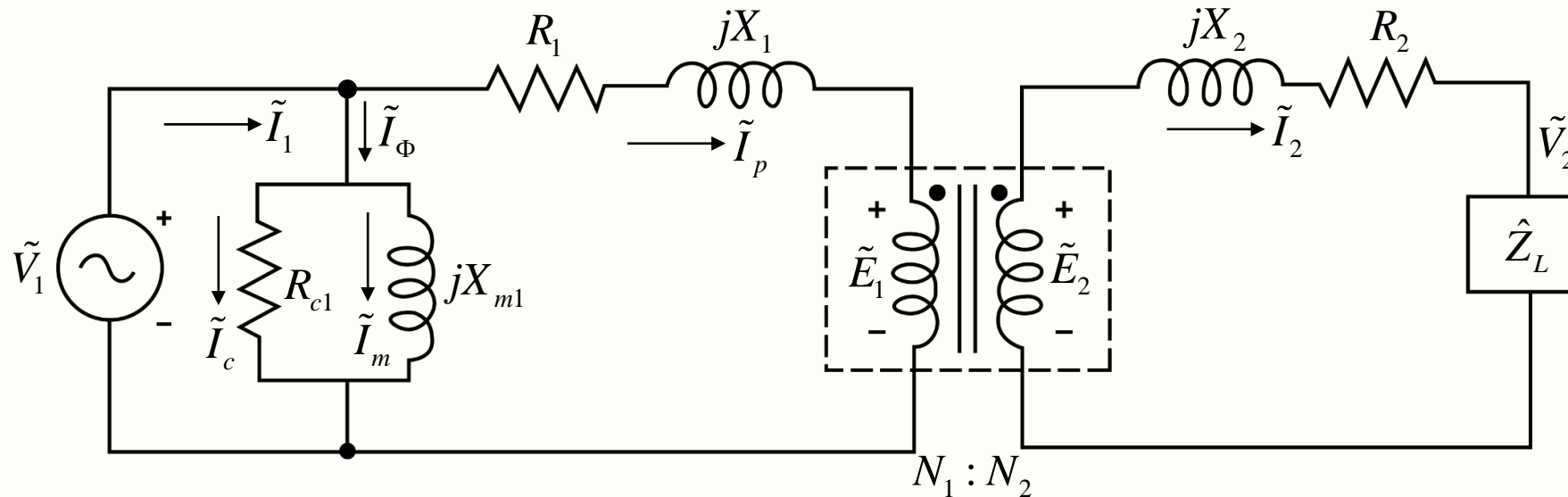


Fig. 22. Approximate equivalent circuit of a transformer.

Approximate Equivalent Circuit Referred to the Primary

- ❖ The series components in the approximate equivalent circuit are in series, and can be combined as

$$R_{e1} = R_1 + a^2 R_2, \text{ and } X_{e1} = X_1 + a^2 X_2$$

- ❖ They are called the total effective resistance and the total effective leakage reactance referred to the primary side (side 1) respectively, as shown in Fig. 23.

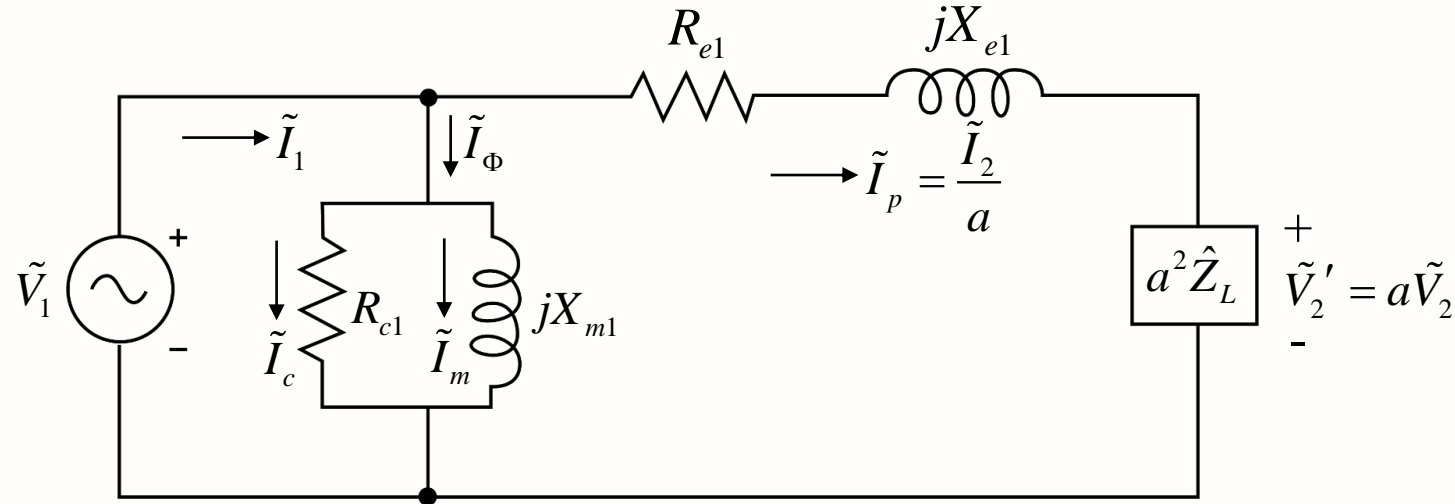


Fig. 23. Approximate equivalent circuit referred to the primary.

Approximate Equivalent Circuit Referred to the Secondary

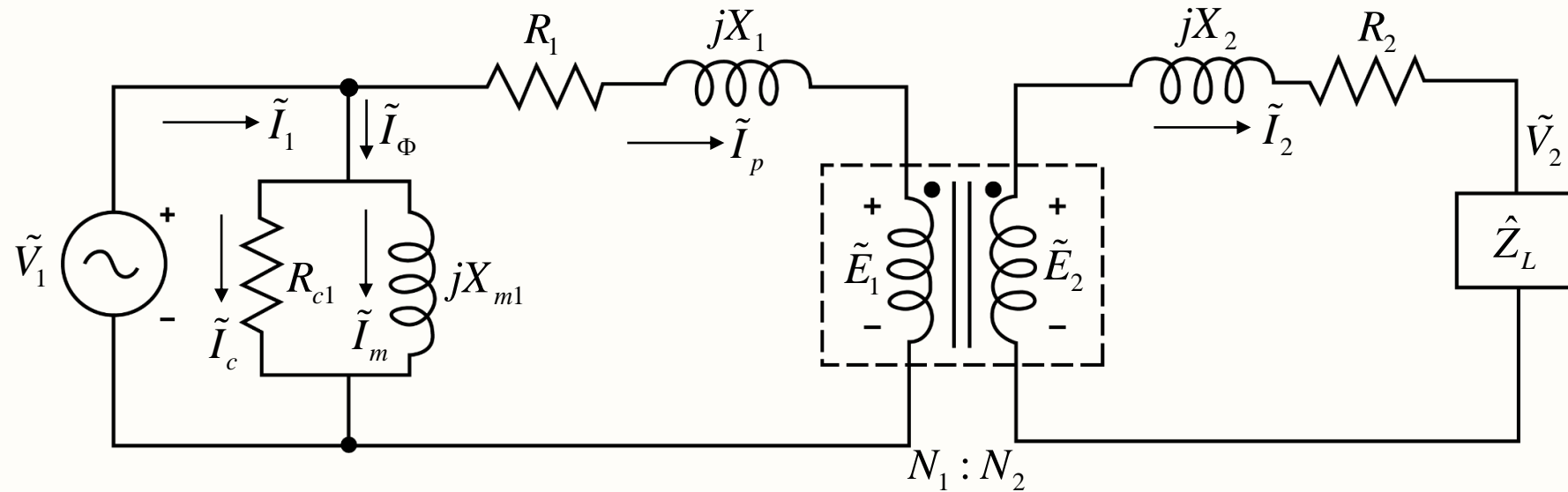


Fig. 24. Approximate equivalent circuit of a transformer.

Approximate Equivalent Circuit Referred to the Secondary

- ❖ Similarly, the circuit may be referred to the secondary side as shown Fig. 25, where

$$R_{e2} = \frac{R_1}{a^2} + R_2, \text{ and } X_{e2} = \frac{X_1}{a^2} + X_2$$

are the total effective resistance and the total effective leakage reactance referred to the secondary side (side 2) respectively.

- ❖ It should further be noted that the shunt components are also referred to the secondary side.

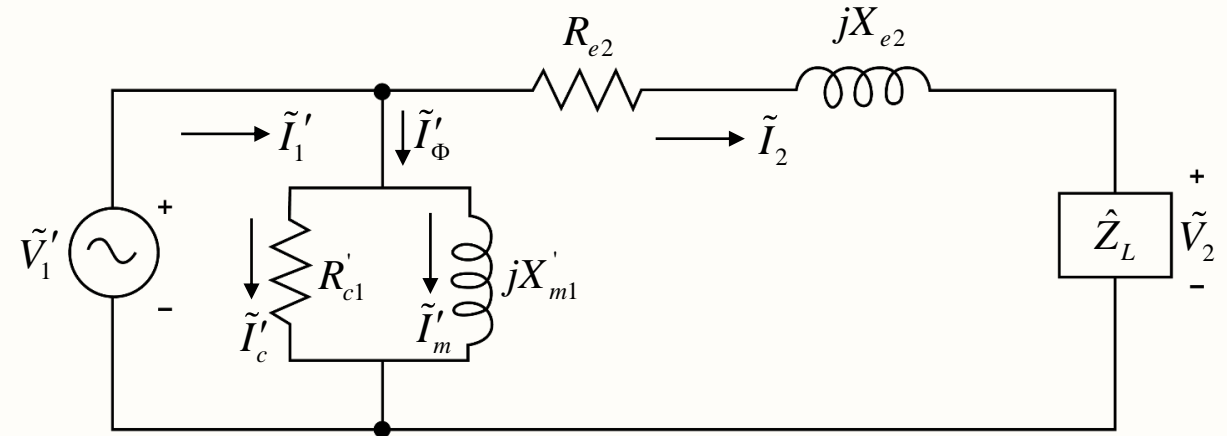


Fig. 25. Approximate equivalent circuit referred to the secondary.

Example 3

A 23-kVA, 2300/230-V, 60-Hz transformer has the following parameters:

$$R_1 = 4 \, \Omega, \, R_2 = 0.04 \, \Omega, \, X_1 = 12 \, \Omega, \, X_2 = 0.12 \, \Omega$$

$$R_{c1} = 20 \, \text{k}\Omega, \, \text{and} \, X_{m1} = 15 \, \text{k}\Omega.$$

If the transformer delivers 75% of its rated load at 0.866 pf (lag) at rated voltage, calculate the input voltage using the approximate equivalent circuit referred to the primary.

(Solutions →)

Example 3 – Solutions

$a = \frac{2300}{230} = 10$, and the circuit is shown in Fig. 26, where

$$R_{e1} = 4 + 10^2 \times 0.04 = 8 \, \Omega, \text{ and}$$

$$X_{e1} = 12 + 10^2 \times 0.12 = 24 \, \Omega$$

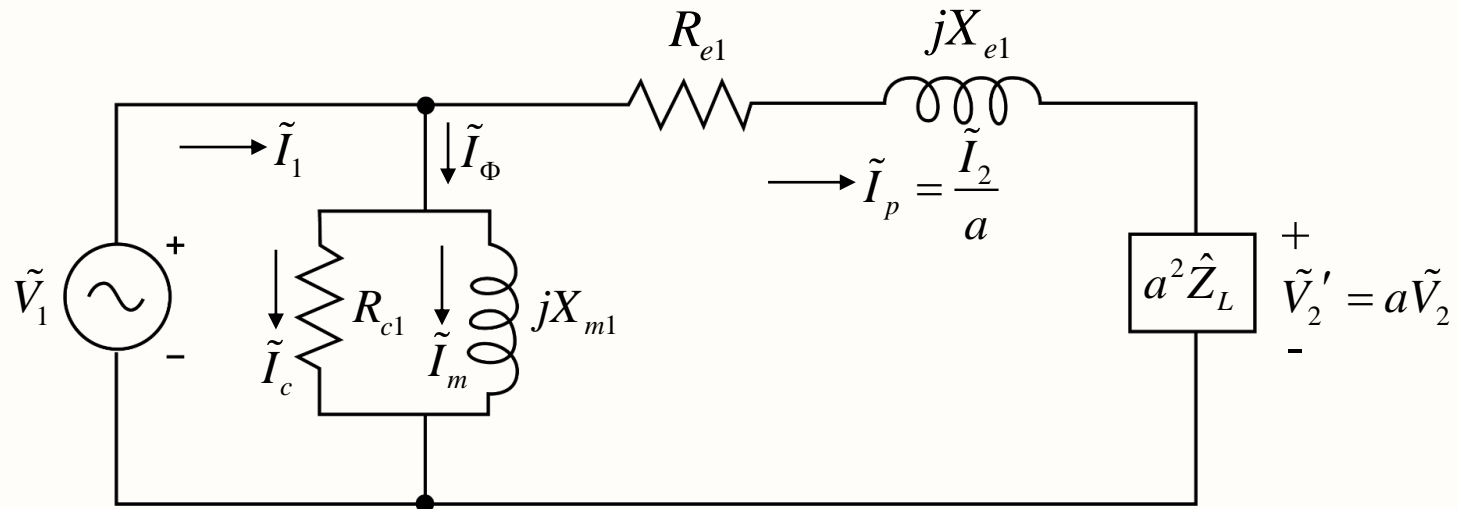


Fig. 26. Approximate equivalent circuit referred to the primary.

Example 3 – Solutions

As before,

$$V_2 = 230 \angle 0^\circ \text{ V (Reference)}$$

$$I_2 = 75 \angle -30^\circ \text{ A, so that}$$

$$V_2' = aV_2 = 10 \times 230 \angle 0^\circ = 2300 \angle 0^\circ \text{ V}$$




$$I_p = I_2' = \frac{I_2}{a} = \frac{75 \angle -30^\circ}{10} = 7.5 \angle -30^\circ \text{ A}$$




$$V_1 = V_2' + I_2' \times (R_{e1} + jX_{e1}) = 2300 \angle 0^\circ + 7.5 \angle -30^\circ \times (8 + j24) = 2445.21 \angle 2.95^\circ$$

- ❖ Compare this with the value obtained by the exact method ($2447.6 \angle 2.97^\circ \text{ V}$).
- ❖ Calculate other values as before and compare the answers.

In this lecture, you have learnt:

- ❖ The methods to develop the exact equivalent circuits and approximate equivalent circuits of a practical transformer.
- ❖ The calculation of input voltage and input current using the exact equivalent circuits and approximate equivalent circuits.
- ❖ The comparison of the results obtained by the approximate method with those obtained by the exact method.

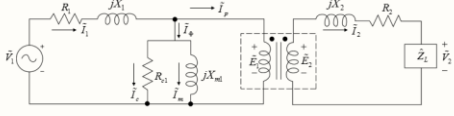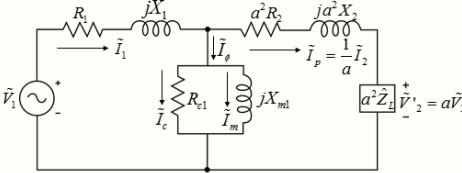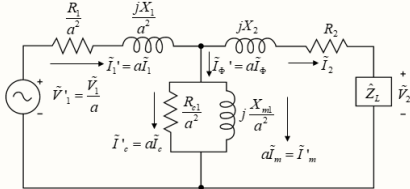No.	Slide No.	Image	Reference
1	4, 8, and 11		Reprinted from <i>Electric Machinery and Transformers, 3rd ed.</i> , (p. 218), by B. S. Guru, & H. R. Hiziroglu, 2001, New York, NY: Oxford University Press. Copyright 2001 by Oxford University Press.
2	5		Reprinted from <i>Electric Machinery and Transformers, 3rd ed.</i> , (p. 219), by B. S. Guru, & H. R. Hiziroglu, 2001, New York, NY: Oxford University Press. Copyright 2001 by Oxford University Press.
3	6 and 7		Reprinted from <i>Electric Machinery and Transformers, 3rd ed.</i> , (p. 219), by B. S. Guru, & H. R. Hiziroglu, 2001, New York, NY: Oxford University Press. Copyright 2001 by Oxford University Press.

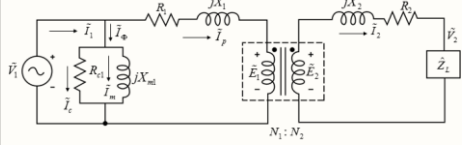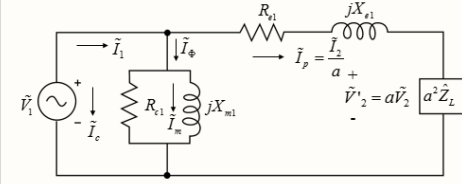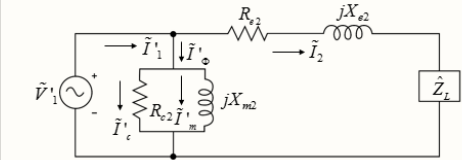No.	Slide No.	Image	Reference
4	12 and 14		Reprinted from <i>Electric Machinery and Transformers, 3rd ed.</i> , (p. 222), by B. S. Guru, & H. R. Hiziroglu, 2001, New York, NY: Oxford University Press. Copyright 2001 by Oxford University Press.
5	13 and 17		Reprinted from <i>Electric Machinery and Transformers, 3rd ed.</i> , (p. 222), by B. S. Guru, & H. R. Hiziroglu, 2001, New York, NY: Oxford University Press. Copyright 2001 by Oxford University Press.
6	15		Reprinted from <i>Electric Machinery and Transformers, 3rd ed.</i> , (p. 223), by B. S. Guru, & H. R. Hiziroglu, 2001, New York, NY: Oxford University Press. Copyright 2001 by Oxford University Press.