

# Lecture 10: Transformers

---

**EE3010: Electrical Devices and Machines**

School of Electrical and Electronic Engineering

Associate Professor So Ping Lam

Tel: +65 6790 5026 | Email: [episo@ntu.edu.sg](mailto:episo@ntu.edu.sg)

The preceding/ following videos contain slides with materials that were originally used for delivery in lecture halls and/ or classrooms in Nanyang Technological University. They might contain adapted materials. While every effort has been made to undertake due diligence to identify the original source, this was not always possible for all materials. The videos are used solely for educational purposes to support the Technology-Enhanced Learning (TEL) aspects of the course. TEL is hosted and deployed in NTULearn and i-NTULearn, a learning management system accessed by students at NTU assigned with a user ID and password. This disclaimer states that no copyright infringement was intended. Should any disagreement or dispute arise, including any claims to rightful ownership, kindly contact CITS, NTU, at +65 6790 5231.

# Learning Objectives

By the end of this lecture, you should be able to:

- ❖ Evaluate the transformer performance using the voltage regulation.
- ❖ Calculate the core losses and copper losses in a practical transformer.
- ❖ Apply the concepts learnt in maximum efficiency and full-load efficiency to evaluate the transformer performance.

## ❖ Voltage Regulation:

- Consider a transformer supplying a **full load** at **rated voltage** as shown in Fig. 27.
- To maintain rated voltage  $V_2$  at the load terminals, the input voltage  $V_1'$  has to be maintained at a level different from  $V_2$  by the amount of voltage drop in the series impedance ( $Z_{e2} = R_{e2} + jX_{e2}$ ).

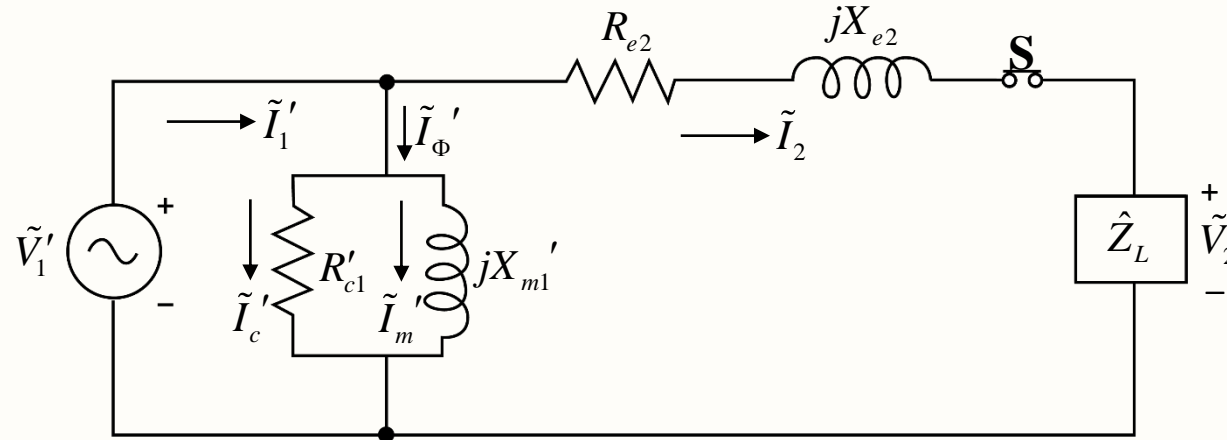


Fig. 27. Approximate equivalent circuit referred to the secondary.

- If the load switch is now opened, there would be no current and so no voltage drop in  $Z_{e2}$ . Hence, the voltage across the load terminals will change from  $V_2$  to  $V_1'$ . The amount of voltage change at the load terminals when the full load operating at rated voltage is disconnected expressed as a percentage of the rated voltage is called the **Voltage Regulation**.
- Ideal transformers will have zero voltage regulation. Smaller voltage regulation is better for transformer operation. Therefore, the voltage regulation is used as a '**figure of merit**' for transformers.

# Transformer Performance

- Voltage regulation (VR) can be quantitatively defined as:

$$VR\% = \frac{V_{2NL} - V_{2FL}}{V_{2FL}} \times 100 = \frac{V'_1 - V_2}{V_2} \times 100 \text{ (referred to secondary as shown in Fig. 28)}$$

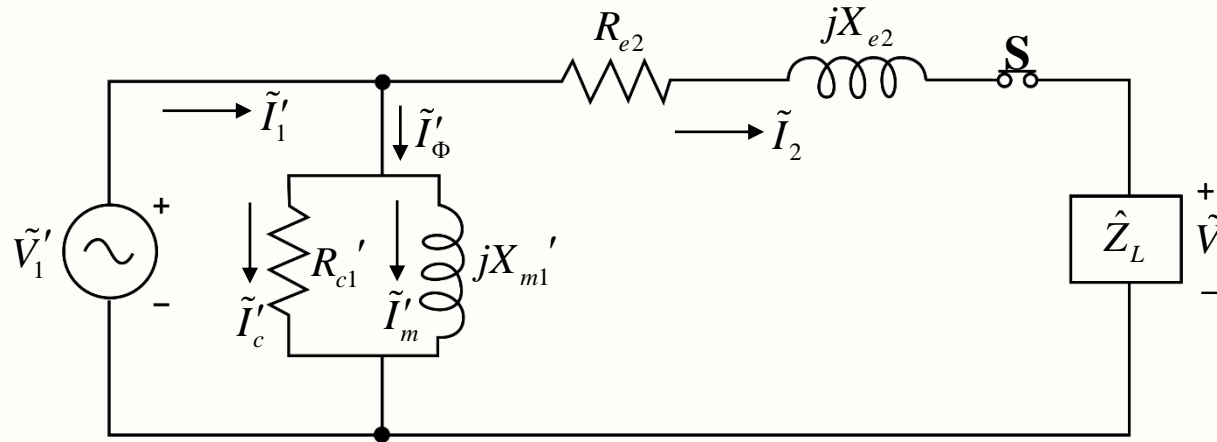


Fig. 28. Approximate equivalent circuit referred to the secondary.

# Transformer Performance

- VR can also be referred to the primary as

$$VR\% = \frac{V_1' - V_2}{V_2} \times 100 = \frac{V_1/a - V_2}{V_2} \times 100 = \frac{V_1 - aV_2}{aV_2} \times 100 = \frac{V_1 - V_2'}{V_2'} \times 100$$

- This is equivalent to the use of the approximate equivalent circuit referred to the primary side, as shown in Fig. 29.

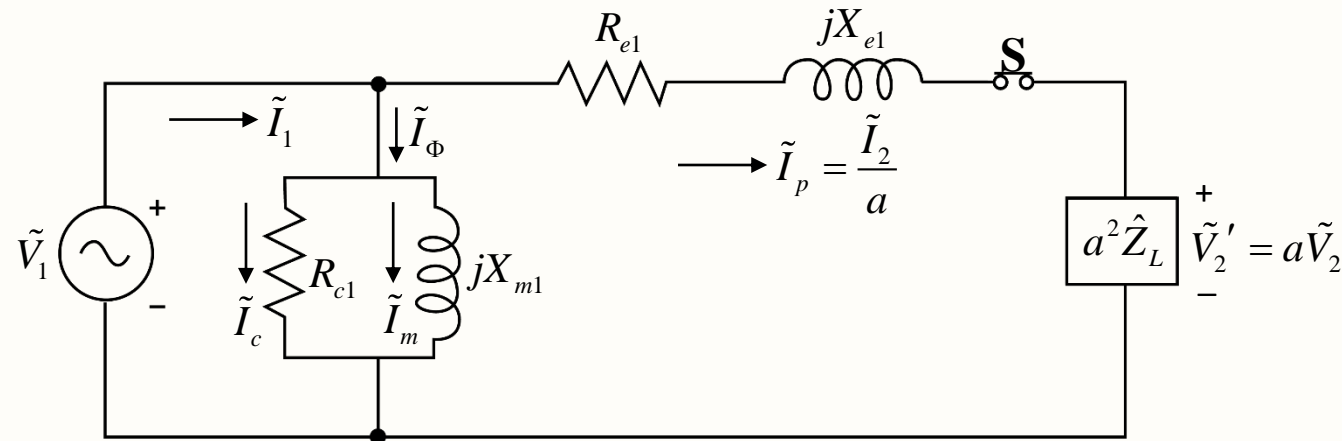


Fig. 29. Approximate equivalent circuit referred to the primary.

- It should be noted that while using the approximate equivalent circuit to calculate the voltage regulation, the shunt branch of  $X_m$  and  $R_c$  does not affect the calculations in any way and can be totally ignored.



## Example 4

A 23-kVA, 2300/230-V, 60-Hz transformer has the following parameters:

$$R_1 = 4 \, \Omega, R_2 = 0.04 \, \Omega, X_1 = 12 \, \Omega, X_2 = 0.12 \, \Omega,$$

$$R_{c1} = 20 \, \text{k}\Omega, \text{ and } X_{m1} = 15 \, \text{k}\Omega$$

Calculate the voltage regulation of the transformer referred to the secondary side when it delivers full load at 0.8 pf (lag) at rated voltage.

(Solutions →)

## Example 4 – Solutions

$$a = \frac{2300}{230} = 10$$

The circuit is shown in Fig. 30, where

$$R_{e2} = \frac{4}{10^2} + 0.04 = 0.08 \, \Omega, \text{ and } X_{e2} = \frac{12}{10^2} + 0.12 = 0.24 \, \Omega$$

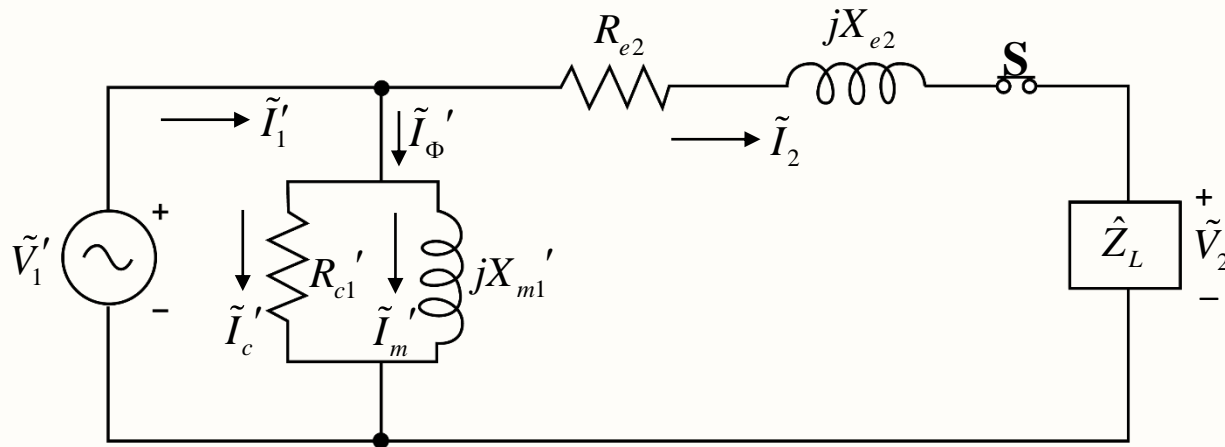


Fig. 30. Approximate equivalent circuit referred to the secondary.

## Example 4 – Solutions

Let  $V_2 = 230 \angle 0^\circ$  V (**Reference**)

At full load,  $I_2 = 23 \times \frac{1000}{230} = 100$  A, and


for 0.8 pf,  $\varphi = \cos^{-1} 0.8 = 36.87^\circ$

For lagging pf,  $I_2 = 100 \angle -36.87^\circ$  A, so that,

$$V_1' = V_2 + I_2(R_{e2} + jX_{e2}) = 230 \angle 0^\circ + 100 \angle -36.87^\circ (0.08 + j0.24) = 251.2 \angle 3.29^\circ \text{ V}$$

$$\text{Therefore, } VR\% = \frac{251.2 - 230}{230} \times 100 = 9.22 \% \text{ (rejected)}$$

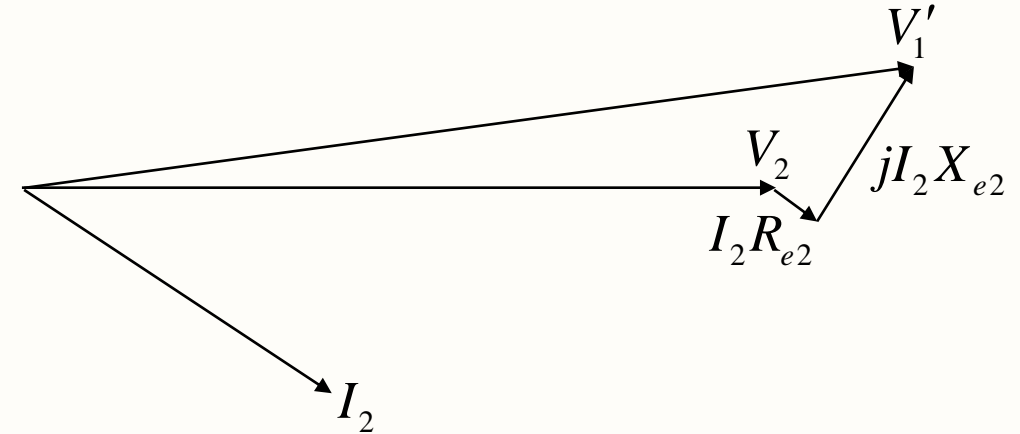- ❖ A sketch of the phasor diagram can be very helpful in understanding the nature of the voltage regulation.
- For the above example with **lagging** power factor, it can be drawn as shown in Fig. 31.
- It is clearly seen that  $V_1'$  is larger than  $V_2$ , and therefore the voltage regulation will be positive.




$$V_1' > V_2 \Rightarrow \text{positive regulation}$$

Fig. 31. Phasor diagram.

Reproduced with permission from [9789810676575, G. B. Shrestha and M. H. Haque, *AC Circuits and Machines*; Pearson Education South Asia Pte. Ltd.]
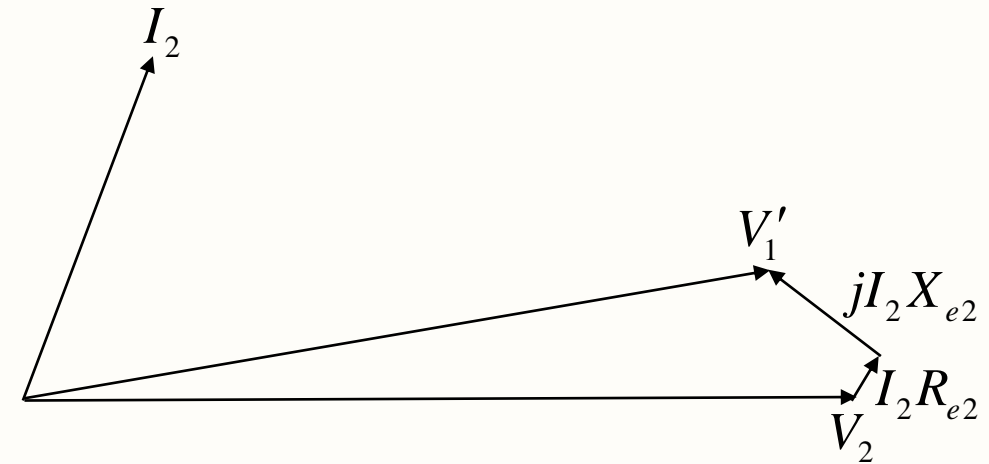
# Phasor Diagrams

- For a sufficiently **leading** power factor, the phasor diagram will look as shown Fig. 32.
  - It can be clearly seen that  $V_1'$  is smaller than  $V_2$ , and therefore the voltage regulation will be negative. This implies that the voltage at the load terminals will decrease when the load is disconnected.
- ❖ Repeat Example 4 for a pf of 0.8 lead to verify that the voltage regulation is negative in this situation.



$$V_1' < V_2 \Rightarrow \text{negative regulation}$$

Fig. 32. Phasor diagram.

Reproduced with permission from [9789810676575, G. B. Shrestha and M. H. Haque, *AC Circuits and Machines*; Pearson Education South Asia Pte. Ltd.]

- ❖ The losses in transformers consist of:
  - The magnetic losses – core losses
  - The copper losses
- ❖ The magnetic core losses  $P_m$  consist of two components:
  - Hysteresis loss
  - Eddy current loss

As the flux and the flux density remain practically constant in a transformer, both these components of the magnetic losses remain constant. Therefore, these losses are also called fixed losses.

# Losses and Efficiency

- ❖ The copper losses  $P_{cu}$  (also known as  $I^2R$  loss) occur in the primary and the secondary windings. These depend on the currents in the windings and therefore on the load supplied by the transformer. These losses are also called variable losses.
- ❖ The power flow diagram of a transformer is shown in Fig. 33, and the input power can be expressed as  $P_{in} = P_o + P_{cu} + P_m$ .

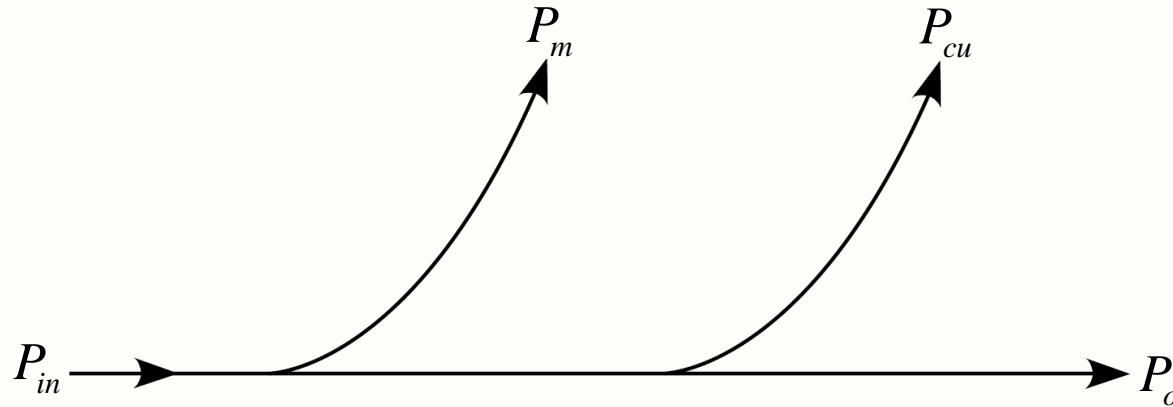


Fig. 33. Power flow diagram of a transformer.

# Losses and Efficiency

- ❖ Consider the approximate equivalent circuit referred to the secondary side as shown in Fig. 34, the copper loss is

$$P_{cu} = I_2^2 R_{e2}$$

It is useful to note that the copper loss at a fraction  $x$  of the rated current, i.e.,  $I_2 = xI_{2fl}$ , can be written as

$$P_{cu} = I_2^2 R_{e2} = \frac{I_2^2}{I_{2fl}^2} I_{2fl}^2 R_{e2} = x^2 P_{cu fl} \quad (\text{since } x = \frac{I_2}{I_{2fl}})$$

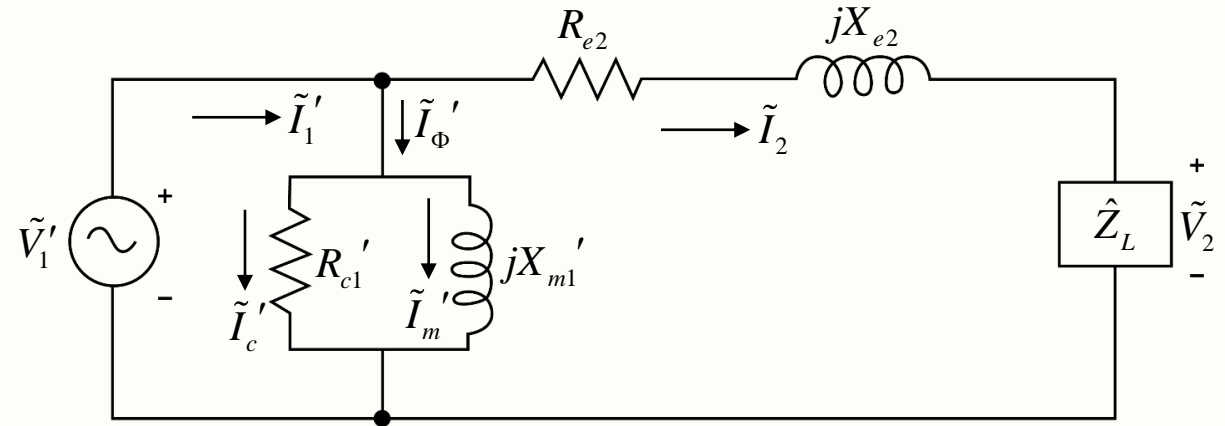


Fig. 34. Approximate equivalent circuit referred to the secondary.



# Losses and Efficiency

- ❖ Noting that output  $P_o = V_2 I_2 \cos \theta$ , the efficiency can be expressed as

$$\eta = \frac{P_o}{P_i} = \frac{V_2 I_2 \cos \theta}{V_2 I_2 \cos \theta + I_2^2 R_{e2} + P_m}$$

- ❖ The variation of efficiency  $\eta$  with load current  $I_2$  is shown in Fig. 35.
- ❖ Clearly, at no load:  $P_o = 0 \Rightarrow \eta = 0$

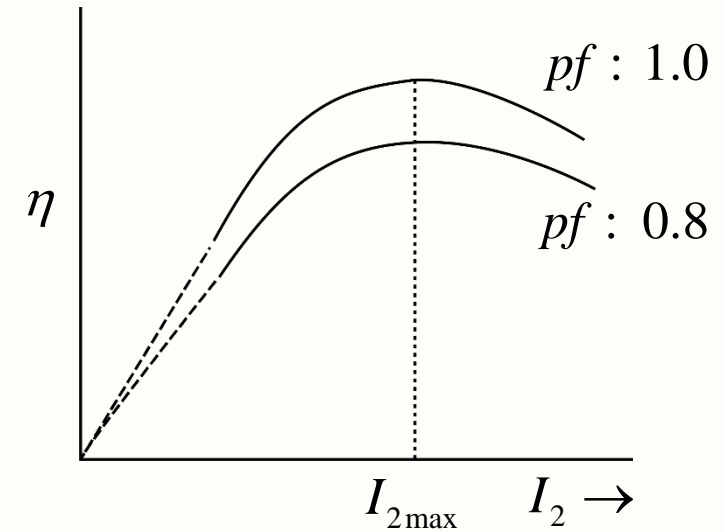


Fig. 35. Variation of efficiency with load current.

Reproduced with permission from [9789810676575, G. B. Shrestha and M. H. Haque, *AC Circuits and Machines*; Pearson Education South Asia Pte. Ltd.]

# Losses and Efficiency

❖ For a given pf, the efficiency increases with increasing  $I_2$  (i.e., increasing load) and reaches a maximum value before it starts to drop.

❖ By equating:  $\frac{d\eta}{dI_2} = 0$ ,

the condition for maximum efficiency  $\eta_{\max}$  is obtained as

$$I_{2\max}^2 R_{e2} = P_m$$

i.e., the maximum efficiency occurs at a current level, at which **the copper losses are equal to the core losses**, as depicted in Fig. 36.

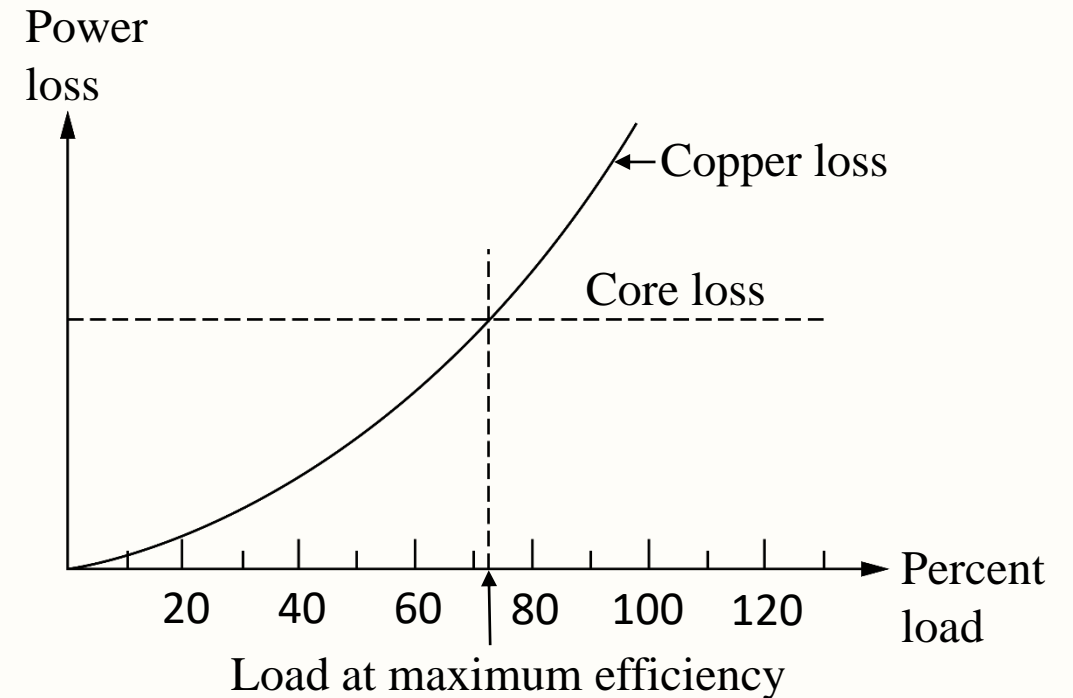


Fig. 36. Losses in a transformer.

## Example 5

A 120-kVA, 2400/240-V transformer has the following parameters:

$$R_1 = 0.75 \, \Omega, X_1 = 0.8 \, \Omega, R_2 = 0.01 \, \Omega, X_2 = 0.02 \, \Omega$$

The transformer is designed to have maximum efficiency at 70 % of its rated load.  
Determine

- a) the kVA loading of the transformer at maximum efficiency,
- b) the maximum efficiency at 0.8 pf lagging,
- c) the full-load efficiency at 0.8 pf lagging, and
- d) the half-load efficiency at 0.8 pf lagging.

(Solutions →)

## Example 5 – Solutions

a) kVA loading at maximum efficiency:  $S_{\max} = 0.7 \times 120 \text{ kVA} = 84 \text{ kVA}$

At full load:

$$I_{1fl} = \frac{S_{fl}}{V_1} = \frac{120000}{2400} = 50 \text{ A}$$

$$I_{2fl} = \frac{S_{fl}}{V_2} = \frac{120000}{240} = 500 \text{ A}$$

Full load copper loss:

$$P_{cu-fl} = I_{1fl}^2 R_1 + I_{2fl}^2 R_2 = 50^2 \times 0.75 + 500^2 \times 0.01 = 4375 \text{ W}$$

Copper loss at maximum efficiency:

$$P_{cu-\max} = 0.7^2 \times 4375 = 2143.75 \text{ W (since } P_{cu} = x^2 P_{cu-fl} \text{)}$$

Therefore, magnetic core losses:  $P_m = 2143.75 \text{ W}$

## Example 5 – Solutions

b) Maximum efficiency at 0.8 pf lagging:

Fraction of load for maximum efficiency =  $x = 0.7$

Power output =  $VIx \cos \theta = 120000 \times 0.7 \times 0.8 = 67200 \text{ W}$

Copper loss =  $0.7^2 \times 4375 = 2143.75 \text{ W}$  (since  $P_{cu} = x^2 P_{cu-fl}$ )

Core loss =  $2143.75 \text{ W}$

$$\eta_{\max} = \frac{P_{o-\max}}{P_{o-\max} + P_{cu-\max} + P_m} \times 100 = \frac{67200}{67200 + 2143.75 + 2143.75} \times 100 = 94.00 \%$$

## Example 5 – Solutions

c) Efficiency at full load and 0.8 pf lagging:

Fraction of full load =  $x = 1$

Power output =  $120000 \times 1 \times 0.8 = 96000 \text{ W}$

Copper loss =  $4375 \text{ W}$

Core loss =  $2143.75 \text{ W}$

$$\text{Efficiency } \eta_{fl} = \frac{P_{o-fl}}{P_{o-fl} + P_{cu-fl} + P_m} \times 100 = \frac{96000}{96000 + 4375 + 2143.75} \times 100 = 93.64 \%$$

## Example 5 – Solutions

d) Efficiency at half load and 0.8 pf:

Fraction of half load =  $x = 0.5$

Power output =  $120000 \times 0.5 \times 0.8 = 48000 \text{ W}$

Copper loss =  $0.5^2 \times 4375 = 1093.75 \text{ W}$




Core loss =  $2143.75 \text{ W}$




$$\eta_{hl} = \frac{P_{o-hl}}{P_{o-hl} + P_{cu-hl} + P_m} \times 100 = \frac{48000}{48000 + 1093.75 + 2143.75} \times 100 = 93.68 \%$$



In this lecture, you have learnt:

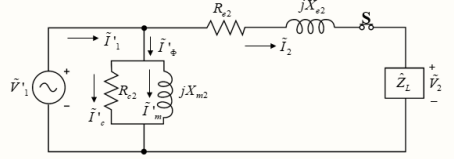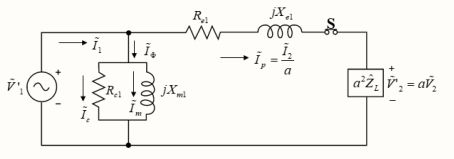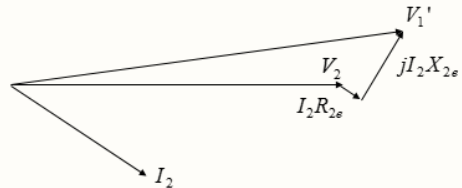- ❖ The evaluation of the transformer performance using the voltage regulation.
- ❖ The calculation of the core losses and copper losses in a practical transformer.
- ❖ The concepts in maximum efficiency and full-load efficiency to evaluate the transformer performance.



No.	Slide No.	Image	Reference
1	4, 6, 10, and 16		Reprinted from <i>Electric Machinery and Transformers, 3rd ed.</i> , (p. 223), by B. S. Guru, & H. R. Hiziroglu, 2001, New York, NY: Oxford University Press. Copyright 2001 by Oxford University Press.
2	7		Reprinted from <i>Electric Machinery and Transformers, 3rd ed.</i> , (p. 222), by B. S. Guru, & H. R. Hiziroglu, 2001, New York, NY: Oxford University Press. Copyright 2001 by Oxford University Press.
3	12		Reprinted from <i>AC Circuits and Machines</i> , (p. 159), by G. B. Shrestha, & M. H. Haque, 2006, Singapore: Pearson Education South Asia Pte. Ltd. Copyright 2006 by Pearson Education South Asia Pte. Ltd. Reprinted with permission.

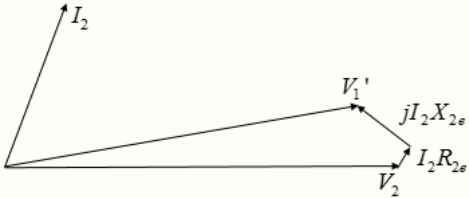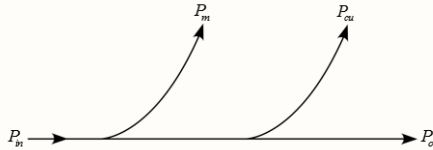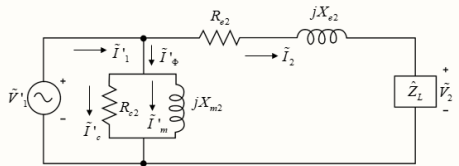No.	Slide No.	Image	Reference
4	13		Reprinted from <i>AC Circuits and Machines</i> , (p. 159), by G. B. Shrestha, & M. H. Haque, 2006, Singapore: Pearson Education South Asia Pte. Ltd. Copyright 2006 by Pearson Education South Asia Pte. Ltd. Reprinted with permission.
5	15		Reprinted from <i>Electric Machinery and Transformers, 3rd ed.</i> , (p. 228), by B. S. Guru, & H. R. Hiziroglu, 2001, New York, NY: Oxford University Press. Copyright 2001 by Oxford University Press.
6	16		Reprinted from <i>Electric Machinery and Transformers, 3rd ed.</i> , (p. 223), by B. S. Guru, & H. R. Hiziroglu, 2001, New York, NY: Oxford University Press. Copyright 2001 by Oxford University Press.

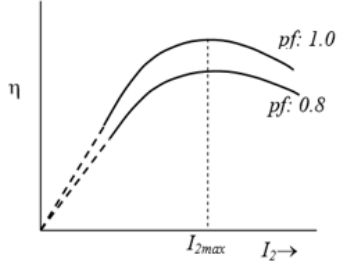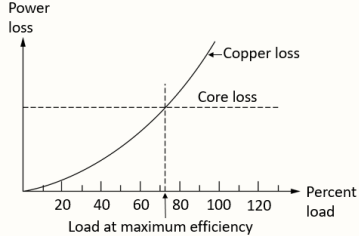No.	Slide No.	Image	Reference
7	17		Reprinted from <i>AC Circuits and Machines</i> , (p. 163), by G. B. Shrestha, & M. H. Haque, 2006, Singapore: Pearson Education South Asia Pte. Ltd. Copyright 2006 by Pearson Education South Asia Pte. Ltd. Reprinted with permission.
8	18		Reprinted from <i>Electric Machinery and Transformers, 3rd ed.</i> , (p. 229), by B. S. Guru, & H. R. Hiziroglu, 2001, New York, NY: Oxford University Press. Copyright 2001 by Oxford University Press.