

**NANYANG TECHNOLOGICAL UNIVERSITY****SEMESTER 1 EXAMINATION 2019-2020****EE2002 – ANALOG ELECTRONICS**

November / December 2019

Time Allowed: 2½ hours

**INSTRUCTIONS**

1. This paper contains 4 questions and comprises 10 pages.
2. Answer all 4 questions.
3. All questions carry equal marks.
4. This is a closed book examination.
5. Unless specifically stated, all symbols have their usual meanings.
6. A List of Formulae is provided in Appendix A on pages 7-10.


1. (a) A non-ideal Op-Amp configured with resistors is shown in Figure 1(a) on page 2. The Op-Amp is powered by  $\pm V_{CC}$  power supplies. It has 2 non-ideal sources,  $I_+$  and  $I_-$  in the absence of the input offset voltage,  $V_{IO} \approx 0$ .

Derive the expression for the output voltage  $v_{OUT}$  when  $v_a = v_b = 0$ , in terms of  $R_1$ ,  $R_2$ ,  $R_3$ ,  $R_4$ ,  $R_5$ ,  $R_6$ ,  $R_7$ ,  $R_8$ ,  $I_+$  and  $I_-$ .

**Note:** Parallel resistance of  $R_x$  and  $R_y$  can be written as  $R_x // R_y$  without expanding it.

(10 Marks)

Note: Question No. 1 continues on page 2.

 **Figure 1(a)**

(b) In Figure 1(b) on page 3, the empirical junction diode equation is:

$$V_D = nV_T \ln[I_D/I_S]$$

for diodes  $D_1$  and  $D_2$ , given that

$$\begin{aligned} V_{D1} &= 0.674 \text{ V at } I_{D1} = 426 \text{ } \mu\text{A} \text{ and} \\ V_{D2} &= 0.794 \text{ V at } I_{D2} = 4.28 \text{ mA.} \end{aligned}$$

Also, given that  $V_1 = 6 \text{ V}$  and  $V_2 = 4.5 \text{ V}$ ,  $R_1 = R_2 = 8 \text{ k}\Omega$ ,  $R_3 = 16 \text{ k}\Omega$ ,  $R_4 = 24 \text{ k}\Omega$ ,  $R_5 = R_6 = 6 \text{ k}\Omega$ , find the DC operating point or quiescent (Q) - point ( $I_D$ ,  $V_D$ ) for the diodes  $D_1$  and  $D_2$  (to 3 decimal places in mA and V, respectively).

**Note:**  $D_1$  and  $D_2$  have the same  $nV_T$  and  $I_S$ .

(15 Marks)

Note: Question No. 1 continues on page 3.

 



Figure 1(b)

2. Consider the source-follower circuit showing a “bootstrapped” resistor  $R_G$  as shown in Figure 2 on page 4. Assume all capacitors have infinite value (open circuit at DC, short circuit at AC). The inductor  $L$  is likewise infinite in value (short circuit at DC, open circuit at AC).
- Given  $R_G = R_S = 2 \text{ k}\Omega$ ,  $K_n = 2 \text{ mA/V}^2$ ,  $V_{TN} = 1 \text{ V}$ , and  $\lambda = 0.01 \text{ V}^{-1}$ , solve for the DC operating point ( $I_D$ ,  $V_{DS}$ ), and hence calculate the small signal parameters  $g_m$  and  $r_o$ . (5 Marks)
  - Determine the AC voltage gain  $A_v = v_o / v_i$ . (5 Marks)
  - Make use of part (b) to determine the AC input resistance  $R_{in}$ . (5 Marks)
  - Determine the AC output resistance  $R_{out}$ . (5 Marks)

Note: Question No. 2 continues on page 4.

- (e) Determine the maximum AC input amplitude  $v_i$  that will satisfy the small signal limit.

(5 Marks)

 

**Figure 2**

3. For the differential circuit in Figure 3 on page 5, assume  $V_{DD} = 12\text{ V}$ ,  $V_{SS} = -12\text{ V}$ ,  $R_{G1} = 100\text{ k}\Omega$ ,  $R_{G2} = 50\text{ k}\Omega$ ,  $R_S = 5\text{ k}\Omega$ ,  $R_D = 8\text{ k}\Omega$ ,  $K_n = 200\text{ }\mu\text{A/V}^2$  and  $V_{TN} = 2\text{ V}$ . Here  $v_{i1}$  and  $v_{i2}$  represent the differential inputs, and  $v_{o1}$  and  $v_{o2}$  represent the differential outputs. Assume all the capacitors have infinite values and  $\lambda = 0$ .

- (a) Determine the Q-points ( $I_D$ ,  $V_{DS}$ ) for the transistors.

(5 Marks)

- (b) Determine the differential-mode gains and common-mode gains for the cases of both single-ended and differential outputs.

(10 Marks)

Note: Question No. 3 continues on page 5.

- (c) Determine the common-mode rejection ratios (CMRRs) for the cases of both single-ended and differential outputs. In addition, discuss the effect of variation of  $R_S$  to the CMRRs. (4 Marks)
- (d) Determine the differential-mode and common-mode input resistances and output resistances. (6 Marks)

 



Figure 3

4. (a) Consider the current mirror circuit shown in Figure 4(a) on page 6. Assume all NMOS transistors are identical with parameters  $K_n = 200 \mu\text{A}/\text{V}^2$ ,  $V_{TN} = 0.5 \text{ V}$ ,  $\lambda = 0.05 \text{ V}^{-1}$  and the power supply voltage  $V_{DD}$  is 5 V. If  $I_{REF} = 100 \mu\text{A}$ , find the gate voltages of  $M_1$  and  $M_2$  denoted by  $V_A$  and  $V_B$  respectively by ignoring the Early effect. Also, find the output current  $I_{out}$  by including the Early effect. (15 Marks)
- (b) Consider the active filter circuit shown in Figure 4(b) on page 6 comprising an ideal operational amplifier, resistors and capacitors.
- (i) Find the transfer function  $H(s) = v_{out} / v_s$  for the circuit in terms of the resistors and capacitors. (5 Marks)


Note: Question No. 4 continues on page 6.

- (ii) How many poles and zeros are there in this transfer function? Write down algebraic expressions for these poles and zeros in terms of the resistors and capacitors.

(5 Marks)

 

**Figure 4(a)**

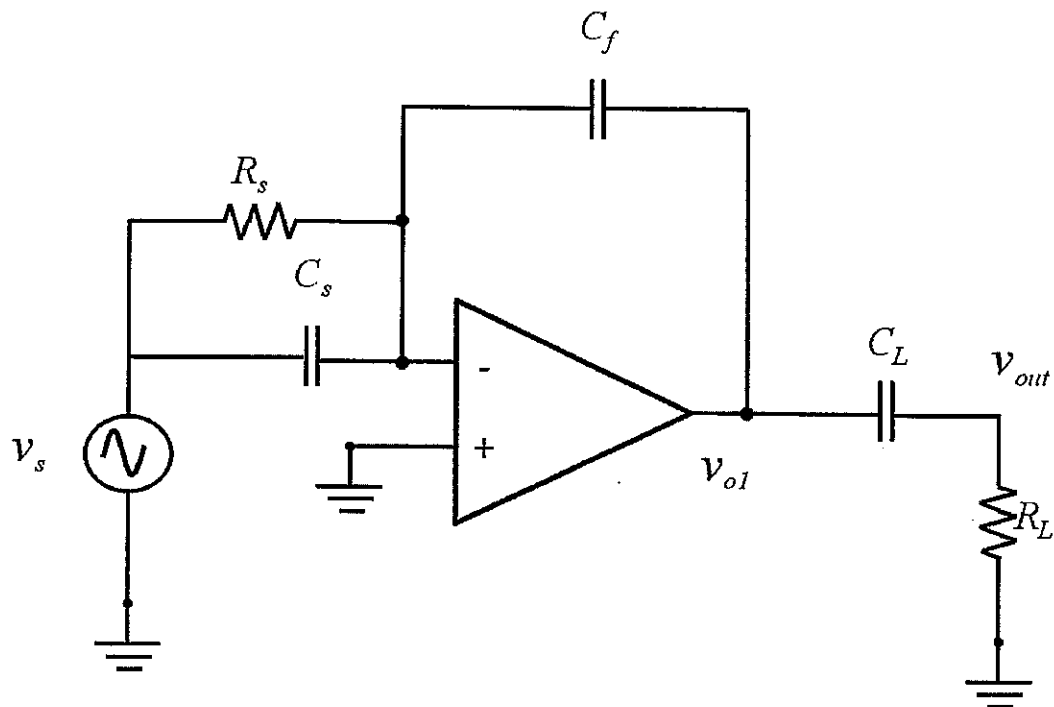

**Figure 4(b)**



## Appendix A

### List of Formulae (with the usual notations)
  
#### Op-Amps:

Closed-Loop Negative Feedback Inverting Gain,  $A_{vCL} = \frac{v_o}{v_i} = -\frac{R_f}{R_i}$  Figure (a)

Closed-Loop Negative Feedback Non-Inverting Gain,  $A_{vCL} = \frac{v_o}{v_i} = \left(1 + \frac{R_f}{R_i}\right)$  Figure (b)



Op-Amp's Slew Rate,  $SR \geq \left| \frac{dv_o}{dt} \right|_{\max} = A_{vCL} \omega a_m = A_{vCL} a_m 2\pi f$ ,


where  $v_i = a_m \sin(\omega t)$ ,  $v_o = A_{vCL} v_i$ ,  $v_o = A_{vCL} a_m \sin(\omega t)$  and  $\left| \frac{dv_o}{dt} \right| = A_{vCL} \omega a_m \cos(\omega t)$

Op-Amp's frequency response:  $A_{vOL}(jf) = \frac{A_o}{\left(1 + \frac{jf}{f_p}\right)}$

Gain-Bandwidth Product:  $A_o f_p = f_o = \frac{1}{\beta} (BW)_{CL}$

where  $\frac{1}{\beta} = \frac{R_f + R_i}{R_i}$

$$t_r = \frac{0.35}{(BW)_{CL}}$$

 

#### Diodes:

$$v_D \approx nV_T \ln\left(\frac{i_D}{I_S}\right) \quad \text{or} \quad i_D \approx I_S e^{\left(\frac{v_D}{nV_T}\right)}$$

where  $e^x = 1 + x + \frac{x^2}{2!} + \frac{x^3}{3!} + \frac{x^4}{4!} + \dots$

$$\text{Diode conductance: } g_D = \frac{1}{r_D} = \frac{I_D}{nV_T}$$

**BJT in Forward Active Region:**

Ignore early effect:  $i_C = I_S \exp\left(\frac{|v_{BE}|}{V_T}\right)$

With early effect:  $i_C = I_S \exp\left(\frac{|v_{BE}|}{V_T}\right) \left(1 + \frac{|v_{CE}|}{V_A}\right)$

where  $I_S$ : Saturation current,

$V_T$ : Thermal voltage, assume 25 mV at room temperature,

$V_A$ : Early voltage.

For npn transistor,  $|v_{BE}| = v_{BE}$  and  $|v_{CE}| = v_{CE}$ ;

For pnp transistor,  $|v_{BE}| = v_{EB}$  and  $|v_{CE}| = v_{EC}$ .

**Small-signal model parameters of BJT:**

$$g_m = \frac{I_C}{V_T}, \quad r_\pi = \frac{\beta}{g_m} \quad \text{and} \quad r_o = \frac{V_A + |V_{CE}|}{I_C} \approx \frac{V_A}{I_C}$$

where  $I_C$ : DC collector current at Q-point

$V_{CE}$ : DC collector-emitter voltage at Q-point

Criterion for small-signal operation of BJT:  $|v_{be}| \leq 0.2V_T$

**MOSFET in Saturation Region:**

Criterion:  $V_{DS} \geq V_{GS} - V_{TN}$  for NMOS;

$|V_{DS}| \geq |V_{GS}| - |V_{TP}|$  for PMOS

where  $V_{TN}, V_{TP}$ : Threshold voltage,

$V_{DS}$ : DC drain-source voltage,

$V_{GS}$ : DC gate-source voltage.

Ignore channel-length modulation effect:

$$i_D = \frac{K_n}{2} (v_{GS} - V_{TN})^2 \quad \text{for NMOS,}$$

$$i_D = \frac{K_p}{2} (|v_{GS}| - |V_{TP}|)^2 \quad \text{for PMOS.}$$

With channel-length modulation effect:  $i_D = \frac{K_n}{2} (v_{GS} - V_{TN})^2 (1 + \lambda v_{DS})$  for NMOS,

$$i_D = \frac{K_p}{2} (|v_{GS}| - |V_{TP}|)^2 (1 + \lambda |v_{DS}|) \quad \text{for PMOS.}$$

where  $\lambda$ : channel length modulation parameter,

For NMOS  $K_n = K'_n \left(\frac{W}{L}\right)$  and  $K'_n = \mu_n C_{ox}$ ; For PMOS  $K_p = K'_p \left(\frac{W}{L}\right)$  and  $K'_p = \mu_p C_{ox}$ .



**MOSFET in Triode Region:**

Criterion:  $V_{DS} < V_{GS} - V_{TN}$  for NMOS;  
 $|V_{DS}| < |V_{GS}| - |V_{TP}|$  for PMOS

Ignore channel-length modulation effect:

$$i_D = K_n \left( v_{GS} - V_{TN} - \frac{v_{DS}}{2} \right) v_{DS} \text{ for NMOS,}$$

$$i_D = K_p \left( |v_{GS}| - |V_{TP}| - \frac{|v_{DS}|}{2} \right) |v_{DS}| \text{ for PMOS.}$$

With channel-length modulation effect:  $i_D = K_n \left( v_{GS} - V_{TN} - \frac{v_{DS}}{2} \right) v_{DS} (1 + \lambda v_{DS})$  for NMOS,

$$i_D = K_p \left( |v_{GS}| - |V_{TP}| - \frac{|v_{DS}|}{2} \right) |v_{DS}| (1 + \lambda |v_{DS}|) \text{ for PMOS.}$$

**Small-signal model parameters of MOSFET**

For NMOS:  $g_m = \sqrt{2K_n I_D (1 + \lambda V_{DS})} \approx \sqrt{2K_n I_D}$  and  $r_o = \frac{\frac{1}{\lambda} + V_{DS}}{I_D} \approx \frac{1}{\lambda I_D}$

For PMOS:  $g_m = \sqrt{2K_p I_D (1 + \lambda |V_{DS}|)} \approx \sqrt{2K_p I_D}$  and  $r_o = \frac{\frac{1}{\lambda} + |V_{DS}|}{I_D} \approx \frac{1}{\lambda I_D}$

where  $I_D$ : DC drain current at Q-point

$V_{DS}$ : DC drain-source voltage at Q-point

Criterion for small-signal operation:

For NMOS:  $|v_{gs}| \leq 0.2(V_{GS} - V_{TN})$

For PMOS:  $|v_{gs}| \leq 0.2(|V_{GS}| - |V_{TP}|)$

where  $V_{GS}$ : DC gate-source voltage at Q-point.

Frequency Response: OCTC and SCTC

0) DISABLE DC sources...

voltage sources → SHORT CIRCUIT, current sources → OPEN CIRCUIT

1) Identify capacitors contributing (reducing  $V_o$  or causing trouble) to the frequency of interest (i.e. lower or higher cut-off).

2) DISABLE all independent AC sources...

voltage sources → SHORT CIRCUIT, current sources → OPEN CIRCUIT

DO NOT remove or “disable” dependent sources!

↓  
higher cut-off  
(OCTC)

↓  
lower cut-off  
(SCTC)

3) Idealize irrelevant capacitors by SHORT CIRCUIT (because at high  $f$ , cap → short)

Next step to find time constant

4) For each contributing capacitor  $C_i$ , set all other capacitors (other than the one you are looking at) removed (i.e. OPEN CIRCUITS) and determine the resistance,  $R_i$  seen by  $C_i$

5) Higher cut-off frequency is estimated as:

$$\omega_{H-3dB} \approx \frac{1}{\sum_i C_i R_i} = \frac{1}{C_1 R_1 + C_2 R_2 + \dots}$$

3) Idealize irrelevant capacitors by OPEN CIRCUIT (because at low  $f$ , cap → open)

Next step to find time constant

4) For each contributing capacitor  $C_i$ , set all other capacitors (other than the one you are looking at) removed (i.e. SHORT CIRCUITS) and determine the resistance,  $R_i$  seen by  $C_i$

5) Lower cut-off frequency is estimated as:

$$\omega_{L-3dB} \approx \sum_i \frac{1}{C_i R_i} = \frac{1}{C_1 R_1} + \frac{1}{C_2 R_2} + \dots$$

END OF PAPER

1. (a) Use superposition theorem

$$V_{out} = V_{out}|_{I_+} + V_{out}|_{I_-}$$

$$= \underbrace{-(R_3 + R_1 || R_2) \left( \frac{R_4 || R_5 + R_6}{R_4 || R_5} \right)}_{V_{IK}} \left( \frac{R_8 + (R_4 || R_5 + R_6) || R_7}{(R_4 || R_5 + R_6) || R_7} \right) I_+ + \underbrace{I_- (R_6)}_{V_{IK}} \left( \frac{R_8 + R_6 || R_7}{R_6 || R_7} \right)$$

(b) First find the value of the 2 constants,  $nV_T$  and  $I_S$ .

$$0.674 = nV_T \ln \frac{426 \times 10^{-6}}{I_S} \quad (1)$$

$$0.794 = nV_T \ln \frac{4.28 \times 10^{-3}}{I_S} \quad (2)$$


Sub (1) to (2)

$$0.794 = 0.674 + nV_T \ln \frac{4.28 \times 10^{-3}}{426 \times 10^{-6}}$$

$$nV_T = 0.052 \text{ V}$$

$$I_S = 1.003 \times 10^{-9} \text{ A}$$

 Find  $V_{th}$  and  $R_{th}$  for  $D_1$  and  $D_2$



$$V_{D1} = \frac{16k}{8k + 38k + 16k} \cdot 6V$$

$$= 3V$$


$$V_{D2} = \frac{24k}{24k + 6k + 6k} \cdot 4.5V$$

$$= 3V$$

$$R_{D1} = 16k || 16k = 8k$$

$$R_{D2} = 24k || 12k = 8k$$

 Since  $V_{D1} = V_{D2}$  and  $R_{D1} = R_{D2}$ , we just need to find  $V_D$  and  $I$  once



$$I_D = \frac{3 - V_D}{8k}$$

$$V_D = nV_T \ln \frac{I_D}{I_S}$$

start with  $V_D = 0.7$

$$I_D = 0.288 \text{ mA} \quad V_D = 0.653$$


$$I_D = 0.293 \text{ mA} \quad V_D = 0.654$$

$$I_D = 0.293 \text{ mA} \quad V_D = 0.654$$

Q point (0.293mA, 0.654V) for both  $D_1$  and  $D_2$

(1)

2. (a)

 

$V_G = 0$  since  $I_G = 0$

$$V_{GS} + I_D R_S = 2V$$

$$I_D = \frac{K_N}{2} (V_{GS} - V_{TN})^2$$

$$V_{GS} + \frac{K_N}{2} (V_{GS} - 1)^2 \cdot 2k = 2$$

$$V_{GS} + 2(V_{GS}^2 - 2V_{GS} + 1) = 2$$

$$2V_{GS}^2 - 3V_{GS} = 0$$

$$V_{GS} = \frac{1.5}{1} = 1.5V$$

$$I_D = 0.25mA$$


KVL 2

$$V_{DS} + I_D R_S = 3V$$

$$V_{DS} = 2.5V$$


$$g_m = \sqrt{2K_N I_D} = 10^{-3} S$$
 
$$r_D = \frac{1}{\lambda + (I_D / V_{DS})} = 410000 \Omega$$



$$\text{gain} = \frac{V_o}{V_i} = \frac{(g_m V_{GS} + \frac{V_{GS}}{R_G}) (\frac{1}{R_S} + \frac{1}{R_L})}{V_{GS} + g_m V_{GS} + \frac{V_{GS}}{R_G}} = \frac{(g_m + \frac{1}{R_G}) R_D || R_S}{1 + g_m R_G + \frac{1}{R_G} R_D || R_S} = 0.749$$
 
$$(c) R_{in} = \frac{V_i}{\frac{V_{GS}}{R_G}} = \frac{V_i}{\frac{V_i - V_o}{R_G}} = \frac{V_i}{V_i - V_o} \times R_G = 4R_G = 8k \Omega$$



use KCL

$$-g_m V_{GS} + \frac{V_o}{R_G} + \frac{V_o}{R_S} + \frac{V_o}{R_L} = 0$$

$$V_o = V_{GS} (g_m + \frac{1}{R_G} + \frac{1}{R_S} + \frac{1}{R_L})$$

$$R_{out} = \frac{1}{g_m + \frac{1}{R_G} + \frac{1}{R_S} + \frac{1}{R_L}} = 499.39 \Omega$$

(e)  $|V_{gs}| \leq 0.2 (V_{gs} - V_{th})$  (1)

$$V_i = V_{gs} + \left( g_m V_{gs} + \frac{V_{gs}}{R_g} \right) (r_o || R_s)$$

$$V_i = V_{gs} \left( 1 + \left( g_m + \frac{1}{R_g} \right) (r_o || R_s) \right)$$


$$V_{gs} = \frac{V_i}{1 + \left( g_m + \frac{1}{R_g} \right) (r_o || R_s)}$$

Sub back to (1)

$$V_i \leq 0.2 (0.5) \left( 1 + \left( g_m + \frac{1}{R_g} \right) (r_o || R_s) \right)$$

$$V_i \leq 0.4 \text{ V}$$

 3. (a) Consider only half of the differential amplifier since it is symmetrical



Replace  $R_{G1}$  and  $R_{G2}$  with  $V_{th}$  for gate of the transistor

$$V_{th} = \frac{R_{G2}}{R_{G1} + R_{G2}} (V_{DD} - 0)$$

$$= 4 \text{ V}$$

No need  $R_{th}$  since no current flows through gate

$$V_{gs} + I_D \cdot 2R_s = 4 - (-12)$$

$$V_{gs} + I_D \cdot 2R_s = 16$$

$$I_D = \frac{K_n}{2} (V_{gs} - V_{th})^2$$

$$V_{gs} + K_n \cdot R_s (V_{gs} - V_{th})^2 = 16$$

$$V_{gs} + V_{gs}^2 - 4V_{gs} + 4 = 16$$

$$V_{gs}^2 - 3V_{gs} - 12 = 0$$

$$V_{gs} = \frac{3 + \sqrt{57}}{2} \text{ V} = 5.275 \text{ V}$$


$$I_D = 1.0725 \text{ mA}$$

KVL 2

$$I_D (R_G + 2R_s) + V_{DS} = 24$$

$$V_{DS} = 4.695 \text{ V}$$

Qpoints (1.0725 mA, 4.695 V)

 


$$g_m = \sqrt{2K_n I_D} = 6.55 \times 10^{-4}$$

diff mode

$$\text{single ended gain} = \frac{-g_m V_{gs} \cdot R_D}{V_i} = \frac{-g_m R_D}{2} = -2.62$$
 
$$\text{diff output gain} = \frac{-g_m V_{gs} \cdot R_D}{V_i} = -g_m R_D = -5.24$$



Common mode gain

single ended gain =  $\frac{-g_m V_s R_D}{V_s + g_m V_s (2R_S)}$

$$= \frac{-g_m R_D}{1 + g_m 2R_S} = -0.694$$

Differential mode gain = 0 since  $V_{o1}$  and  $V_{o2}$  are the same

c) CMRR (single ended) =  $\frac{\text{diff mode se}}{\text{common mode se}} = \left| \frac{\frac{-g_m R_D}{2}}{\frac{-g_m R_D}{1 + g_m 2R_S}} \right| = \frac{1 + g_m 2R_S}{2} = 3.775$


CMRR (differential output) =  $\frac{\text{diff mode diff}}{\text{common mode diff}} = \left| \frac{-g_m R_D}{0} \right| = \infty$

If  $R_S$  is increased,  $V_{GS}$  (in DC) will decrease and as a result  $g_m$  will decrease and the gain for all mode will be uncertain and a better configuration is to add a current source to replace  $R_S$  so that  $I_D$  is constant and  $g_m$  is constant

d) input resistance for all mode is  $\infty$

Output resistance


For diff mode

 

$$R_{out} = R_D + R_D = 2R_D$$



For common mode

 


Since  $V_b$  and  $V_s = 0$

$$-V_{GS} = g_m V_{GS} \cdot 2R_S$$

$$V_{GS} = 0 \text{ since } 1 \neq g_m \cdot 2R_S$$

$$R_{out} = R_D || R_D = \frac{R_D}{2}$$

 

$$4. (a) I_D = \frac{K}{2} (V_{GS} - V_{TN})^2$$

$$V_{GS} = \sqrt{\frac{2I_D}{K_n}} + V_{TN} = 1.5$$

$$M_1 = 1.5 \text{ V} = V_A$$

$$M_2 = M_1 + V_{GS}$$

$$= 3 \text{ V} = V_B$$

$$M_2 = M_3$$

$$I_D = \frac{K_n}{2} (V_{GS} - V_{TN})^2 (1 + \lambda V_{GS})$$

$$V_{GS} = 5 \text{ V}$$

$$= 0.125 \text{ mA}$$

$$(b) i. V_{out} = \frac{R_L}{R_L + \frac{1}{sC_L}} \cdot \frac{-\frac{1}{sC_f}}{\frac{R_S}{sC_f} + \frac{1}{sC_f}} \quad V_S$$

$$= \frac{sC_L R_L}{sC_L R_L + 1} \cdot \frac{-\frac{1}{sC_f}}{\frac{R_S}{sC_f} + \frac{1}{sC_f}}$$

$$= \frac{sC_L R_L}{sC_L R_L + 1} \cdot \frac{sC_f R_S + 1}{R_S + 1}$$

$$= \frac{C_L R_L}{C_f R_S} \cdot \frac{sC_f R_S + 1}{sC_L R_L + 1}$$

$$\equiv 1 \text{ pole and 1 zero}$$

$$\text{pole} = -\frac{1}{C_L R_L}$$

$$\text{zero} = -\frac{1}{C_f R_S}$$

(5)

## Tips & Trick

1. The structure of the question will always be the same
  - a. No 1 will always be op amp and diode
  - b. No 2 will always be single stage BJT/MOSFET
  - c. Differential amplifier, multistage amplifier and Current mirror, 2 of them will come out at Number 3 & 4.
  - d. Transfer function will come out in the last part
2. Always do number 1 first since it's the easiest
3. Do multistage amplifier last (if it comes out)
4. Practice P4P a lot since the structure of the questions are very similar each year