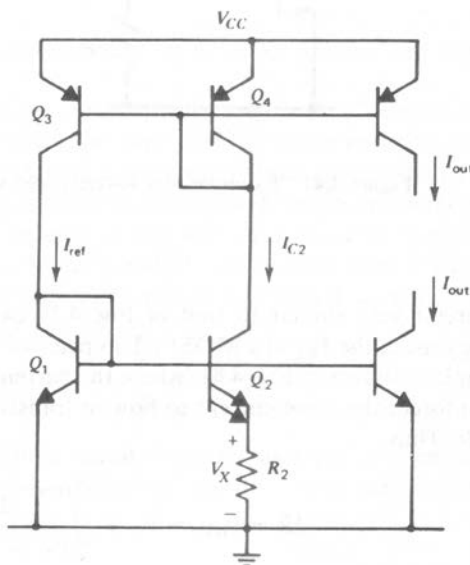



## EE3019 - Integrated Electronics    Tutorial 10

1. A bias source is depicted in Figure 10.1 where  $Q_2$  is twice the size of  $Q_1$ . The other transistors are the same size as  $Q_1$ .
  - (a) State the basic mechanism of this bias source.
  - (b) Derive the variation of the fractional temperature coefficient for the output current.
  - (c) Determine the resistance  $R_2$  for the current bias reference circuit to obtain an output of  $100\mu\text{A}$  and the resultant  $TC_F$  at room temperature ( $T=300\text{K}$ ). Assume that the resistor temperature coefficient is  $1500\text{ ppm}/^\circ\text{C}$ .

[(c)  $180\Omega$ ,  $1800\text{ppm}/^\circ\text{C}$ ]



**Figure 10.1**

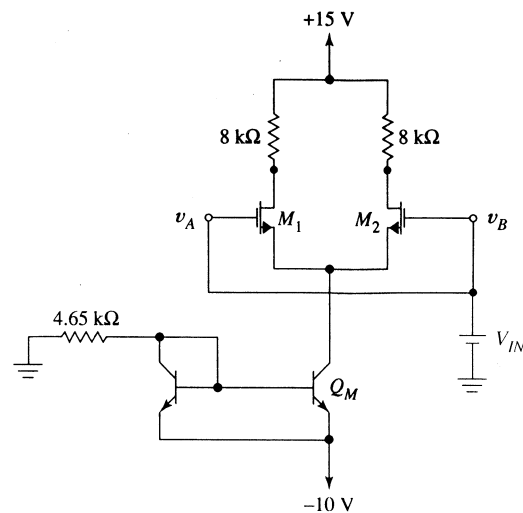

**Figure 10.2**

2. A differential amplifier depicted in Figure 10.2 comprises 4 transistors where
 

MOS transistors:  $\mu_n C_{ox} W/L = 0.2 \times 10^{-3} \text{ A/V}^2$ ,  $V_t = 0.5 \text{ V}$

Bipolar transistors:  $V_{CE(\text{sat})} = 0.2 \text{ V}$ .

Assume that the two MOSFETs have an identical aspect (i.e.  $W/L$ ) ratio and that the two BJTs have identical emitter areas.

  - (d) Show that all the MOSFETs and BJTs are active for the zero-input condition, i.e.  $V_{in} = 0$ .
  - (e) Find the maximum and minimum common-mode input voltages, i.e. the limits of operation where the circuit remains in active operation.

[(b)  $-6.14\text{V} \leq V_{in} \leq 7.5\text{V}$ ]

3. Explain the function of each transistor in the op amp shown in Figure 10.3.

**Figure 10.3**

