

EE3019

NANYANG TECHNOLOGICAL UNIVERSITY**SEMESTER 2 EXAMINATION 2021-2022****EE3019 – INTEGRATED ELECTRONICS**

April / May 2022

Time Allowed: 2 hours

INSTRUCTIONS

1. This paper contains 4 questions and comprises 7 pages.
 2. Answer all 4 questions.
 3. All questions carry equal marks.
 4. This is a closed book examination.
 5. Unless specifically stated, all symbols have their usual meanings.
 6. A List of Formulae is provided in the Appendix on page 7.
-

1. (a) Consider a CMOS NAND gate depicted in Figure 1(a) on page 2 where both inputs are connected to V_{in} . Assume that $V_{DD} = 1.5\text{V}$, $C_{parasitic} = 3\text{fF}$ and $C_{gate} = 7\text{fF}$. The parameters of the pMOS and nMOS transistors are given below:

$$\text{pMOS} \quad V_{tp} = -0.47 \text{ V} \quad \mu_p C_{ox} = 25 \text{ } \mu\text{A/V}^2 \quad \left(\frac{W}{L}\right)_p = 2$$

$$\text{nMOS} \quad V_{tn} = 0.52 \text{ V} \quad \mu_n C_{ox} = 65 \text{ } \mu\text{A/V}^2 \quad \left(\frac{W}{L}\right)_n = 1$$

- (i) Identify the regions of operation of both the pMOS and nMOS transistors when V_{out} is at $V_{OH(10\%)}$ and determine the output current, i_{out} , at $V_{OH(10\%)}$.
- (ii) Identify the regions of operation of both the pMOS and nMOS transistors when V_{out} is at $V_{OH(90\%)}$ and determine the output current, i_{out} , at $V_{OH(90\%)}$.

Note: Question No. 1 continues on page 2.

EE3019

- (iii) Determine the rise time, t_r , when V_{out} changes from $V_{OH(10\%)}$ to $V_{OH(90\%)}$.

State all your assumptions clearly.

 


Figure 1(a)

(12 Marks)

- (b) A pull-down network of a CMOS logic circuit is depicted in Figure 1(b).

 


Figure 1(b)

- Complete the CMOS logic circuit by designing the corresponding pull-up network (PUN). Derive the logic function of the circuit.
- Determine the width of the different pMOS transistors in the PUN such that the driving capability of the PUN is equal to that of an inverter designed for the worst-case scenario. Assume that the $\left(\frac{W}{L}\right)$ ratio of the pMOS transistor for the inverter is $\left(\frac{3}{1}\right)$ and the length of all transistors is 28nm.

(10 Marks)

Note: Question No. 1 continues on page 3.

EE3019

- (c) Briefly discuss how the circuit delay and power dissipation could be affected by the variations of the process threshold voltage.

(3 Marks)

2. (a) Derive an expression for the closed-loop gain of a single-loop feedback amplifier. Show that the signal-to-noise ratio of a closed loop amplifier is lower than an open-loop amplifier.

(7 Marks)

- (b) A negative feedback amplifier is depicted in Figure 2. Assume that $R_s = 1\text{k}\Omega$, $R_L = 3\text{k}\Omega$, $R_{id} = 100\text{k}\Omega$, $r_o = 1\text{k}\Omega$, $R_1 = 200\text{k}\Omega$, $R_2 = 200\text{k}\Omega$ and $R_3 = 1\text{k}\Omega$.

- (i) Identify the feedback topology and determine the feedback factor, β . Determine the input and output impedances, $R_{\beta i}$ and $R_{\beta o}$, respectively, of the feedback network.
- (ii) Determine the voltage gain, $\frac{V_o}{V_s}$, for two cases of the open-loop gain of the op-amp: $A = \infty$, and $A = 10^5$.
- (iii) Determine the input and output impedances, R_{if} and R_{of} , respectively, of the feedback amplifier.

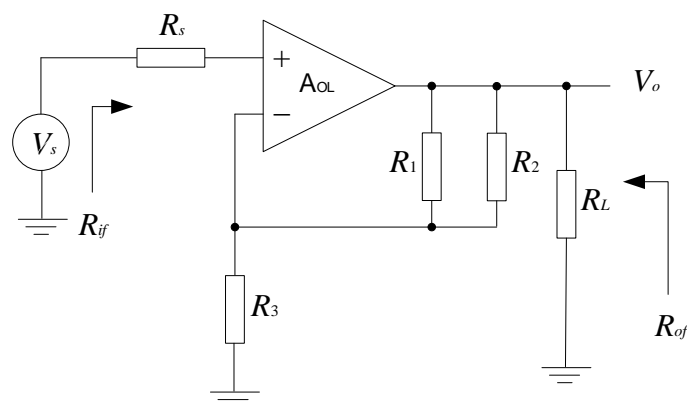


Figure 2

(15 Marks)

- (c) Explain the -3 dB points in the lower and upper cut-off frequencies of an amplifier and their power gain relationship with the mid-band gain.

(3 Marks)

EE3019

3. (a) Explain why a Bandgap voltage reference is preferred over a V_{BE} -based voltage reference.
- (3 Marks)
- (b) A Bandgap voltage reference is depicted in Figure 3. Derive the expression for V_{OUT} in terms of $V_{BE} + KV_T$ where K and V_T are a constant and the thermal voltage, respectively.
- (16 Marks)
- (c) Redesign the Bandgap voltage reference such that the current in the two transistors is not drawn from V_{CC} .
- (4 Marks)
- (d) The bipolar transistor Q1 and the bipolar op-amp A in the Bandgap voltage reference in Figure 3 are replaced by a PMOS transistor and a CMOS op-amp, respectively. Explain if these replacements are appropriate.
- (2 Marks)

 


Figure 3

EE3019

4. A multi-stage bipolar op-amp is depicted in Figure 4 on page 6. Assume the following parameters for the bipolar transistors:

$$|V_{BE(on)}| = 0.7V, \beta \rightarrow \infty, V_T = 25mV \text{ and } |V_A| = 100.$$

- (a) Transistors Q_3 and Q_8 constitute a simple current mirror. State and explain two important attributes of the simple current mirror.

(5 Marks)

- (b) Determine the following for transistor Q_5 :

- (i) DC bias current, and
- (ii) DC voltage at the collector.

(8 Marks)

- (c) Assuming that the output impedance of Q_3 and the input impedance of Q_4 and Q_5 are very large, determine the differential DC voltage gain of the first-stage of the op-amp.

(9 Marks)

- (d) An engineer remarked that the op-amp in Figure 4 is not well designed. Explain if you agree or disagree with the engineer's remark, and suggest improvements, if any.

(3 Marks)

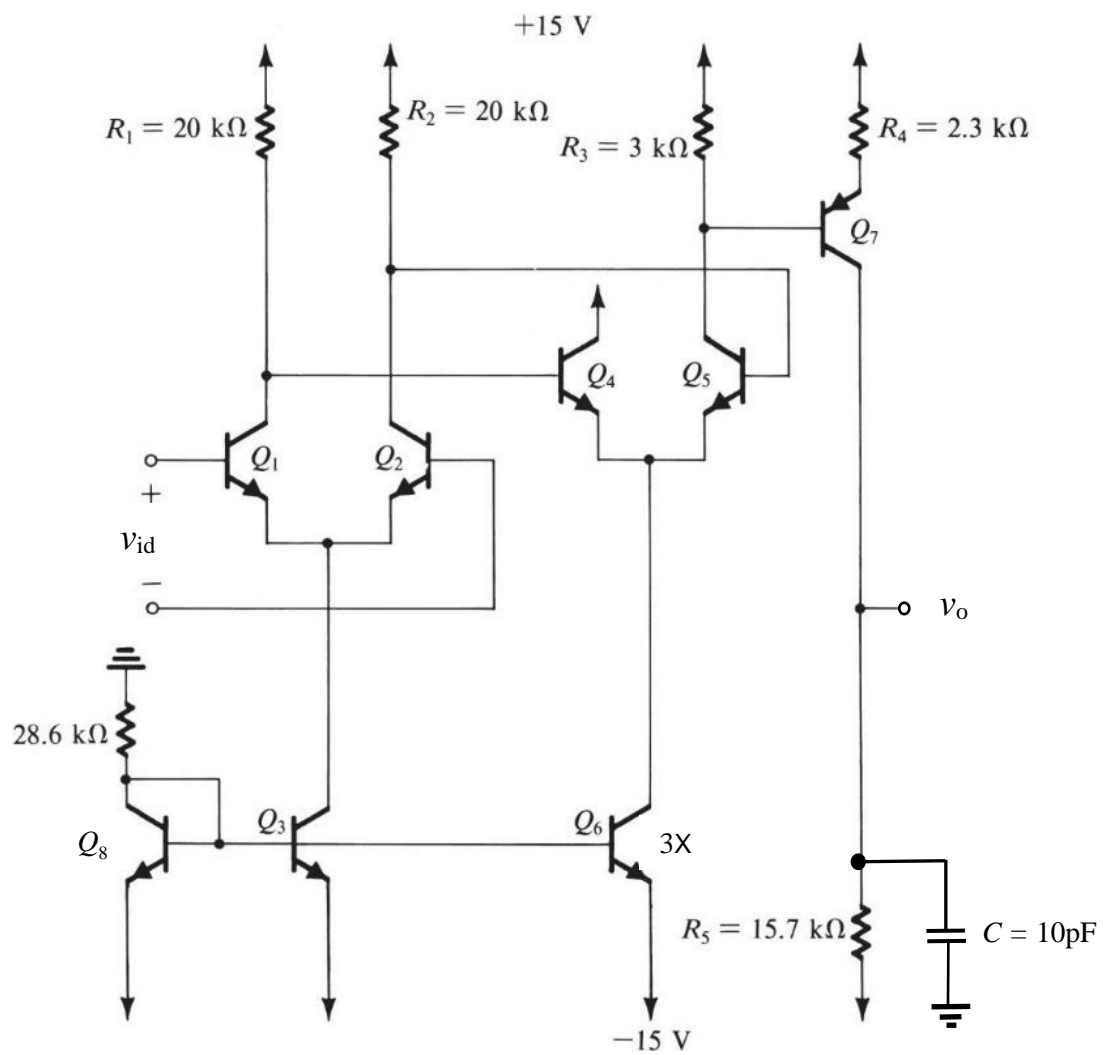


Figure 4

Appendix

List of Formulae

$$V = I Z$$

$$Z_L = j\omega L$$

$$\sum_{m=1}^M v_m = 0$$

$$v = L \frac{di}{dt}$$

$$S = V I^*$$

$$V_T = \frac{kT}{q}$$

$$i_E = i_C + i_B$$

$$\alpha = \frac{\beta}{1 + \beta}$$

$$ABC = \overline{\overline{A} + \overline{B} + \overline{C}}$$

$$i_{Dn(LIN)} = (\mu_n C_{ox}) \left(\frac{W}{L} \right) \left((v_{GS} - V_t) v_{DS} - \frac{1}{2} v_{DS}^2 \right)$$

$$i_{Dn(SAT)} = \frac{1}{2} (\mu_n C_{ox}) \left(\frac{W}{L} \right) (v_{GS} - V_t)^2$$

$$A(s) = A_m F_H(s) = \frac{A_m}{\left(1 + \frac{s}{\omega_{P1}}\right) \left(1 + \frac{s}{\omega_{P2}}\right)}$$

$$g_m = 2 \frac{I_D}{(V_{GS} - V_t)}$$

$$g_m = \frac{I_C}{V_T}$$

$$P = I V$$

$$Z_C = \frac{1}{j\omega C}$$

$$\sum_{n=1}^N i_n = 0$$

$$i = C \frac{dv}{dt}$$

$$i_D = I_S \left[\exp\left(\frac{v_D}{nV_T}\right) - 1 \right]$$

$$i_C \approx I_S \left[\exp\left(\frac{v_{BE}}{V_T}\right) \right]$$

$$\beta = \frac{i_C}{i_B}$$

$$A + B + C = \overline{\overline{A} \overline{B} \overline{C}}$$

$$\tau_p = \frac{C_{load} \times \Delta V}{I_{avg}}$$

$$A_f = \frac{A}{1 + A\beta}$$

$$f = \frac{1}{2n\tau_p}$$

$$V_o = A_1 A_2 (V_i - \beta V_o) + A_1 V_n$$

$$r_o = \frac{V_A}{I_D}$$

END OF PAPER