

- Figure 6.1 shows a non-inverting buffer op-amp configuration. Assuming that the op-amp has  $A = 10$ , infinite input resistance and zero output resistance, what is  $\beta$ ? What is the closed-loop voltage gain? What is the amount of feedback in dB? For  $v_s = 1$  V, find  $v_o$ , and  $V_i$ . If  $A$  decreases by 10%, what is the corresponding decrease in  $A_f$ ?


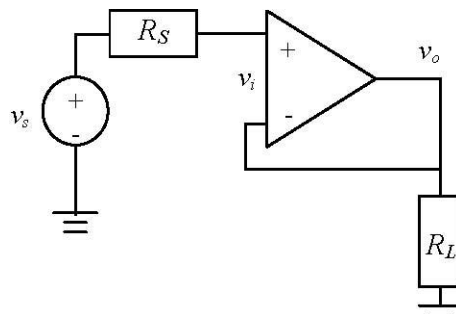


Figure 6.1

- An amplifier has an open loop gain of  $5000 \pm 500$  V/V, and a dominant pole at 4 kHz. If the amplifier is used in the design of a feedback amplifier with a gain variation of no more than  $\pm 1\%$ , find the feedback factor of the feedback network used, the closed-loop gain, and the bandwidth of the feedback amplifier.

[Answer:  $1.8 \times 10^{-3}$ , 500, 40 kHz]

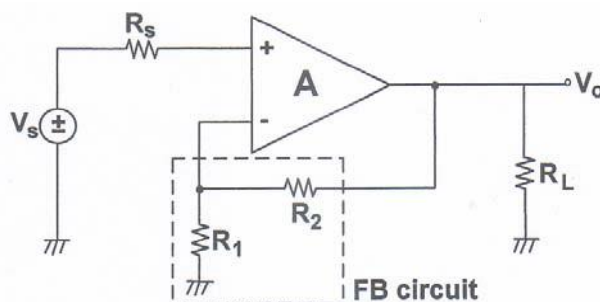- Figure 6.2 shows a non-inverting op-amp. If the open loop voltage gain  $A = 10^5$ , find the ratio of  $R_2/R_1$  to obtain a closed-loop voltage gain of 100. If there is a 15% change in the value of  $A$ , find the corresponding change in the closed-loop gain.



[Answer: 99, 0.015%]

Figure 6.2