



AC Analysis of BJT and MOSFET Voltage Followers

Assoc Prof Chang Chip Hong

email: echchang@ntu.edu.sg

EE2002 Analog Electronics




Lesson Objectives

At the end of this lesson, you should be able to:

- Identify BJT and MOSFET voltage follower circuits
- Draw small-signal AC equivalent circuits of C-C and C-D amplifiers
- Calculate the following performance characteristics of C-C and C-D amplifiers
 - Voltage gain
 - Input resistance
 - Output resistance

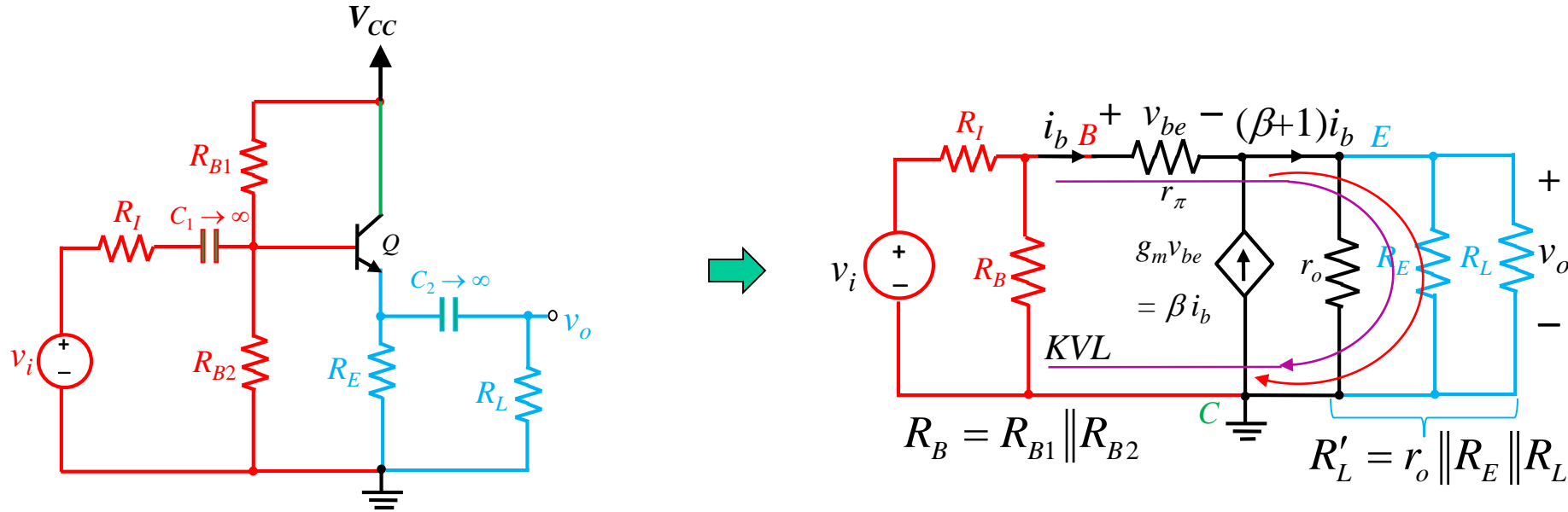
C-C Amplifier (Voltage Follower): Terminal Voltage Gain



$$A_{vt} = \frac{v_e}{v_b} = \frac{(\beta + 1)i_b R'_L}{i_b r_\pi + (\beta + 1)i_b R'_L} = \frac{(\beta + 1)R'_L}{r_\pi + (\beta + 1)R'_L} \approx \frac{g_m R'_L}{1 + g_m R'_L}$$

$$\text{If } g_m R'_L \gg 1, A_{vt} \approx 1 \Rightarrow v_o \approx v_b.$$

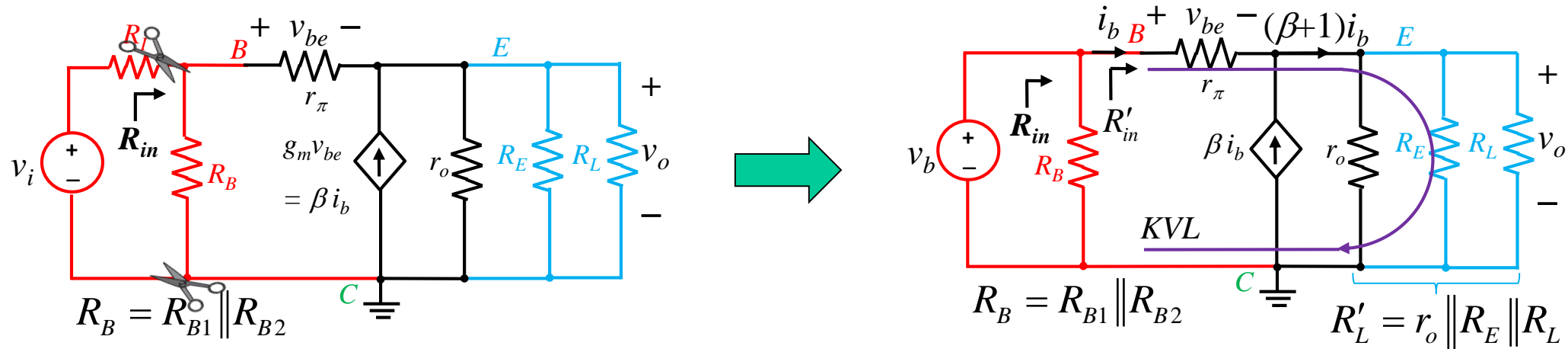C-C Amplifier (Voltage Follower): Input Resistance





$$v_b = i_b r_\pi + (\beta + 1) i_b R'_L$$


$$R'_{in} = \frac{v_b}{i_b} = r_\pi + (\beta + 1) R'_L$$

$$R_{in} = R'_{in} \parallel R_B$$

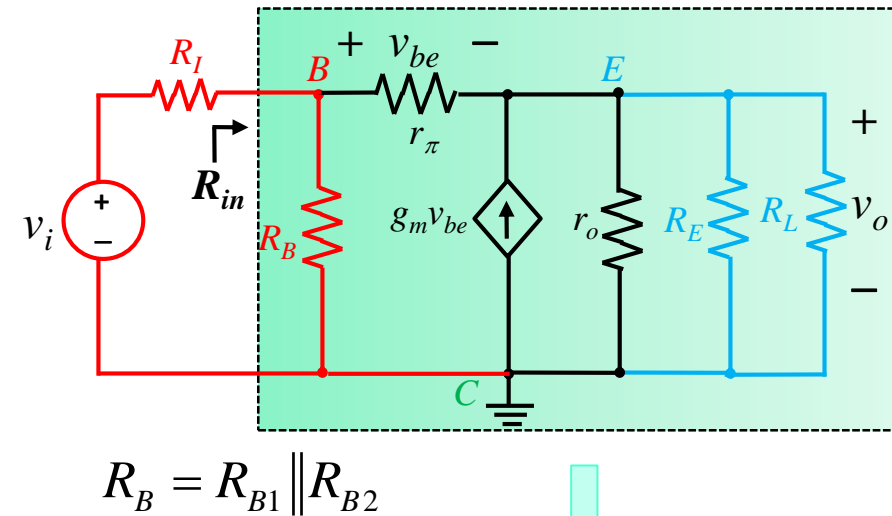
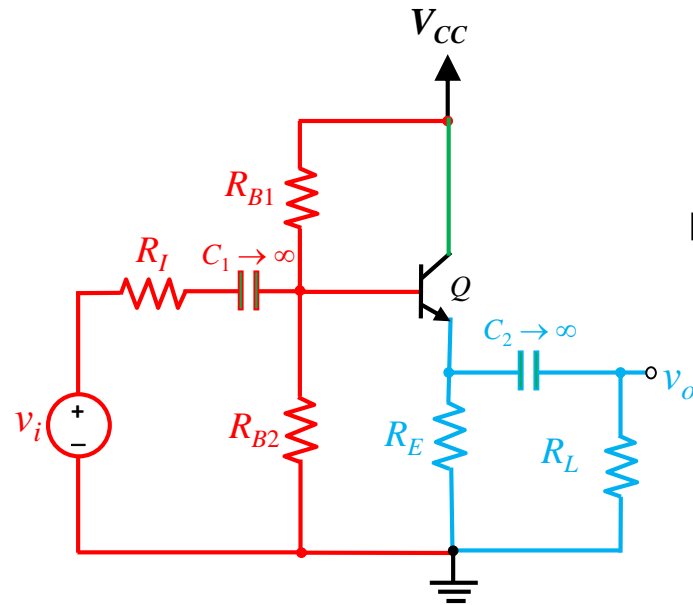
C-C Amplifier (Voltage Follower): Overall Voltage Gain



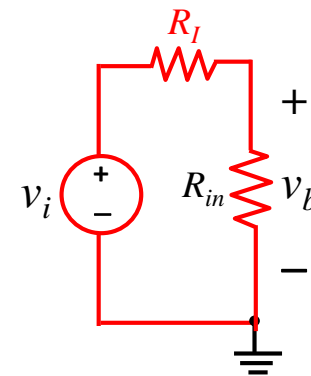
$$A_v = \frac{v_o}{v_i} = \frac{v_o}{v_b} \times \frac{v_b}{v_i} = A_{vt} \times \frac{R_{in}}{R_I + R_{in}}$$



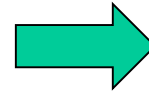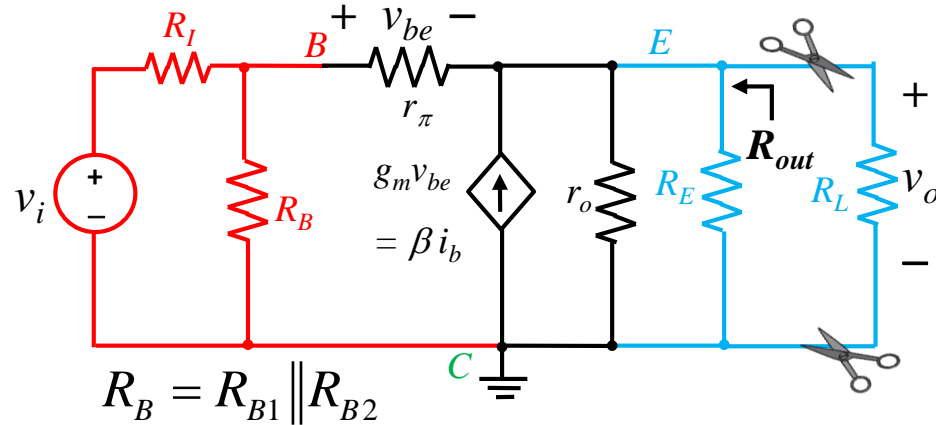C-C Amplifier (Voltage Follower): Output Resistance


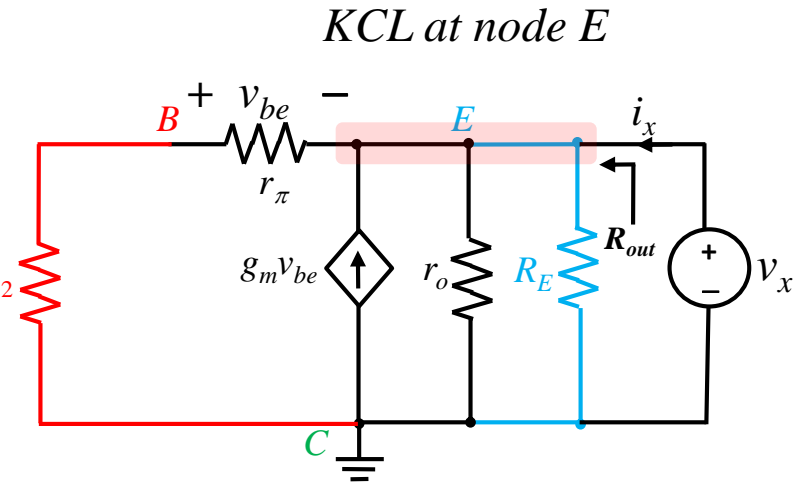
$$R_{th} = R_I \parallel R_{B1} \parallel R_{B2}$$





$$i_x = \frac{v_x}{R_E} + \frac{v_x}{r_o} - g_m v_{be} + \frac{v_x}{r_\pi + R_{th}}$$

$$v_{be} = - \left(\frac{r_\pi}{r_\pi + R_{th}} \right) v_x$$

$$\begin{aligned} i_x &= \frac{v_x}{R_E} + \frac{v_x}{r_o} + \frac{g_m r_\pi v_x}{r_\pi + R_{th}} + \frac{v_x}{r_\pi + R_{th}} \\ &= \left(\frac{1}{R_E} + \frac{1}{r_o} + \frac{\beta}{r_\pi + R_{th}} + \frac{1}{r_\pi + R_{th}} \right) v_x \end{aligned}$$

$$\begin{aligned} R_{out} &= \frac{v_x}{i_x} = \left(\frac{1}{R_E} + \frac{1}{r_o} + \frac{\beta + 1}{r_\pi + R_{th}} \right)^{-1} \\ &= R_E \parallel r_o \parallel \left(\frac{r_\pi + R_{th}}{\beta + 1} \right) \end{aligned}$$

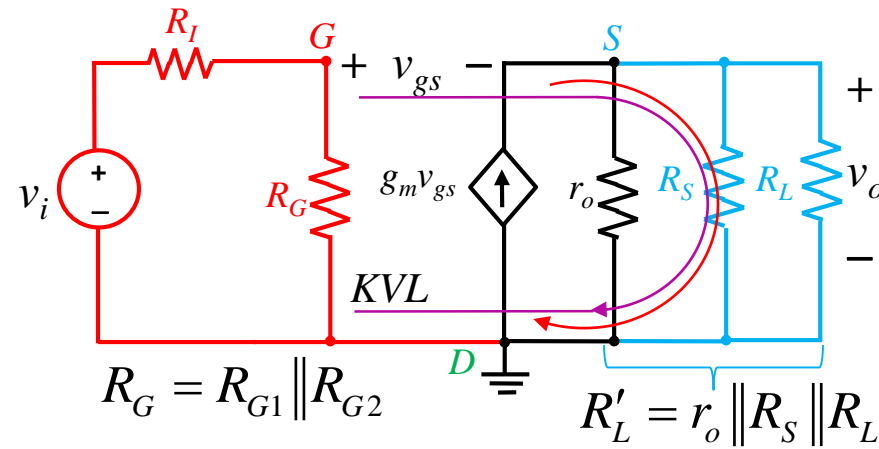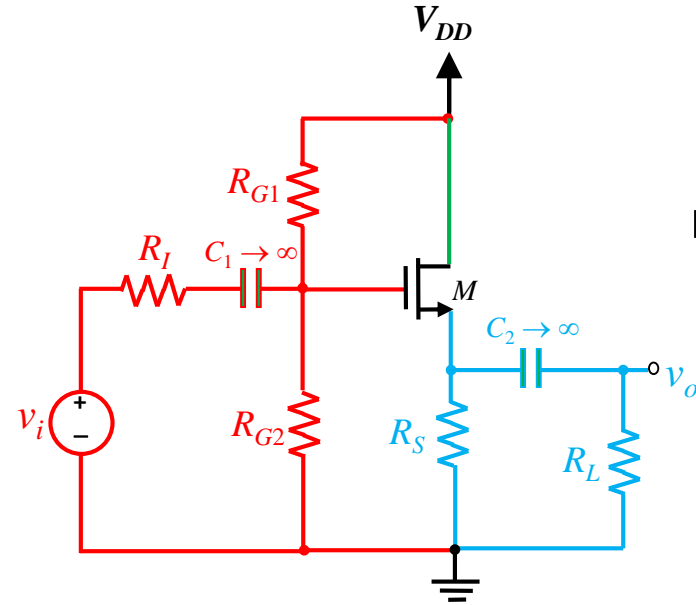
C-D Amplifier (Voltage Follower): Terminal Voltage Gain



$$A_{vt} = \frac{v_s}{v_g} = \frac{g_m v_{gs} R'_L}{v_{gs} + g_m v_{gs} R'_L} = \frac{g_m R'_L}{1 + g_m R'_L}$$


$$\text{If } g_m R'_L \gg 1, A_{vt} \approx 1 \Rightarrow v_o \approx v_g.$$

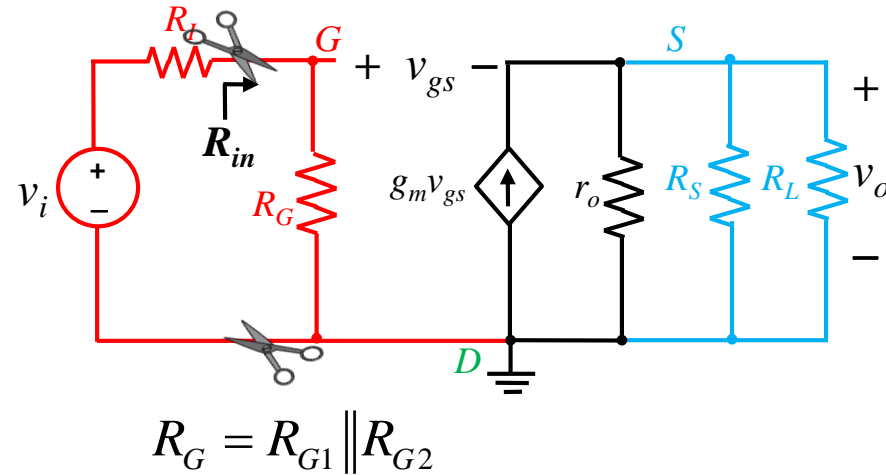C-D Amplifier (Voltage Follower): Input Resistance



$$R_{in} = R_G$$


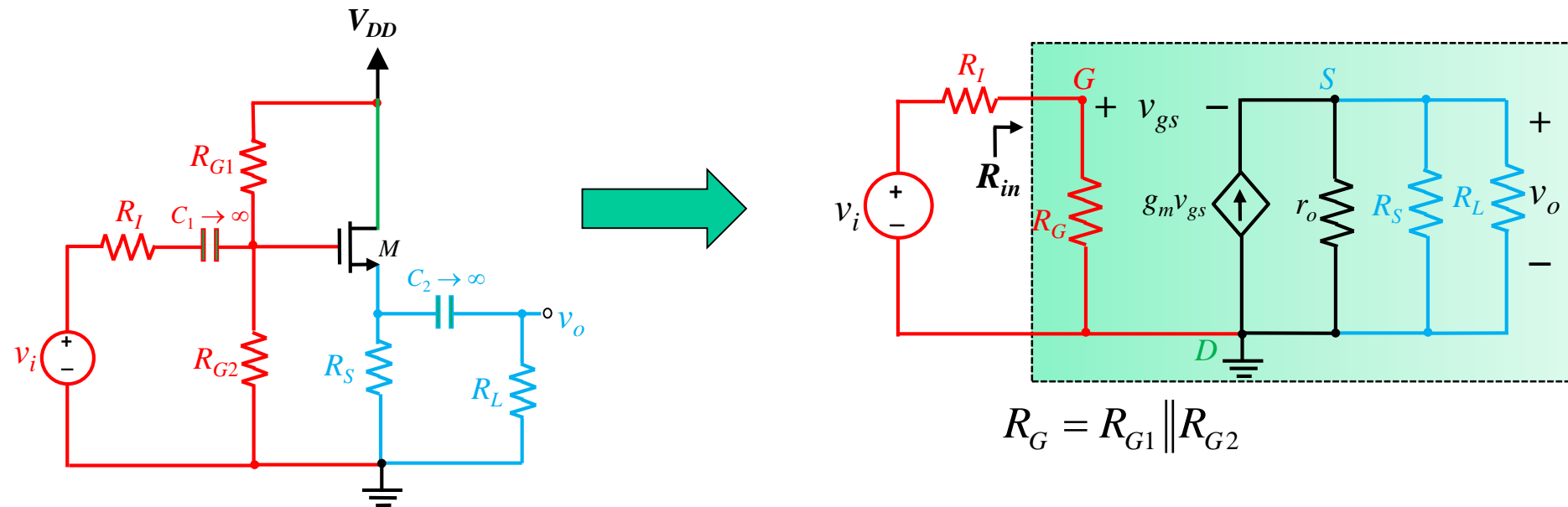
C-D Amplifier (Voltage Follower): Overall Voltage Gain




$$R_G = R_{G1} \parallel R_{G2}$$

$$A_v = \frac{v_o}{v_i} = \frac{v_o}{v_g} \times \frac{v_g}{v_i} = A_{vt} \times \frac{R_G}{R_I + R_G}$$

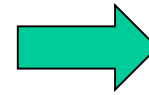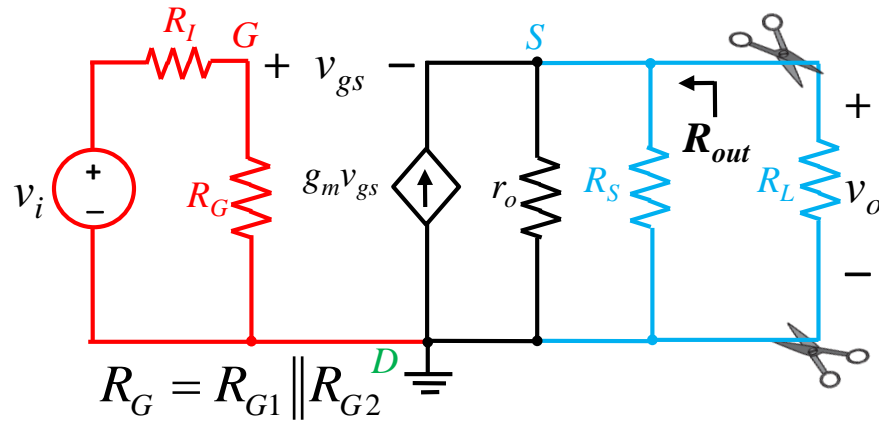C-D Amplifier (Voltage Follower): Output Resistance


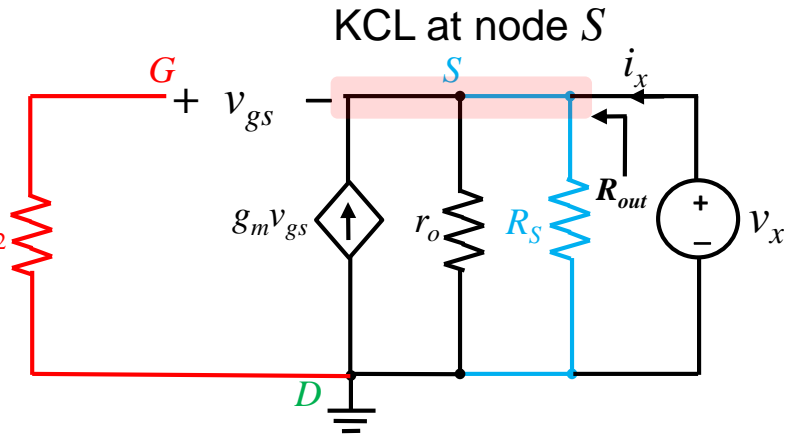
$$R_{th} = R_I \parallel R_{G1} \parallel R_{G2}$$



$$i_x = \frac{v_x}{R_S} + \frac{v_x}{r_o} - g_m v_{gs}$$

$$v_{gs} = -v_x$$

$$i_x = \frac{v_x}{R_S} + \frac{v_x}{r_o} + g_m v_x = \left(\frac{1}{R_S} + \frac{1}{r_o} + g_m \right) v_x$$

$$R_{out} = \frac{v_x}{i_x} = \left(\frac{1}{R_S} + \frac{1}{r_o} + g_m \right)^{-1}$$

$$= R_S \parallel r_o \parallel \frac{1}{g_m}$$